 


Single-Cycle CPU Datapath Design

"The Do-It-Yourself CPU Kit"

The Big Picture: Where are We Now?

- The Five Classic Components of a Computer




- Today's Topic: Datapath Design, then Control Design

The Big Picture: The Performance Perspective

- Processor design (datapath and control) will determine:
 - Clock cycle time
 - Clock cycles per instruction
- Starting today:
 - Single cycle processor:
 - Advantage: One clock cycle per instruction
 - Disadvantage: long cycle time

- $ET = Insts * CPI * Cycle\ Time$

 


The Processor: Datapath & Control

- We're ready to look at an implementation of the MIPS simplified to contain only:
 - memory-reference instructions: `lw`, `sw`
 - arithmetic-logical instructions: `add`, `sub`, `and`, `or`, `slt`
 - control flow instructions: `beq`
- Generic Implementation:
 - use the program counter (PC) to supply instruction address
 - get the instruction from memory
 - read registers
 - use the instruction to decide exactly what to do
- All instructions use the ALU after reading the registers
 - memory-reference? arithmetic? control flow?

Review: The MIPS Instruction Formats

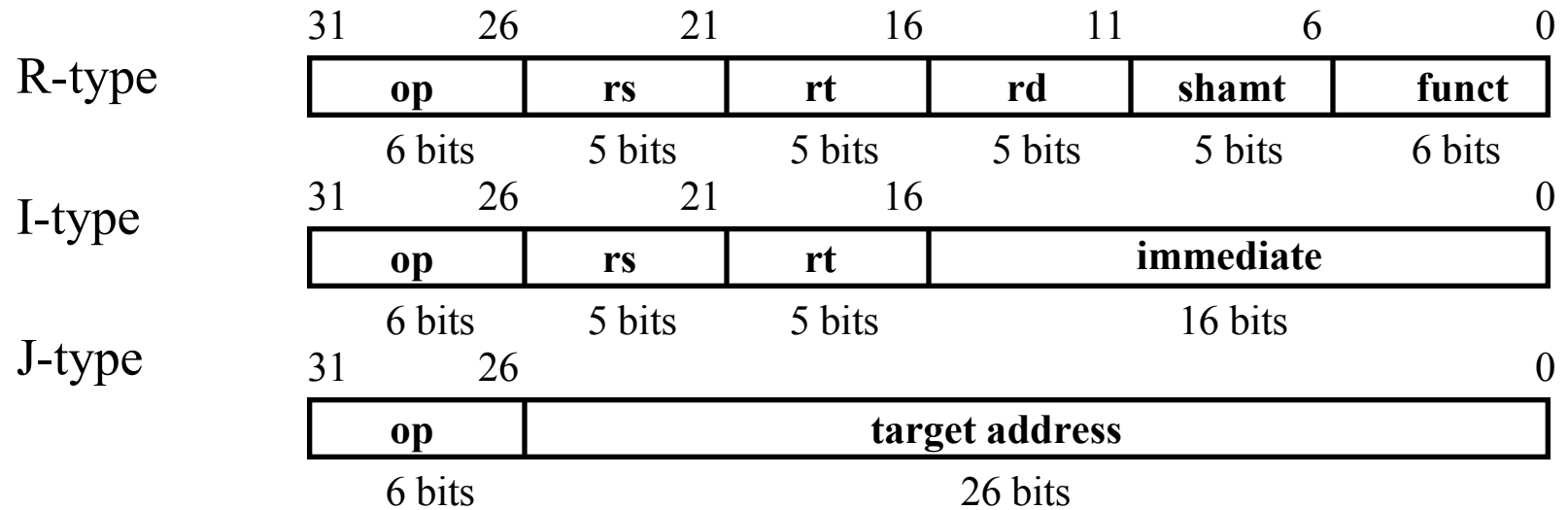
- All MIPS instructions are 32 bits long. The three instruction formats:



The MIPS Subset


- R-type

- *add rd, rs, rt*
- *sub, and, or, slt*

 


- LOAD and STORE

 - *lw rt, rs, imm16*
- *sw rt, rs, imm16*




- BRANCH:



- *beq rs, rt, imm16*

 


Where We're Going – The High-level View

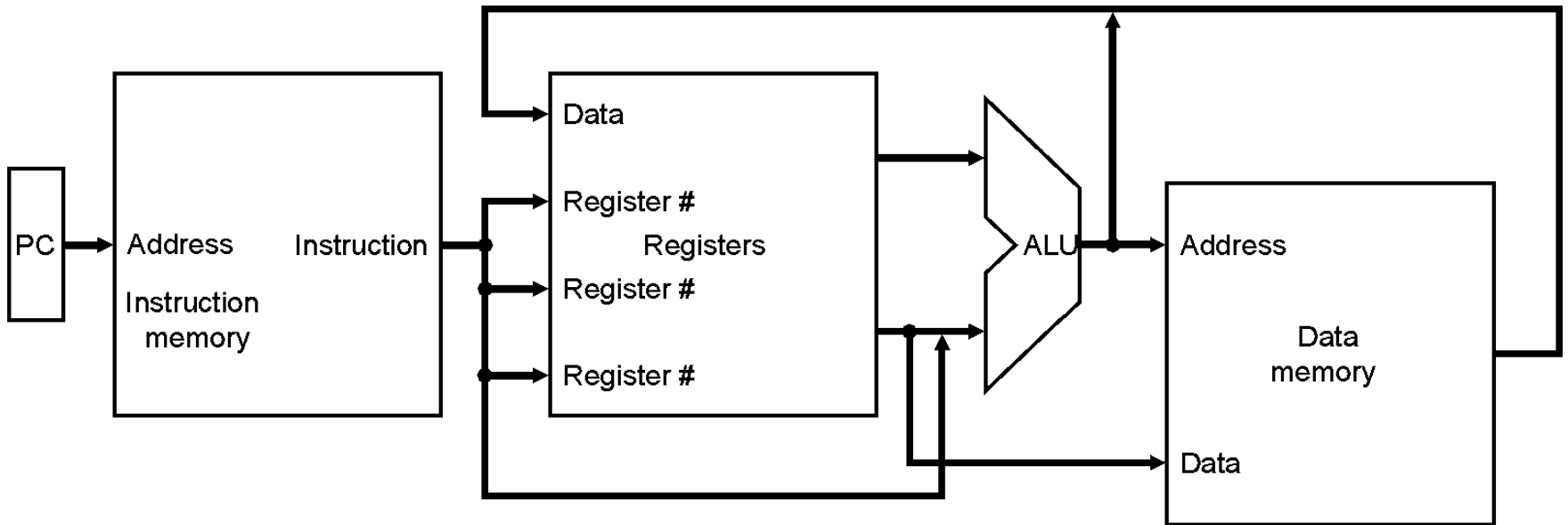

Review: Two Types of Logic Components

 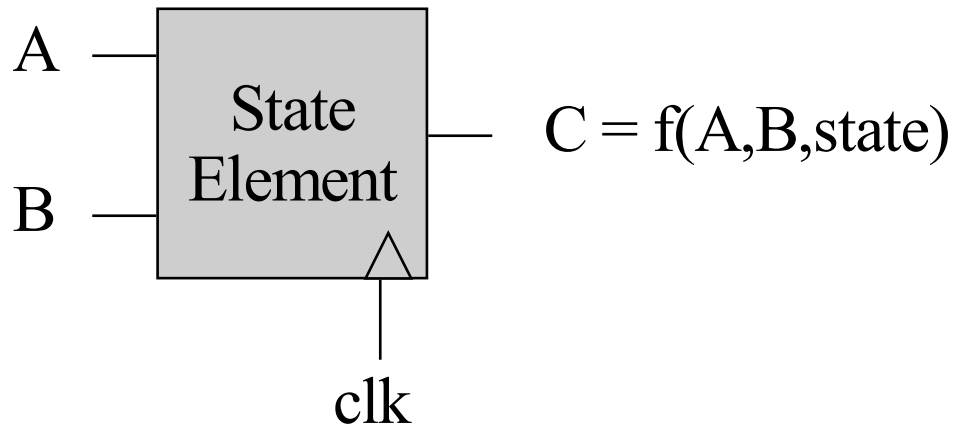

Clocking Methodology

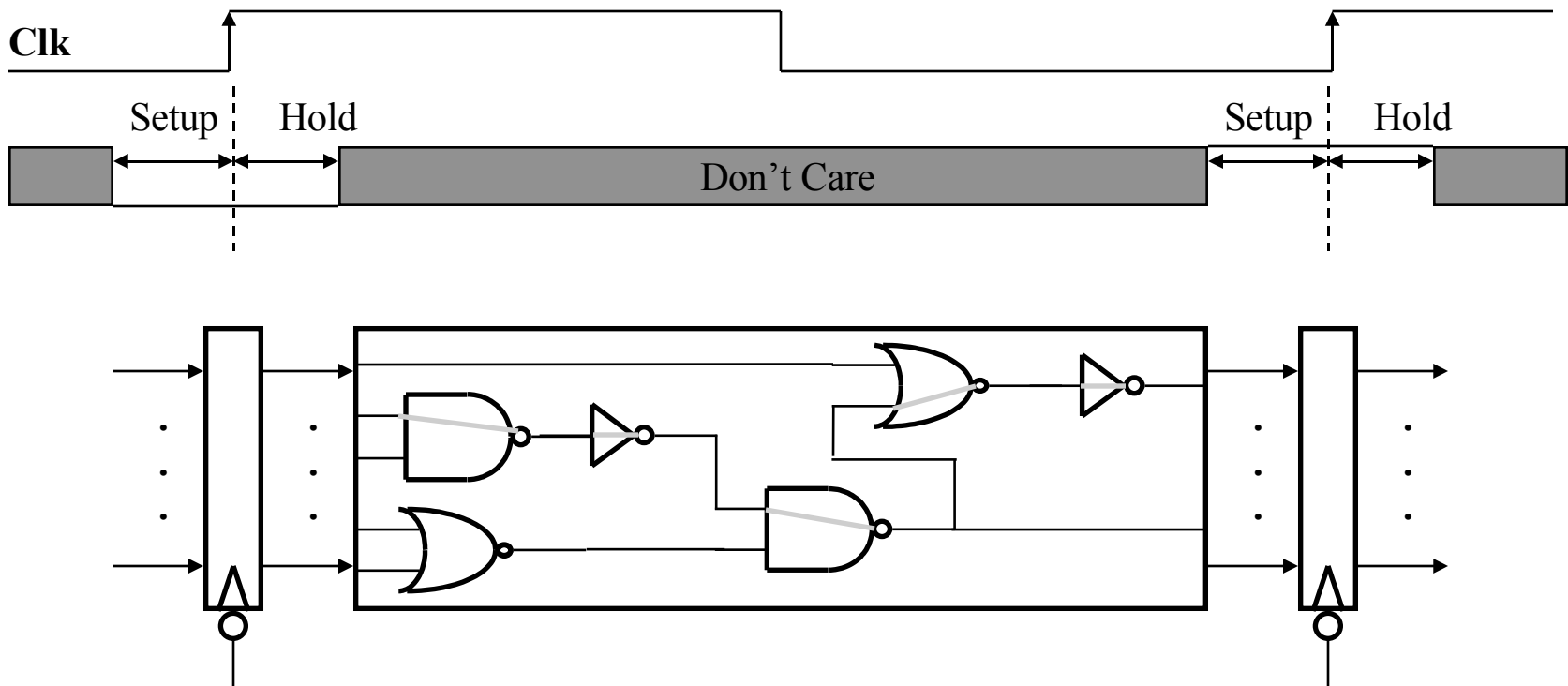

- All storage elements are clocked by the same clock edge

Storage Element: Register


- Register

- Similar to the D Flip Flop except

- N-bit input and output
- Write Enable input


- Write Enable:

 - 0: Data Out will not change
- 1: Data Out will become Data In (on the clock edge)




Storage Element: Register File

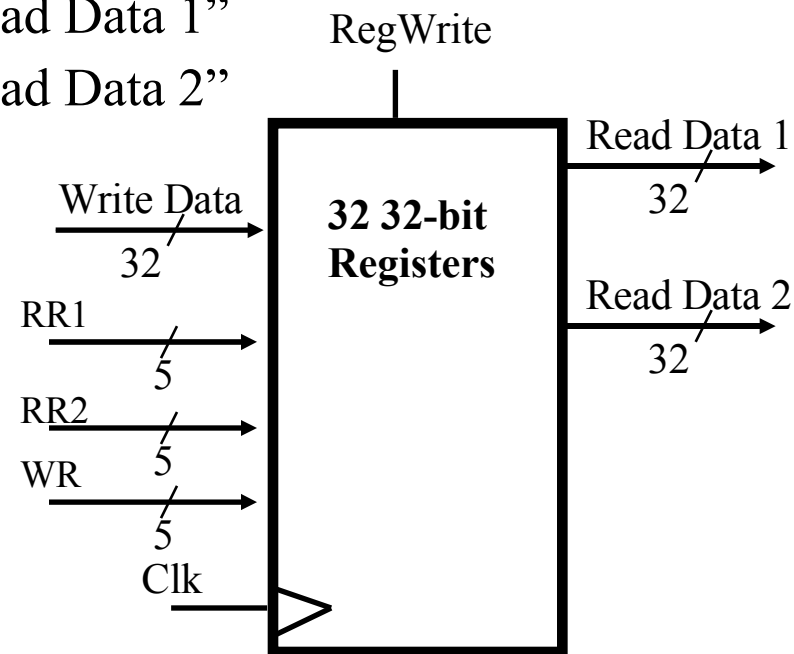- Register File consists of (32) registers:
 - Two 32-bit output buses:
 - One 32-bit input bus: busW
- Register is selected by:
 - **RR1** selects the register to put on bus “Read Data 1”
 - **RR2** selects the register to put on bus “Read Data 2”
 - **WR** selects the register to be written via WriteData when RegWrite is 1
- Clock input (CLK)



Storage Element: Memory

- Memory
 - Two input buses: WriteData, Address
 - One output bus: ReadData
- Memory word is selected by:
 - Address selects the word to put on ReadData bus
 - MemWrite = 1: address selects the memory word to be written via the WriteData bus
- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - Address valid => ReadData valid after “access time.”

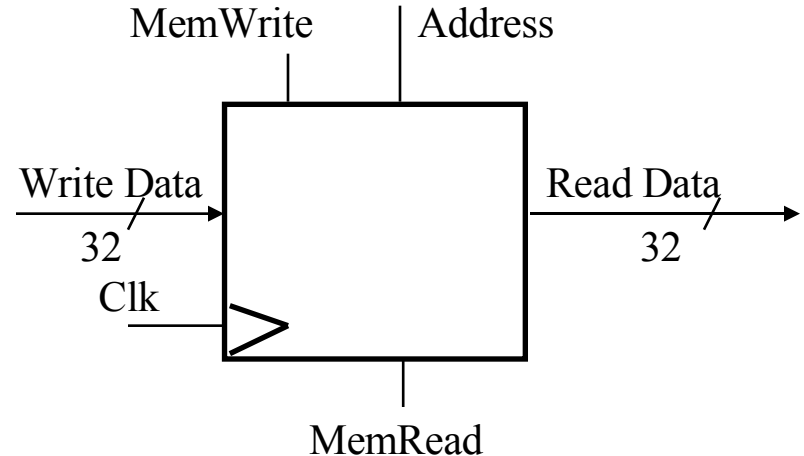

Register Transfer Language (RTL)

- is a mechanism for describing the movement and manipulation of data between storage elements:


$R[3] \leftarrow R[5] + R[7]$

$PC \leftarrow PC + 4 + R[5]$

$R[rd] \leftarrow R[rs] + R[rt]$


$R[rt] \leftarrow Mem[R[rs] + immed]$

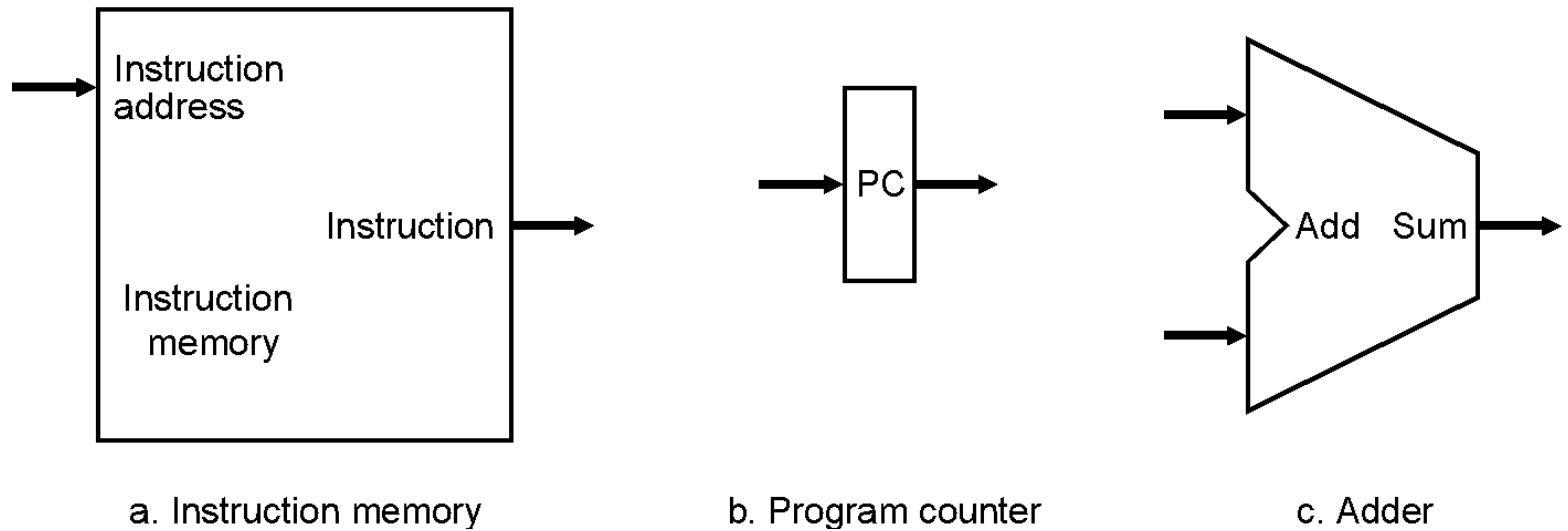Instruction Fetch and Program Counter Management





Overview of the Instruction Fetch Unit

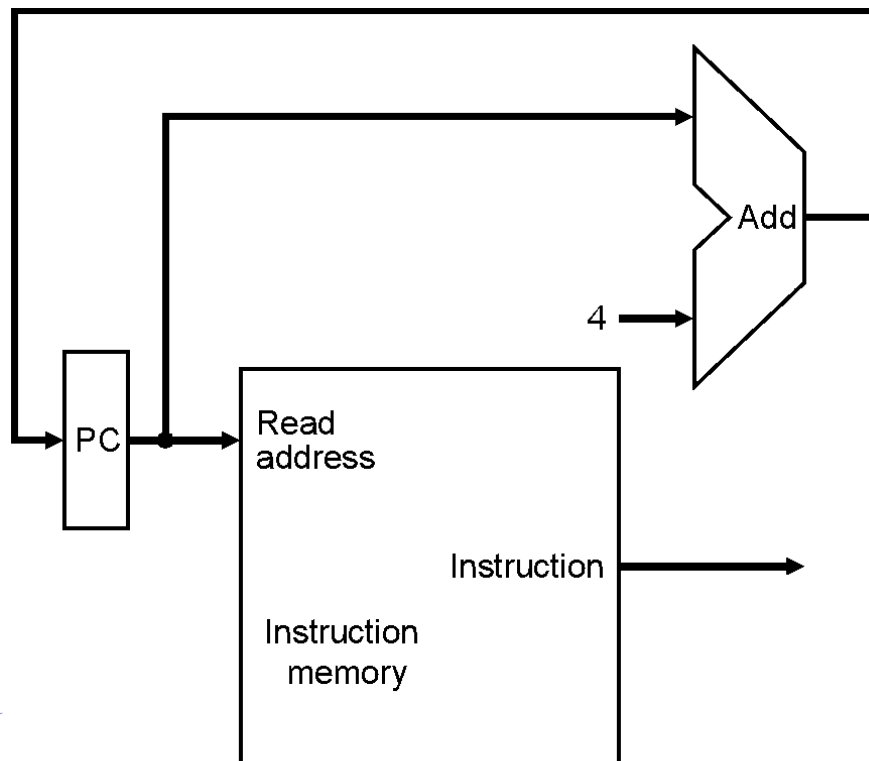- The common RTL operations
 - Fetch the Instruction: $inst \leftarrow mem[PC]$
 - Update the program counter:
 - Sequential Code: $PC \leftarrow PC + 4$
 - Branch and Jump $PC \leftarrow$ “something else”



Datapath for Register-Register Operations

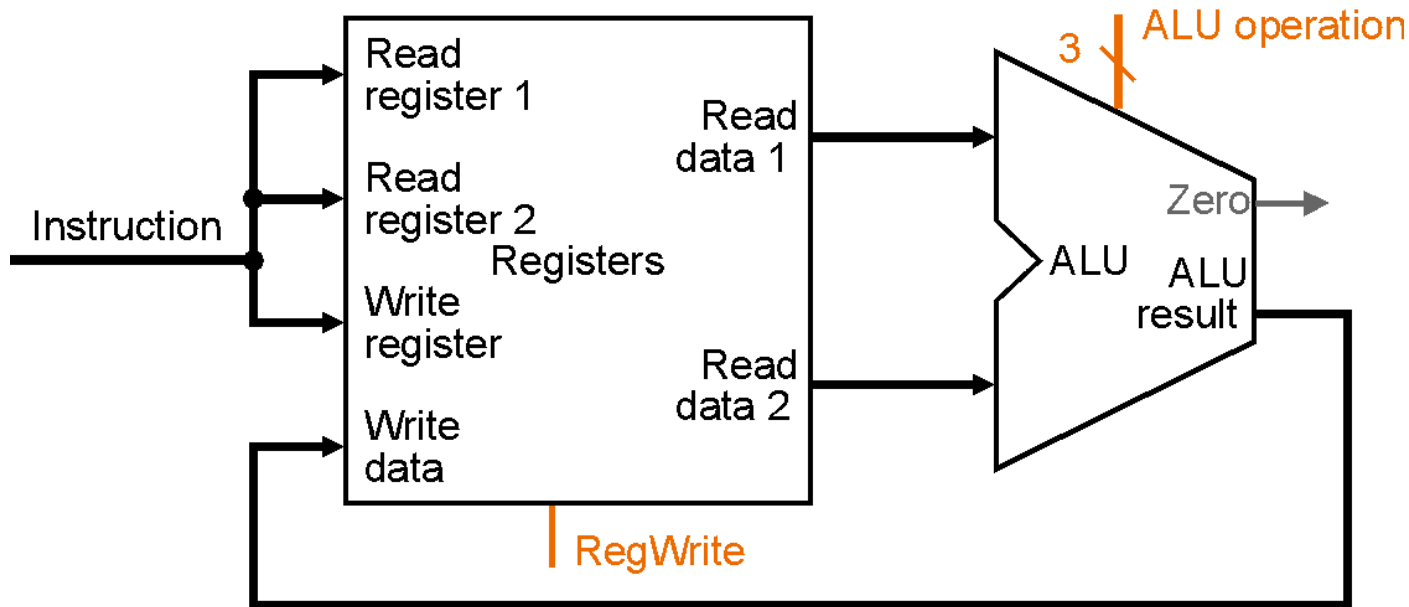
 
- $R[rd] \leftarrow R[rs] \text{ op } R[rt]$ Example: *add rd, rs, rt*
 - RR1, RR2, and WR comes from instruction's rs, rt, and rd fields
 - *ALUoperation* and *RegWrite*: control logic after decoding instruction



Datapath for Load Operations

$R[rt] \leftarrow \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$



Example: *lw rt, rs, imm16*

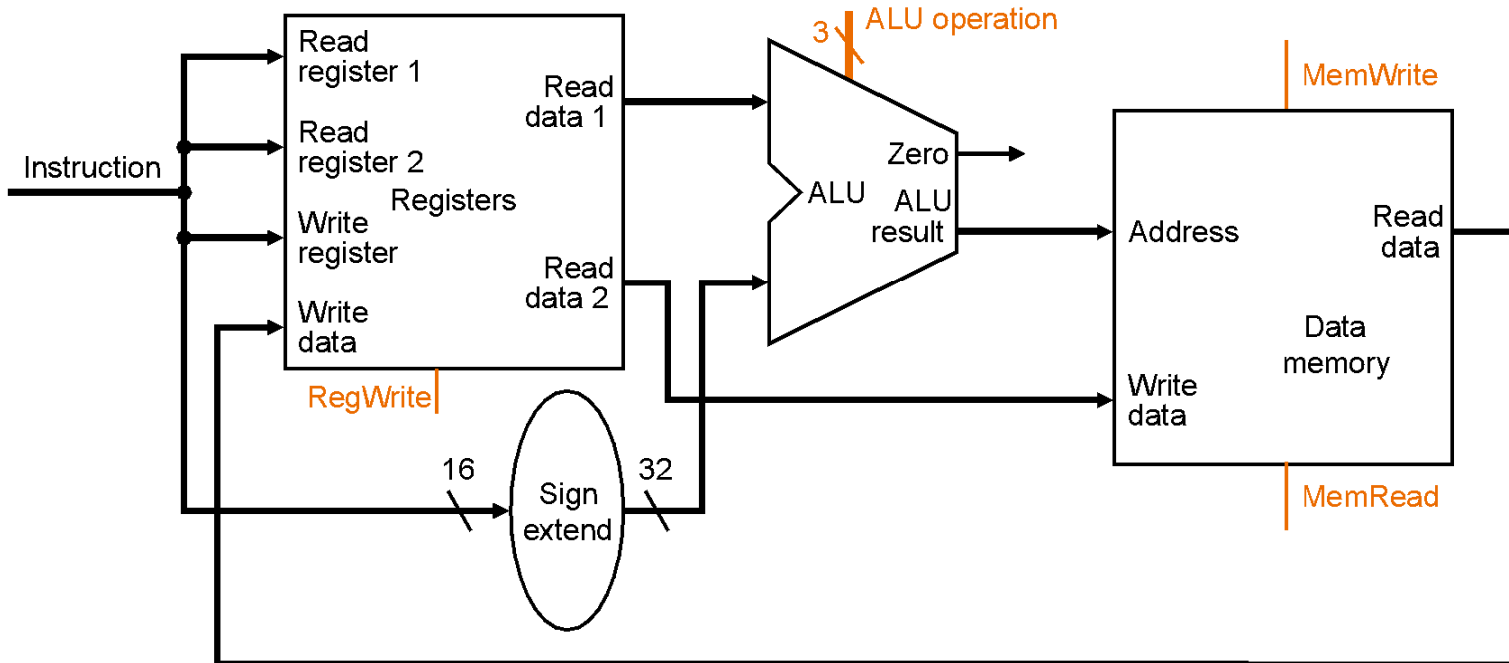 

Datapath for Store Operations

$\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] \leftarrow \text{R}[\text{rt}]$



Example: *sw rt, rs, imm16*

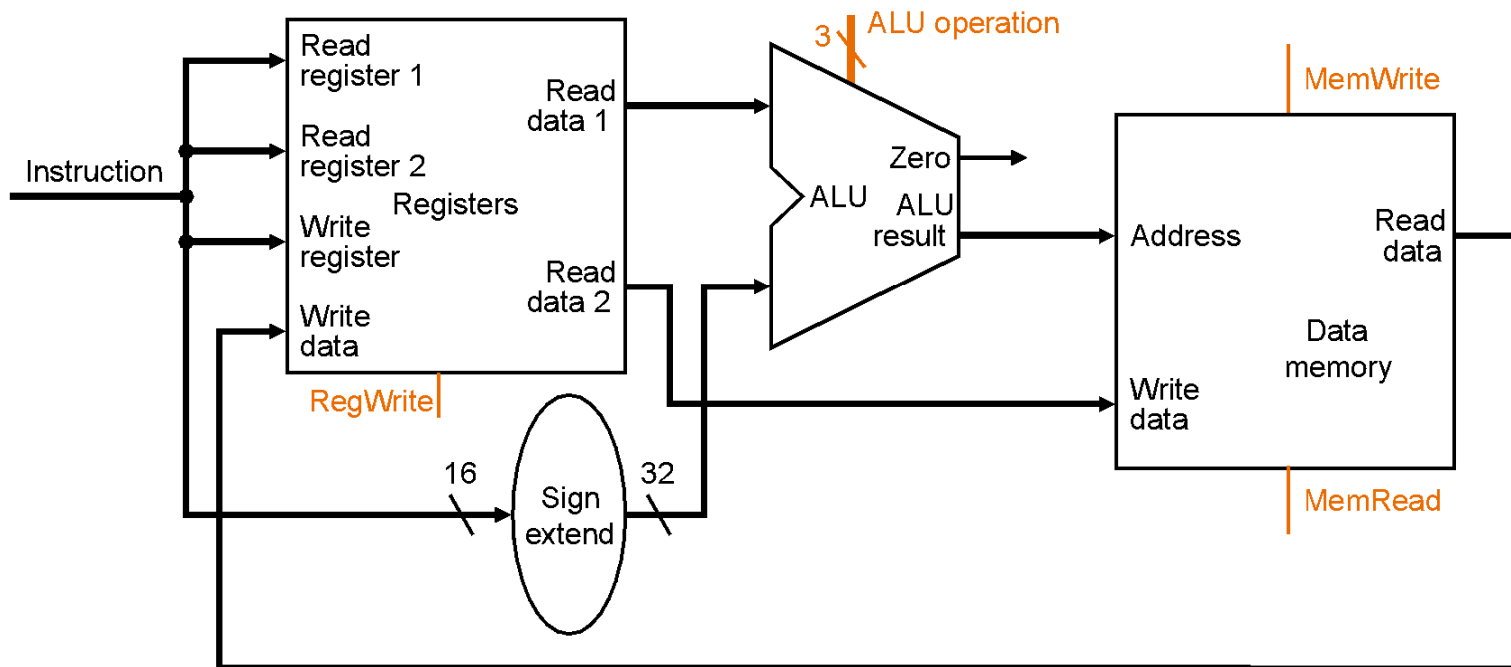 

Datapath for Branch Operations

$Z \leftarrow (rs == rt); \text{ if } Z, PC = PC + 4 + \text{imm16}; \text{ else } PC = PC + 4$

beq rs, rt, imm16

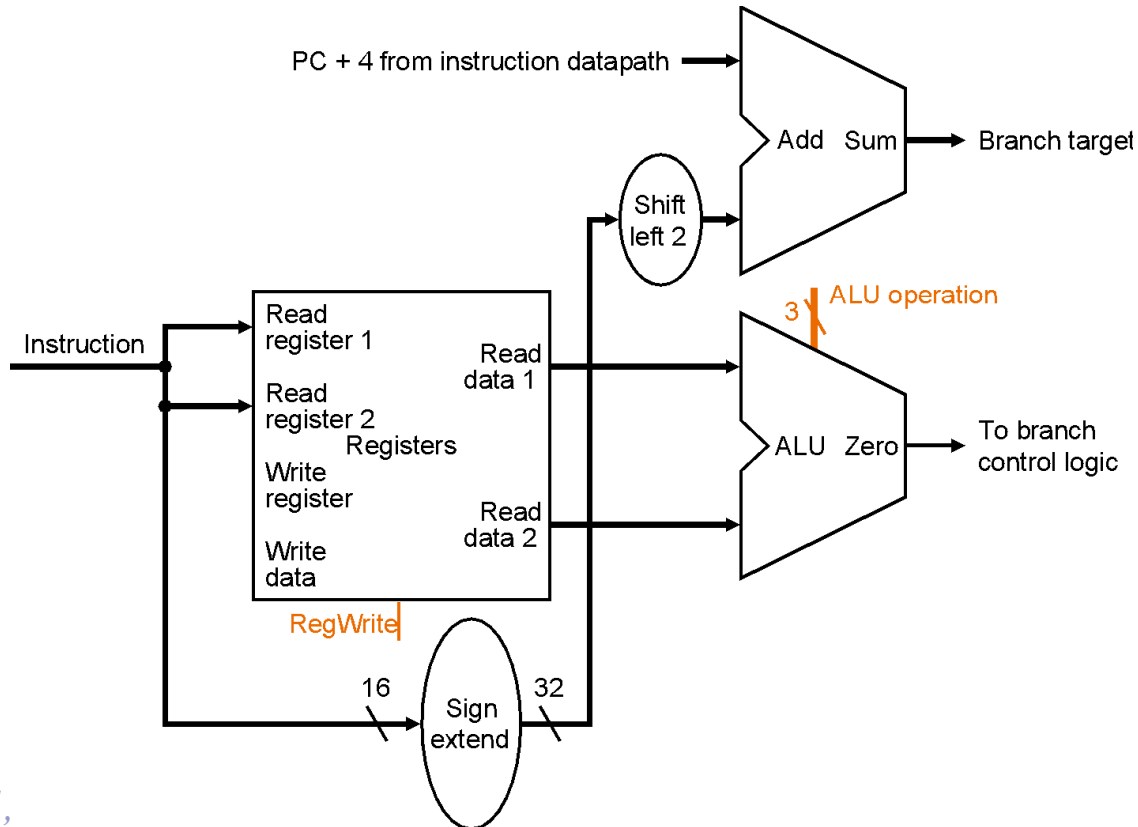 


Binary Arithmetic for the Next Address


- In theory, the PC is a 32-bit byte address into the instruction memory:
 - Sequential operation: $PC\langle 31:0 \rangle = PC\langle 31:0 \rangle + 4$
 - Branch operation: $PC\langle 31:0 \rangle = PC\langle 31:0 \rangle + 4 + \text{SignExt}[\text{Imm16}] * 4$
- The magic number “4” always comes up because:
 - The 32-bit PC is a byte address
 - And all our instructions are 4 bytes (32 bits) long
 - The 2 LSBs of the 32-bit PC are always zeros
 - There is no reason to have hardware to keep the 2 LSBs
- In practice, we can simplify the hardware by using a 30-bit $PC\langle 31:2 \rangle$:
 - Sequential operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1$
 - Branch operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1 + \text{SignExt}[\text{Imm16}]$
 - In either case: Instruction Memory Address = $PC\langle 31:2 \rangle$ concat “00”

Putting it All Together: A Single Cycle Datapath

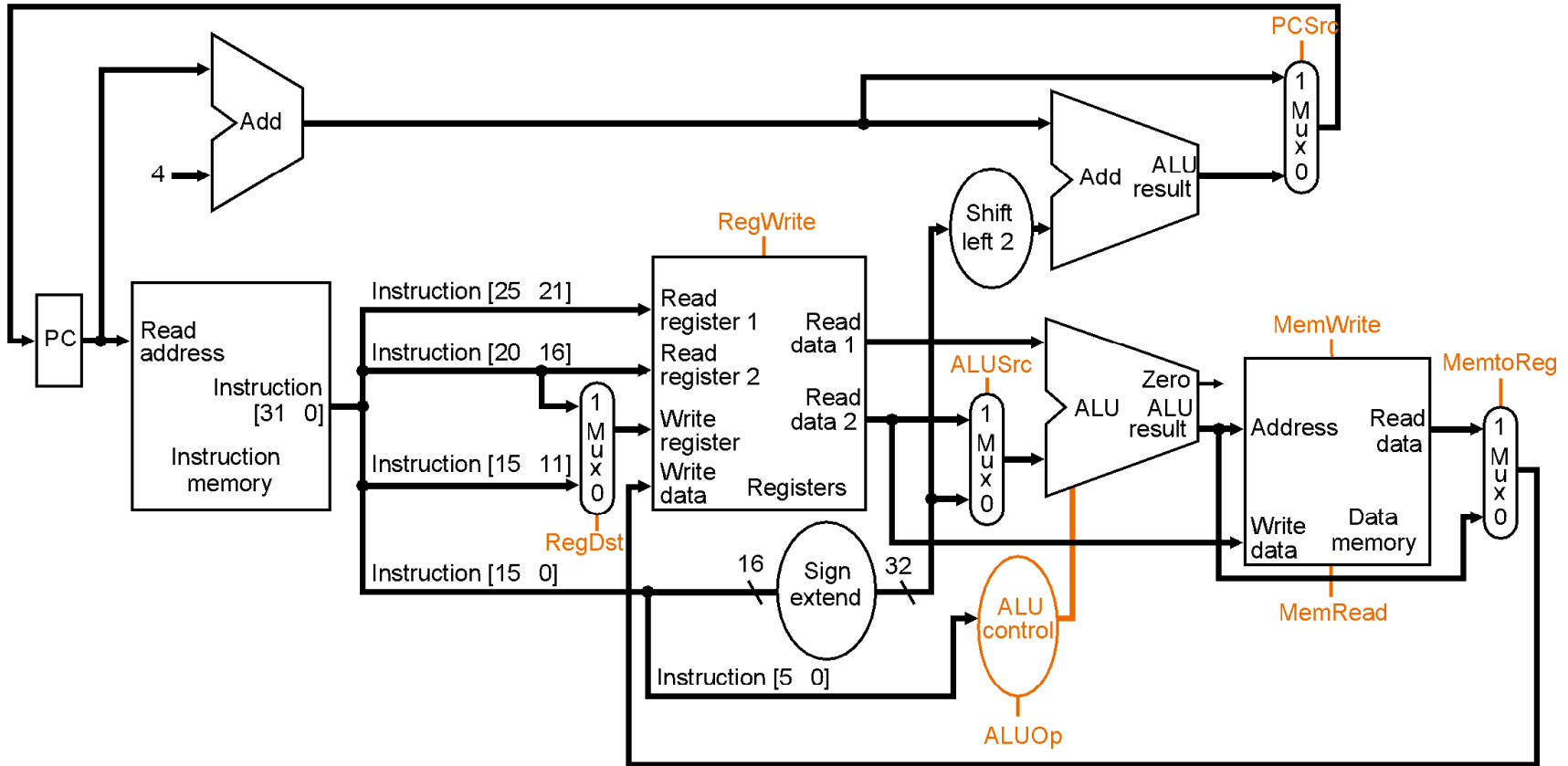
- We have everything except control signals




The R-Format (e.g. *add*) Datapath

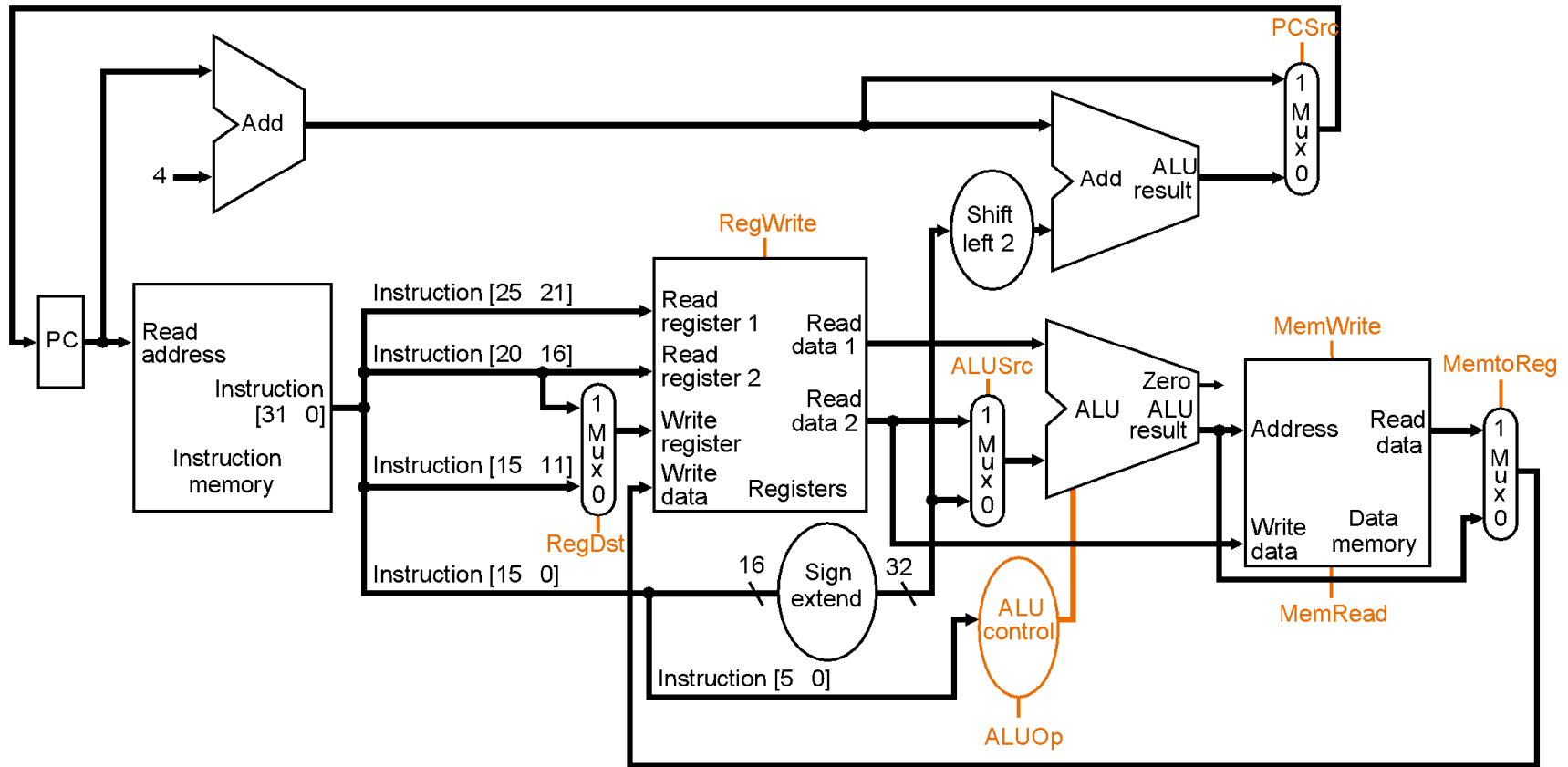


The Load Datapath

 

The store Datapath

 

The beq Datapath

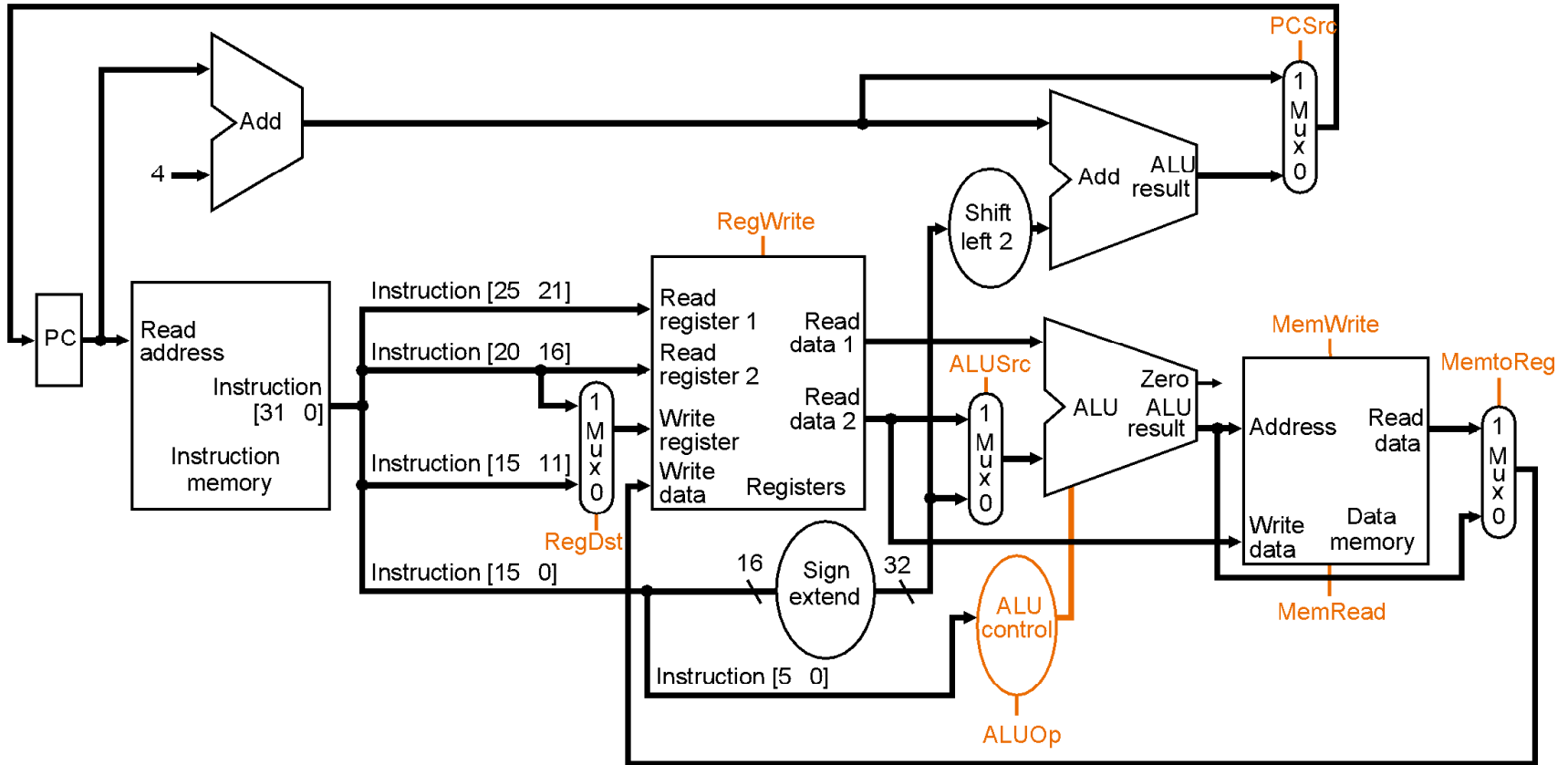

Key Points

- CPU is just a collection of state and combinational logic
- We just designed a very rich processor, at least in terms of functionality
- Performance = Insts * CPI * Cycle Time
 - where does the single-cycle machine fit in?