



# **Power Electronics**

## **Single Phase Controlled Rectifiers**

**Dr. Firas Obeidat**

# Table of contents

1

- **Single Phase Controlled Half Wave Rectifier- Resistive Load**

2

- **Single Phase Controlled Half Wave Rectifier- RL Load**

3

- **Single Phase Full Wave Rectifier- Resistive Load**

4

- **Single Phase Full Wave Rectifier- RL Load, Discontinuous Current**

5

- **Single Phase Full Wave Rectifier- RL Load, Continuous Current**

6

- **Single Phase Full Wave Rectifier- RL Load,  $L \gg R$**



6

- **Single-Phase Bridge Half-Controlled Rectifier**

# Single Phase Controlled Half Wave Rectifier
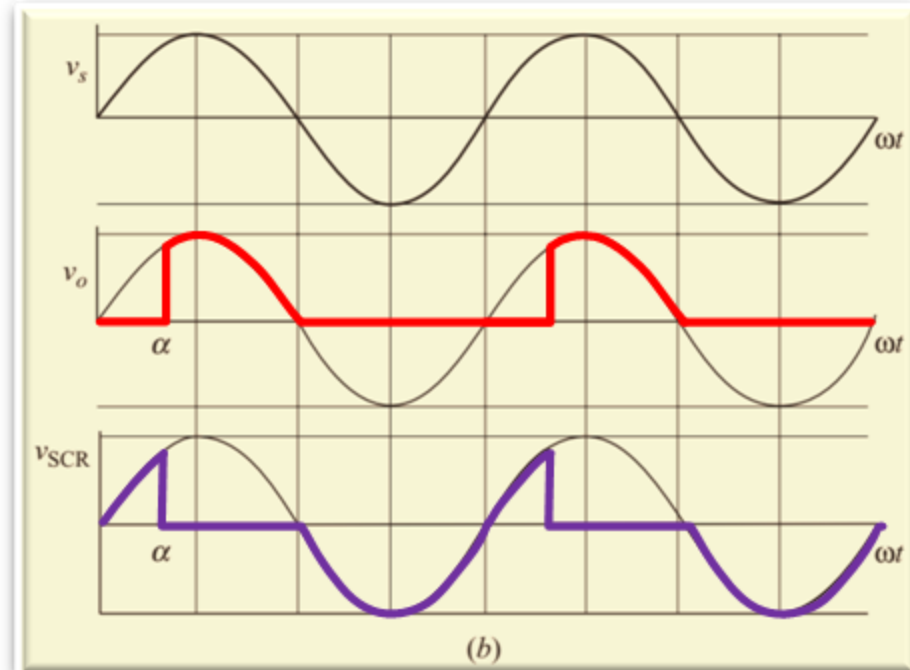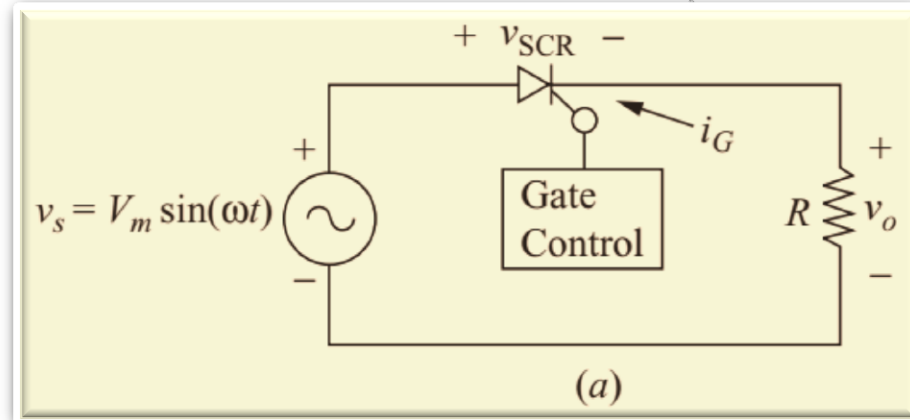
## Resistive Load

- A way to control the output of a half-wave rectifier is to use an SCR instead of a diode.
- Two conditions must be met before the SCR can conduct:
  1. The SCR must be forward-biased ( $v_{SCR} > 0$ ).
  2. A current must be applied to the gate of the SCR.
- The SCR will not begin to conduct as soon as the source becomes positive. Conduction is delayed until a gate current is applied, which is the basis for using the SCR as a means of control. Once the SCR is conducting, the gate current can be removed and the SCR remains on until the current goes to zero.



# Single Phase Controlled Half Wave Rectifier

## Resistive Load

- If a gate signal is applied to the SCR at  $\omega t = \alpha$ , where  $\alpha$  is the delay (firing or triggering) angle. The average (dc) voltage across the load resistor and the average (dc) current are

$$V_{dc} = V_o = \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d(\omega t) = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

- The *rms* voltage across the resistor and the *rms* current are computed from

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_o^2(\omega t) d(\omega t)} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\pi} [V_m \sin(\omega t)]^2 d(\omega t)} = \frac{V_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

$$V_{rms} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{V_m}{2R} \sqrt{\frac{1}{\pi} \left( \pi - \alpha + \frac{\sin 2\alpha}{2} \right)}$$

- The power absorbed by the resistor is

$$P_{ac} = \frac{V_{rms}^2}{R}$$

# Single Phase Controlled Half Wave Rectifier

## Resistive Load

**Example:** The single-phase half wave rectifier has a purely resistive load of  $R$  and the delay angle is  $\alpha=\pi/2$ , determine:  $V_{dc}$ ,  $I_{dc}$ ,  $V_{rms}$ ,  $I_{rms}$ .

$$V_{dc} = \frac{V_m}{2\pi} \left(1 + \cos \frac{\pi}{2}\right) = 0.1592V_m$$

$$I_{dc} = \frac{V_m}{2\pi R} \left(1 + \cos \frac{\pi}{2}\right) = 0.1592 \frac{V_m}{R}$$

$$V_{rms} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left(\pi - \frac{\pi}{2} + \frac{\sin(2\frac{\pi}{2})}{2}\right)} = 0.3536V_m$$

$$I_{rms} = \frac{V_m}{2R} \sqrt{\frac{1}{\pi} \left(\pi - \frac{\pi}{2} + \frac{\sin(2\frac{\pi}{2})}{2}\right)} = 0.3536 \frac{V_m}{R}$$

# Single Phase Controlled Half Wave Rectifier

## Resistive Load

**Example:** Design a circuit to produce an average voltage of 40V across a 100Ω load resistor from a 120V<sub>rms</sub> 60-Hz ac source. Determine the power absorbed by the resistance and the power factor.

$$V_{dc} = \frac{V_m}{2\pi} (1 + \cos \alpha) \quad \text{SO} \quad \alpha = \cos^{-1} \left[ V_o \left( \frac{2\pi}{V_m} \right) - 1 \right]$$
$$= \cos^{-1} \left\{ 40 \left[ \frac{2\pi}{\sqrt{2}(120)} \right] - 1 \right\} = 61.2^\circ = 1.07 \text{ rad}$$

$$V_{rms} = \frac{V_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$
$$V_{rms} = \frac{\sqrt{2}(120)}{2} \sqrt{1 - \frac{1.07}{\pi} + \frac{\sin[2(1.07)]}{2\pi}} = 75.6 \text{ V}$$

$$P_R = \frac{V_{rms}^2}{R} = \frac{(75.6)^2}{100} = 57.1 \text{ W}$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{75.6}{100} = 0.756 \text{ A}$$

$$S = V_{s,rms} I_{rms} = 120 \times 0.756 = 90.72 \text{ VA}$$

$$pf = \frac{P_R}{S} = \frac{57.1}{90.72} = 0.629$$

# Single Phase Controlled Half Wave Rectifier

## RL Load

The current is the sum of the forced and natural responses.

$$i(\omega t) = i_f(\omega t) + i_n(\omega t) = \frac{V_m}{Z} \sin(\omega t - \theta) + Ae^{-\omega t/\omega\tau}$$

The constant  $A$  is determined from the initial condition  $\omega t = \alpha$   
 $i(\alpha) = 0$ :

$$i(\alpha) = 0 = \frac{V_m}{Z} \sin(\alpha - \theta) + Ae^{-\alpha/\omega\tau}$$



$$A = \left[ -\frac{V_m}{Z} \sin(\alpha - \theta) \right] e^{\alpha/\omega\tau}$$

Substituting for  $A$  and simplifying,

$$i(\omega t) = \begin{cases} \frac{V_m}{Z} \left[ \sin(\omega t - \theta) - \sin(\alpha - \theta)e^{(\alpha - \omega t)/\omega\tau} \right] & \text{for } \alpha \leq \omega t \leq \beta \\ 0 & \text{otherwise} \end{cases}$$

The **extinction angle  $\beta$**  is defined as the angle at which the current returns to zero, as in the case of the uncontrolled rectifier. When  $\omega t = \beta$
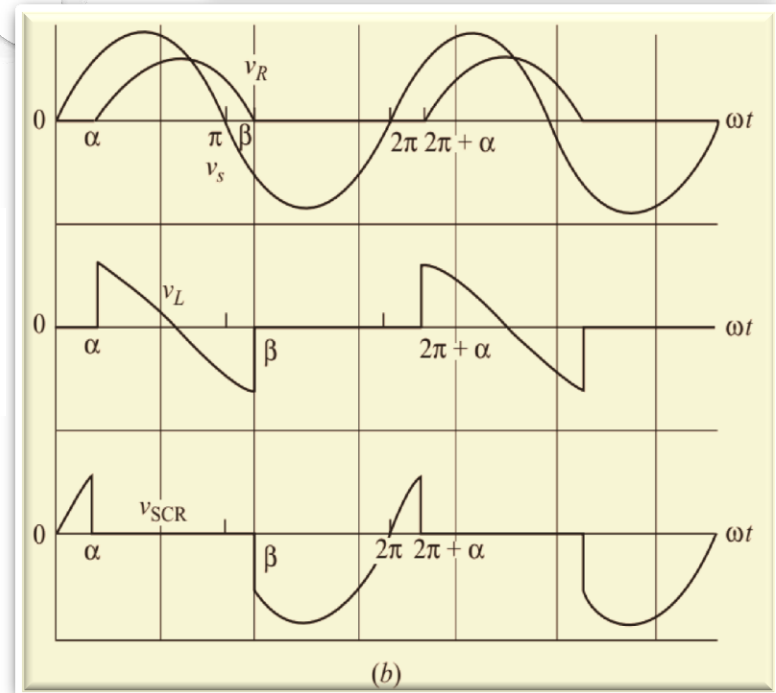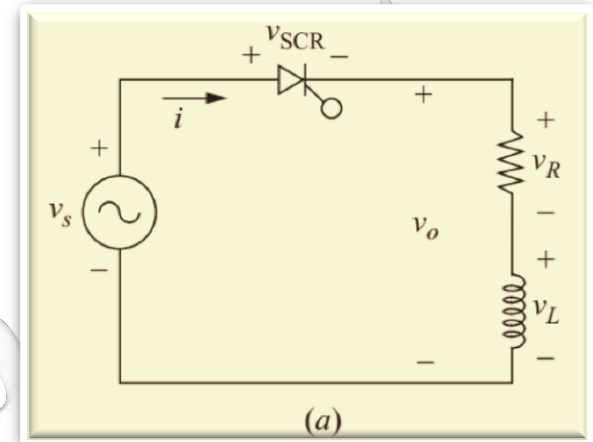
$$i(\beta) = 0 = \frac{V_m}{Z} \left[ \sin(\beta - \theta) - \sin(\alpha - \theta)e^{(\alpha - \beta)/\omega\tau} \right]$$



# Single Phase Controlled Half Wave Rectifier

## RL Load

The above equation must be solved numerically for  $\beta$ . The angle  $(\beta - \alpha)$  is called the conduction angle  $\gamma$ .

The average (dc) output voltage is

$$V_{dc} = V_o = \frac{1}{2\pi} \int_{\alpha}^{\beta} V_m \sin(\omega t) d(\omega t) = \frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$$

The average (dc) output current is

$$I_{dc} = I_o = \frac{1}{2\pi} \int_{\alpha}^{\beta} i(\omega t) d(\omega t) \quad \text{or} \quad I_{dc} = I_o = \frac{V_m}{2\pi R} (\cos \alpha - \cos \beta)$$

The *rms* current is computed from

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} i^2(\omega t) d(\omega t)}$$

Or it can be written as

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} (V_m \sin \omega t)^2 d\omega t} = \sqrt{\frac{V_m^2}{4\pi} (\beta - \alpha - \frac{1}{2} \sin 2\beta + \frac{1}{2} \sin 2\alpha)}$$

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{V_{rms}}{\sqrt{R^2 + (\omega L)^2}} = \frac{1}{\sqrt{R^2 + (\omega L)^2}} \sqrt{\frac{V_m^2}{4\pi} (\beta - \alpha - \frac{1}{2} \sin 2\beta + \frac{1}{2} \sin 2\alpha)}$$



# Single Phase Controlled Half Wave Rectifier

## RL Load

**Example:** For the circuit of controlled half-wave rectifier with RL Load, the source is  $120V_{\text{rms}}$  at 60 Hz,  $R=20\Omega$ ,  $L=0.04\text{H}$ , and the delay angle is  $45^\circ$ . Determine (a) an expression for  $i(\omega t)$ , (b) the *rms* current, (c) the power absorbed by the load, and (d) the power factor.

(a)

$$V_m = 120\sqrt{2} = 169.7 \text{ V}$$

$$Z = [R^2 + (\omega L)^2]^{0.5} = [20^2 + (377*0.04)^2]^{0.5} = 25.0 \Omega$$

$$\theta = \tan^{-1}(\omega L/R) = \tan^{-1}(377*0.04/20) = 0.646 \text{ rad}$$

$$\omega\tau = \omega L/R = 377*0.04/20 = 0.754$$

$$\alpha = 45^\circ = 0.785 \text{ rad}$$

$$i(\omega t) = 6.78 \sin(\omega t - 0.646) - 2.67e^{-\omega t/0.754} \quad \text{A} \quad \text{for } \alpha \leq \omega t \leq \beta$$

(b)

$$I_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_{0.785}^{3.79} [6.78 \sin(\omega t - 0.646) - 2.67e^{-\omega t/0.754}]^2 d(\omega t)} = 3.26 \text{ A}$$

(c)


$$P = I_{\text{rms}}^2 R = (3.26)^2(20) = 213 \text{ W}$$

(c)


$$\text{pf} = \frac{P}{S} = \frac{213}{(120)(3.26)} = 0.54$$
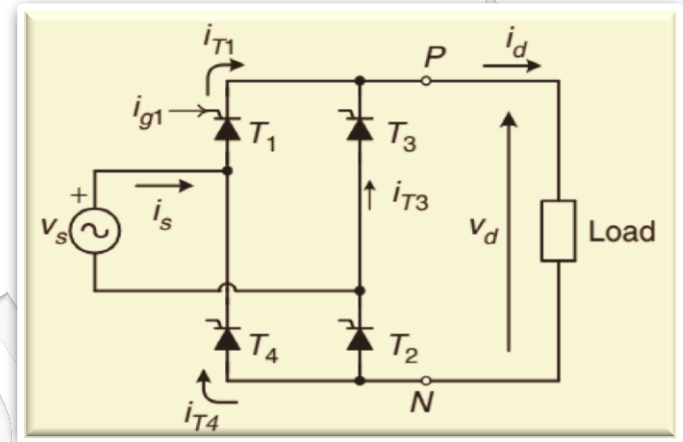
# Single Phase Controlled Full Wave Rectifier

- The first figure shows a fully controlled bridge rectifier, which uses four thyristors to control the average load voltage.
- Thyristors  $T_1$  and  $T_2$  must be fired simultaneously during the positive half wave of the source voltage  $v_s$  to allow conduction of current. To ensure simultaneous firing, thyristors  $T_1$  and  $T_2$  use the same firing signal.
- Alternatively, thyristors  $T_3$  and  $T_4$  must be fired simultaneously during the negative half wave of the source voltage.



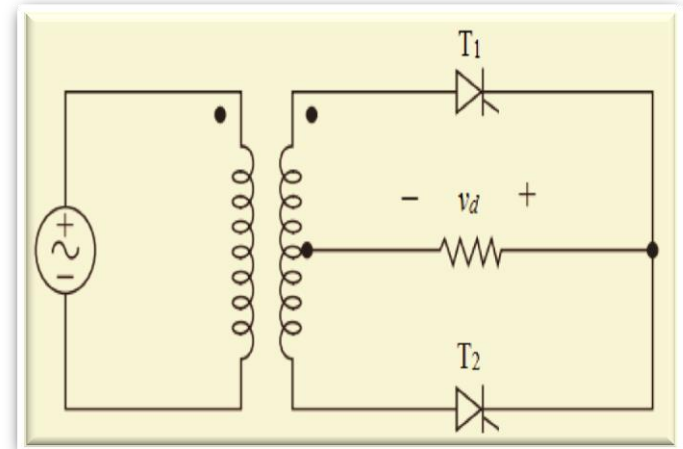- For the center-tapped transformer rectifier,  $T_1$  is forward-biased when  $v_s$  is positive, and  $T_2$  is forward-biased when  $v_s$  is negative, but each will not conduct until it receives a gate signal.



- The delay angle is the angle interval between the forward biasing of the SCR and the gate signal application. If the delay angle is zero, the rectifiers behave exactly as uncontrolled rectifiers with diodes.

# Single Phase Controlled Full Wave Rectifier

## Resistive Load

The average component of the output voltage and current waveforms are determined from

$$V_{dc} = V_o = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin(\omega t) d(\omega t) = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{\pi R} (1 + \cos \alpha)$$

The *rms* component of the output voltage and current waveforms are determined from


$$V_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 d\omega t} = V_m \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{V_m}{R} \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}$$

The power delivered to the load is

$$p = I_{rms}^2 R$$

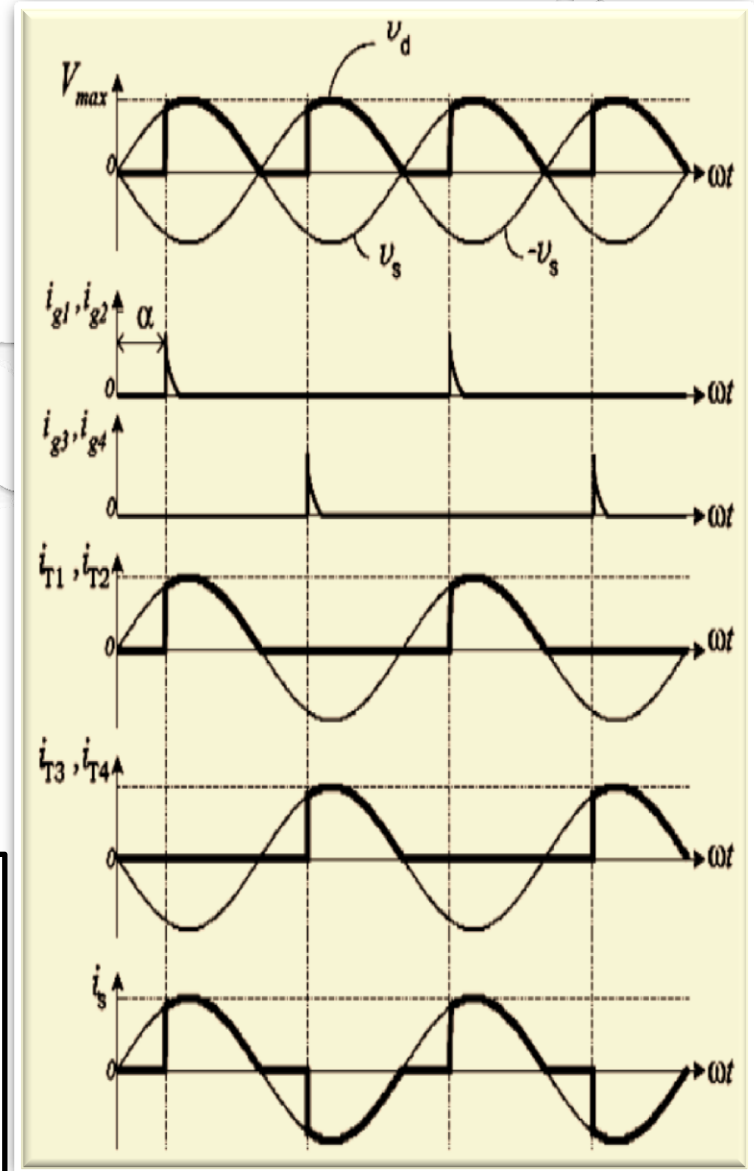The *rms* current in the source is the same as the *rms* current in the load.



# Single Phase Controlled Full Wave Rectifier

## Resistive Load

**Example:** The full-wave controlled bridge rectifier has an ac input of  $120V_{\text{rms}}$  at 60 Hz and a  $20\Omega$  load resistor. The delay angle is  $40^\circ$ . Determine the average current in the load, the power absorbed by the load, and the source voltamperes.

$$V_{dc} = \frac{V_m}{\pi} (1 + \cos \alpha) = \frac{\sqrt{2}(120)}{\pi} (1 + \cos 40^\circ) = 95.4 \text{ V}$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{95.6}{20} = 4.77 \text{ A}$$

$$I_{\text{rms}} = \frac{\sqrt{2}(120)}{20} \sqrt{\frac{1}{2} - \frac{0.698}{2\pi} + \frac{\sin[2(0.698)]}{4\pi}} = 5.80 \text{ A}$$

$$P = I_{\text{rms}}^2 R = (5.80)^2 (20) = 673 \text{ W}$$

The *rms* current in the source is also 5.80 A, and the apparent power of the source is


$$S = V_{\text{rms}} I_{\text{rms}} = (120)(5.80) = 696 \text{ VA}$$

$$\text{pf} = \frac{P}{S} = \frac{672}{696} = 0.967$$

# Single Phase Controlled Full Wave Rectifier
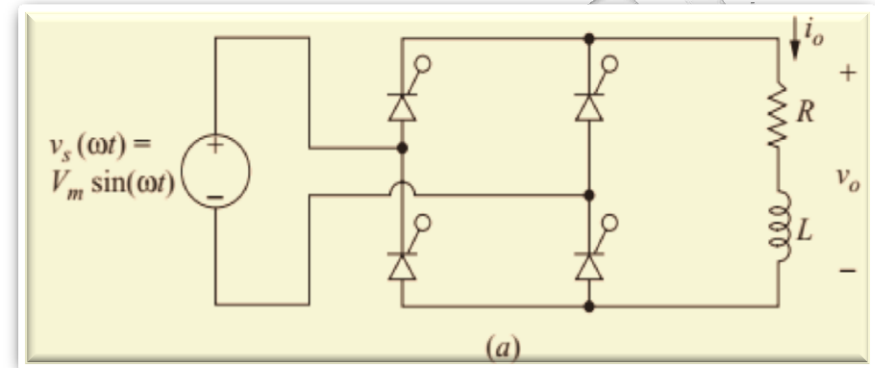
## RL Load, Discontinuous Current

Load current for a controlled full-wave rectifier with an  $RL$  load (fig. a) can be either continuous or discontinuous.



➤ For discontinuous current

1- at  $\omega t=0$  with zero load current, SCRs  $T_1$  and  $T_2$  in the bridge rectifier will be forward-biased and  $T_3$  and  $T_4$  will be reverse-biased as the source voltage becomes positive.

2- Gate signals are applied to  $T_1$  and  $T_2$  at  $\omega t=\alpha$ , turning  $T_1$  and  $T_2$  on. With  $T_1$  and  $T_2$  on, the load voltage is equal to the source voltage.

The output current can be given as

$$i_o(\omega t) = \frac{V_m}{Z} \left[ \sin(\omega t - \theta) - \sin(\alpha - \theta) e^{-(\omega t - \alpha)/\omega\tau} \right] \quad \text{for } \alpha \leq \omega t \leq \beta$$


$$Z = \sqrt{R^2 + (\omega L)^2} \quad \theta = \tan^{-1}\left(\frac{\omega L}{R}\right) \quad \text{and} \quad \tau = \frac{L}{R}$$

# Single Phase Controlled Full Wave Rectifier
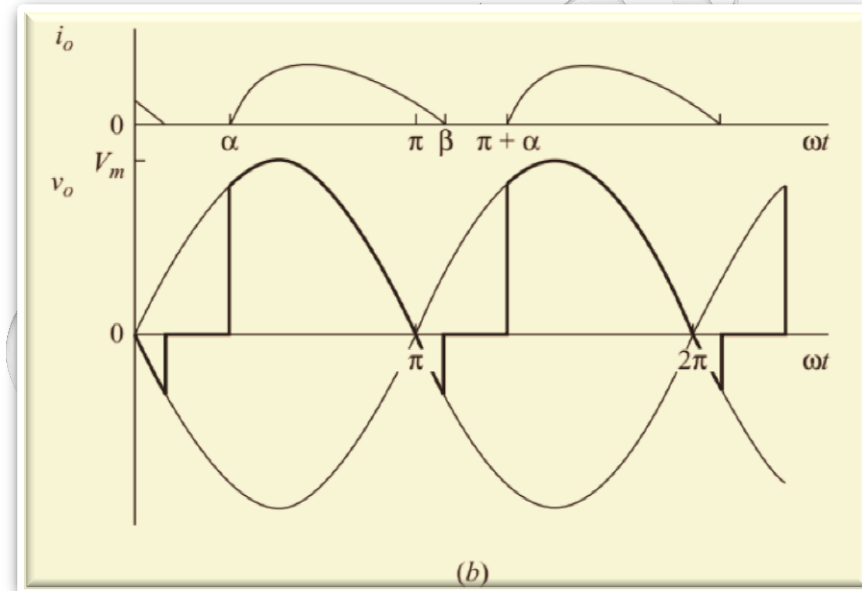
## RL Load, Discontinuous Current

The above current function becomes zero at  $\omega t = \beta$ . If  $\beta < \pi + \alpha$ , the current remains at zero until  $\omega t = \pi + \alpha$  when gate signals are applied to  $T_3$  and  $T_4$  which are then forward-biased and begin to conduct. This mode of operation is called *discontinuous current* as shown in fig. b.

$$\beta < \pi + \alpha \rightarrow \text{Discontinuous current}$$



Analysis of the controlled full-wave rectifier operating in the discontinuous current mode is identical to that of the controlled half-wave rectifier except that the period for the output current is  $\pi$  rather than  $2\pi$  rad.

# Single Phase Controlled Full Wave Rectifier

## RL Load, Discontinuous Current

The average (dc) output voltage is

$$V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\beta} V_m \sin \omega t \, d\omega t = \frac{V_m}{\pi} (\cos \alpha - \cos \beta)$$

The average (dc) output current is

$$I_{dc} = I_o = \frac{1}{2\pi} \int_{\alpha}^{\beta} i(\omega t) \, d(\omega t) \quad \text{or} \quad I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{\pi R} (\cos \alpha - \cos \beta)$$

The *rms* voltage is computed from

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\beta} (V_m \sin \omega t)^2 \, d\omega t} = \sqrt{\frac{V_m^2}{2\pi} (\beta - \alpha - \frac{1}{2} \sin 2\beta + \frac{1}{2} \sin 2\alpha)}$$

The *rms* current is computed from

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_{\alpha}^{\beta} i^2(\omega t) \, d(\omega t)}$$

Or it can be written as

$$I_{rms} = \frac{V_{rms}}{Z} = \frac{V_{rms}}{\sqrt{R^2 + (\omega L)^2}} = \frac{1}{\sqrt{R^2 + (\omega L)^2}} \sqrt{\frac{V_m^2}{2\pi} (\beta - \alpha - \frac{1}{2} \sin 2\beta + \frac{1}{2} \sin 2\alpha)}$$

# Single Phase Controlled Full Wave Rectifier

## RL Load, Discontinuous Current

**Example:** A controlled full-wave bridge rectifier has a source of  $120V_{\text{rms}}$  at  $60\text{Hz}$ ,  $R=10\Omega$ ,  $L=20\text{mH}$ , and  $\alpha=60^\circ$ . Determine (a) an expression for load current, (b) the average load current, and (c) the power absorbed by the load.

$$V_m = \frac{120}{\sqrt{2}} = 169.7 \text{ V}$$

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right) = \tan^{-1}\left[\frac{(377)(0.02)}{10}\right] = 0.646 \text{ rad}$$

$$Z = \sqrt{R^2 + (\omega L)^2} = \sqrt{10^2 + [(377)(0.02)]^2} = 12.5 \Omega$$

$$\omega\tau = \frac{\omega L}{R} = \frac{(377)(0.02)}{10} = 0.754 \text{ rad}$$

$$\alpha = 60^\circ = 1.047 \text{ rad}$$

(a) 
$$i_o(\omega t) = 13.6 \sin(\omega t - 0.646) - 21.2e^{-\omega t/0.754} \text{ A} \quad \text{for } \alpha \leq \omega t \leq \beta$$

Solving  $i_o(\beta) = 0$  numerically for  $\beta$ ,  $\beta = 3.78 \text{ rad}$  ( $216^\circ$ ). Since  $\pi + \alpha = 4.19 > \beta$ , the current is discontinuous, and the above expression for current is valid.

(b) 
$$I_{dc} = \frac{1}{2\pi} \int_{\alpha}^{\beta} i(\omega t) d(\omega t) = \frac{V_m}{\pi R} (\cos\alpha - \cos\beta) = \frac{169.7}{\pi 10} (\cos 60 - \cos 216) = 7.07 \text{ A}$$

(c) 
$$I_{rms} = \frac{1}{\sqrt{R^2 + (\omega L)^2}} \sqrt{\frac{V_m^2}{2\pi} \left(\beta - \alpha - \frac{1}{2} \sin 2\beta + \frac{1}{2} \sin 2\alpha\right)}$$

$$I_{rms} = \frac{1}{12.5} \sqrt{\frac{169.7^2}{2\pi} (3.78 - 1.047 - \frac{1}{2} \sin(2 \times 216) + \frac{1}{2} \sin(2 \times 60))} = 8.8 \text{ A}$$

(d) 
$$p = I_{rms}^2 R = 8.8^2 \times 10 = 774.4 \text{ W}$$



# Single Phase Controlled Full Wave Rectifier

## RL Load, Continuous Current

- If the load current is still positive at  $\omega t = \pi + \alpha$  when gate signals are applied to  $T_3$  and  $T_4$  in the above analysis,  $T_3$  and  $T_4$  are turned ON and  $T_1$  and  $T_2$  are forced OFF.
- The initial condition for current in the second half-cycle is not zero.

In continuous current  $\omega t = \pi + \alpha$ . The current at  $\omega t = \pi + \alpha$  must be greater than zero for continuous-current operation.


$$i(\pi + \alpha) \geq 0$$

$$\sin(\pi + \alpha - \theta) - \sin(\pi + \alpha - \theta) e^{-(\pi + \alpha - \alpha)/\omega\tau} \geq 0$$

Using

$$\sin(\pi + \alpha - \theta) = \sin(\theta - \alpha)$$
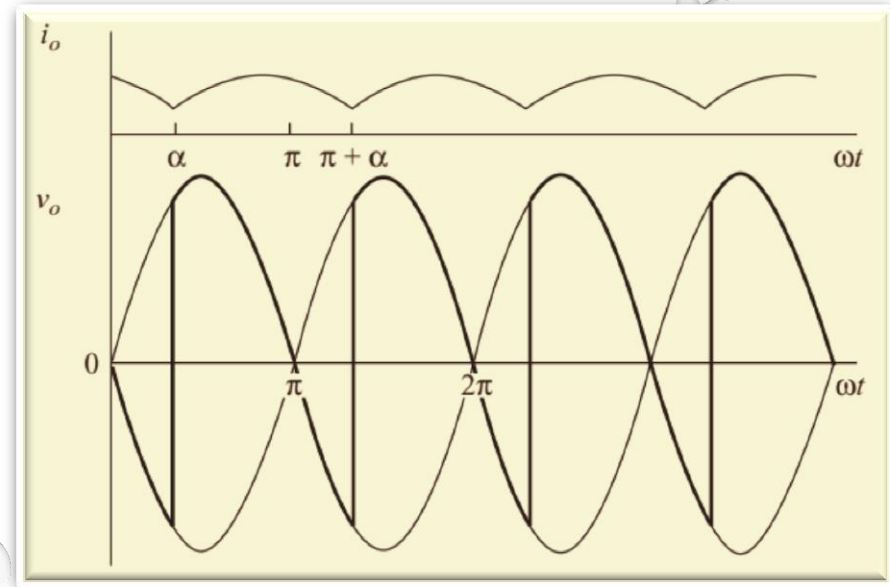
$$\sin(\theta - \alpha) (1 - e^{-(\pi/\omega\tau)}) \geq 0$$



# Single Phase Controlled Full Wave Rectifier

## RL Load, Continuous Current

Solving for  $\alpha$   $\alpha \leq \theta$

Using  $\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$

$$\alpha \leq \tan^{-1}\left(\frac{\omega L}{R}\right) \rightarrow \text{Continuous current}$$

The average (dc) output voltage and current are

$$V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d\omega t = \frac{2V_m}{\pi} \cos \alpha$$
$$I_{dc} = \frac{V_{dc}}{R} = \frac{2V_m}{\pi R} \cos \alpha$$


The *rms* voltage and current are computed from

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} (V_m \sin \omega t)^2 \, d\omega t} = \frac{V_m}{\sqrt{2}}$$
$$I_{rms} = \frac{V_{rms}}{Z} = \frac{V_{rms}}{\sqrt{R^2 + (\omega L)^2}} = \frac{V_m}{\sqrt{2} \sqrt{R^2 + (\omega L)^2}}$$

# Single Phase Controlled Full Wave Rectifier
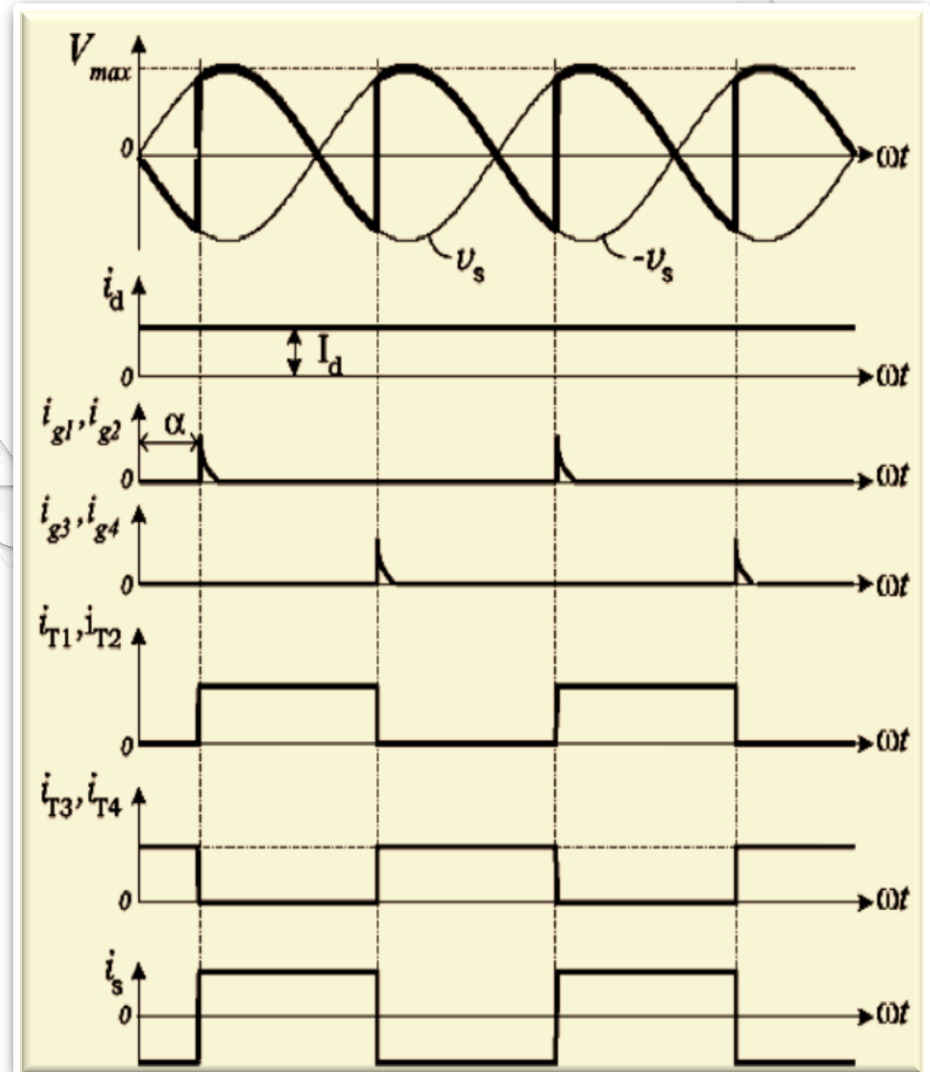
## Highly Inductive Load, $L \gg R$

- The behavior of the fully controlled rectifier with resistive-inductive load (with highly inductive load) is shown in the figure. The high-load inductance generates a perfectly filtered current and the rectifier behaves like a current source. With continuous load current, thyristors  $T_1$  and  $T_2$  remain in the ON-state beyond the positive half-wave of the source voltage  $v_s$ . For this reason, the load voltage can have a negative instantaneous value.
- The firing of thyristors  $T_3$  and  $T_4$  has two effects:
  - i) They turn off thyristors  $T_1$  and  $T_2$ .
  - ii) After the commutation they conduct the load current.



# Single Phase Controlled Full Wave Rectifier

Highly Inductive Load,  $L \gg R$

The average (dc) output voltage and current are

$$V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin \omega t \, d\omega t = \frac{2V_m}{\pi} \cos \alpha$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{2V_m}{\pi R} \cos \alpha$$

The *rms* voltage and current are computed from

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} (V_m \sin \omega t)^2 \, d\omega t} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = I_{dc} = I_a$$


**Example:** A controlled full-wave bridge rectifier has a source of  $120V_{rms}$  at 60Hz,  $R=10\Omega$ ,  $L=100\text{mH}$ , and  $\alpha=60^\circ$ . Determine (a) Verify that the load current is continuous. (b) the average load current, and (c) the power absorbed by the load.

$$\tan^{-1}\left(\frac{\omega L}{R}\right) = \tan^{-1}\left[\frac{(377)(0.1)}{10}\right] = 75^\circ$$

$$\alpha = 60^\circ < 75^\circ \quad \therefore \text{continuous current}$$
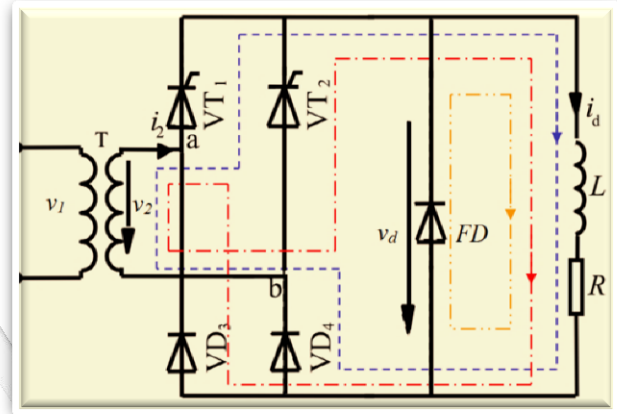
# Single-Phase Bridge Half-Controlled Rectifier

- The rectifier shown in the figure consists of a combination of thyristors and diodes and used to eliminate any negative voltage occurrence at the load terminals. This is because the diode  $D_{FD}$  is always activated (forward biased) whenever the load voltage tends to be negative. For one total period of operation of this circuit.



The average (dc) voltage across the load and the average (dc) current are

$$V_{dc} = \frac{1}{\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$I_{dc} = \frac{V_{dc}}{R} = \frac{V_m}{\pi R} (1 + \cos \alpha)$$


The *rms* component of the output voltage and current waveforms are determined from

$$V_{rms} = \sqrt{\frac{1}{\pi} \int_{\alpha}^{\pi} (V_m \sin \omega t)^2 \, d\omega t} = V_m \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}$$

$$I_{rms} = \frac{V_{rms}}{R} = \frac{V_m}{R} \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}$$

The power delivered to the load is

$$p = I_{rms}^2 R$$

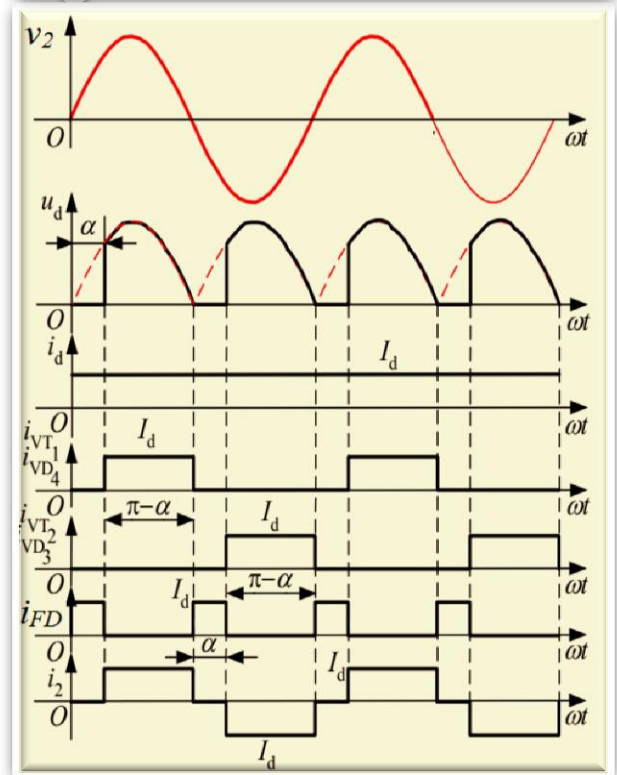

Dr. Firas Obeidat

