


73 Tests

the Knight-Kit P-2

SWR/Power Meter

Standing wave ratio is a subject of discussion and controversy on the amateur airwaves, and is of special concern to those limited in transmitter power. Like the weather, everyone talks about swr, but no one seems to know much about it! However, Allied Radio (100 N. Western Ave., Chicago 80, Illinois) has just made a new Knight-Kit available which is bound to stir up the curiosity of newcomers and old-timers alike regarding swr.

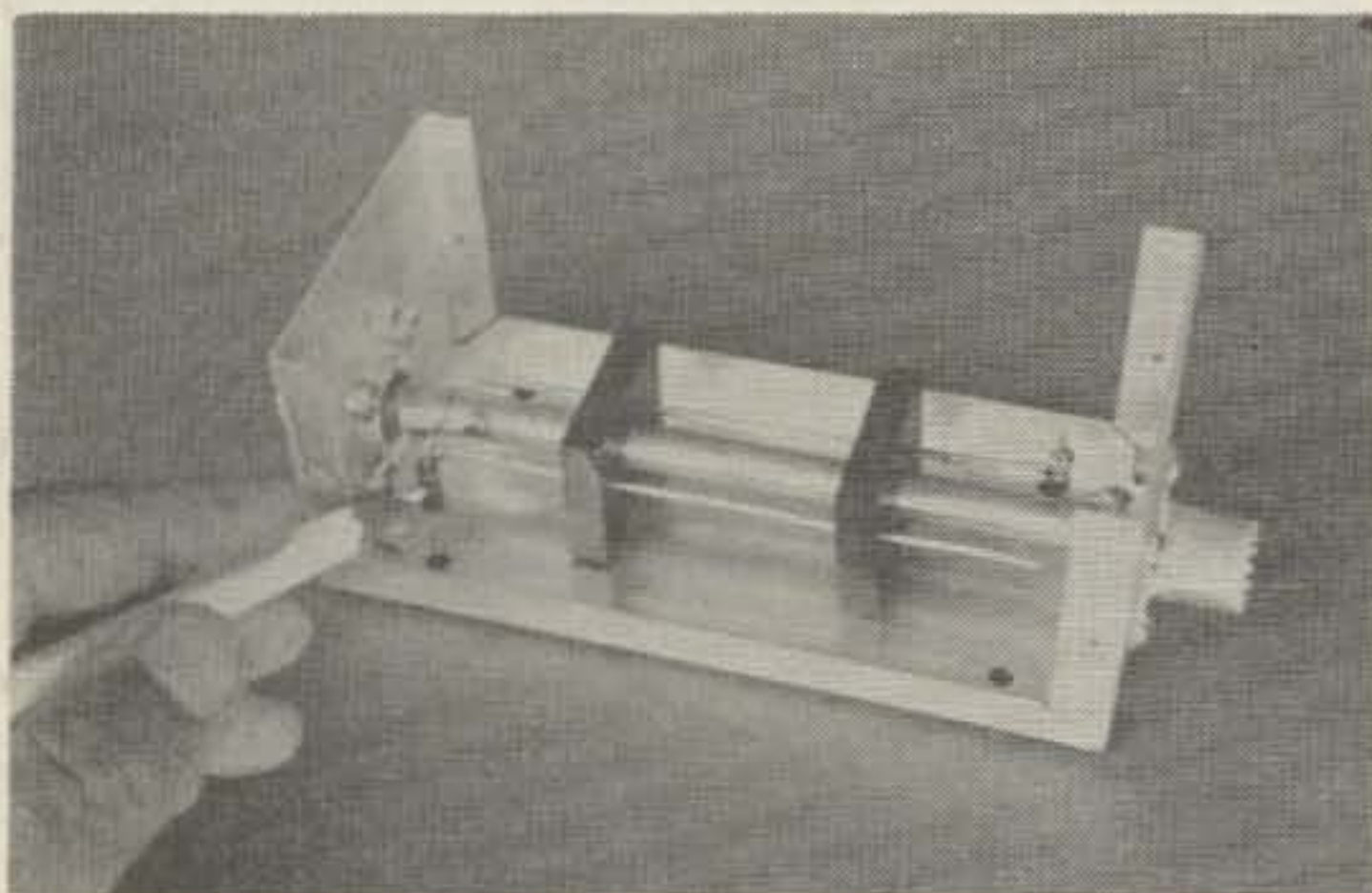The P-2 SWR/Power Meter Kit (Catalog # 83 YX 627R) sells for \$14.95, and consists of two units, a 2 x 5 x 2½ inch coupler and a 2¾ x 6¼ x 3 inch indicator, connected by a 4-foot shielded cable. Standard SO-239 rf coaxial receptacles are part of the coupler unit, which may be left in the transmission line permanently with negligible power loss.



The "coupler" is built in a separate enclosure, with standard coaxial connectors to allow convenient attachment to the transmission line.


The resistor value used depends on the impedance value of the transmission line with which the coupler is to be used.

The coupler may be assembled for use with either 52 or 72 ohm coaxial transmission line, and may be used from 3.5 to 432 megacycles. No external ac power or batteries are required for its operation. It will handle a kilowatt of rf power, yet requires less than a watt at 432 mc for a full scale reading of the 100 micro-amp meter in the indicator unit. Unfortunately, the red and black meter scales are on a gray background (to match the unit two-tone gray color scheme); a white meter background would enhance visibility in subdued lighting, since the meter is not illuminated.

Assembly of the units is very clearly shown in the detailed assembly manual and the photos accompanying this article. No real problems were encountered in the construction, which takes about 1½ hours if done carefully, as it should be. The author's unit worked perfectly when completed, and no adjustments were required.

During construction of the indicator unit, it would be wise to mount the knobs on the power switch and sensitivity potentiometer shafts right after placing the meter dress panel on the meter sub-panel. This makes it much easier to handle the panel as it is being installed in its case. The black sheet metal screws used to hold the rubber mounting feet are rather brittle, and should be installed without too much "brute force" to avoid breaking the tips of the screws. Also, avoid over-tightening these screws, or they will go *through* the rubber feet; just tighten until the feet are snug, or use a flat washer under the head of each screw.

When assembling the coupler, the place-

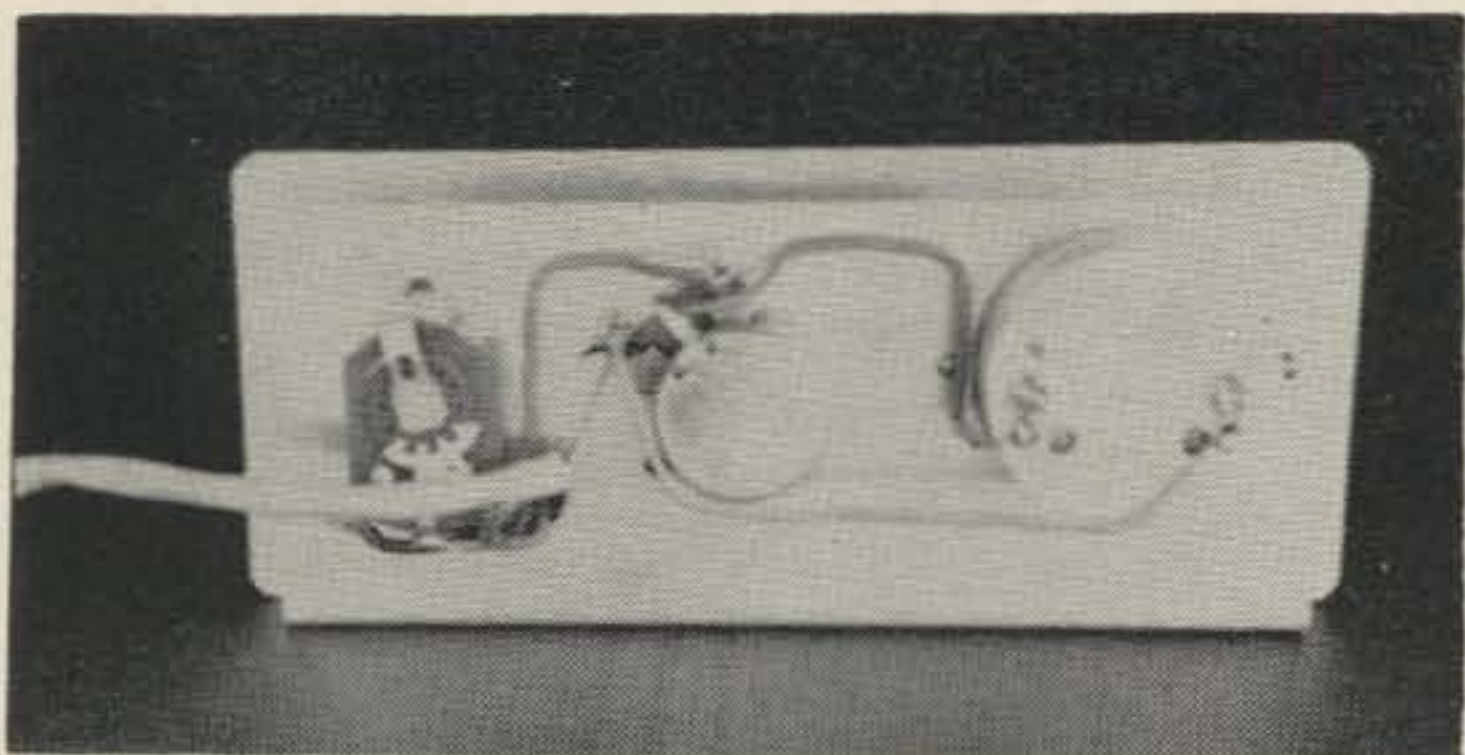

The complete wiring of the indicator sub-panel involves only a few wires, and a 2-conductor shielded cable which goes to the coupler unit.

ment of several of the parts is critical, and the instructions should be followed closely. Two sets of resistors are supplied with the unit. If you intend to use the coupler with 52 ohm transmission line use the 160 ohm resistors; for 72 ohm line, use the 100 ohm resistors. If the parts tend to shift during handling, use pencil marks on the copper rod and chassis to allow you to return the parts to the proper location when ready to solder. The coupler has no markings on it, and it would be wise to mark J1 XMTR on the end with the connecting cable, and J2 ANT on the other end.

The schematic diagram of the P-2 SWR Meter is shown in Fig. 1. The design of the instrument follows that of the time-proven and justly popular Monimatch of QST and ARRL Handbook fame. This instrument, sometimes known as a reflectometer, consists of a short section of coaxial transmission line with two pickup loops which are connected to rf voltmeter circuits. One of these circuits is so positioned with respect to the center conductor of the transmission line section as to read the incident or forward power component of voltage in the line while the other reads the reflected component. In the P-2 instrument, the circuit associated with diode CR-1 is the forward power voltmeter and the circuit associated with CR-2 is the reflected power voltmeter. Resistors R-1 and R-2 must be adjusted to match the characteristic impedance of the line being measured to balance out the undesired voltage component. In use, the instrument is switched

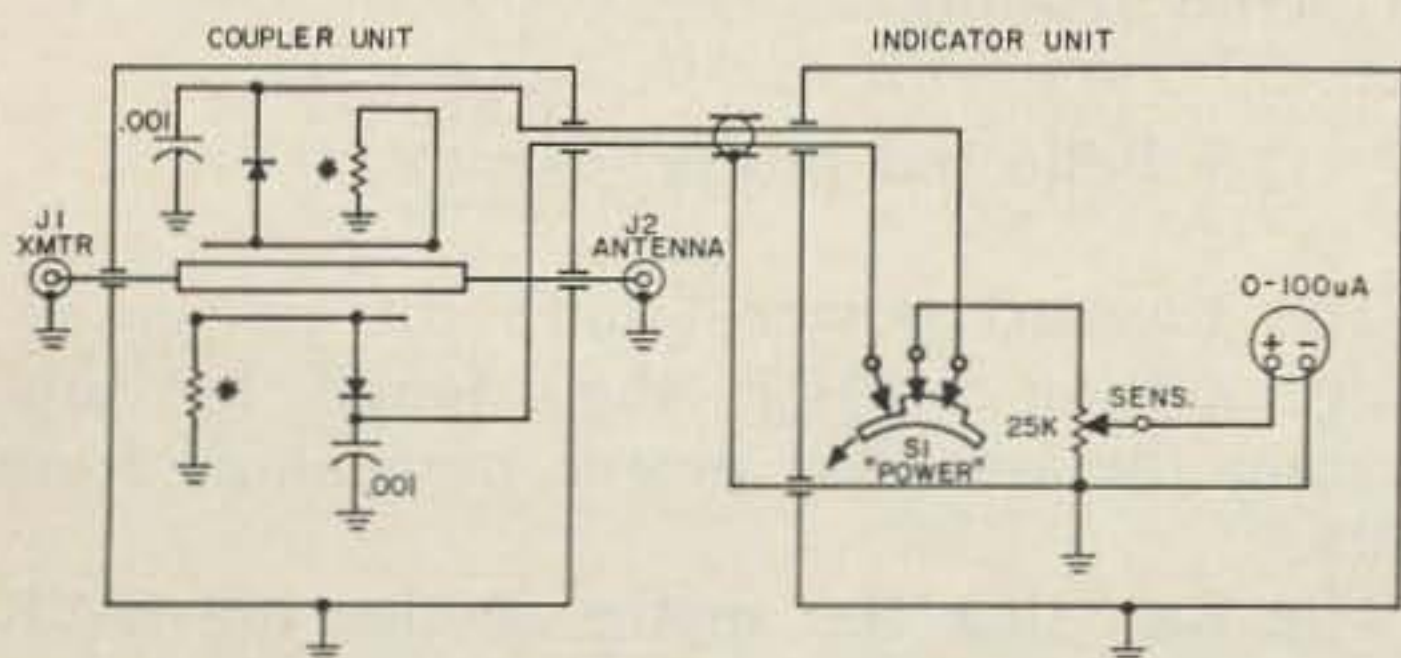


FIGURE 1

GENERALIZE YOURSELF! LEARN RADIO CODE


The EASY WAY

No Books To Read—No Visual Gimmicks To Distract You. Just listen and learn

Based on modern psychological techniques — This course will take you beyond 13 w.p.m. in LESS THAN 1/2 THE TIME

Available also on magnetic tape

See Your Dealer Now!

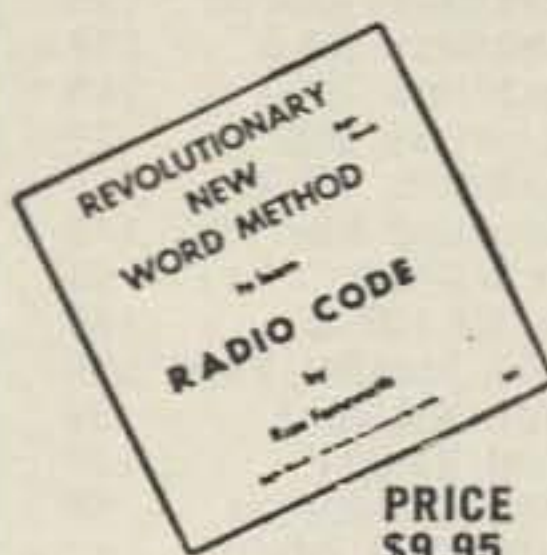

PRICE \$9.95

Album Contains Three 12" LP's 2 1/2 Hr. Instruction

Life Story of Nikola Tesla

Now, learn code and something else at the same time. Fascinating story and code practice at same time. \$2.49



EPSILON RECORDS

2769 CAROLINA REDWOOD CITY, CALIF.

2 METER CONVERTER

Now at last a 2 meter converter complete with 3 VHF transistors and crystal for output in the 6 meter band. Operates on 12 V. D.C. A real bargain, for only \$10.00 while supply lasts.

For output in other bands use this with our 6 meter converter advertised in 73.

VANGUARD ELECTRONIC LABS Dept. H-5
190-48-99th Ave. Hollis 23, N. Y.

CALAMAR Electronics Co.

K6HYU
WA6HYU

COLLINS, HAMMARLUND, MOSLEY,
SWAN, SIDEBAND ENGINEERING,
NATIONAL, GONSET

2163A FULTON AVE, SACRAMENTO, CAL.

NEW! GROUND RADIAL SYSTEM KITS

Take the work out of fabricating your antenna ground system

Here are ground radial systems for getting improved performance from long-wire, vertical and other "HAM" and "SWL" antennas which are operated against ground. These radial systems will also improve the efficiency of ungrounded antennas such as doublets, zepps and directive arrays reducing the losses resulting from ground imperfections. Excellent as permanent or temporary ("Field Day") installations. Complete, ready to roll out radial systems in two sizes to satisfy most "HAM" and "SWL" requirements. Uses No. 14 gauge solid copper radial wires electrically and mechanically bonded to central hub. Drive pegs are provided for securing radial wire ends. Just locate center hub where you want it, roll out the radials and you're in business. Radials can be easily buried to preserve the beauty of your front or back yard lawn. Full instructions in kit. Send for free antenna ground system fact sheet.

1,000 FOOT KIT (10-60', 8-33', 8-17' RADIALS) . . . \$24.95

2,000 FOOT KIT (20-60', 16-33', 16-17' RADIALS) . . \$42.95

Send only \$5.00 (cash, ck., M. O.) and pay balance COD plus express or postage charges on arrival or send full price for prepaid delivery.

Ready-Radials

P. O. Box 5496
Winston-Salem, N. C.

FANTASTIC BARGAINS ON RECONDITIONED EQUIPMENT!

Central Electronics		Hallicrafter S-53A	59
20-A	\$149	Hallicrafters SX-100	195
Central Electronics		Hallicrafters HA-6	249
MM-2	89	Hallicrafters HA-2	249
Central Electronics		Hallicrafters P26	79
MM-1	75	Hallicrafters HT-37	375
Central Electronics		Hammarlund HQ-110	179
600L	249	Heath DX-100	159
Collins KWM-2	895	Heath DX-100-B	169
Collins 75A-4	495	Johnson Invader 2000	895
Collins 312B-2	89	Johnson Viking I	99
Drake 1A receiver	149	Johnson Ranger	179
Eico 723	55	Johnson Challenger	89
Elmac AF-67	89	Johnson 500 excint	
Elmac PMR-7	99	cond	499
Elmac A54H	44	Johnson Valiant	299
Elmac PMR6A & Elmac		Johnson 250-23-3	65
PSR116S	59	Mosley CM-1	150
Elmac M-1470	39	National NC-300	239
Globe Champ 300A	225	P&H 6-150 6 mtr.	
Globe King 500A	279	xmting converter	189
Globe Scout 680A	59	RME VHF-152A	45
Globe 755 VFO	29	RME 84 receiver	49
Gonset GSB-101	229	Swan SW-120	199
Gonset Communicator		Tecraft TR-20-50	39
I 6 mtr	89	Tecraft PTR-2 supply	
Hallicrafter SX-101A	299	(new)	30
Hallicrafter SX-111	189	Tecraft TR-20-144	
Hallicrafter HT-40	79	(new)	45

Box
37A

Burghardt
RADIO SUPPLY, Inc.

Phone
886
5749

Ask for our new equipment catalog #163 just out. Also our latest used gear bulletin, revised monthly.

WATERTOWN, SOUTH DAKOTA

SEMI-CONDUCTOR SALE!

NO CHANCE TO TEST 'EM! FULLY GUARANTEED!

- () 20 Amp Power Rect. Stud, Silicon \$1
- () 15 Silicon Diodes, 'Epoxy' \$1
- () 20 Top Hat Rects. to 750 ma, silicon \$1
- () 15 PNP Transistors, asst types \$
- () 15 NPN Transistors, asst types \$
- () 10 Surface Barrier Trans't'rs, pnp \$
- () 5 Power Transistors, 2N155 case \$1
- () 2 40W Power Transistors, 2N174 case \$1
- () 10 2-Amp Rects, stud, silicon \$1
- () 25 Rect, Trans't'rs, Diodes, asst \$1
- () 15 CK722 Type Transistors, pnp \$
- () 10 Transistors, 5 pnp, 5 npn \$
- () 25 Silicon Germanium Diodes \$
- FACTORY TESTED! GUARANTEED!
- () 1 Watt Zener, choose 3 to 30V \$
- () 25 Amp Trans't'rs, Car Ignition \$
- () 30 'Klip-in' Diodes, Germanium \$1
- () 15 IN34 Diodes, Glass, Submini \$
- () 4 2N35 Type Trans't'rs, npn \$
- () 4 2N107 Type Trans't'rs, pnp \$
- () 3 2N170 RF, OSC Trans't'rs, npn \$1
- () 6 2N377 Transistors, npn \$

FREE!

**WE
PAY
THE
POSTAGE**

() CAR IGNITION BASIC
incl: 2N174,
zeners, rect,
sink, instruc-
tions \$7.99

POLY PAKS

P. O. Box 942A
S. Lynnfield, Mass.

Send 10c
for parts
catalog!

SKYLANE QUADS


"famous the world over!"

\$59.95 Three Bands **\$99.95**

Bamboo

40 M QUAD KITS AVAILABLE


Fiberglass

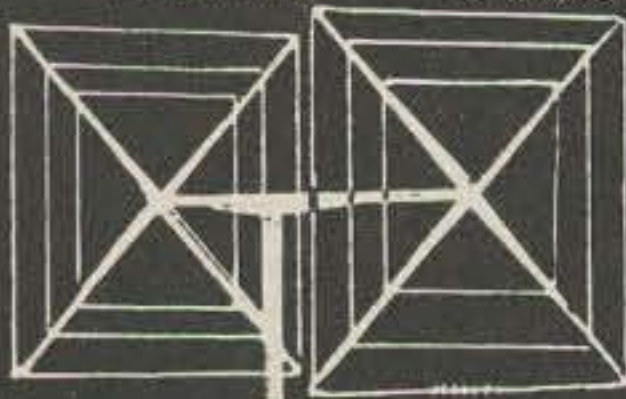

FOR FREE LITERATURE
WRITE DEPT. C

- HIGH F/B RATIO
- VERY LOW SWR
- HIGH GAIN
- LOW Q - BROADLY TUNED
- EASY TO MATCH
- LOW WIND RESISTANCE
- RUGGED CONSTRUCTION

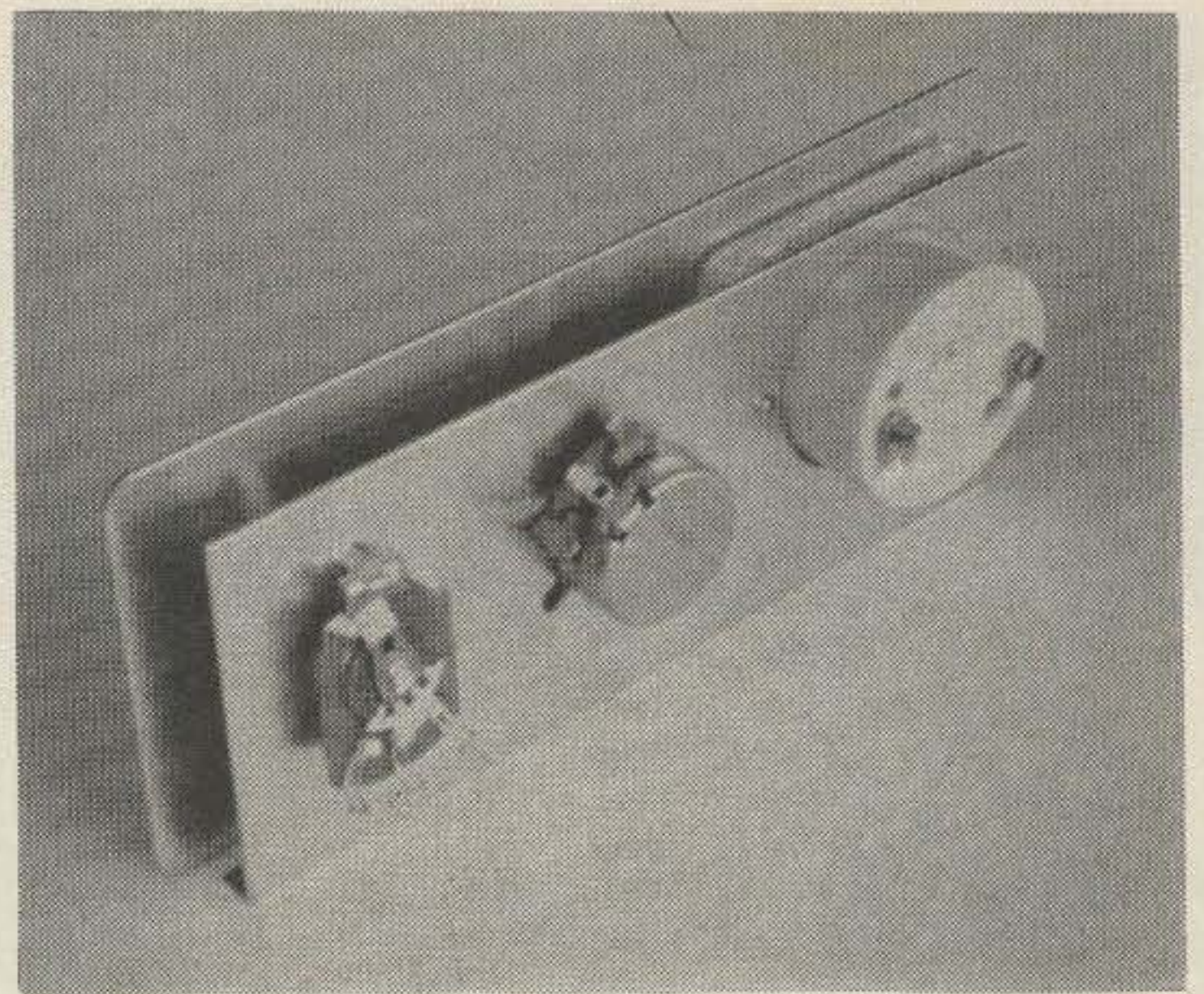SkyLane PRODUCTS 406 BON AIR DR.
TEMPLE TERRACE, FLA.



The indicator unit contains a sub-panel to hold the meter, switch and pot, with a "dress" panel for the nomenclature.

to the forward power position and the sensitivity control adjusted for full scale meter deflection. The instrument is then switched to the reflected power position and the existing standing wave ratio read directly from the meter scale.

In use, the J1 receptacle of the coupler is connected to the transmitter output connector (using a jumper cable or a double-male connector) and J2 goes to the transmission line feeding the antenna. The transmitter is turned on and tuned in the normal manner, with the sensitivity control on the indicator unit positioned to keep the meter on scale. (The swr meter Power switch must be in the Forward position. You can peak your transmitter output very conveniently by tuning for maximum deflection of the swr meter). Adjust the sensitivity control, once you are tuned up, so the meter reads CAL. (full scale). Now switch the Power switch to Reflected, and read the swr directly on the meter top scale. Although the operating instructions fail to mention it, the REL. POWER scale of the meter, if multiplied by 10, reads the percentage of reflected power! Notice that only 11% power is reflected at an SWR of 2.0, and 25% is reflected at SWR of 3.0. You may calculate the reflected power percentage quite simply from the SWR reading:

$$\% \text{ Reflected power} = \left(\frac{\text{swr}-1}{\text{swr}+1} \right)^2$$


The forward power (that's the power actually getting out) is then found by subtracting the reflected power percentage from 100%.

The fact that the meter of the P-2 SWR Meter is calibrated in relative power deserves

some explanation. The reflectometer type of SWR meter is quite dependent on frequency for any given output indication. Note that 45 watts is required for full scale deflection at 1.8 mc while only 1/2 watt is required for full scale deflection at 432 mc. This ratio is perfectly normal for this type of meter. However, it prevents the inclusion of absolute power scales in an all band instrument. Despite this, the relative power scale is quite convenient for transmitter tuning, etc.

The calibration of the completed unit may be checked several ways. The instructions go through an alignment procedure which requires a non-reactive dummy load. At the higher frequencies and for high power this might pose a problem. A simple way to make a quick check is to reverse the coupler in the transmission line, connecting J2 to the transmitter output, and J1 to the transmission line. Now set CAL on the meter with the Power switch in the Reflected position, and read swr in the Forward position. If the same swr is obtained as using the coupler the correct way, the unit is well balanced. If not, the position of the diode connections to the pick-up wires in the coupler must be adjusted slightly, as described in the manual. The author's unit required no adjustments.

Be careful about quoting your swr readings with too much certainty. You see, it just so happens that the swr read at the transmitter is *always lower* than the actual swr at the transmitter. The reason is simple: the forward power is attenuated on its way to the antenna by line loss, and the power reflected at the antenna is also attenuated by the transmission line on its way back to the transmitter. Therefore, the percentage of reflected power reaching the swr meter is less than it should be, compared to the outgoing forward power.

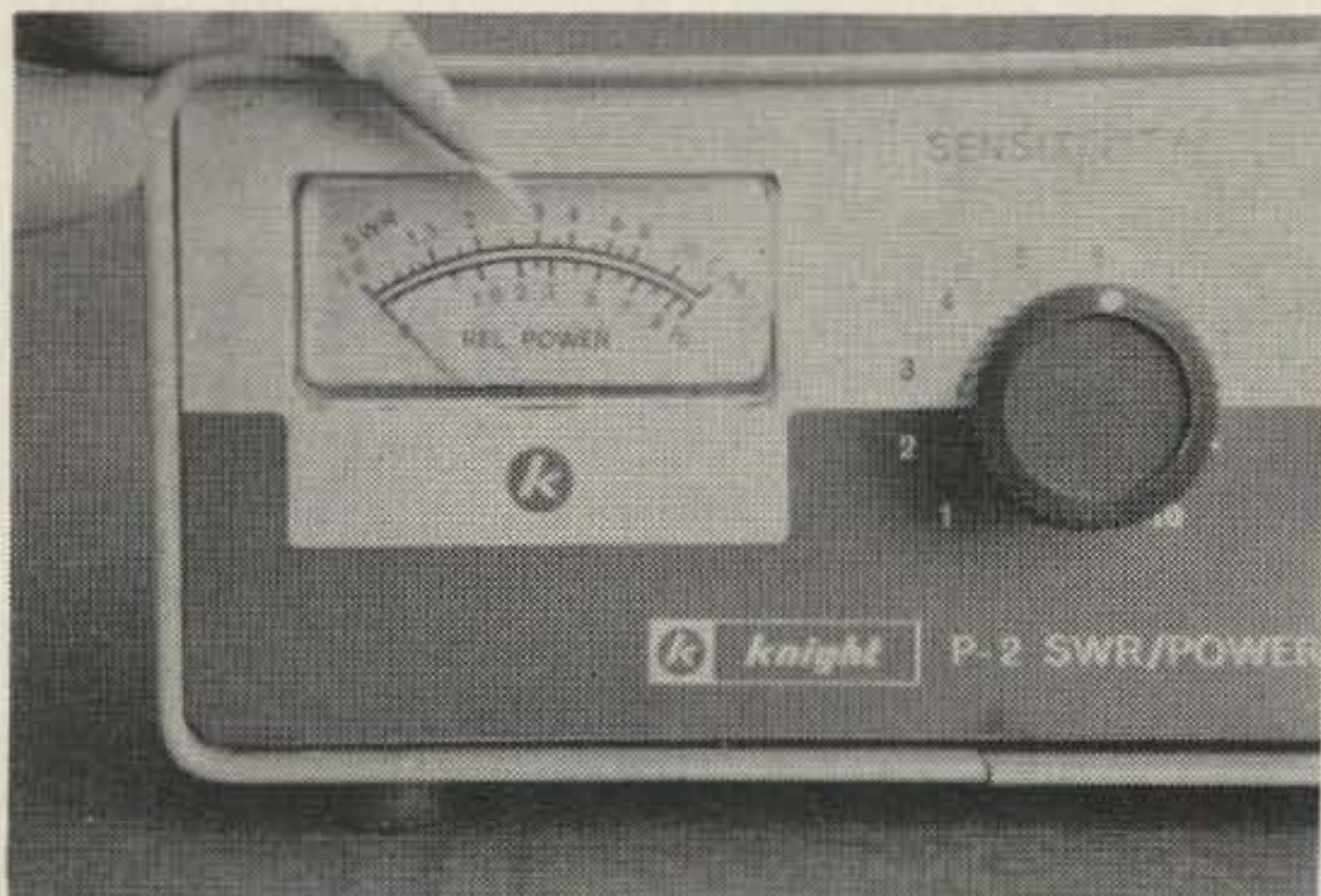

The meter is calibrated to SWR of 20. The lower scale, multiplied by 10, reads percent reflected power. For example, at SWR of 3, 25% power is reflected from the load.

CONVERTER SALE

6 meter converter \$8.00 postpaid. Complete with 3 high frequency transistors and 49.4 mc. crystal for output in broadcast band or 36 mc. crystal for output in 14-18 mc. band. Low noise and better than 1 microvolt sensitivity. Operates on 6-12 V D.C.

Limited quantity—send your order today.

VANGUARD ELECTRONIC LABS Dept. H-5
190-48-99th Ave. Hollis 23, N. Y.

IMPROVED VHF—UHF RESULTS

J Beam Skeleton Slots for 50-144-220-432 Mc.
Tremendous results at moderate costs.

Specials

300 to 52 ohm waterproof baluns—83 connectors 50-54 megacycles
\$10.75; 144-148 megacycles \$8.60

RG8U Name Brand Polyfoam Insulated cable ft. .13


FOR THE DX BOYS

G4ZU Minibeams 10-15-20 A low, low \$74.95

BE PROUD OF YOUR SIGNAL

GAIN, Inc., Dept. 73-5, 1209 West 74,
Chicago 36 — Ph.: 874 2610

TV CAMERA

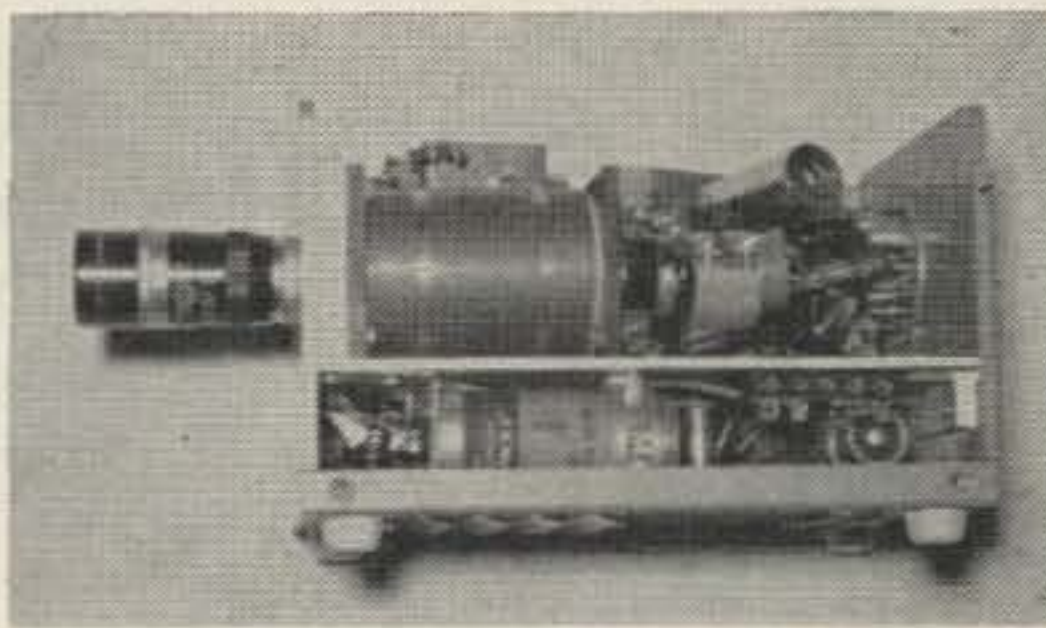

\$99.50

and up

Basic
Parts
Kit

Details—FREE List #771

DENSON ELECTRONICS CORP.

Rockville, Connecticut

FREE Catalog

OF THE WORLD'S FINEST
ELECTRONIC GOV'T
SURPLUS BARGAINS



HUNDREDS OF TOP QUALITY

ITEMS—Receivers, Transmitters, Microphones, Inverters, Power Supplies, Meters, Phones, Antennas, Indicators, Filters, Transformers, Amplifiers, Headsets, Converters, Control Boxes, Dynamotors, Test Equipment, Motors, Blowers, Cable, Keyers, Chokes, Handsets, Switches, etc., etc. Send for Free Catalog—Dept. 73.

FAIR RADIO SALES
2133 ELIDA RD. • Box 1105 • LIMA, OHIO

LOOK!

BC-221 Freq Meter with orig. calib. book and xtal, lab checked out, XLNT cond. \$69.50

Crystal Oven—Bliley crystal stabilizer, type TCO-1 for 1HC/6 crystal. Requires 6.3v at 0.85 a, 1 1/4" dia. x 1 1/2" octal plug in base. BRAND NEW \$2.75

85 kc if Transformers—spares for ARC-12. Same as BC-453 with ceramic base & air trimmers except higher "Q" & different base pins. BRAND NEW 79c ea, 3/\$2.25

RF Crystal Probes—for VOM with Klipzon tips, made by General Cement. List \$4.35, BRAND NEW in cello. bag \$1.25


Super Midget Relay—P&B SM-50S. Herm. sealed plug-in, fit 7 pin min. tube socket, SPDT, 250 ma contacts. Coil 6 vdc, 80 ohms \$1.25

ART-13 Calib. Crystals. 200 kc. herm. sealed w/octal plug-in base \$1.50

Write for Bulletin #38 "Loads of Bargains"

R. W. Electronics, Inc.

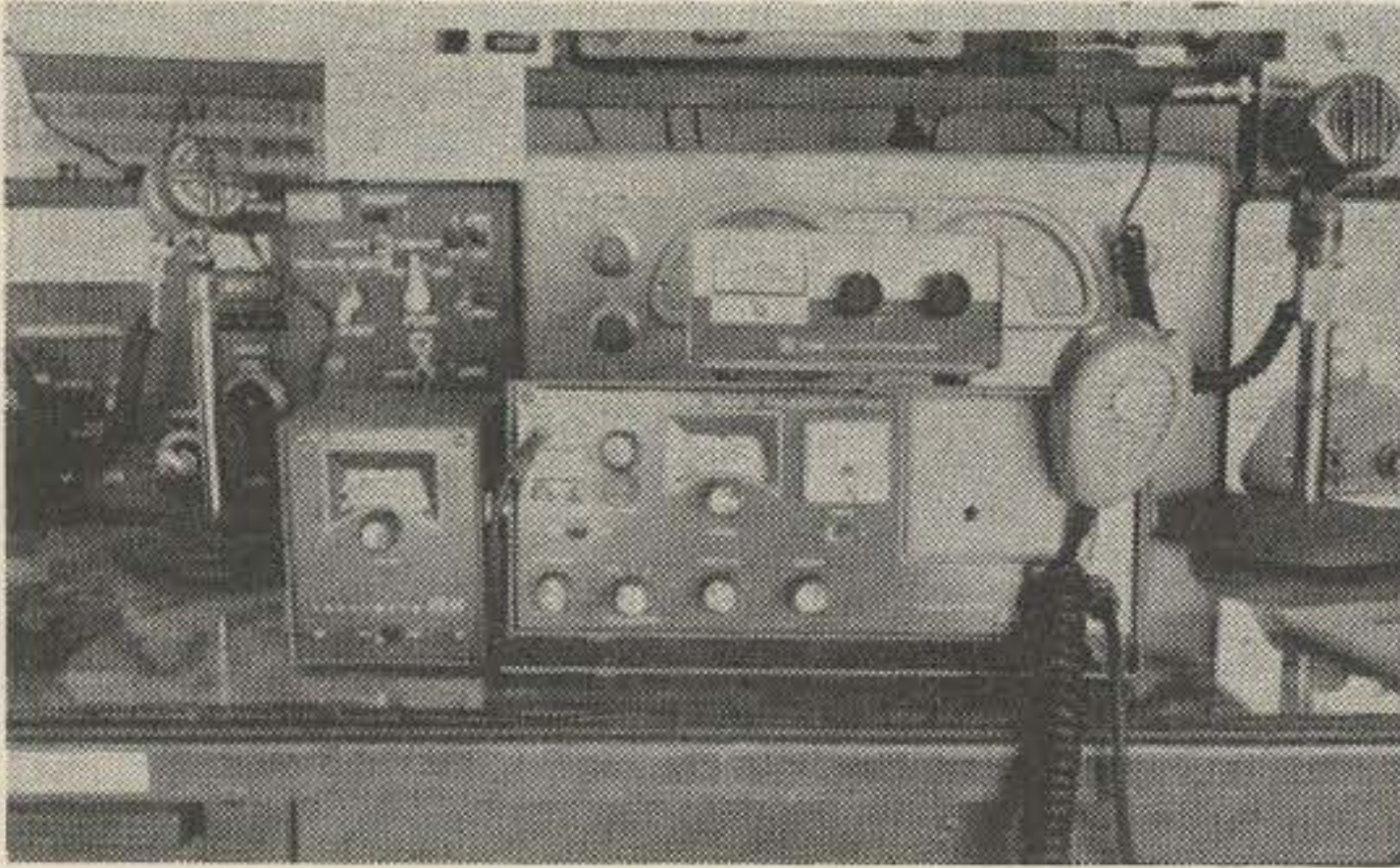2430 South Michigan Ave. Dept. 735 Chicago 16, Illinois
Phone: CAlumet 5-1281



A typical "neat" station!

Since the swr meter is usually located at the transmitter, this variation can be considerable. Look at Fig. 2 for a shock. If the basic transmission line loss (at swr of 1.0) is 6 db, and the swr at the antenna is 4.0, the swr meter will only read 1.37. You can estimate your basic line loss from tables that list the loss per 100 feet for different types of transmission line at various frequencies; the *Radio Amateur's Handbook* has this information in a graph in the transmission line section.

Swr has a couple of other villainous features: it increases your transmission line loss, and lowers the power limitation of the transmission line. Fig. 3 shows the added loss to a transmission line due to swr. For example, if the line loss at swr of 1.0 is 6 db, but the actual swr at the antenna is 2.5, the line loss will be increased by another .79 db. At higher swr this effect can be a lot worse; at swr of 10, with a basic line loss of 6 db, the

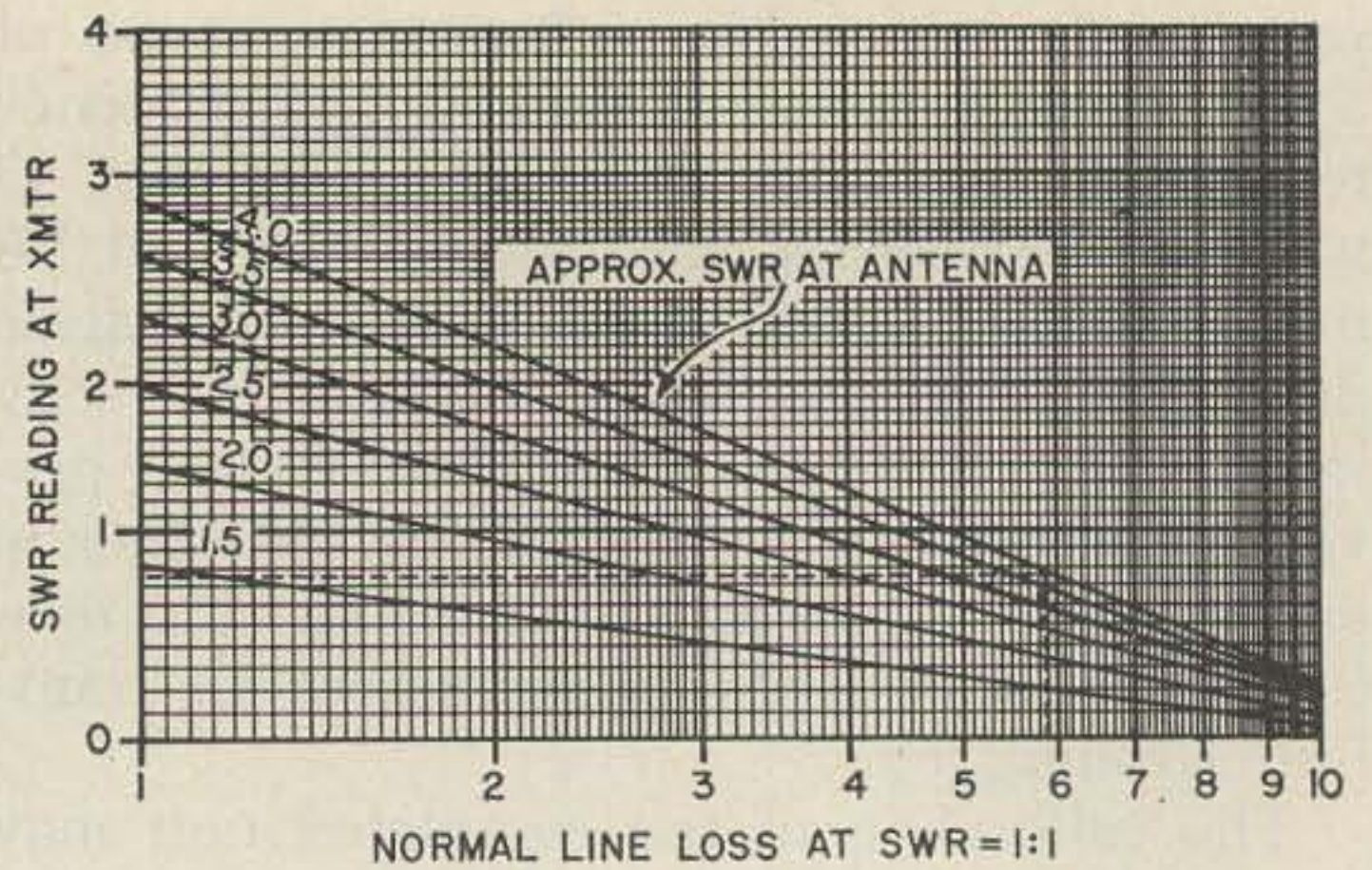


FIGURE 2

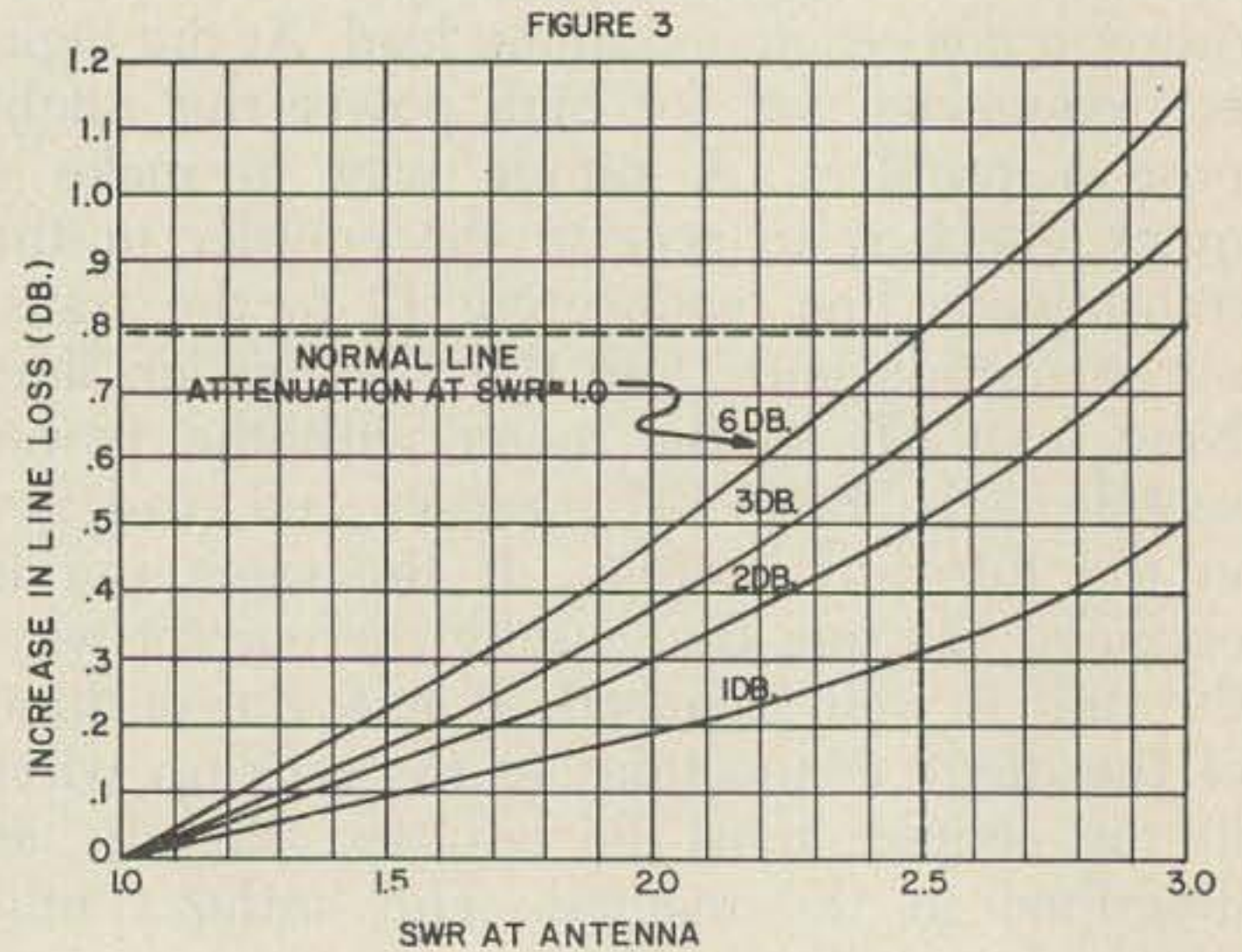


FIGURE 3

increase in loss will be 4.5 db. As for the power limitation, caused by the increased peak voltages of the standing waves, the allowable power is equal to the rated power (at swr of 1.0) divided by the swr:

$$\text{Allowable power} = \left(\frac{\text{Rated power}}{\text{SWR}} \right)$$

Generally speaking, unless you have high transmission line losses to begin with, an swr of 3.0 or less will make very little difference at the receiving end. Remember, one S unit is 6 db. at the receiver. But it all makes for good conversation on the air.

Specifications of the Knight-Kit P-2 SWR/Power Meter

Minimum rf power for full scale deflection	45 watts at 1.8 mc 1/2 watt at 432 mc
Maximum rf power	1 kilowatt
Input and output impedance	52 or 72 ohms
Power requirements	none
Frequency coverage	1.8 to 432 mc
Meter sensitivity	100 microamperes full scale
Meter scales, standing wave ratio	1:1 to 20:1
Relative power	0 to 10
Kit assembly time	1 to 2 hours
Cost	\$14.95 in kit form

REPEAT-Best Sellers in 73

NUVISTORS — price includes postage and insurance.

6CW4 or 6DS4 Triodes choice, any 3 \$5.25

7587, industrial tetrode, \$3.65; 3 for \$10.50

3 sockets, with order of 3 nuvistors 50c

1625 tubes, Syl. NU, RCA, Ken-Rad or Tung-Sol

BRAND NEW, minimum mail order 12 for \$2.00

902P-1, 2" CRT \$3.00; 6DQ5 \$1.75; 6DQ6B \$1.00;

3B28 \$3.25; 807 \$1.00; 5933 \$1.85; 837 \$1.50;

6146 \$3.00; 6AN5 \$1.00; 5T4 60c; 1616 \$1.00.

MD7/ARC-5, plate modulator, ex., used \$5.50

85 KC IF, for BC-453, \$1.00 ea.; 3 for \$2.75

85 KC IF, later type, ceramic form, male plugs, higher "Q", \$1.25; 3/\$3.50

"GOODIE" sheet free with orders only. Flyer only, please send self addressed, stamped envelope. PLEASE include sufficient for postage & insurance. Excess returned.

SAVE YOUR LOOT, I'll be at

Rochester, N. Y. May 11

Breezshooters hamfest, near Pittsburgh May 26

Starved Rock, near Ottawa, Ill. June 2

BC ELECTRONICS

2333 S. MICHIGAN AVE.

CHICAGO 16, ILL. CALumet 5-2235