 

Timing & Synchronization

January 31, 2006




Sarah Harris
Engineering Department
Harvey Mudd College
sarah_harris@hmc.edu

A Quick Overview

- Synchronization
 - determining an event order
 - used for
 - moving a signal into a clock domain
 - asynchronous arbitration
- Synchronization Failure
 - as the time between two signals decreases it becomes more difficult to tell which came first
 - synchronizer may hang in a metastable state, unable to decide
 - different parts of the circuit may interpret result differently
- Failure Probability
 - is proportional to fraction of *vulnerable* time
 - exponentially decreases with waiting period
- exponentially increases with flip-flop regeneration time constant
- failure rate is proportional to event rate
- Synchronization Hierarchy
- Mesochronous Synchronizers
 - delay-line synchronizer
 - two-register synchronizer
 - FIFO synchronizer
- Plesiochronous Synchronizers
 - phase slip and flow control
- Periodic Synchronizers
 - clock prediction - looking into the future

What is Synchronization?

 - A *synchronizer* determines the order of events on two signals
- Which event came first?
 - Does it matter? Some times synchronization is unnecessary
- Often one signal is a clock
 - did the data go high before or after the clock went high?
- Why is this problem hard?



Uses of Synchronization



- Sampling asynchronous inputs with a clock
 - e.g., particle counter or pushbutton
- Crossing clock domains
 - sampling a synchronous signal with a *different* clock
 - this is an easier problem if both clocks are periodic
- Arbitration of asynchronous signals
 - e.g., request line for shared resource
 - game-show pushbutton

Synchronization Failure

- Which came first, event on A or event on B?
- The closer the race, the harder it is to call
- When the events are very close, the synchronizer may enter a *metastable* state
- The synchronizer may take an arbitrary amount of time to *exit* this state
- Synchronizer output may be interpreted inconsistently in the meantime



Static Flip-Flop Dynamics

  - Initial voltage difference depends on Δt
- Voltage difference increases exponentially after clock rises




A Brute-Force (Waiting) Synchronizer

  - To sample an asynchronous signal with a clock
- Sample signal with FF1
 - may go into a metastable state
- Wait for possible metastable stages to decay
 - time t_w
- Sample output of FF1



Synchronization Failure

 - What happens if FF1 is still in a metastable state when FF2 is clocked?
- What is the probability that this will happen?




Calculating Synchronization Failure (The Big Picture)

$$P(\text{failure}) = P(\text{enter metastable state}) \times P(\text{still in state after } t_w)$$

Probability of Entering a Metastable State

 - FF1 may enter the metastable state if the input signal transitions during the *aperture* time of the flip flop
- Probability of a given transition being in the aperture time is the fraction of time that *is* aperture time



$$P_E = \frac{t_a}{t_{cy}} = f_{cy} t_a$$


Probability of Staying in the Metastable State

- Still in metastable state if initial voltage difference was too small to be exponentially amplified during wait time

- Probability of starting with this voltage is proportion of total voltage range that is 'too small'

$$\Delta V_S = \Delta V_F \exp\left(\frac{-t_w}{\tau_S}\right)$$
 
$$P_S = \exp\left(\frac{-t_w}{\tau_S}\right)$$



Example Failure Rate Calculation

- Suppose a 500MHz clock samples a 10MHz asynchronous signal
- Flip-flops have aperture and regeneration time of 100ps
- What is the probability of synchronization failure?
- What is the failure frequency?


t_a	1.0E-10
f_cy	5.0E+08
τ_s	1.0E-10
t_w	2.0E-09
P_E	5.0E-02
P_S	2.1E-10
P_F	1.0E-11
f_e	1.0E+07
f_F	1.0E-04

Failure Probability and Error Rate

- Each event can potentially fail.
- Failure rate = event rate x failure probability

$$P_F = P_E P_S = t_a f_{cy} \exp\left(\frac{-t_w}{\tau_S}\right)$$



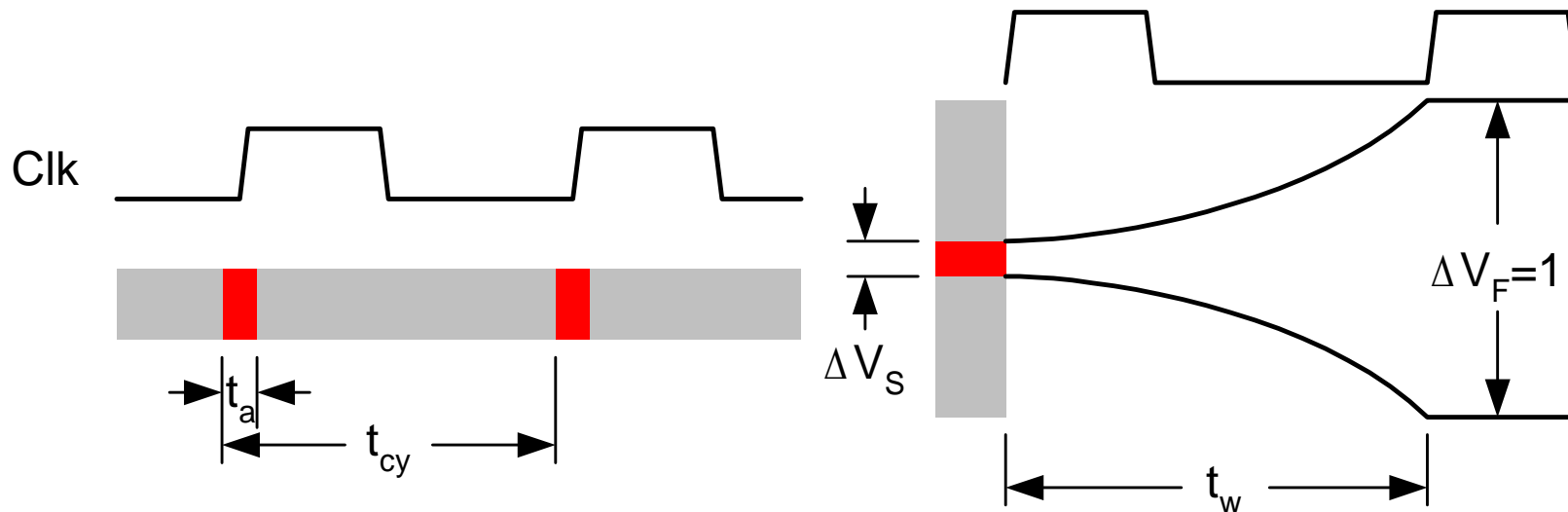
$$f_F = f_e P_F = t_a f_e f_{cy} \exp\left(\frac{-t_w}{\tau_S}\right)$$



Common Pitfalls

- Its easy to get a synchronizer design wrong
- The two most common pitfalls are:
 - using a non-restoring (or slowly restoring) flip-flop
 - τ_s needs to be small
 - not isolating the flip-flop feedback loop
   
$$P_F = t_a f_{cy} \exp\left(\frac{-t_w}{\tau_s}\right)$$



Synchronization Hierarchy


- The difficulty of synchronization depends on the relationship between events on the signal and events on the clock
- Synchronous
 - signal events always happen outside of the clock's keep-out region
 - same clock
- Mesochronous
 - signal events happen with a fixed but unknown phase relative to the clock
 - same frequency clock
- Plesiochronous
 - phase of signal events changes slowly with time
 - slightly different frequency clock
- Periodic
 - signal events are periodic
 - includes meso- and pleisochronous
 - signal is synchronized to some periodic clock
- Asynchronous
 - signal events may occur at any time

Synchronization Hierarchy Summary

Type	Frequency	Phase
Synchronous	Same	Same
Mesochronous	Same	Constant
Plesiochronous	Small Difference	Slowly Varying
Periodic	Different	Periodic Variation
Asynchronous	N/A	Arbitrary

The Brute-Force Synchronizer

 - How do we compare synchronizers?
 - synchronizer delay
 - failure rate
- For the brute-force synchronizer
 - $t_d = t_w + 2(t_s + t_{dCQ})$
 - $f_f = t_a f_e f_{cy} \exp(-t_w / \tau_s)$
- Can we do better?




Periodic Synchronizers

The Big Picture

- If an input signal is synchronized to *some* periodic clock, we can predict when its events are allowed to happen arbitrarily far into the future
- Thus, we can determine well in advance if the signal is *safe* to sample on a given clock cycle
 - if it is, we just sample it
 - if it isn't, we delay the signal (or the clock) to make it safe
- This allows us to move the waiting time, t_w , out of the critical path.
 - we can make it very long without adding latency

Periodic Synchronizers

The Illustration

 


Mesochronous Synchronization

- The phase difference between the signal and the clock is **constant**
 - typical of systems where we distribute a master clock with no deskew
- Thus, we only need to synchronize once for all time!
- During reset check the phase
 - if its OK, sample the signal directly for ever
 - if its not, sample the signal after delay for ever
 - this phase check is the only asynchronous event we ever sample - and we can afford to wait a long time




Delay-Line Synchronizer

 - For mesochronous and plesiochronous signals
- Delay signal as needed to keep transitions out of the *keep-out* region of the synchronizer clock
- How do we set the delay line?




Detecting an Unsafe Signal

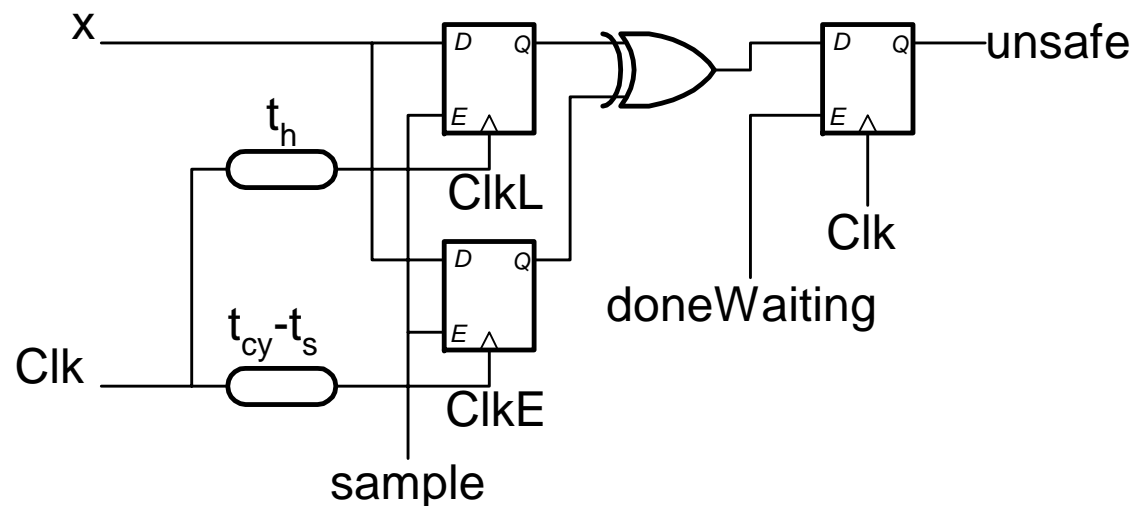- To see if a signal is unsafe, see if it changes in the forbidden region
 - sample just before and after the forbidden region and see if result is different
- These samples may hang the flip-flop in a metastable state
 - need to wait for this state to decay
 - if mesochronous we can wait a very long time since we only have to do this once




Two-Register Synchronizer

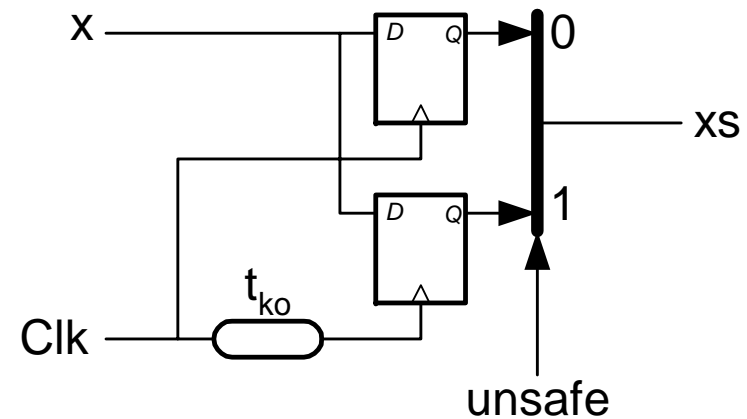- The delay-line synchronizer has two problems
 1. Its expensive, we need a delay line for each input
 2. We can't use it with clocked receivers
- Both problems are solved by the *two-register synchronizer*
- We delay the clock rather than the data
 - sample the data with normal and delayed clock
 - pick the 'safe' output
- Can we just mux the clock?



FIFO Synchronizer

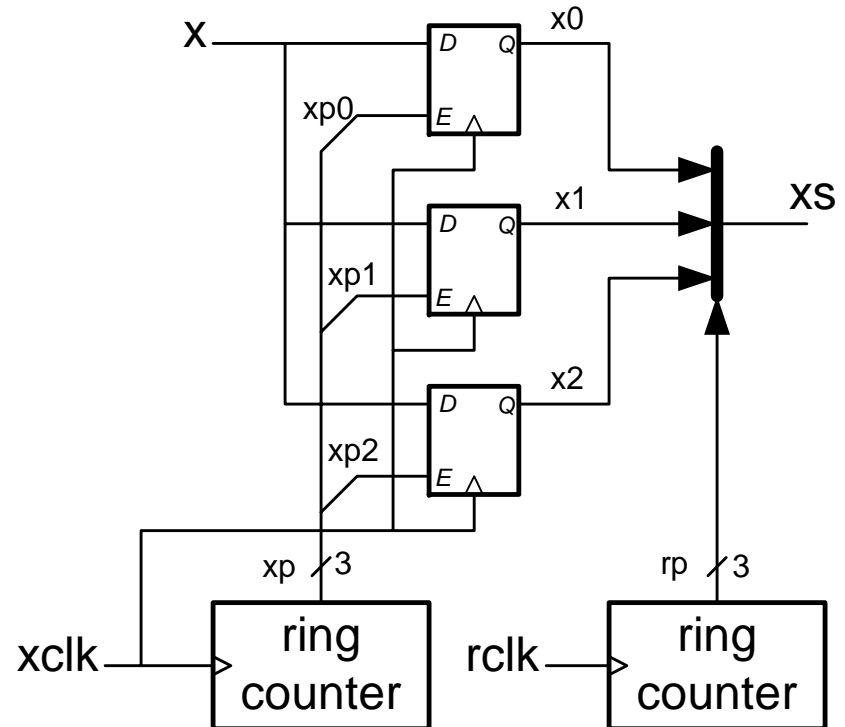- A first-in-first-out (FIFO) buffer can be used to move the synchronization out of the data path
- Clock the data into the FIFO in one clock domain (*xclk*)
- Mux the data out of the FIFO in a second clock domain (*clk*)




Plesiochronous Timing

- With plesiochronous timing, one clock is running slightly faster than the other
 - e.g., system with independent crystal oscillators with same nominal frequency ($\pm 200\text{ppm}$)
- The same basic synchronizer types apply
 - delay line
 - two-register
 - FIFO
- But...
- we need to resynchronize periodically
 - e.g., once every 1,000 clocks
- we need flow control
 - have to match data rate of tx and rx even if clock rate is different
 - eventually the phase *wraps* and we either get 2 or 0 data elements during a particular clock
 - unless we make sure we are not sending data when the phase wraps

A Plesiochronous FIFO Synchronizer

 - Insert data with transmit clock (xclk)
- Remove data with receive clock (rclk)
- Periodically update the receive pointer (rp) by synchronizing the transmit pointer (xp) to the receive clock
 - how do we know when to do this?
 - what do we do if rp increments by 2 or 0 when we update it?





Open-Loop and Closed-Loop Flow Control

- We need to keep a fast transmitter from overrunning a receiver
- (or a slow transmitter from underrunning the receiver)
- Open-loop approach
 - insert *lots of nulls* into the data stream at the transmitter
 - enough so that rate of non-nulls is less than the rate of the slowest possible receiver
 - when the receiver underruns it inserts another null
- Closed-loop approach
 - receiver applies *back pressure* when it is about to be overrun
 - still has to insert nulls when it is underrun



Example Synchronizer Design

- Designing an interface where clocks nominally match but might differ by as much as 1000ppm.
- Channel sends data in blocks of 10^4 symbols separated by fields of at least 20 NULL symbols

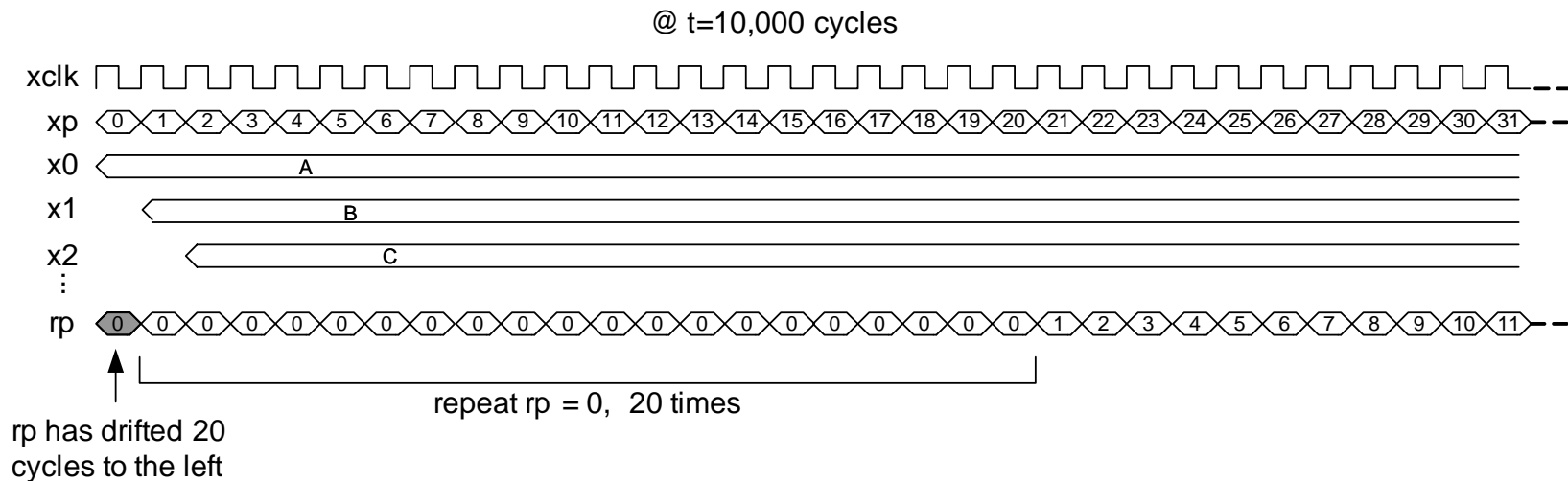 Example Synchronizer Design: rclk fast, xclk slow



  Example Synchronizer Design: rclk slow, xclk fast




Periodic Timing

- Transmit and receive clocks are periodic but at unrelated frequencies
 - e.g., modules in a system operate off of separate oscillators with independent frequencies
 - case where one is rationally derived from the other is an interesting special case
- In this situation, a single synchronization won't last forever (like mesochronous) or even for a long time (like plesiochronous)
- However, we can still look into the future and predict clock conflicts far enough ahead to reduce synchronizer delay

Clock-Predictor Circuit

 - Suppose we want to know the value of $xclk$, one $rclk$ cycle (t_{rcy}) in the future
- This is just a phase shift of $t_{xcy} - t_{rcy}$
- It is easy to generate this phase shift using a simple timing loop
- Note that we could just as easily predict $xclk$ several $rclk$ cycles in the future
- So how do we build a synchronizer using this?



Asynchronous Timing

- Sometimes we need to sample a signal that is truly asynchronous
- We can still move the synchronization out of the datapath by using an asynchronous FIFO synchronizer
- However this still incurs a high latency on the full and empty signals as we have to wait for a brute force synchronizer to make its decision
- We can still avoid delay in this case if we don't *really* need to synchronize
 - often synchronization is just an expensive convenience