

ESE 570: Digital Integrated Circuits and VLSI Fundamentals

Lec 25: December 9, 2020
Transmission Lines



Lecture Outline


- Transmission Lines
 - Where transmission lines arise?
 - Lossless Transmission Line
 - Termination
 - Lossy Transmission Line

Where Transmission Lines Arise



Transmission Lines

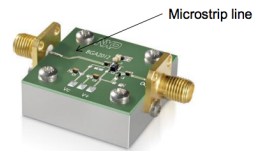- Cable: coaxial
- PCB
 - Strip line
 - Microstrip line
- Twisted Pair (Cat5)



Transmission Lines


- This is what wires/cables look like
 - Aren't an ideal equipotential
 - Signals do take time to propagate
 - Maintain shape of input signal
 - Within limits
 - Shape and topology of wiring effects how signals propagate
- Need theory/model to support design
 - Reason about behavior
 - Understand what can cause noise
 - Engineer high performance/speed communication

Wire Formulation



Wires

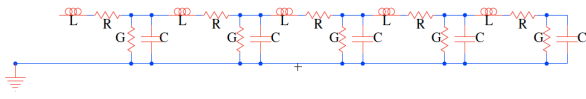- In general, our "wires" have distributed R, L, C components




Penn ESE 570 Fall 2020 – Khanna

7

7

RC Wire

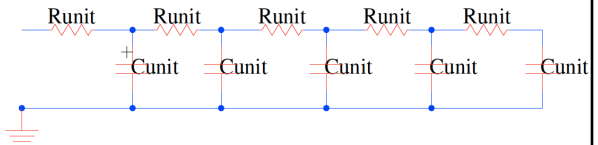- When R dominates L
 - We have the distributed RC Wires
 - Typical of on-chip wires in ICs




Penn ESE 570 Fall 2020 – Khanna

8

8

Lossless Transmission Line

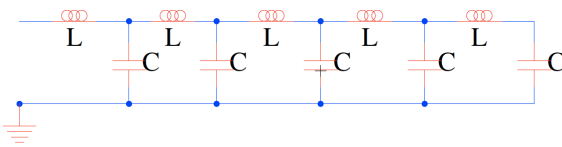- When resistance is negligible
 - Have LC wire = Lossless Transmission Line
 - No energy dissipation (loss) through R's
 - More typical of Printed Circuit Board wires and bond wires



Penn ESE 570 Fall 2020 – Khanna

9

9

Intuitive: Lossless


- Pulses travel as waves without distortion
 - (up to a characteristic frequency)

Penn ESE 570 Fall 2020 – Khanna

10

10

SPICE Simulation


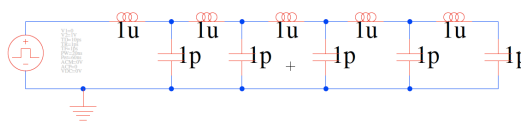


Penn ESE 570 Fall 2020 – Khanna

11

11


Step Response SPICE

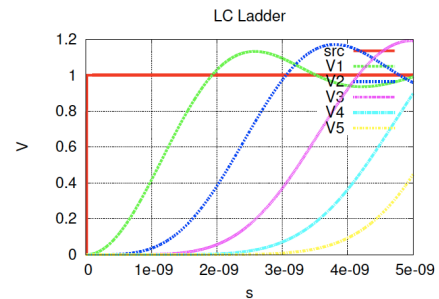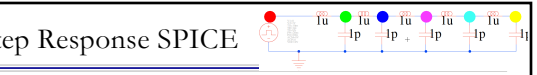


Penn ESE 570 Fall 2020 – Khanna

12

12

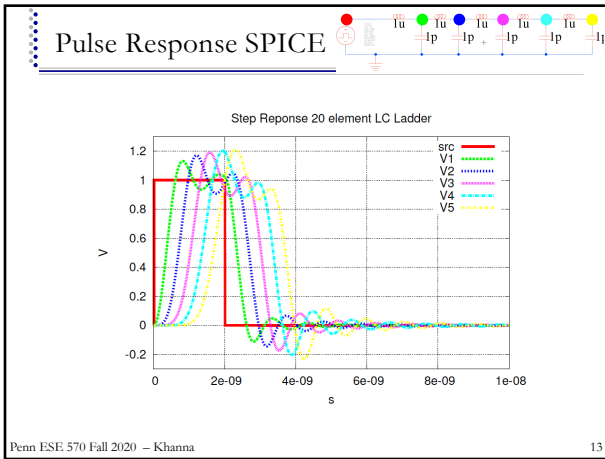

13

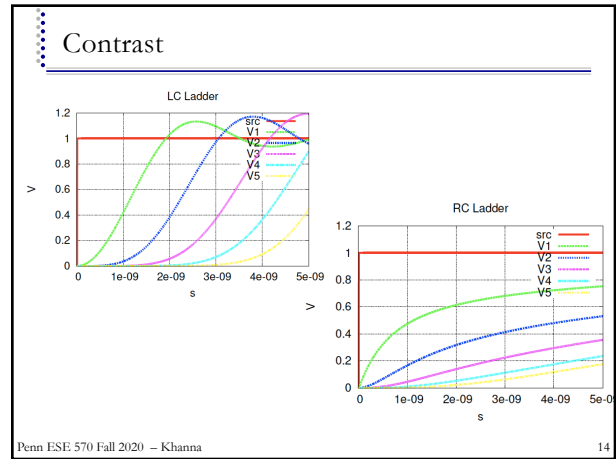


14

Model

- Now voltage is a function of time **and** position
 - Position along wire – distance from source
- Want to get $V(x,t)$
 - And $I(x,t)$

Penn ESE 570 Fall 2020 – Khanna 15

15

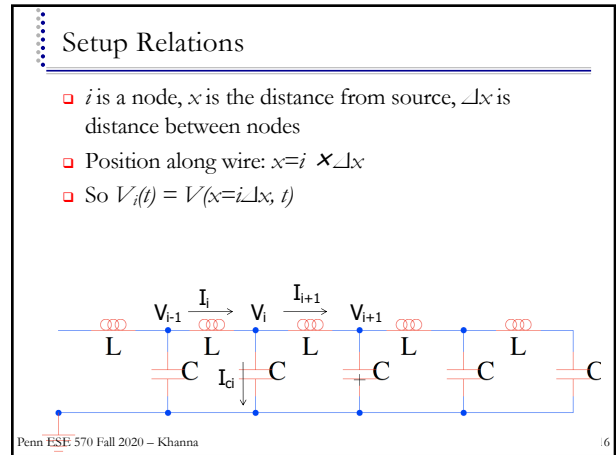

16

Implication

- Wave equation:

$$\frac{\partial^2 V}{\partial x^2} = LC \frac{\partial^2 V}{\partial t^2}$$
- Solution:


$$V(x,t) = A + Be^{x-wt}$$
- What is w ?

$$Be^{x-wt} = LCw^2 Be^{x-wt}$$


$$w = \sqrt{\frac{1}{LC}} \quad \text{w is the rate of propagation}$$

Penn ESE 570 Fall 2020 – Khanna 17


17

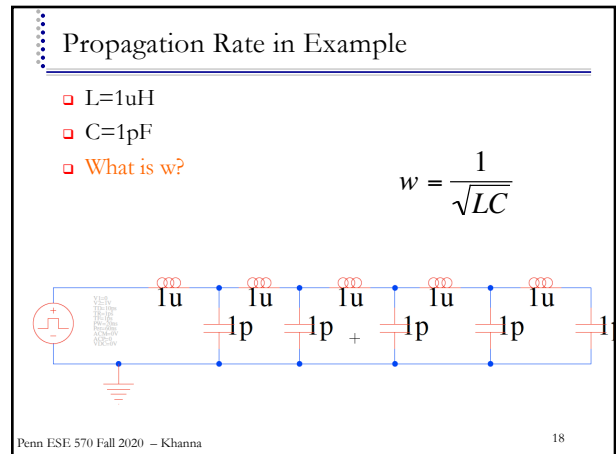


18

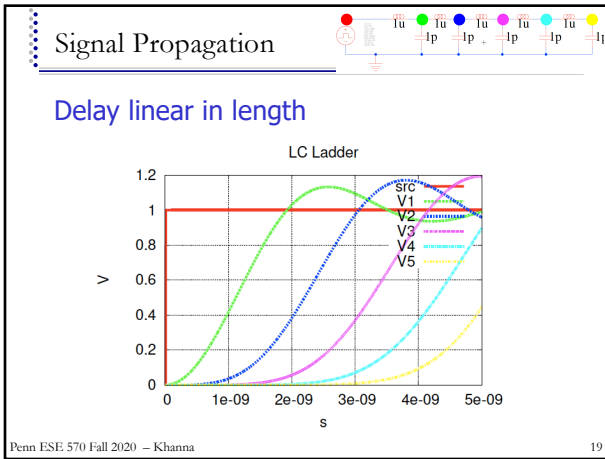


19

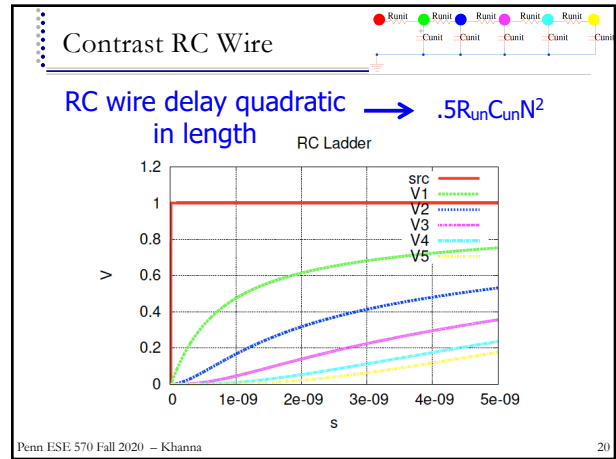


20

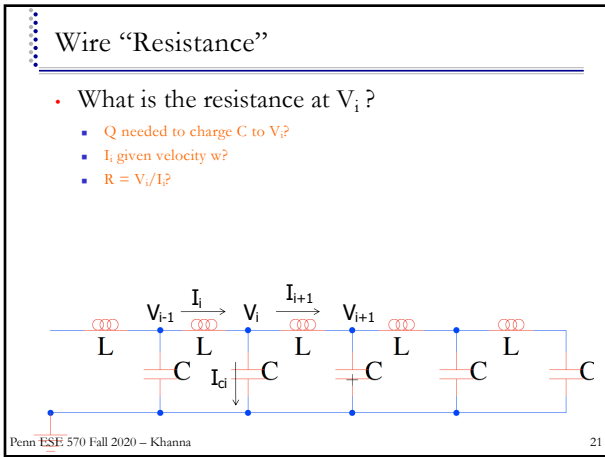


21

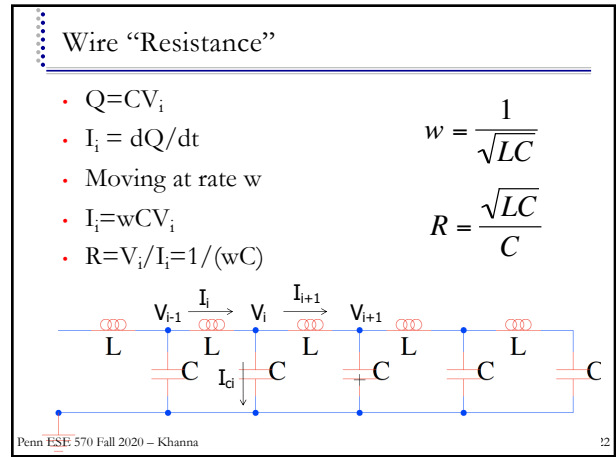

22

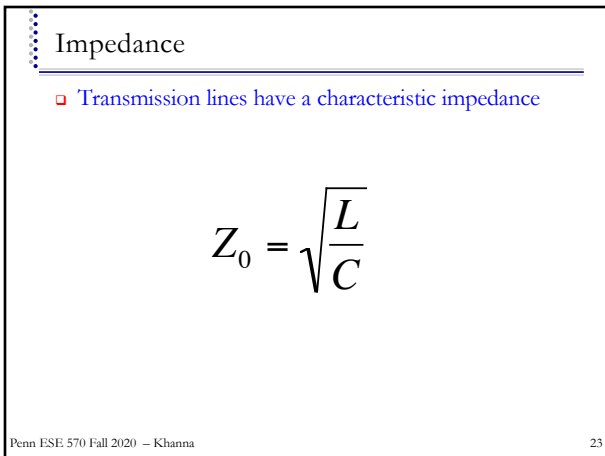

23

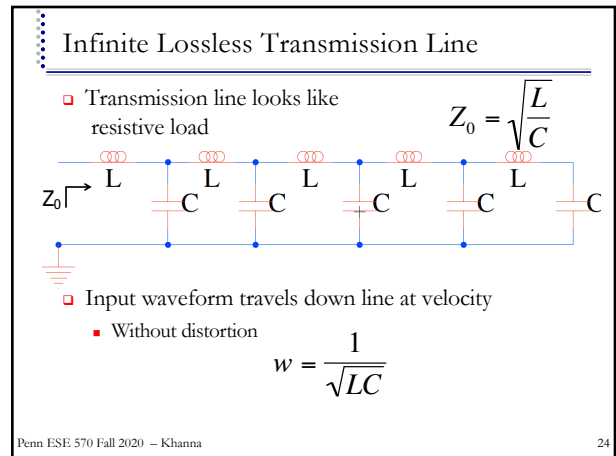

24

Termination




Penn ESE 570 Fall 2020 – Khanna

25

End of Line

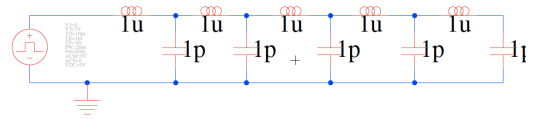- What happens at the end of the transmission line?




Penn ESE 570 Fall 2020 – Khanna

26

Analyze End of Line

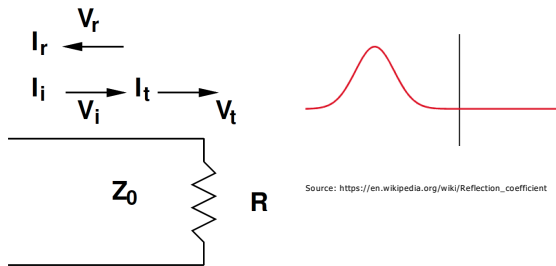- Incident Wave, Reflected Wave, Transverse Wave



Penn ESE 570 Fall 2020 – Khanna


27

27

Reflection

Reflection coefficient
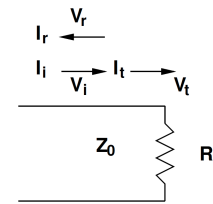
$$V_r = V_i \left(\frac{R - Z_0}{R + Z_0} \right)$$



Penn ESE 570 Fall 2020 – Khanna

28

28

Analyze End of Line

- $V_i + V_r = V_t$

$$V_i \left(\frac{R - Z_0}{R + Z_0} \right) = V_r$$

$$V_i \left(\frac{R - Z_0}{R + Z_0} \right) = V_t - V_i$$

$$V_i \left(\frac{R - Z_0}{R + Z_0} + 1 \right) = V_t$$

$$V_i \left(\frac{2R}{R + Z_0} \right) = V_t \quad \text{Transmission coefficient}$$

Penn ESE 570 Fall 2020 – Khanna


29

29

End of Line

- What happens at the end of the transmission line?

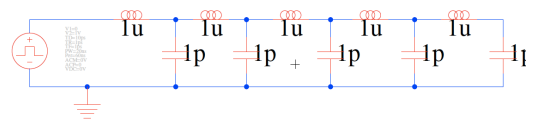
- Short Circuit, $R=0$
 - Hint: what must happen in steady state?
- Terminate with $R=Z_0$
- Open Circuit, $R=\infty$




Penn ESE 570 Fall 2020 – Khanna

30


30

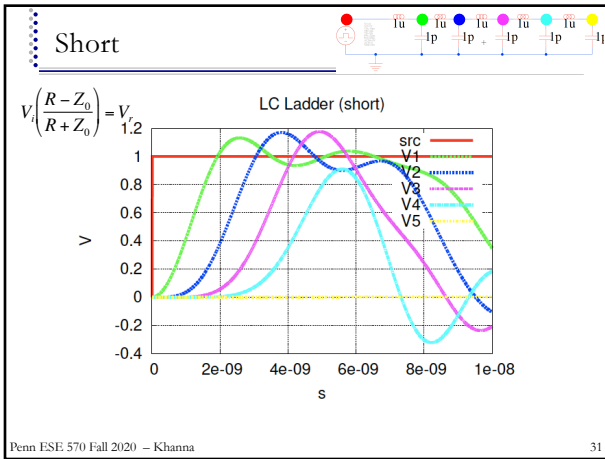

31

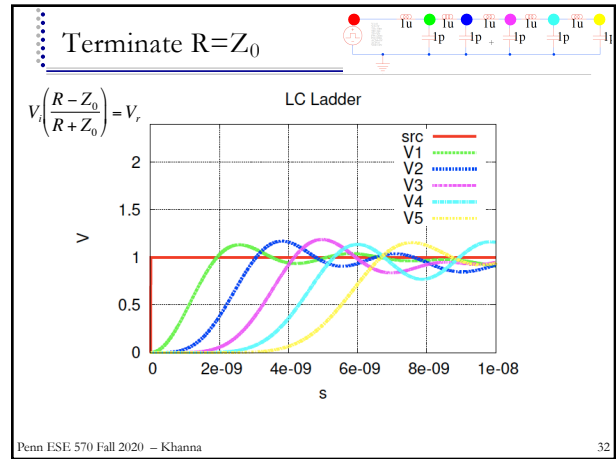

32

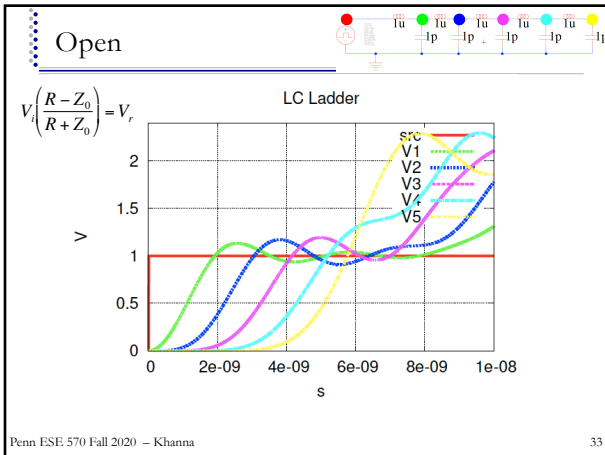

33

Longer LC (open)

- 40 Stages
- $L=100\text{nH}$
- $C=1\text{pF}$


$$w = \frac{1}{\sqrt{LC}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$

Stage delay? How long to propagate?

- Drive with 2ns Pulse
- No termination (open circuit)
 - What reflection do we expect?

Penn ESE 570 Fall 2020 – Khanna 34

34

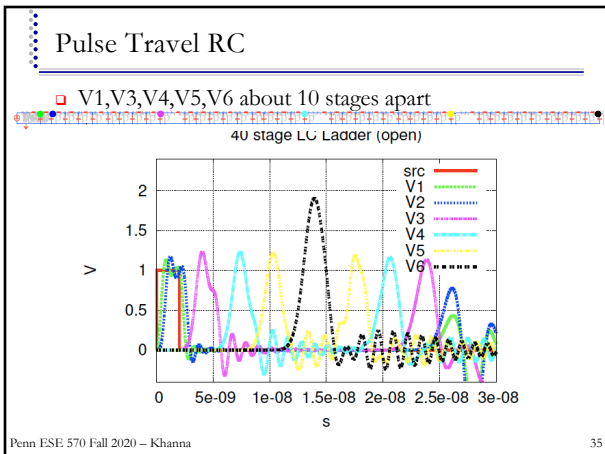

35

Visualization

<http://educyclopedia.karadimov.info/electronics/javatransmissionlines.htm>

Penn ESE 570 Fall 2020 – Khanna 36

36

Back to Source



Back at Source?


- What happens at source?
 - Depends on how it's terminated

$R \neq Z_0$

- What happens?
 - 75 Ω termination on 50 Ω line


Transmission Line Symbol

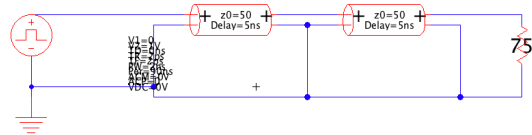- Specify delay of full Tline and characteristic impedance
- Need reference




Simulation

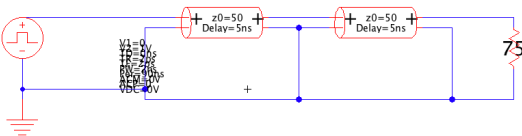- For these, with direct drive from voltage source
 - Source looks like short circuit (not typical of CMOS)
 - Source cannot be changed




50 Ω line, 75 Ω termination


Mismatch Termination

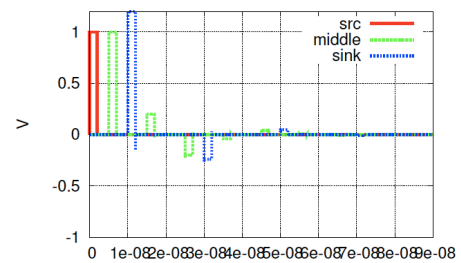

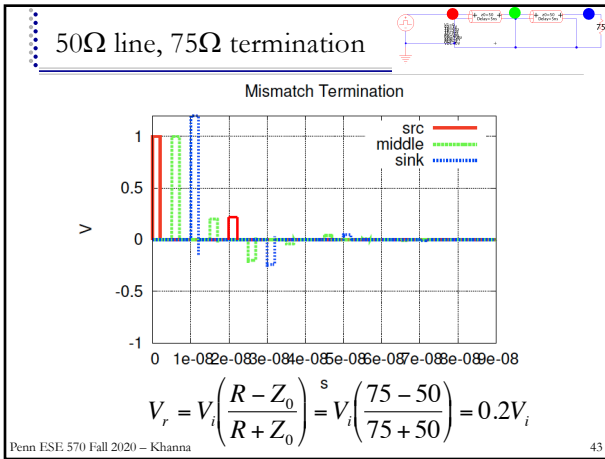
$$V_r = V_i \left(\frac{R - Z_0}{R + Z_0} \right) = V_i \left(\frac{75 - 50}{75 + 50} \right) = 0.2V_i$$




43

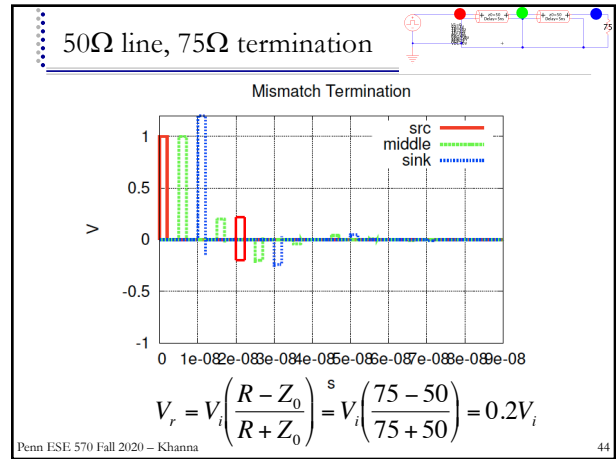


44

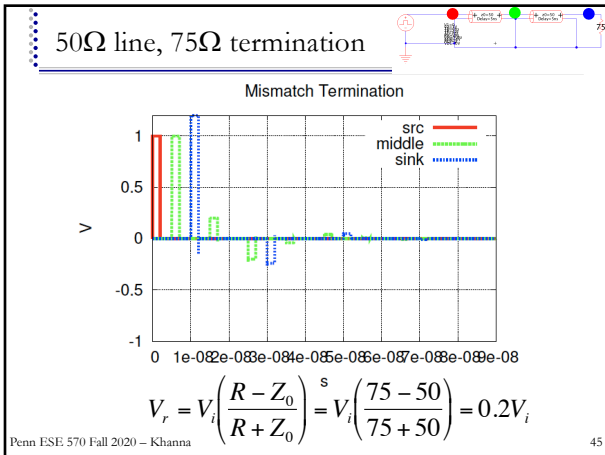

45

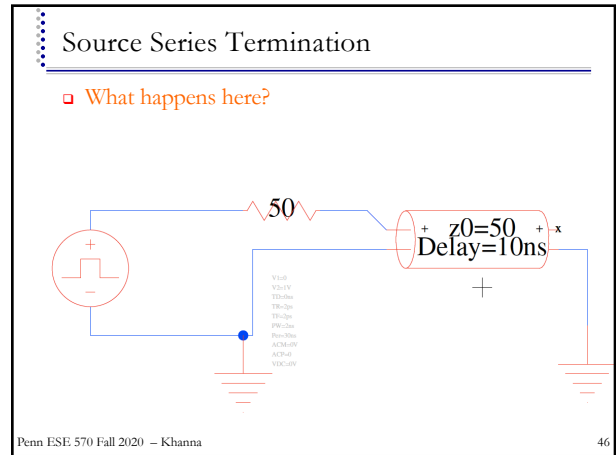

46

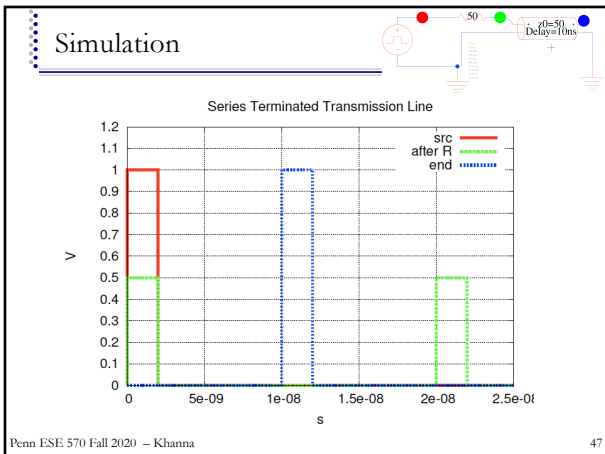

47

Series Termination


- $R_{series} = Z_0$
- Initial voltage divider
 - Half voltage pulse propagates down Tline
- End of line open circuit
 - Sees single transition to full voltage (full reflection)
- Reflection returns to source and sees termination $R_{series} = Z_0$
- No further reflections

Penn ESE 570 Fall 2020 – Khanna 48

48

CMOS Driver / Receiver

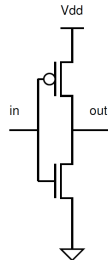- Driver: What does a CMOS driver look like at the source?
 - $I_{d,sat}=1200\mu\text{A}/\mu\text{m}$ @ 45nm, $V_{dd}=1\text{V}$
- Receiver: What does a CMOS inverter look like at the sink?




Penn ESE 570 Fall 2020 – Khanna

49

49

CMOS Driver / Receiver

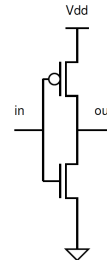- Driver: What does a CMOS driver look like at the source?
 - $I_{d,sat}=1200\mu\text{A}/\mu\text{m}$ @ 45nm, $V_{dd}=1\text{V}$
- Receiver: What does a CMOS inverter look like at the sink?
 - Infinite resistance \rightarrow Open circuit




Penn ESE 570 Fall 2020 – Khanna

50

50

CMOS Driver

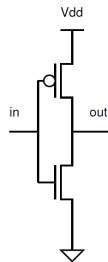- Driver: What does a CMOS driver look like at the source?
 - $I_{d,sat}=1200\mu\text{A}/\mu\text{m}$ @ 45nm, $V_{dd}=1\text{V}$
 - Min size:
 - $I_{drive}=1200\mu\text{A}/\mu\text{m} * 45\text{nm} = 54\mu\text{A}$
 - $R_{out}=V_{dd}/I_{drive}=18\text{k}\Omega$




Penn ESE 570 Fall 2020 – Khanna

51

51

CMOS Driver

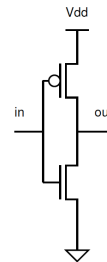- Driver: What does a CMOS driver look like at the source?
 - $I_{d,sat}=1200\mu\text{A}/\mu\text{m}$ @ 45nm, $V_{dd}=1\text{V}$
 - Min size:
 - $I_{drive}=1200\mu\text{A}/\mu\text{m} * 45\text{nm} = 54\mu\text{A}$
 - $R_{out}=V_{dd}/I_{drive}=18\text{k}\Omega$
 - $W=370$
 - $I_{drive}=1200\mu\text{A}/\mu\text{m} * 45\text{nm} * 370 = 20\text{mA}$
 - $R_{out}=V_{dd}/I_{drive}=50\Omega$




Penn ESE 570 Fall 2020 – Khanna

52

52

Lossy Transmission Line

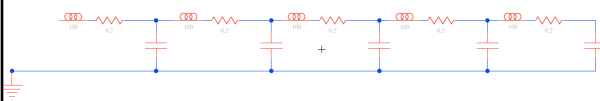- How do addition of R's change?
 - Concretely, discretely think about $R=0.2\Omega$ every meter on $Z_0=100\Omega$
 - what does each R do?



Penn ESE 570 Fall 2020 – Khanna

53


53

Lossy Transmission Line

- Each R is a mismatched termination
- Each R is a voltage divider

$$V_t = V_i \left(\frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right)$$
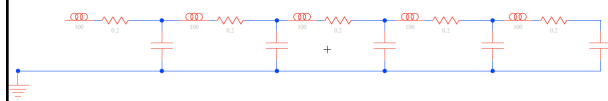
$$V_{i+1} = V_t \left(\frac{Z_0}{R + Z_0} \right)$$



Penn ESE 570 Fall 2020 – Khanna


54

54

Lossy Transmission Line

$$V_{i+1} = V_i \left(\frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right) \left(\frac{Z_0}{R + Z_0} \right)$$
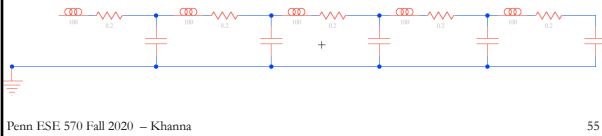
$$V_{snk} = V_{src} \left(\left(\frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right) \left(\frac{Z_0}{R + Z_0} \right) \right)^N$$



Penn ESE 570 Fall 2020 – Khanna


55

55

Lossy Transmission Line

- How long before drop voltage by half?
 $R=0.2\Omega$ every meter on $Z_0=100\Omega$
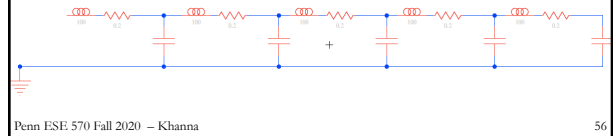
$$V_{snk} = V_{src} \left(\left(\frac{2(R + Z_0)}{(R + Z_0) + Z_0} \right) \left(\frac{Z_0}{R + Z_0} \right) \right)^N$$



Penn ESE 570 Fall 2020 – Khanna

56

56

More Examples...

Time Permitting




Penn ESE 570 Fall 2020 – Khanna

57

57

Impedance Change (Preclass 5)

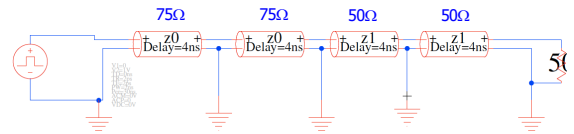- What happens if there is an impedance change in the wire? $Z_0=75\Omega$, $Z_1=50\Omega$
 - What reflections and transmission do we get?



Penn ESE 570 Fall 2020 – Khanna

58

58

$Z_0=75, Z_1=50$ (Preclass 5)

- At junction:

- Reflects

- $V_r = (50 - 75) / (50 + 75) V_i = -0.2V_i$

- Transmits

- $V_t = (100 / (50 + 75)) V_i = 0.8V_i$

$$V_i \left(\frac{R - Z_0}{R + Z_0} \right) = V_r \quad V_i \left(\frac{2R}{R + Z_0} \right) = V_t$$

Penn ESE 570 Fall 2020 – Khanna

59

59

Impedance Change $Z_0=75, Z_1=50$ (Preclass 5)


- At junction:

- Reflects

- $V_r = -0.2V_i$

- Transmits

- $V_t = 0.8V_i$

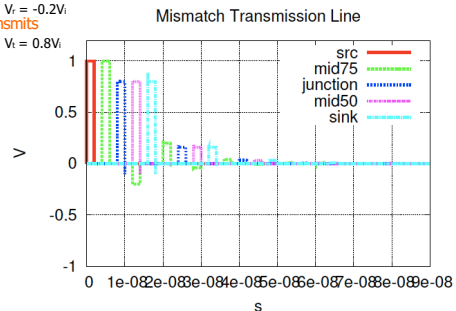


Penn ESE 570 Fall 2020 – Khanna

60

60

What happens at branch?

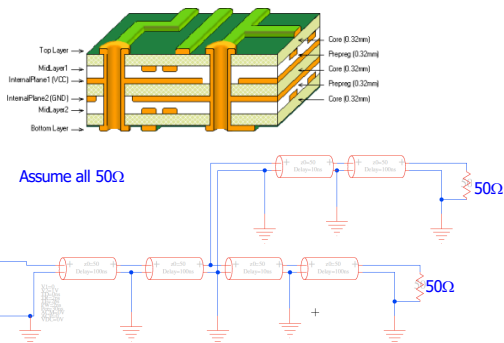


Penn ESE 570 Fall 2020 – Khanna

61

Branch

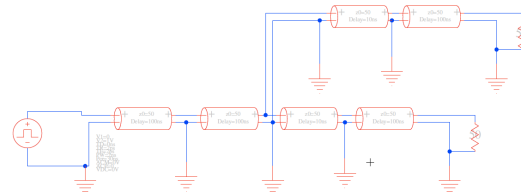- Transmission line sees two Z_0 in parallel
 - Looks like $Z_0/2$



Penn ESE 570 Fall 2020 – Khanna

62

$$Z_0=50, Z_1=25$$

- At junction:

- Reflects
 - $V_r = (25-50)/(25+50)V_i = -0.33V_i$
- Transmits
 - $V_t = (50/(25+50))V_i = 0.67V_i$


$$V_i \left(\frac{R - Z_0}{R + Z_0} \right) = V_r \quad V_i \left(\frac{2R}{R + Z_0} \right) = V_t$$

Penn ESE 570 Fall 2020 – Khanna

63

End of Branch

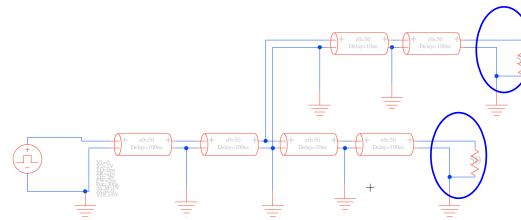- What happens at end?
- If ends in matched, parallel termination
 - No further reflections




Penn ESE 570 Fall 2020 – Khanna

64

Branch Simulation

- At junction:

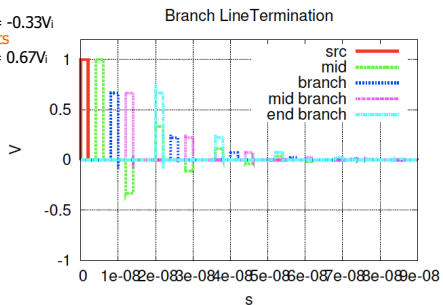- Reflects
 - $V_r = -0.33V_i$
- Transmits
 - $V_t = 0.67V_i$




Penn ESE 570 Fall 2020 – Khanna

65

Branch with Open Circuit?

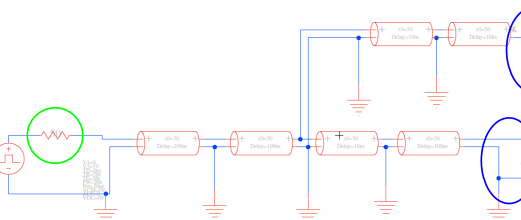- What happens if branch open circuit?
- And source termination?




Penn ESE 570 Fall 2020 – Khanna

66

Branch with Open Circuit

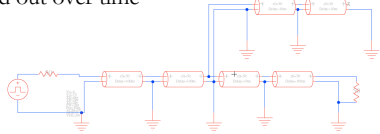- Reflects at end of open-circuit stub
- Reflection returns to branch
 - ...and encounters branch again
 - Send transmission pulse to both
 - Source and other branch
- Sink sees original pulse as multiple smaller pulses spread out over time





Penn ESE 570 Fall 2020 – Khanna

67

67

Open Branch Simulation

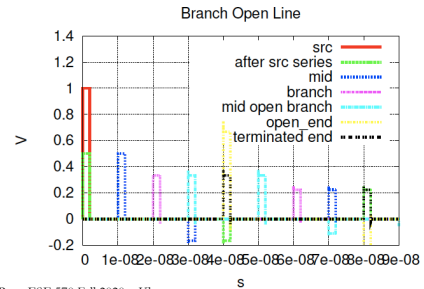
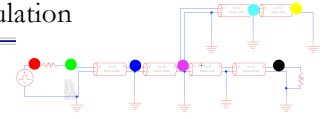


Penn ESE 570 Fall 2020 – Khanna

68

68

Open Branch Simulation

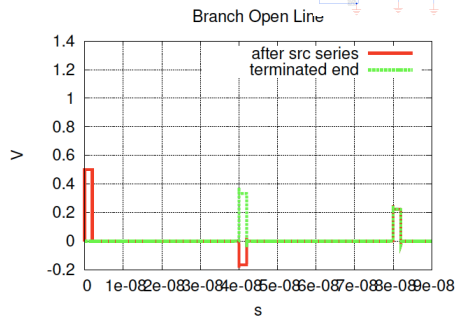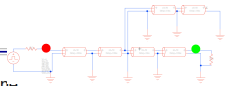

Penn ESE 570 Fall 2020 – Khanna

69

69

Idea

- Transmission lines
 - high-speed
 - high throughput
 - long-distance signaling
 - termination

Penn ESE 570 Fall 2020 – Khanna

70

70

Admin

- Final Project
 - Design CLB
 - EC for best figure of merits
 - $FOM = Area * avgEnergy / maxFrequency$
 - Due 12/10 (last day of class)
 - Can turn in up to 12/17 with no penalty

Penn ESE 570 Fall 2020 – Khanna

71

71