

EE 330

Lecture 32

Two-Port Amplifier Models


Basic amplifier architectures

- Common Emitter/Source
- Common Collector/Drain
- Common Base/Gate


Exam 3
Friday November 22

Two-port representation of amplifiers

Unilateral amplifiers:

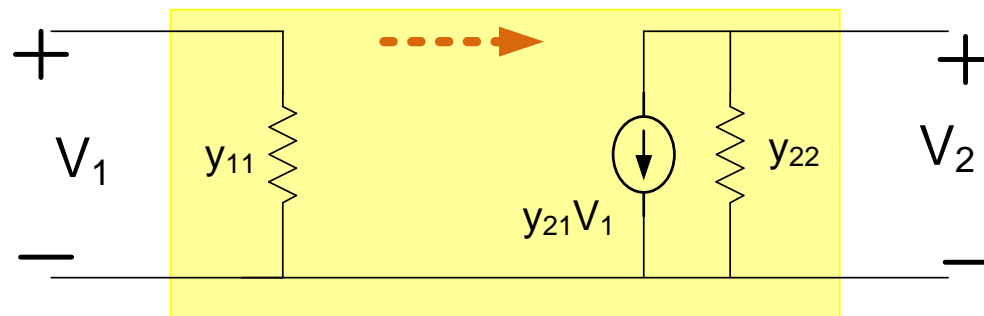

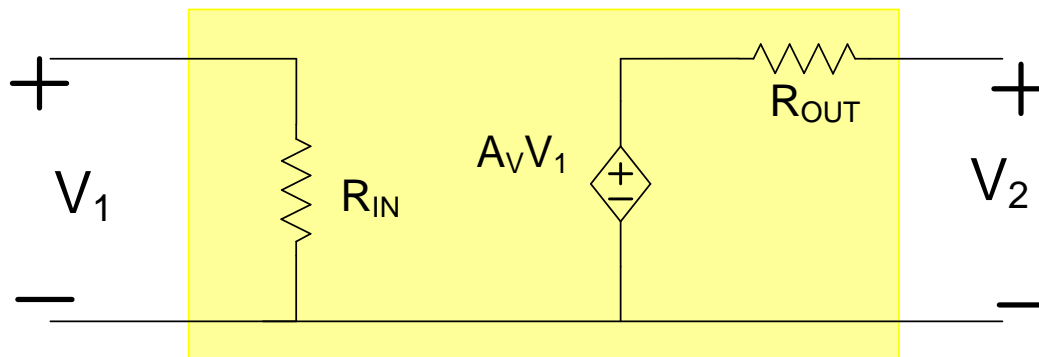
- Thevenin equivalent output port often more standard
- R_{IN} , A_V , and R_{OUT} often used to characterize the two-port of amplifiers




Unilateral amplifier in terms of “amplifier” parameters

$$R_{IN} = \frac{1}{y_{11}} \quad A_V = -\frac{y_{21}}{y_{22}} \quad R_{OUT} = \frac{1}{y_{22}}$$

Relationship with Dependent Sources ?

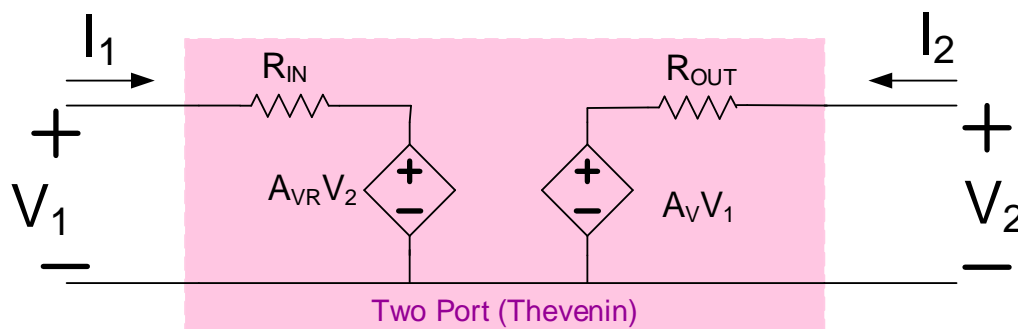


Dependent sources from EE 201

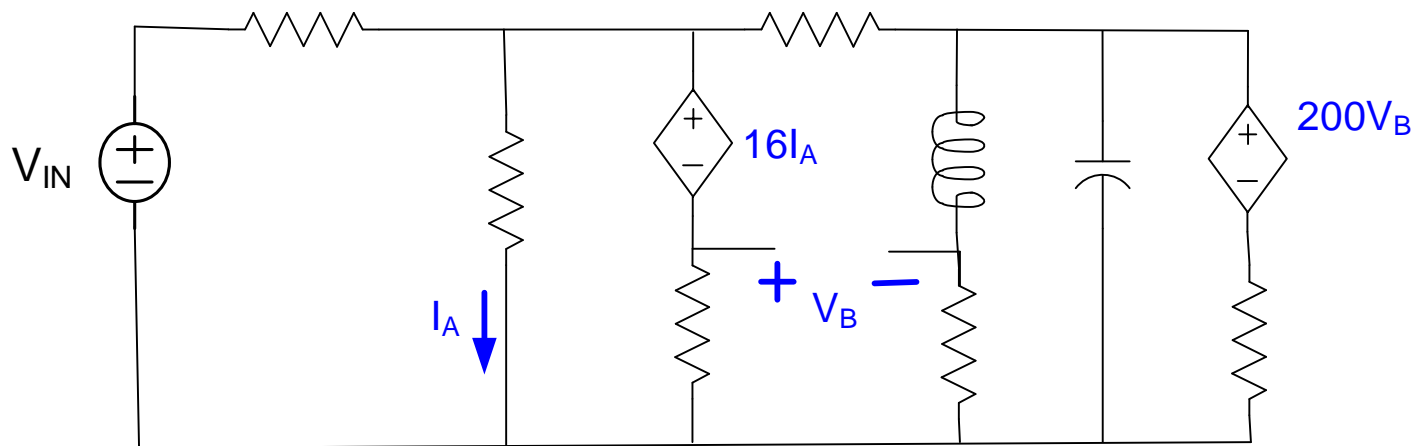

Example showing two dependent sources

Relationship with Dependent Sources ?

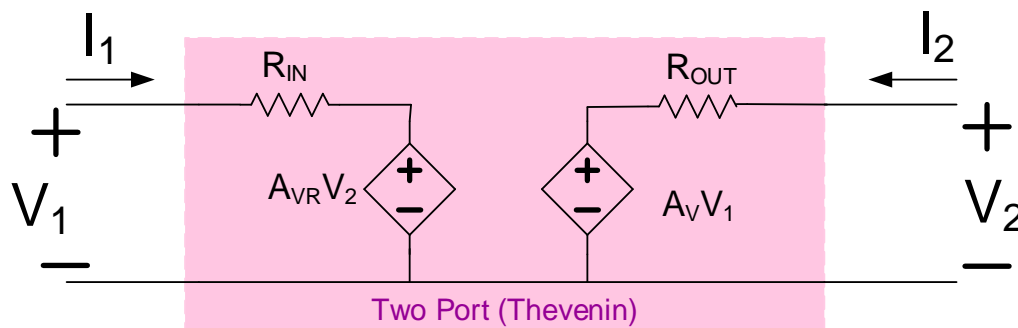


Dependent sources from EE 201

Voltage
Amplifier


$$v_s = \mu v_x$$

Voltage Dependent
Voltage Source

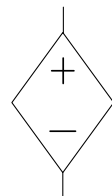

$$I_s = \alpha v_x$$

Voltage Dependent
Current Source

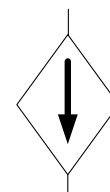


Transconductance
Amplifier

Transresistance
Amplifier


$$v_s = \rho I_x$$

Current Dependent
Voltage Source

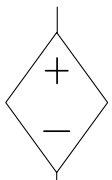


$$I_s = \beta I_x$$

Current Dependent
Current Source

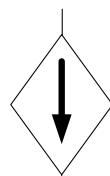


Current
Amplifier

Relationship with Dependent Sources ?

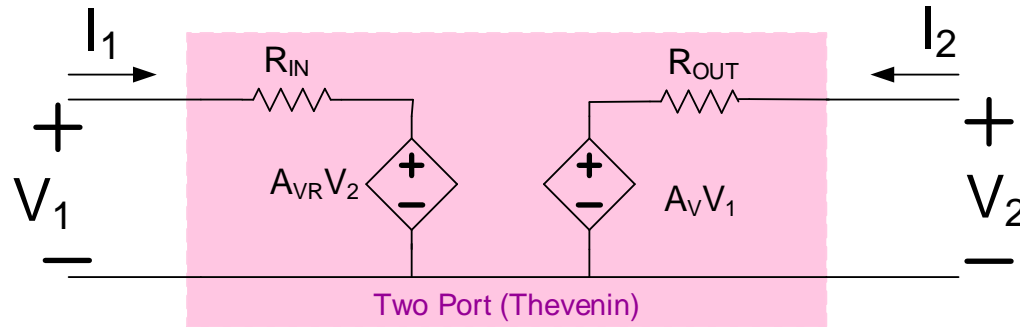


It follows that

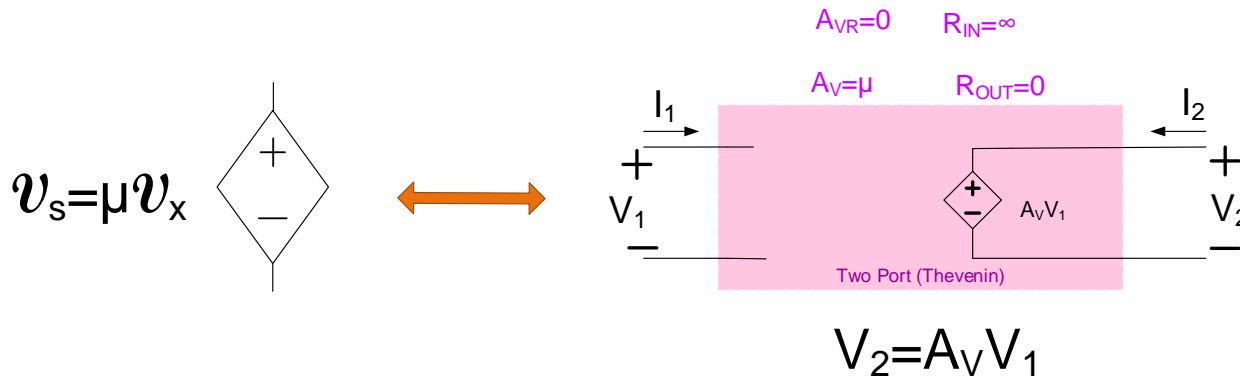


Voltage dependent voltage source is a unilateral floating two-port voltage amplifier with $R_{IN} = \infty$ and $R_{OUT} = 0$

Relationship with Dependent Sources ?

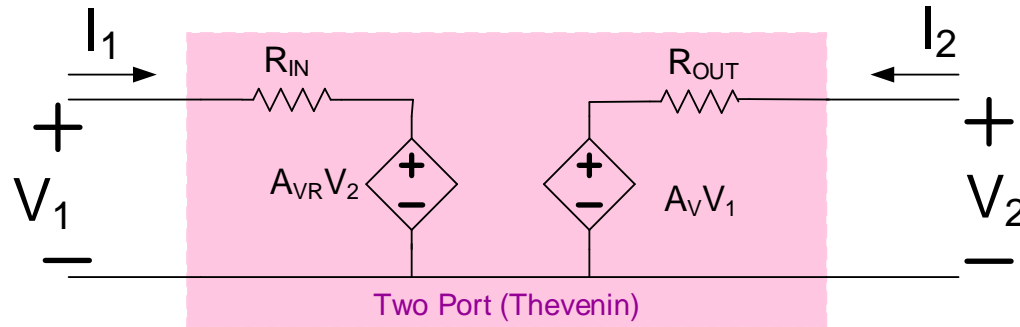


It follows that

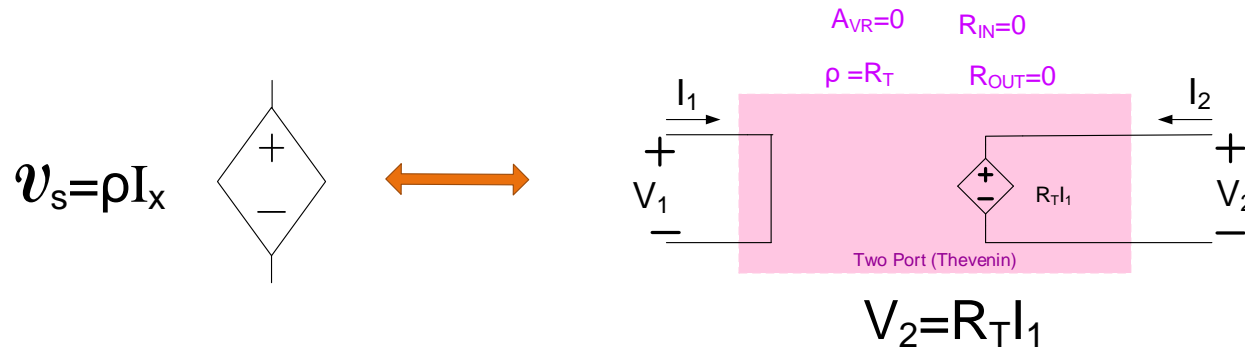


Current dependent voltage source is a unilateral floating two-port transresistance amplifier with $R_{IN}=0$ and $R_{OUT}=0$

Relationship with Dependent Sources ?

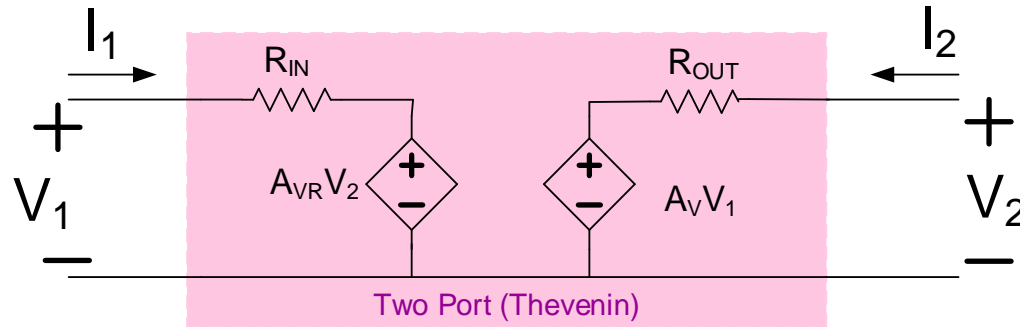


It follows that

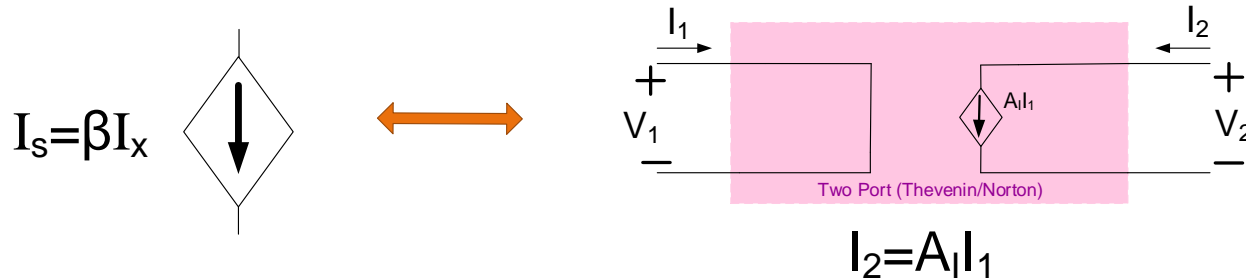


Current dependent current source is a floating unilateral two-port current amplifier with $R_{IN}=0$ and $R_{OUT}=\infty$

Relationship with Dependent Sources ?


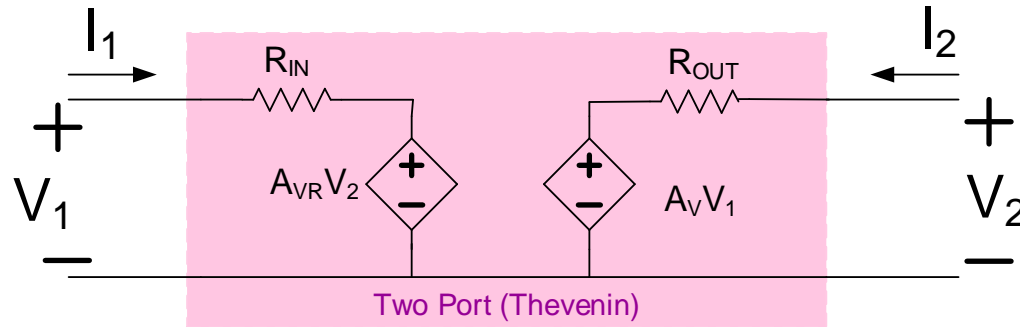


It follows that

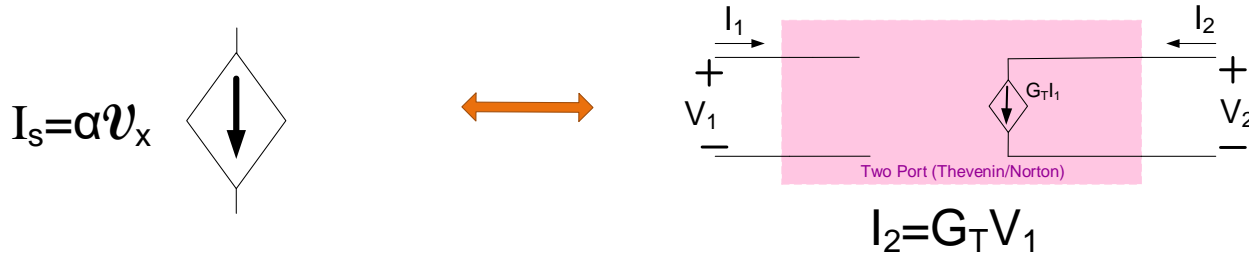

Voltage dependent current source is a floating unilateral two-port transconductance amplifier with $R_{IN} = \infty$ and $R_{OUT} = \infty$

Dependent Sources

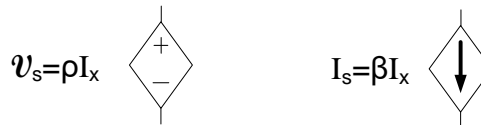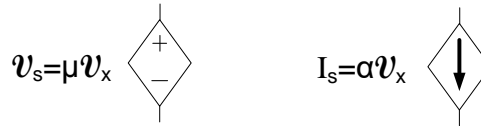

Dependent sources are unilateral two-port amplifiers with ideal input and output impedances

Dependent sources do not exist as basic circuit elements but amplifiers can be designed to perform approximately like a dependent source




- Practical dependent sources typically are not floating on input or output
- One terminal is usually grounded
- Input and output impedances of realistic structures are usually not ideal

Why were “dependent sources” introduced as basic circuit elements instead of two-port amplifiers in the basic circuits courses???

Why was the concept of “dependent sources” not discussed in the basic electronics courses???



Basic Amplifier Structures

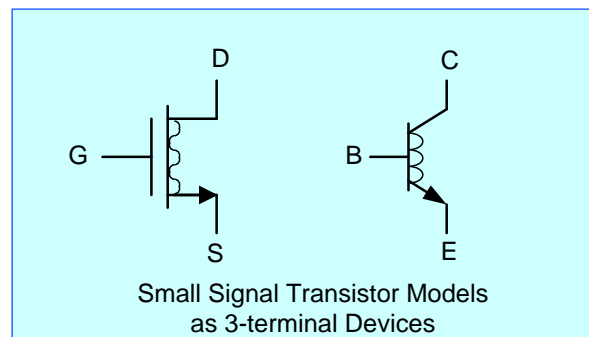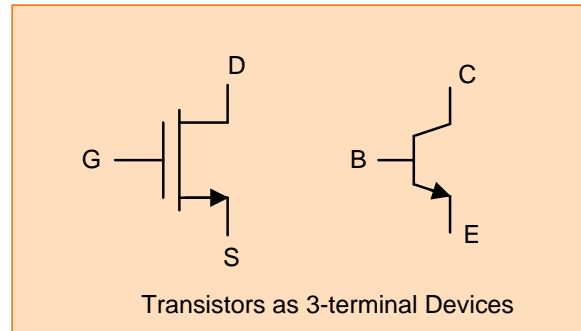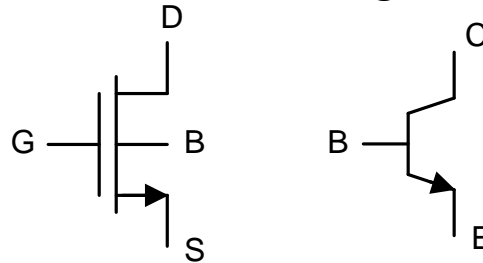- MOS and Bipolar Transistors both have 3 primary terminals
- MOS transistor has a fourth terminal that is generally considered a parasitic terminal



Basic Amplifier Structures

Observation:

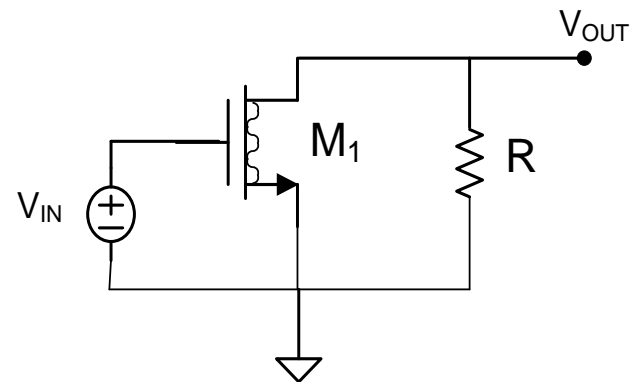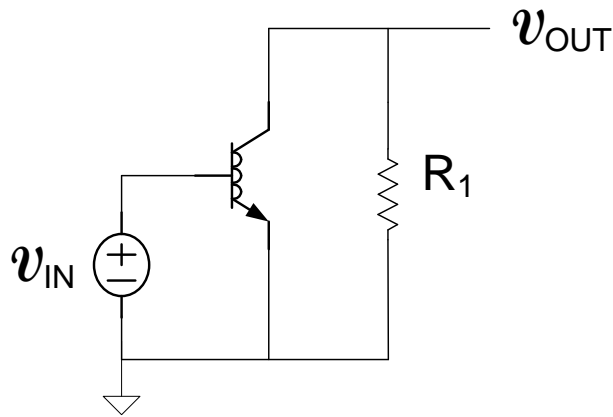

These circuits considered previously have a terminal (emitter or source) common to the input and output in the small-signal equivalent circuit


For BJT, E is common, input on B, output on C

Termed “Common Emitter”

For MOSFET, S is common, input on G, output on D

Termed “Common Source”

Basic Amplifier Structures

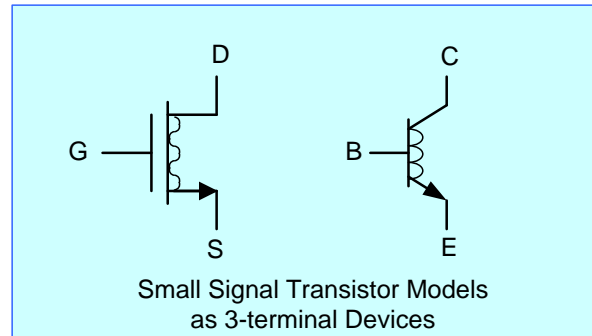


Amplifiers using these devices generally have one terminal common and use remaining terminals as input and output

Since devices are nearly unilateral, designation of input and output terminals is uniquely determined

Three different ways to designate the common terminal

Source or Emitter	termed Common Source or Common Emitter
Gate or Base	termed Common Gate or Common Base
Drain or Collector	termed Common Drain or Common Collector

Basic Amplifier Structures

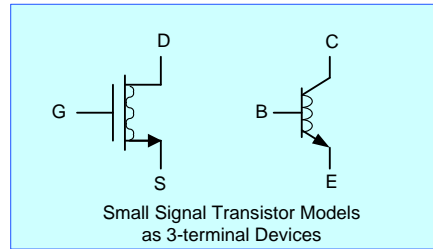

Common Source or Common Emitter

Common Gate or Common Base

Common Drain or Common Collector


	MOS		
	Common	Input	Output
Common Source or Common Emitter	S	G	D
Common Gate or Common Base	G	S	D
Common Drain or Common Collector	D	G	S

	BJT		
	Common	Input	Output
Common Source or Common Emitter	E	B	C
Common Gate or Common Base	B	E	C
Common Drain or Common Collector	C	B	E

Identification of Input and Output Terminals is not arbitrary

It will be shown that all 3 of the basic amplifiers are useful !

Basic Amplifier Structures

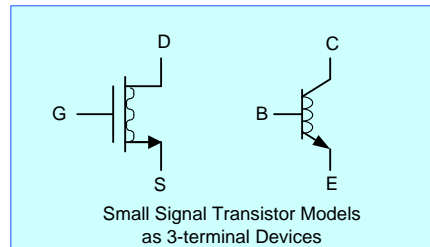


Common Source or Common Emitter

Common Gate or Common Base


Common Drain or Common Collector

Objectives in Study of Basic Amplifier Structures

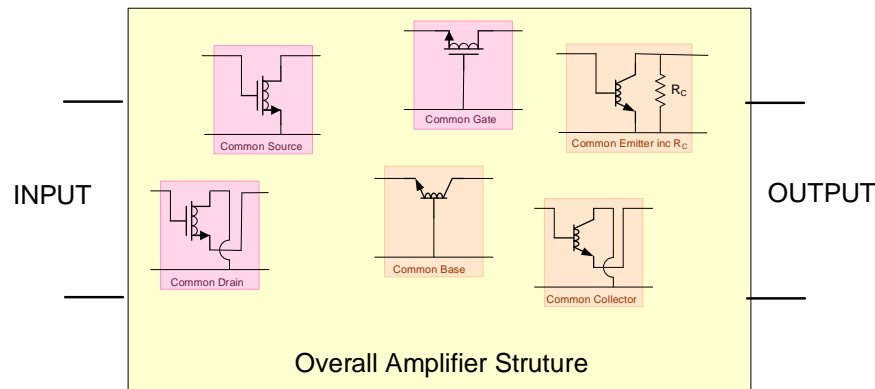
1. Obtain key properties of each basic amplifier
2. Develop method of designing amplifiers with specific characteristics using basic amplifier structures








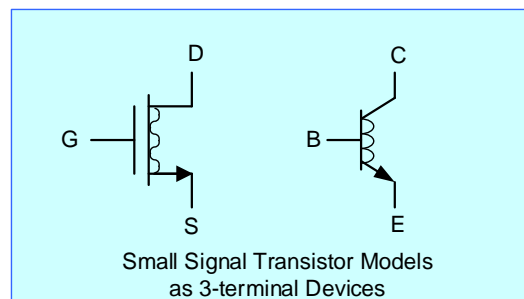
Characterization of Basic Amplifier Structures



- Observe that the small-signal equivalent of any 3-terminal network is a two-port
- Thus to characterize any of the 3 basic amplifier structures, it suffices to determine the two-port equivalent network
- Since small signal model when expressed in terms of small-signal parameters of BJT and MOSFET differ only in the presence/absence of g_{π} term, can analyze the BJT structures and then obtain characteristics of corresponding MOS structure by setting $g_{\pi}=0$


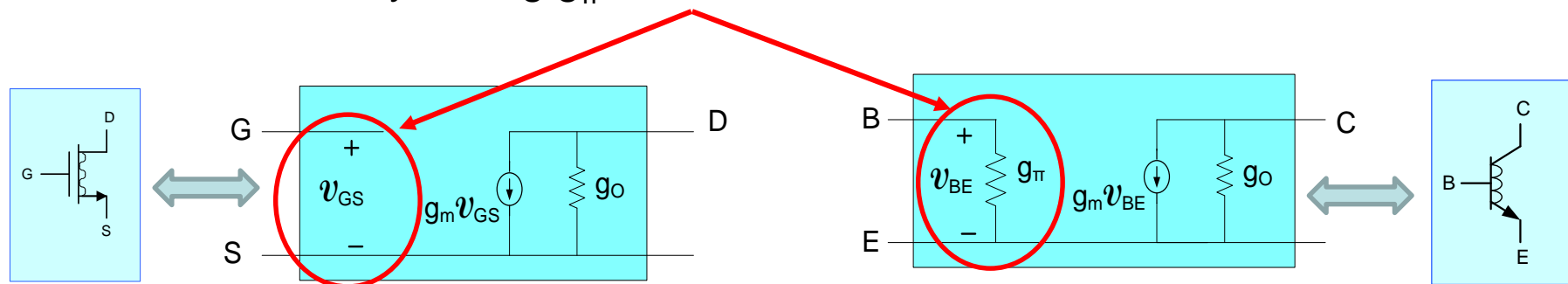


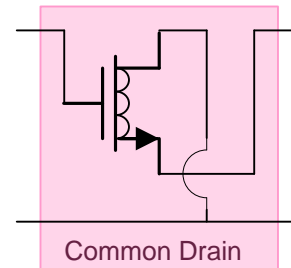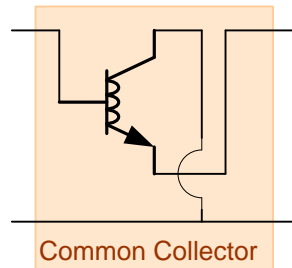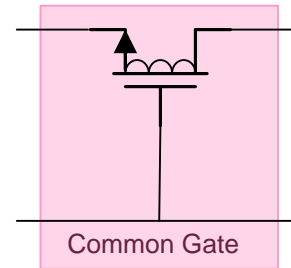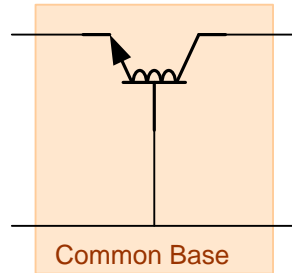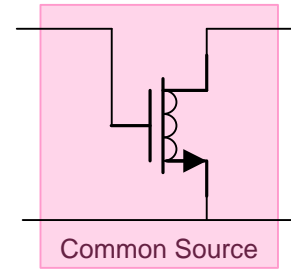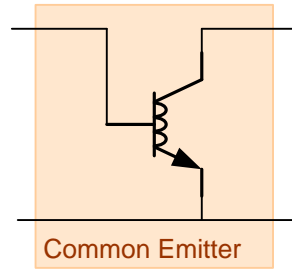The three basic amplifier types for both MOS and bipolar processes





Will focus on the performance of the bipolar structures and then obtain performance of the MOS structures by observation

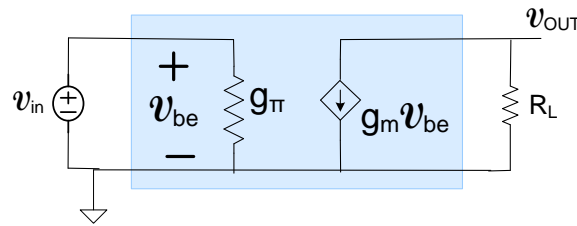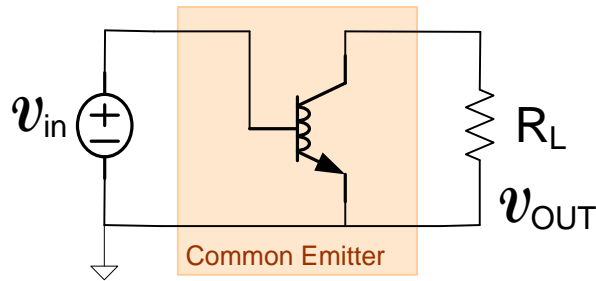The three basic amplifier types for both MOS and bipolar processes





$$\left. \begin{aligned} v_{OUT} &= -g_m R_L v_{be} \\ v_{IN} &= v_{be} \end{aligned} \right\}$$
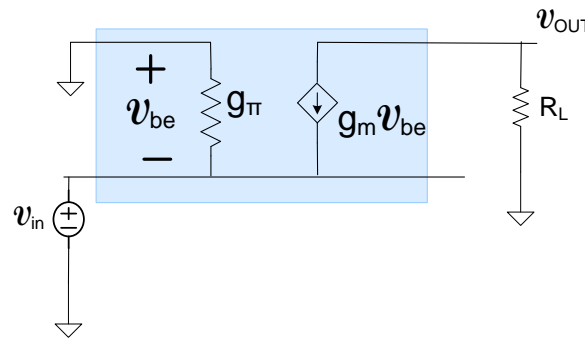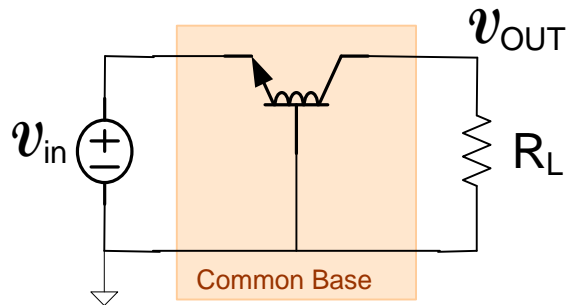
$$A_V = \frac{v_{OUT}}{v_{IN}} = -g_m R_L$$



$$\left. \begin{aligned} v_{OUT} &= -g_m R_L v_{be} \\ v_{IN} &= -v_{be} \end{aligned} \right\}$$
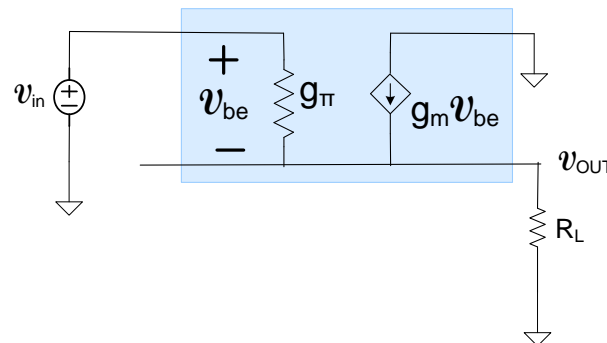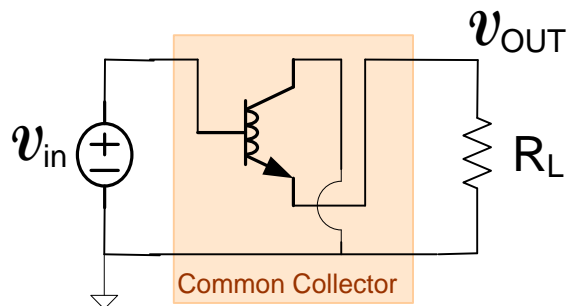
$$A_V = \frac{v_{OUT}}{v_{IN}} = g_m R_L$$












$$\left. \begin{aligned} v_{OUT} &= (g_m + g_\pi) v_{be} R_L \\ v_{IN} &= v_{be} + (g_m + g_\pi) v_{be} R_L \end{aligned} \right\}$$

$$A_V = \frac{v_{OUT}}{v_{IN}} = \frac{(g_m + g_\pi) R_L}{1 + (g_m + g_\pi) R_L} \cong 1$$

- Significantly different gain characteristics for the three basic amplifiers
- There are other significant differences too (R_{IN} , R_{OUT} , ...) as well

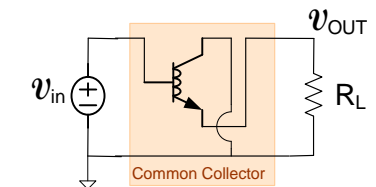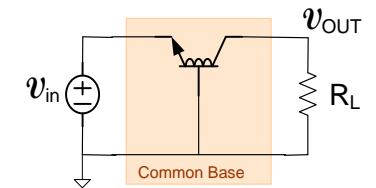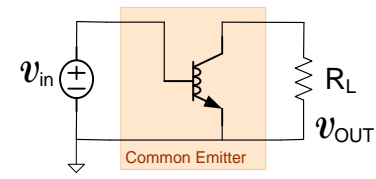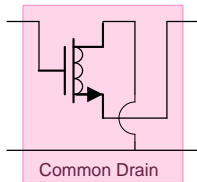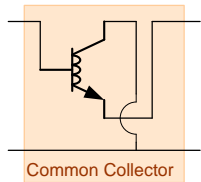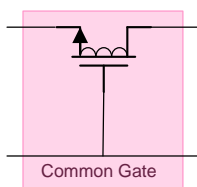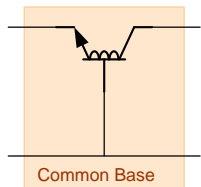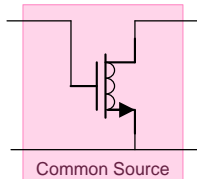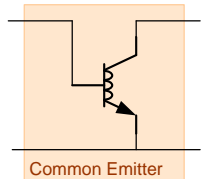The three basic amplifier types for both MOS and bipolar processes




More general models are needed to accommodate biasing, understand performance capabilities, and include effects of loading of the basic structures

Two-port models are useful for characterizing the basic amplifier structures

How can the two-port parameters be obtained for these or any other linear two-port networks?

Two-Port Models of Basic Amplifiers widely used for Analysis and Design of Amplifier Circuits

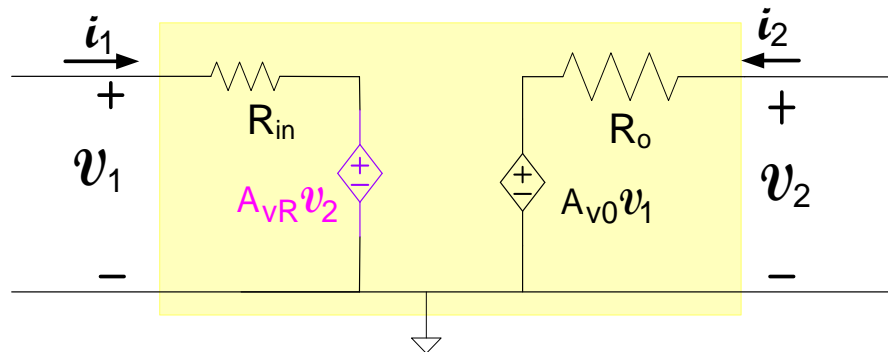Methods of Obtaining Amplifier Two-Port Network



1. $v_{\text{TEST}} : i_{\text{TEST}}$ Method (considered in a previous lecture)

2. Write $v_1 : v_2$ equations in standard form

$$v_1 = i_1 R_{\text{IN}} + A_{\text{VR}} v_2$$

$$v_2 = i_2 R_{\text{O}} + A_{\text{V0}} v_1$$


3. Thevenin-Norton Transformations

4. Ad Hoc Approaches


Any of these methods can be used to obtain the two-port model

$v_{\text{test}} : i_{\text{test}}$ Method for Obtaining Two-Port Amplifier Parameters


SUMMARY from PREVIOUS LECTURE

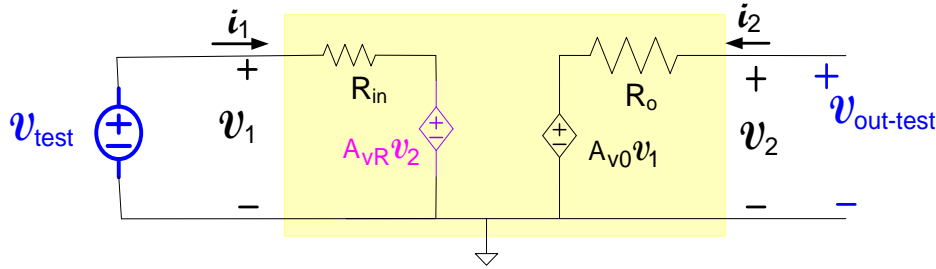

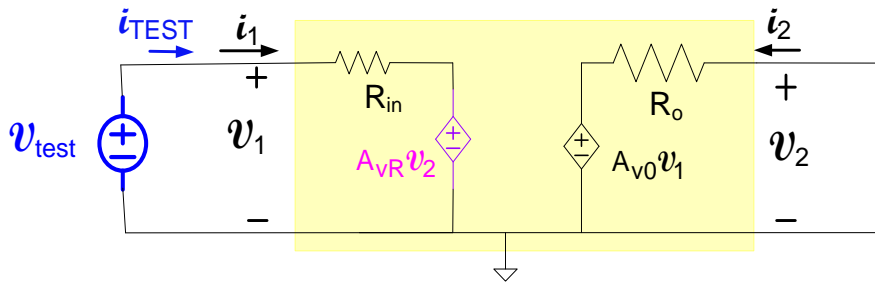
$$A_{V0} = \frac{v_{\text{out-test}}}{v_{\text{test}}}$$


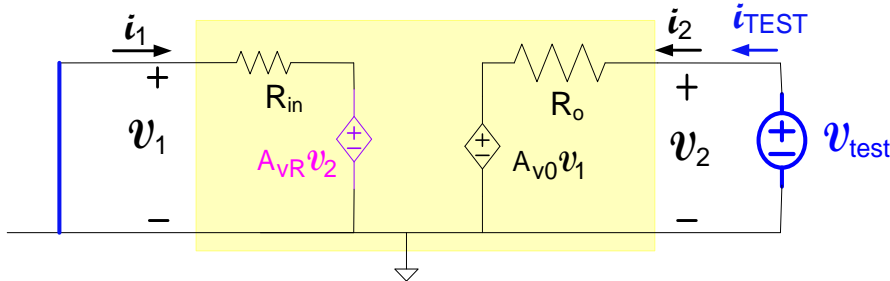
$$R_{\text{in}} = \frac{v_{\text{test}}}{i_{\text{test}}}$$



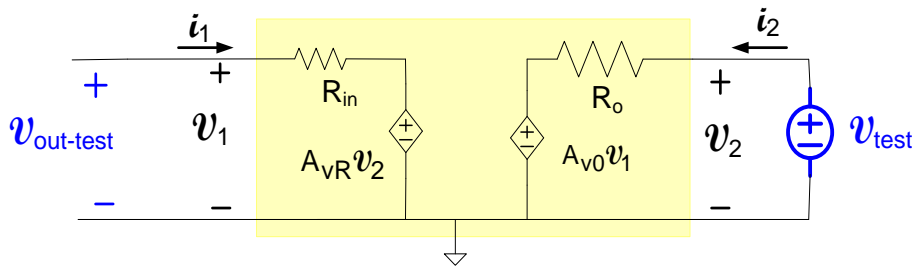
$$R_0 = \frac{v_{\text{test}}}{i_{\text{test}}}$$




$$A_{VR} = \frac{v_{\text{out-test}}}{v_{\text{test}}}$$

If Unilateral $A_{VR} = 0$

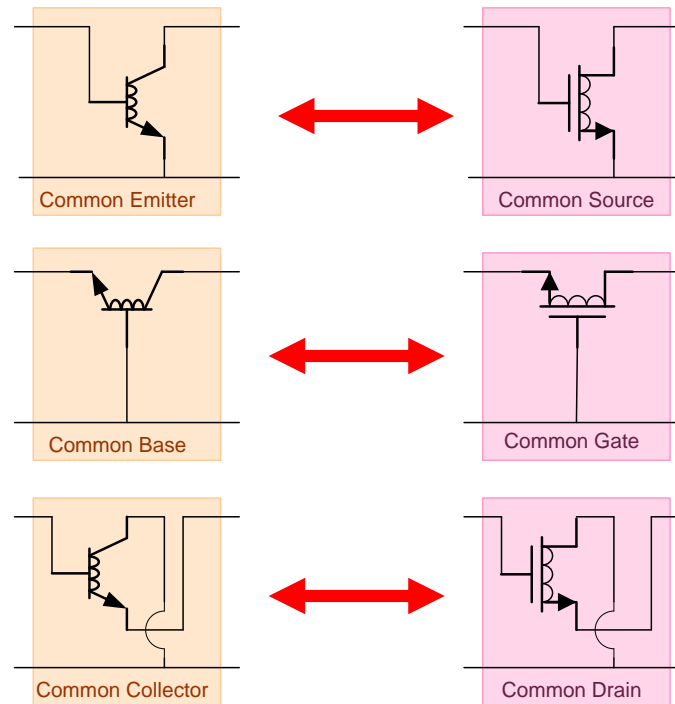Will now develop two-port model for each of the three basic amplifiers and look at one widely used application of each







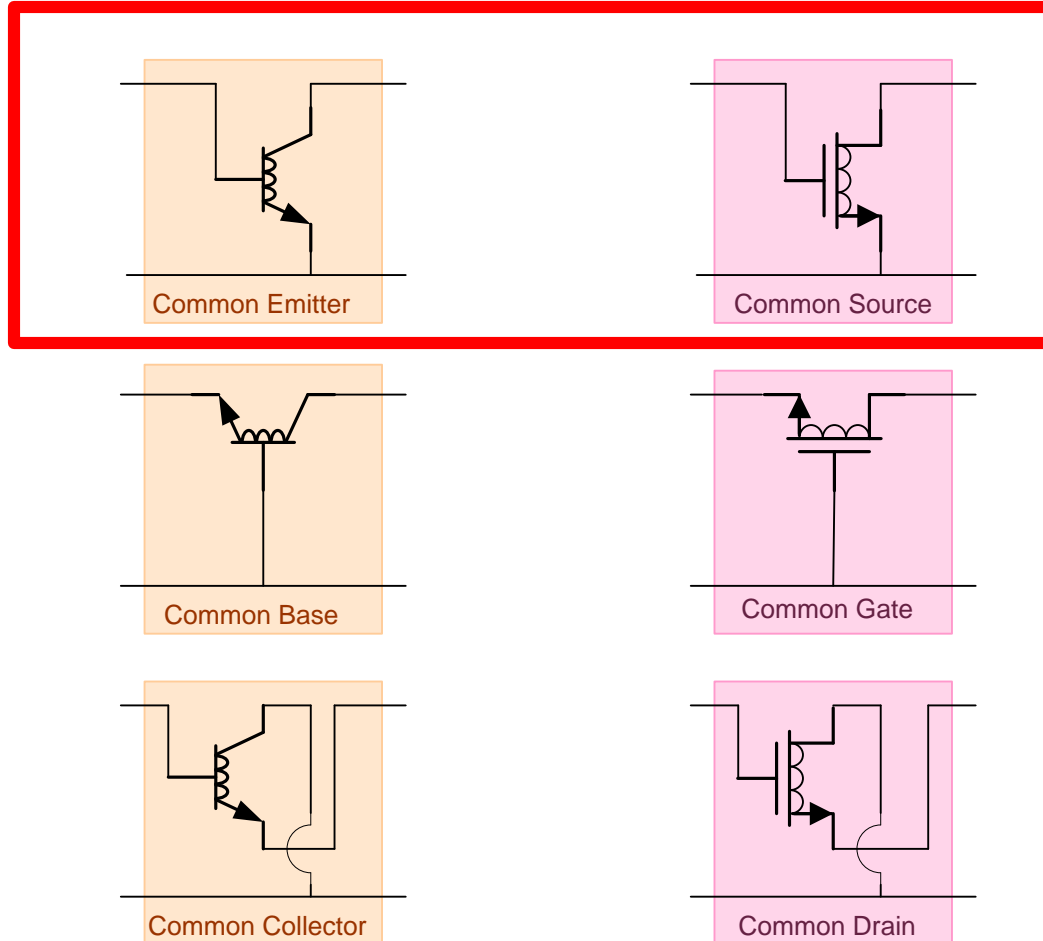Consider Common Emitter/Common Source Two-port Models



Will focus on Bipolar Circuit since MOS counterpart is a special case obtained by setting $g_{\pi}=0$




Basic CE/CS Amplifier Structures

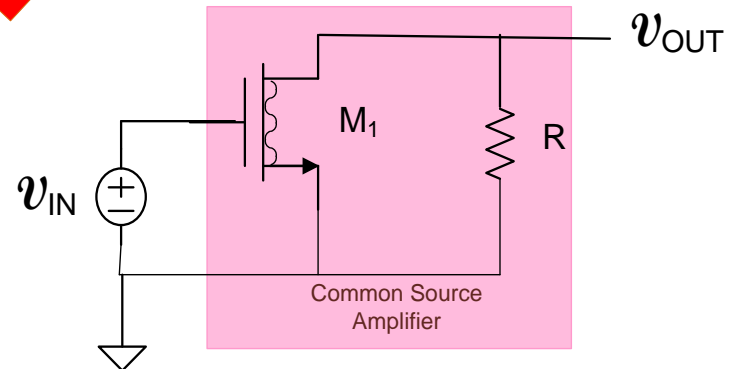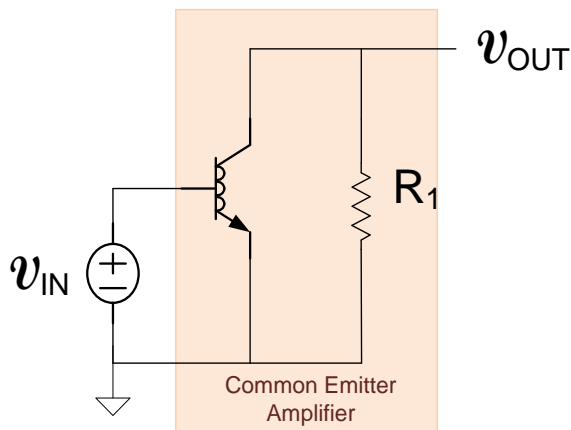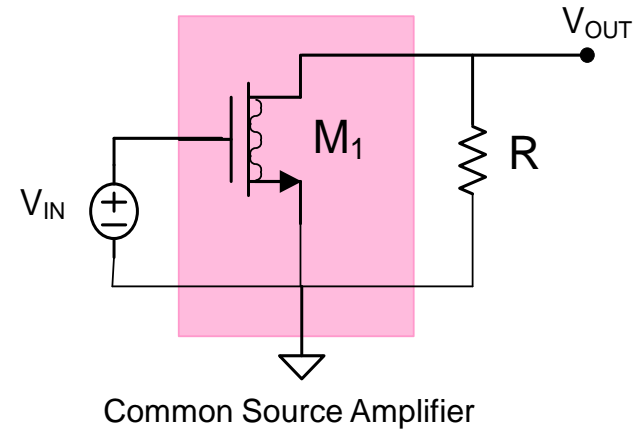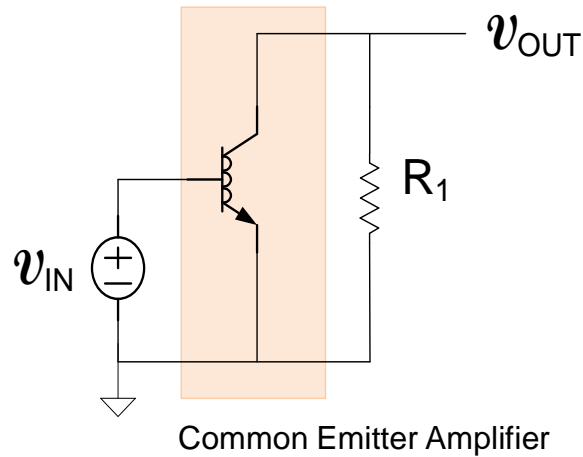

Can include or exclude R and R_1 in two-port models (of course they are different circuits)

The CE and CS amplifiers are themselves two-ports !

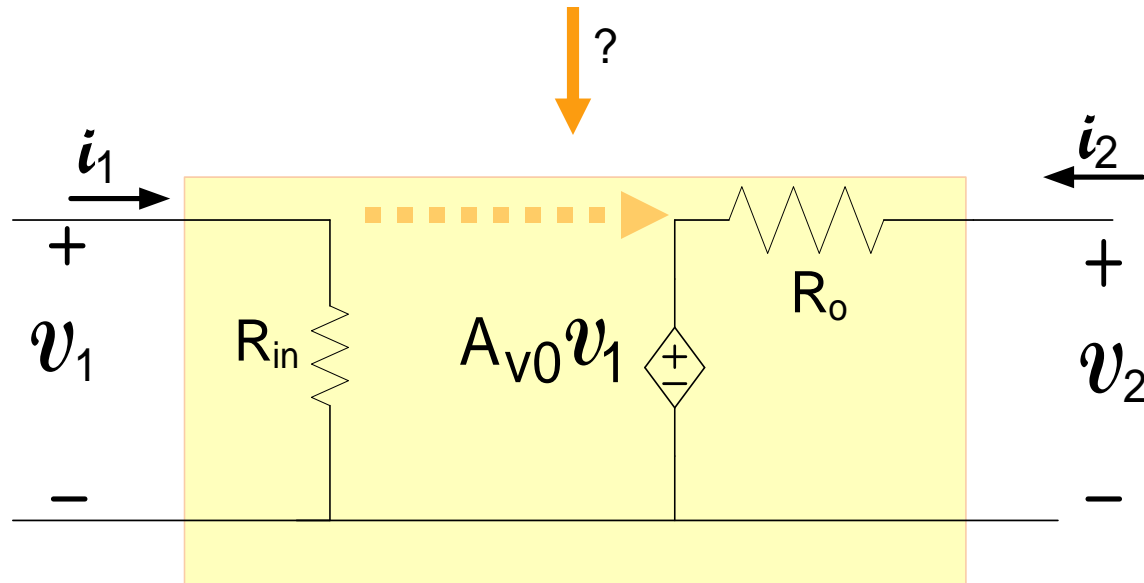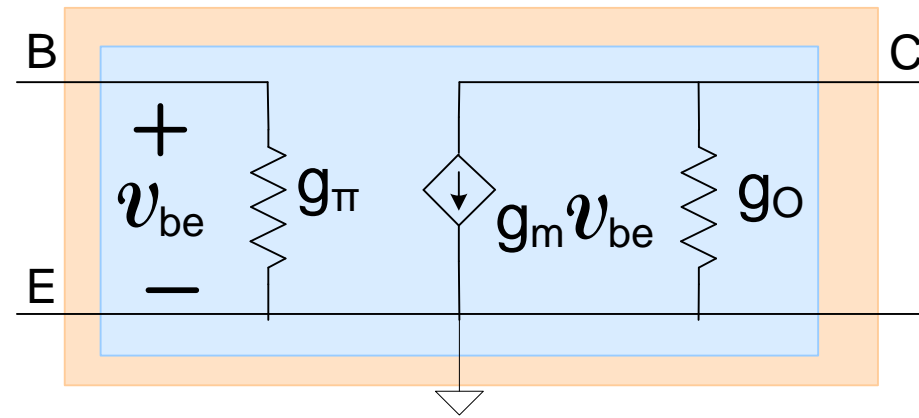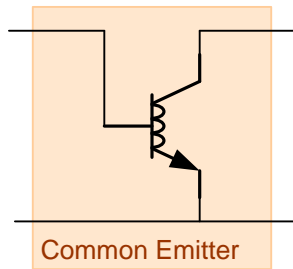
Two-port model for Common Emitter Configuration



{ R_i , A_{v0} and R_o }

Two-Port Models of Basic Amplifiers widely used for Analysis and Design of Amplifier Circuits

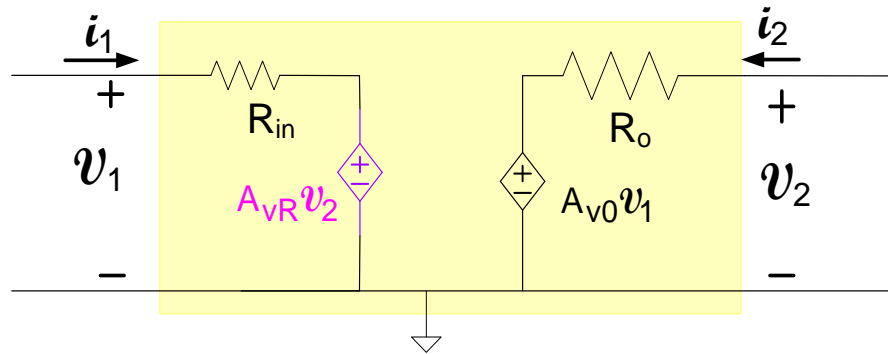Methods of Obtaining Amplifier Two-Port Network






1. $v_{\text{TEST}} : i_{\text{TEST}}$ Method
2. Write $v_1 : v_2$ equations in standard form
$$v_1 = i_1 R_{\text{IN}} + A_{\text{VR}} v_2$$
$$v_2 = i_2 R_{\text{O}} + A_{\text{V0}} v_1$$



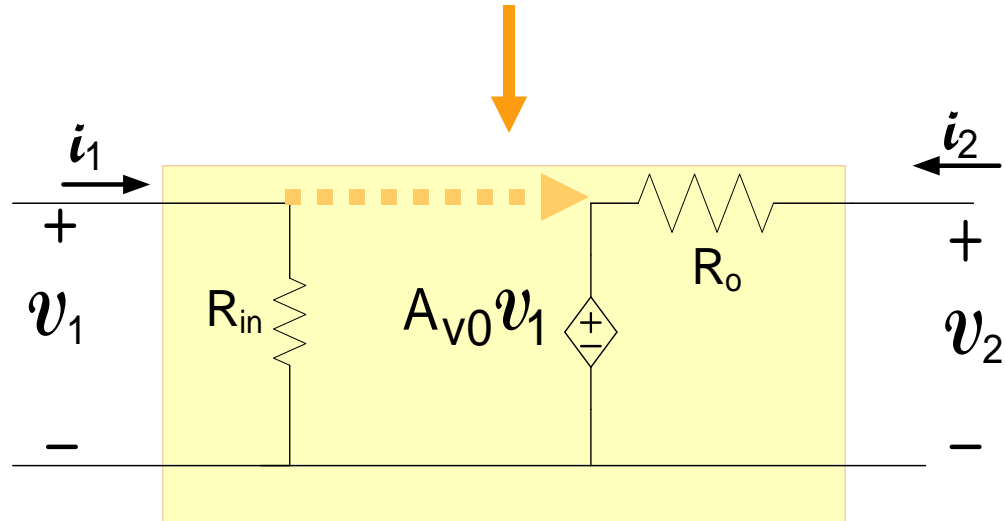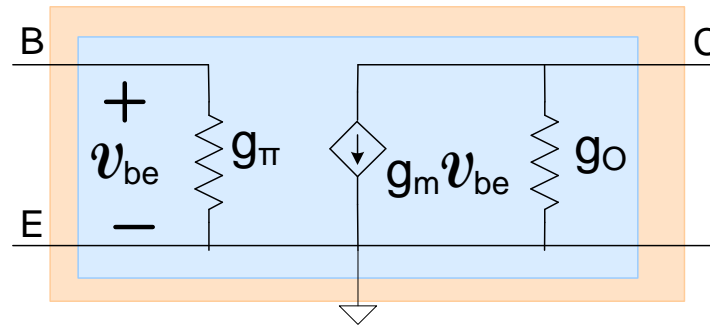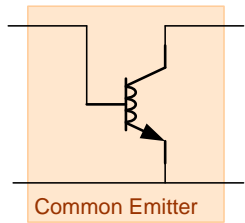3. Thevenin-Norton Transformations
4. Ad Hoc Approaches

Two-port model for Common Emitter Configuration



By Thevenin : Norton Transformations

$$R_{in} = \frac{1}{g_{\pi}}$$


$$A_{V0} = -\frac{g_m}{g_o}$$

$$R_o = \frac{1}{g_o}$$

$$A_{VR} = 0$$

Two-Port Models of Basic Amplifiers widely used for Analysis and Design of Amplifier Circuits

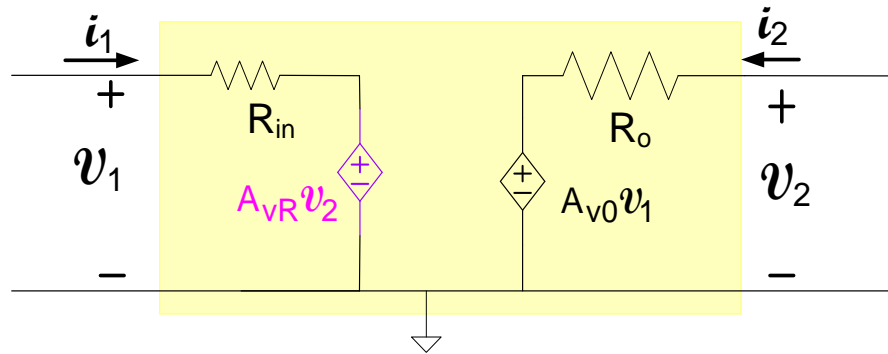Methods of Obtaining Amplifier Two-Port Network






1. $v_{TEST} : i_{TEST}$ method
2. Write $v_1 : v_2$ equations in standard form
$$v_1 = i_1 R_{IN} + A_{VR} v_2$$
$$v_2 = i_2 R_O + A_{V0} v_1$$
3. Thevenin-Norton Transformations
4. Ad Hoc Approaches



Two-port model for Common Emitter Configuration

Alternately, by $v_{\text{TEST}} : i_{\text{TEST}}$ Method

To obtain R_{in}

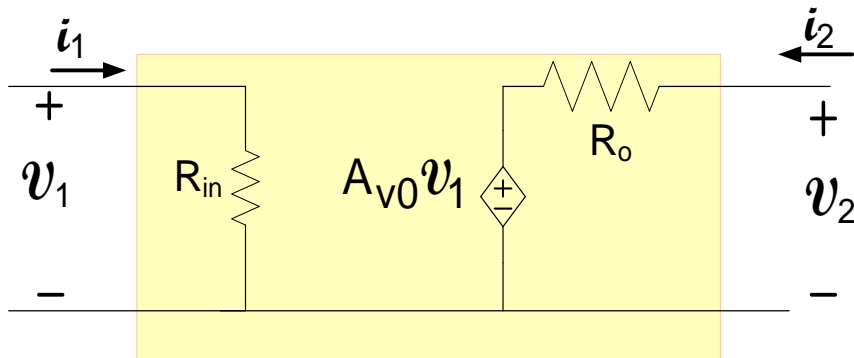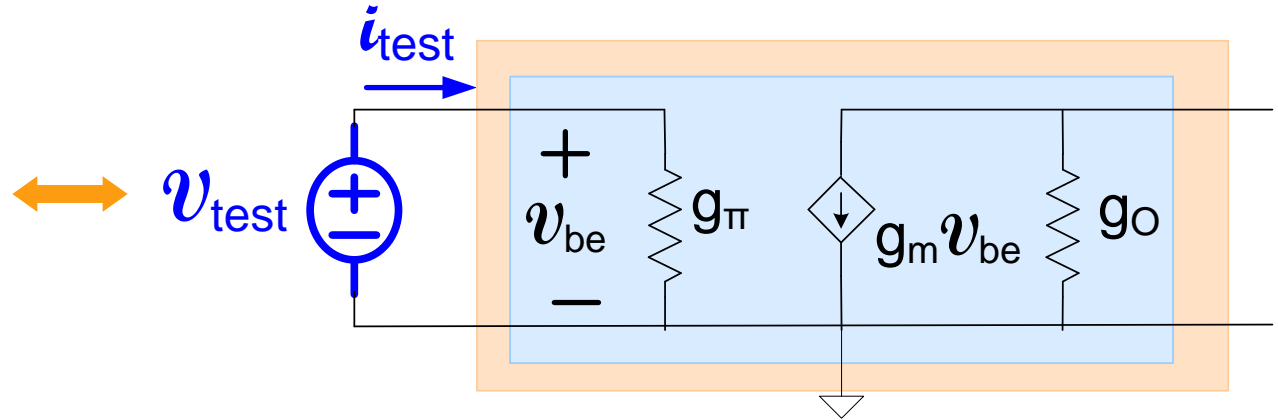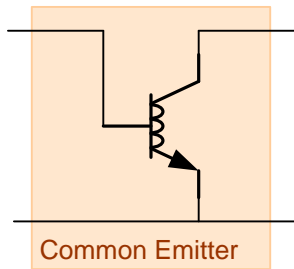

$$R_{\text{in}} = \frac{v_{\text{test}}}{i_{\text{test}}}$$




$$R_{\text{in}} = \frac{1}{g_{\pi}}$$

$\{R_{\text{in}}, A_{v0} \text{ and } R_o\}$



Two-port model for Common Emitter Configuration

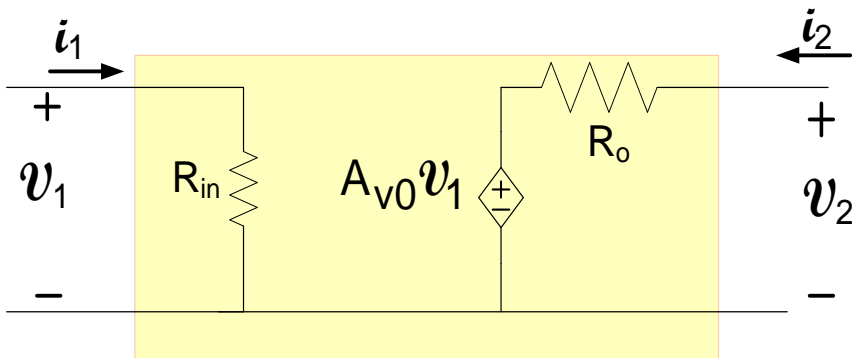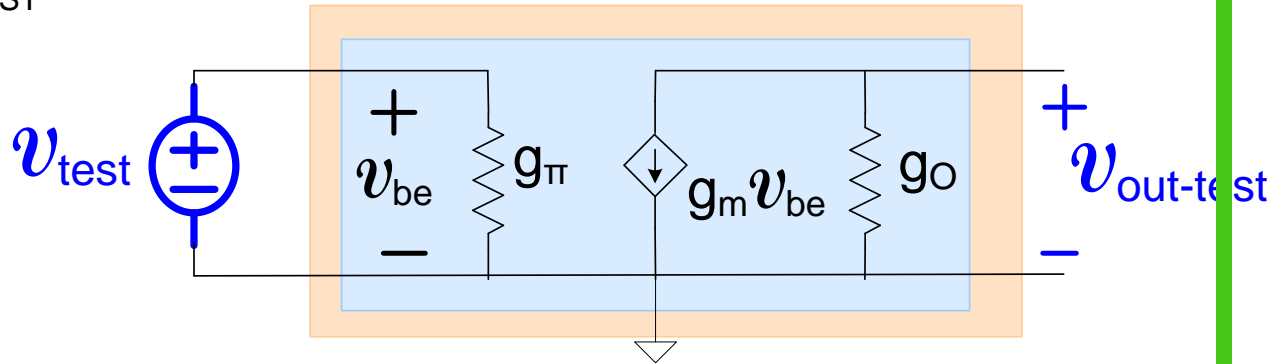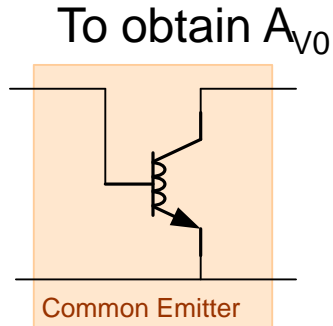Alternately, by $v_{\text{TEST}} : i_{\text{TEST}}$ Method



$$A_{V0} = \frac{v_{\text{out-test}}}{v_{\text{test}}}$$

$$v_{\text{out-test}} = v_{\text{test}} \left(-\frac{g_m}{g_o} \right)$$

$$A_{V0} = -\frac{g_m}{g_o}$$



$\{R_{\text{in}}, A_{V0} \text{ and } R_o\}$



Two-port model for Common Emitter Configuration

Alternately, by $v_{TEST} : i_{TEST}$ Method


To obtain g_o

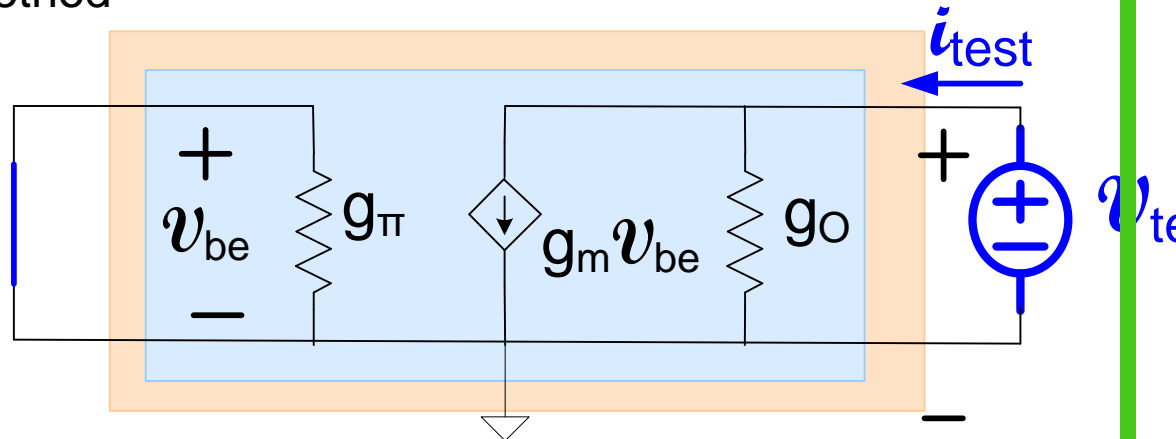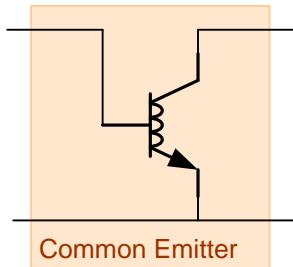

$$R_0 = \frac{v_{test}}{i_{test}}$$

$$v_{test} = i_{test} (g_o)$$


$$R_0 = \frac{1}{g_o}$$

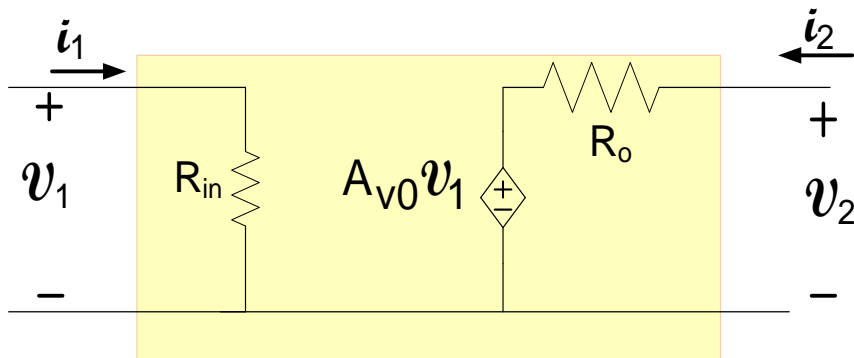

$\{R_{in}, A_{v0}$ and $R_o\}$



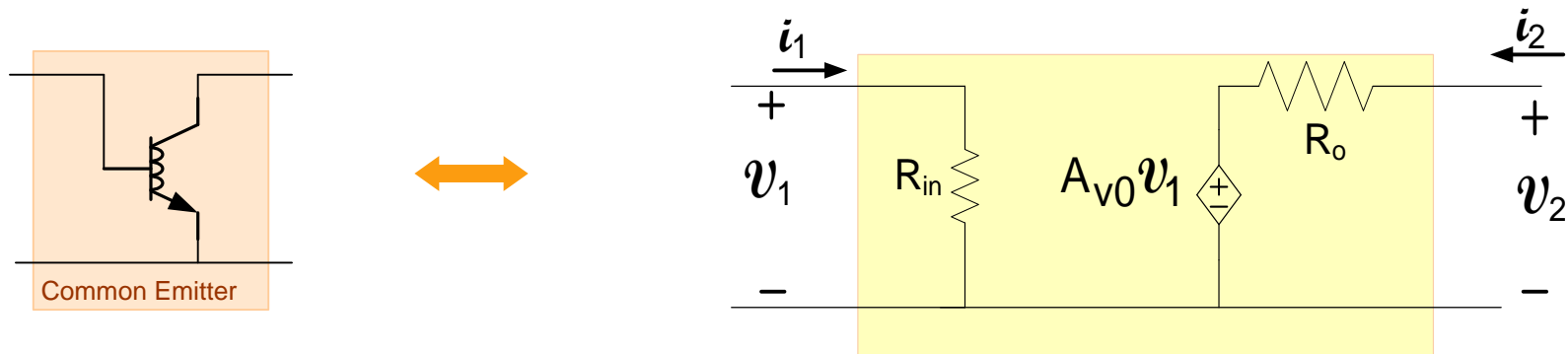Two-port model for Common Emitter Configuration



In terms of small signal model parameters:

$$R_{in} = \frac{1}{g_{\pi}} \quad A_{V0} = -\frac{g_m}{g_o} \quad R_o = \frac{1}{g_o} \quad A_{VR} = 0$$

In terms of operating point and model parameters:

$$R_i = \frac{\beta V_t}{I_{CQ}} \quad A_{V0} = -\frac{V_{AF}}{V_t} \quad R_o = \frac{V_{AF}}{I_{CQ}} \quad A_{VR} = 0$$




Characteristics:

- Input impedance is mid-range
- Voltage Gain is Large and Inverting
- Output impedance is large
- Unilateral
- Widely used to build voltage amplifiers

Common Emitter Configuration

Consider the following CE application

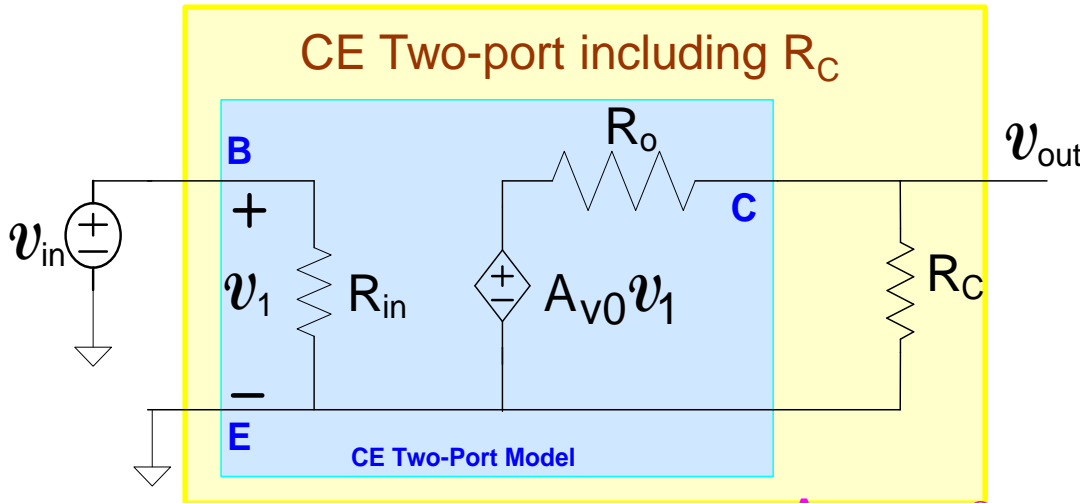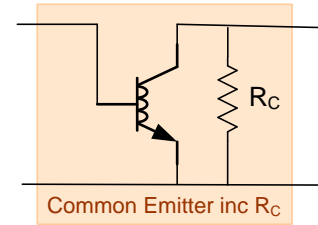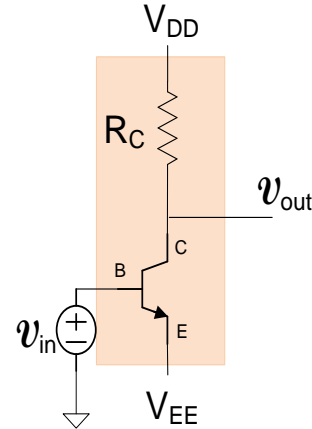(this will also generate a two-port model for this CE application)



$$v_{out} (g_C + g_0) = g_0 A_{V0} v_{in} \quad \rightarrow \quad A_{VR} = 0$$

$$A_{VC} = \frac{v_{out}}{v_{in}} = \frac{g_0 A_{V0}}{g_0 + g_C} = \frac{-g_m}{g_0 + g_C} \stackrel{g_0 \ll g_C}{\cong} -g_m R_C$$


$$R_{inC} = R_{in} = r_{\pi}$$

$$R_{outC} = R_o // R_C \quad \rightarrow \quad R_{outC} = R_o // R_C = \frac{1}{g_0 + g_C} \stackrel{g_0 \ll g_C}{\cong} R_C$$


Common Emitter Configuration

Consider the following CE application

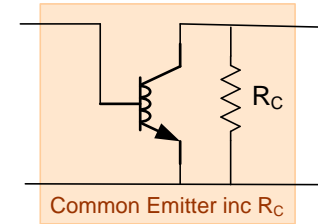(this will also generate a two-port model for this CE application)



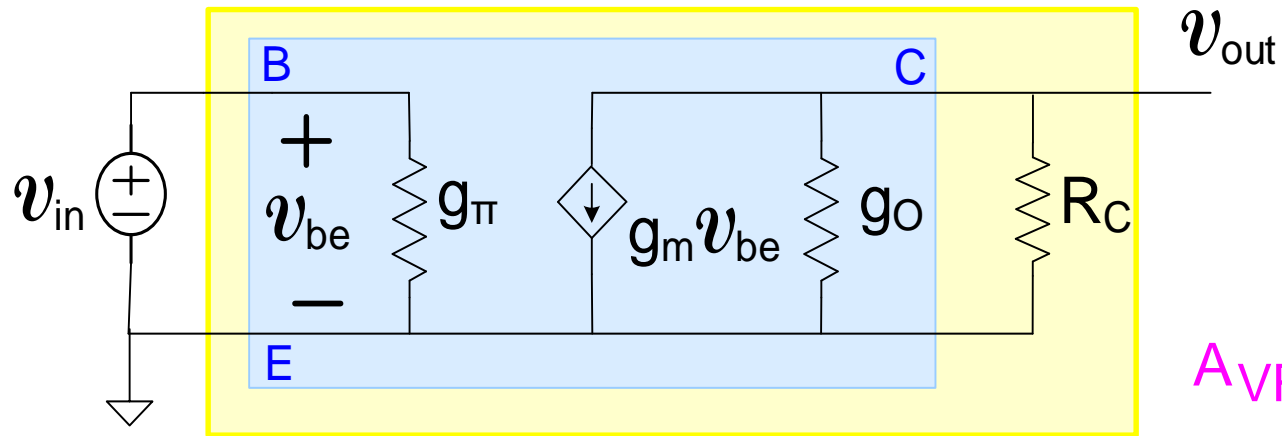This circuit can also be analyzed directly without using 2-port model for CE configuration




$$v_{out} = -g_m v_{in} \left(\frac{1}{g_o + g_C} \right) \quad \longrightarrow \quad A_v = \frac{v_{out}}{v_{in}} = - \left(\frac{g_m}{g_o + g_C} \right) \stackrel{g_o \ll g_C}{\cong} -g_m R_C$$

$$R_{in} = r_{\pi} \qquad R_{out} = \frac{1}{g_o + g_C} \stackrel{g_o \ll g_C}{\cong} R_C$$

Common Emitter Configuration

Consider the following CE application

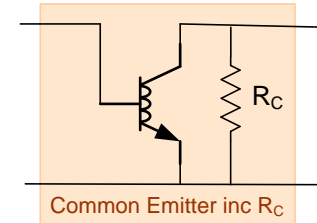(this is also a two-port model for this CE application)



Small signal parameter domain

$$A_v \stackrel{g_o \ll g_c}{\cong} -g_m R_C$$

$$R_{out} = \frac{1}{g_o + g_c} \stackrel{g_o \ll g_c}{\cong} R_C$$

$$R_{in} = r_{\pi}$$

$$A_{VR} = 0$$

Operating point and model parameter domain

$$A_v \stackrel{g_o \ll g_c}{\cong} -\frac{I_{CQ} R_C}{V_t}$$


$$R_{out} \stackrel{g_o \ll g_c}{\cong} R_C$$

$$R_{in} = \frac{\beta V_t}{I_{CQ}}$$

Characteristics:

- Input impedance is mid-range
- Voltage Gain is large and Inverting
- Output impedance is mid-range
- Unilateral
- Widely used as a voltage amplifier

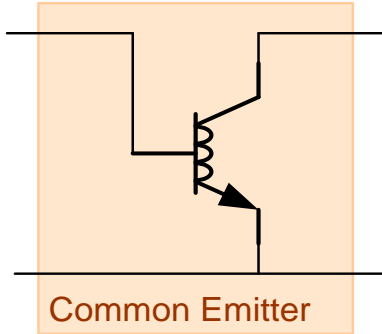Common Source/ Common Emitter Configurations



$$R_{in} = \frac{1}{g_{\pi}}$$


$$A_{V0} = -\frac{g_m}{g_o}$$

$$R_o = \frac{1}{g_o}$$

$$A_{VR} = 0$$

$$A_{VR} = 0$$

$$R_{in} = \infty$$

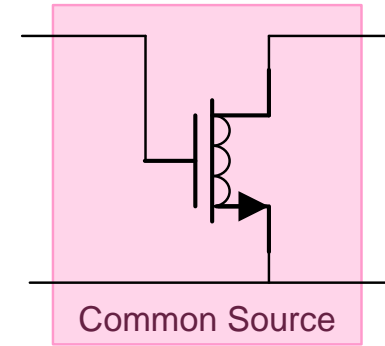

$$A_{V0} = -\frac{g_m}{g_o}$$

$$R_o = \frac{1}{g_o}$$

In terms of operating point and model parameters:

$$R_{in} = \frac{\beta V_t}{I_{CQ}}$$

$$A_{V0} = -\frac{V_{AF}}{V_t}$$

$$R_o = \frac{V_{AF}}{I_{CQ}}$$

$$R_{in} = \infty$$



$$R_o = \frac{1}{\lambda I_{DQ}} = \frac{V_{AF}}{I_{DQ}}$$

$$A_{V0} = -\frac{2}{\lambda V_{EBQ}} = -2 \frac{V_{AF}}{V_{EBQ}}$$

Characteristics:

- Input impedance is mid-range (infinite for MOS)
- Voltage Gain is Large and Inverting
- Output impedance is large
- Unilateral
- Widely used to build voltage amplifiers

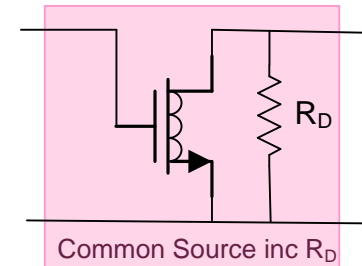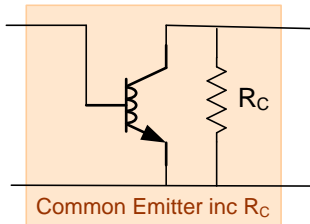Common Source/Common Emitter Configuration



$$R_{out} = \frac{1}{g_0 + g_C} \stackrel{g_0 \ll g_C}{\cong} R_C$$

$$A_v \stackrel{g_0 \ll g_C}{\cong} -g_m R_C$$

$$R_{in} = r_{\pi}$$

$$A_{VR} = 0 \quad | \quad A_{VR} = 0$$

$$R_{out} = \frac{1}{g_0 + g_D} \stackrel{g_0 \ll g_D}{\cong} R_D$$

$$A_v \stackrel{g_0 \ll g_D}{\cong} -g_m R_D$$

$$R_{in} = \infty$$

In terms of operating point and model parameters:

$$A_v \stackrel{g_0 \ll g_C}{\cong} -\frac{I_{CQ} R_C}{V_t}$$

$$R_{out} \stackrel{g_0 \ll g_C}{\cong} R_C$$

$$R_{in} = \frac{\beta V_t}{I_{CQ}}$$

$$A_v \stackrel{g_0 \ll g_D}{\cong} -\frac{2I_{DQ} R_D}{V_{EBQ}}$$







$$R_{in} = \infty$$

$$R_{out} \stackrel{g_0 \ll g_D}{\cong} R_D$$

Characteristics:




- Input impedance is mid-range (infinite for MOS)
- Voltage Gain is Large and Inverting
- Output impedance is mid-range
- Unilateral
- Widely used as a voltage amplifier

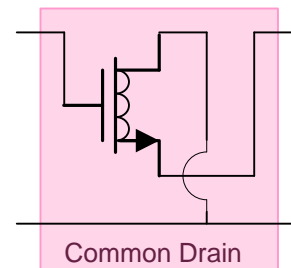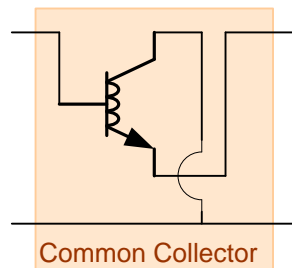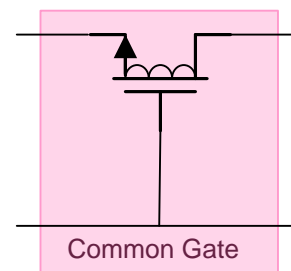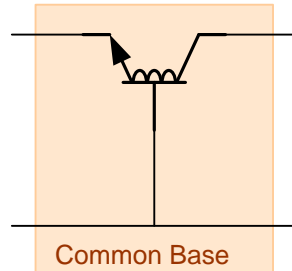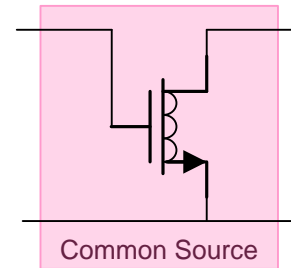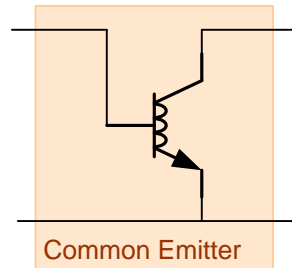Consider Common Collector/Common Drain Two-port Models



Will focus on Bipolar Circuit since MOS counterpart is a special case obtained by setting $g_{\pi}=0$

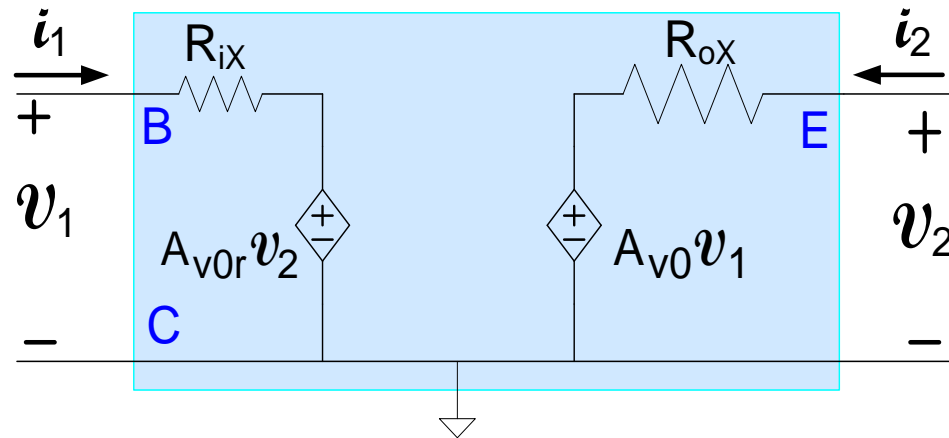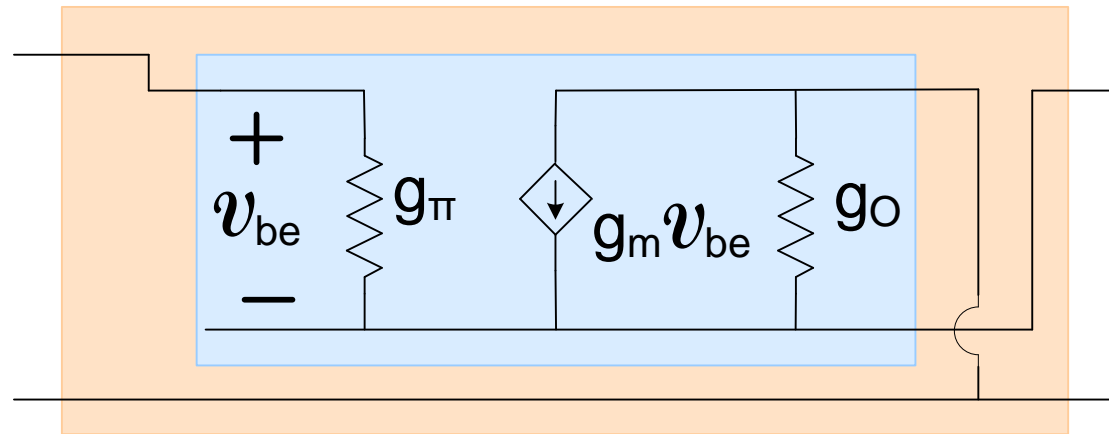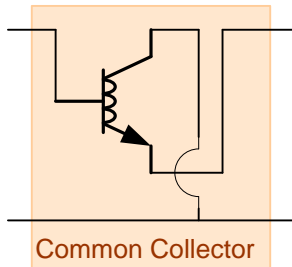
Two-port model for Common Collector Configuration



$\{R_{ix}, A_{v0}, A_{v0r} \text{ and } R_{ox}\}$

Two-Port Models of Basic Amplifiers widely used for Analysis and Design of Amplifier Circuits

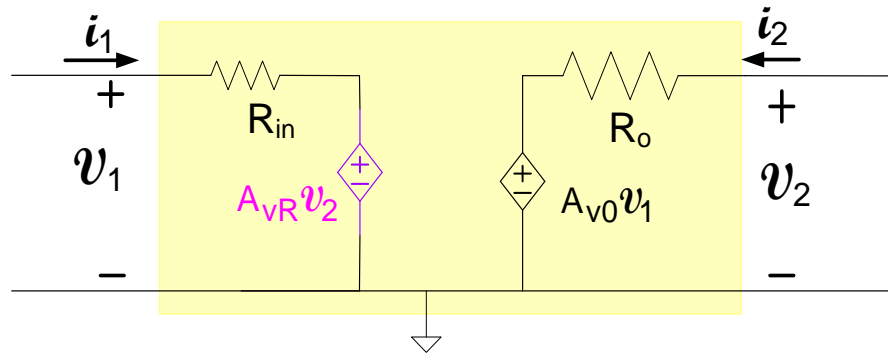Methods of Obtaining Amplifier Two-Port Network



1. $v_{\text{TEST}} : i_{\text{TEST}}$ Method

→ 2. Write $v_1 : v_2$ equations in standard form


$$v_1 = i_1 R_{\text{IN}} + A_{\text{VR}} v_2$$

$$v_2 = i_2 R_{\text{O}} + A_{\text{V0}} v_1$$

3. Thevenin-Norton Transformations

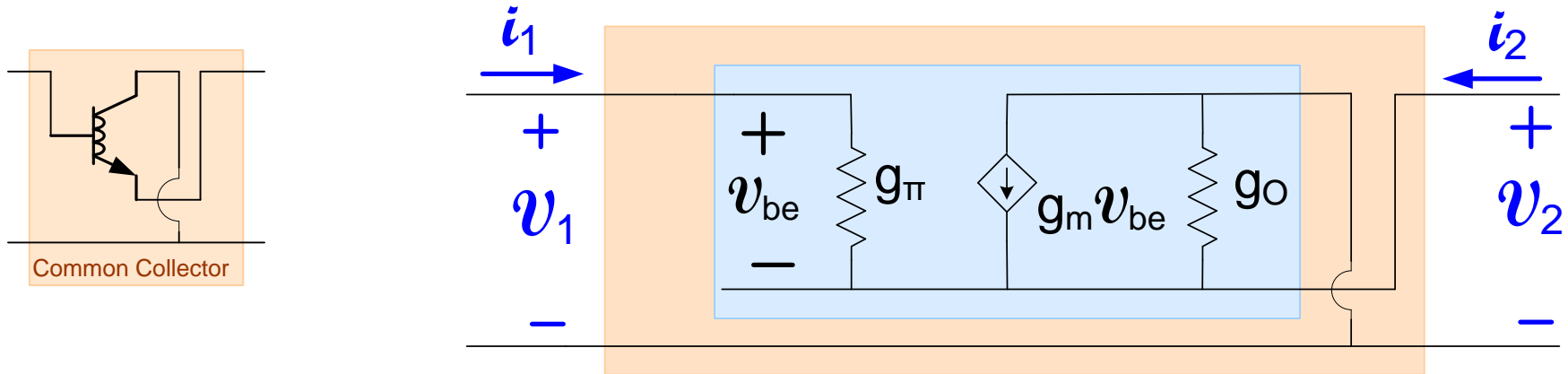4. Ad Hoc Approaches

Two-port model for Common Collector Configuration




Applying KCL at the input and output node, obtain

$$\left. \begin{aligned} i_1 &= (v_1 - v_2) g_\pi \\ i_2 &= (g_m + g_\pi + g_o) v_2 - (g_m + g_\pi) v_1 \end{aligned} \right\}$$

These can be rewritten as

$$\left. \begin{aligned} v_1 &= i_1 r_\pi + v_2 \\ v_2 &= \left(\frac{1}{g_m + g_\pi + g_o} \right) i_2 + \left(\frac{g_m + g_\pi}{g_m + g_\pi + g_o} \right) v_1 \end{aligned} \right\}$$

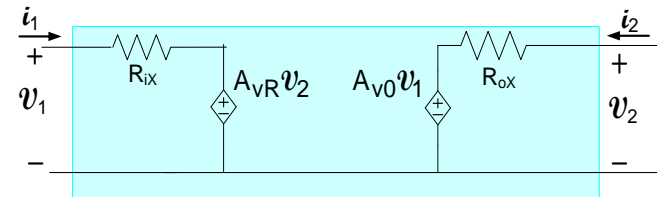Standard Two-Port Amplifier Representation



$$v_1 = i_1 R_{ix} + A_{VR} v_2$$




$$v_2 = i_2 R_{ox} + A_V v_1$$

$v_1 : v_2$ equations in standard form

It thus follows that

$$R_{ix} = r_\pi \quad A_{VR} = 1 \quad R_{ox} = \left(\frac{1}{g_m + g_\pi + g_o} \right) \quad A_{V0} = \left(\frac{g_m + g_\pi}{g_m + g_\pi + g_o} \right)$$

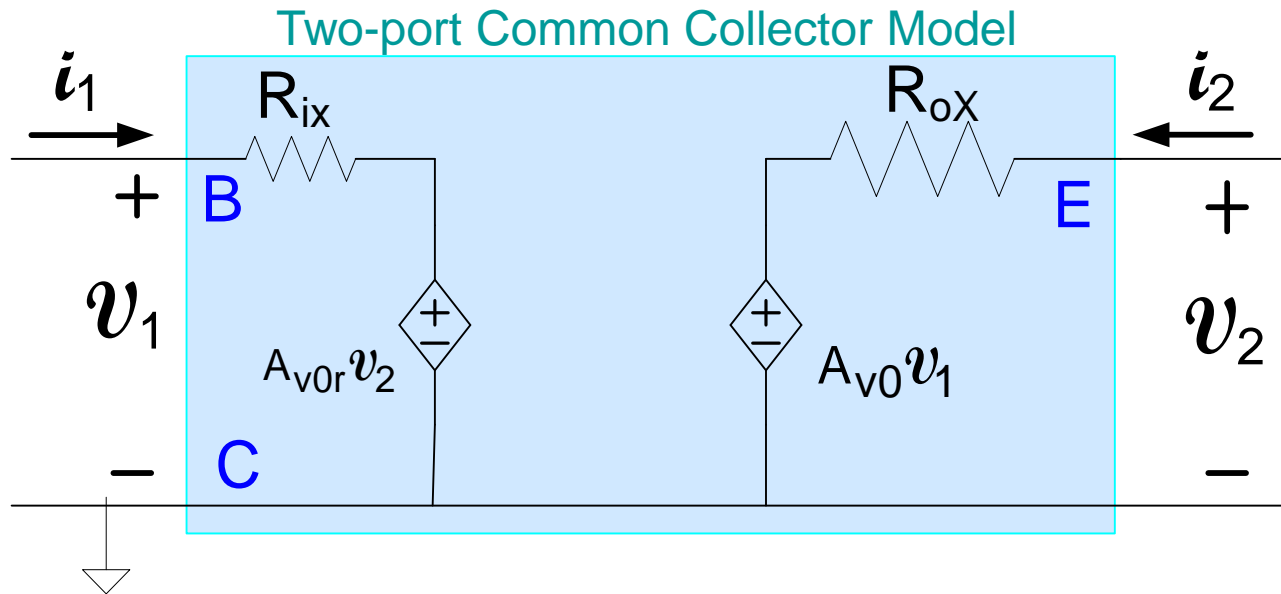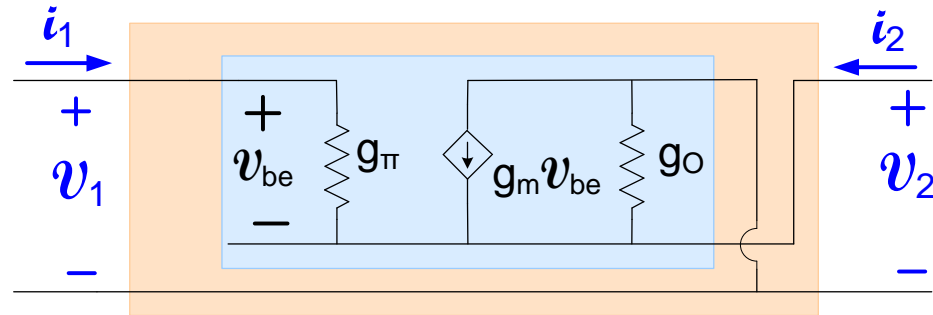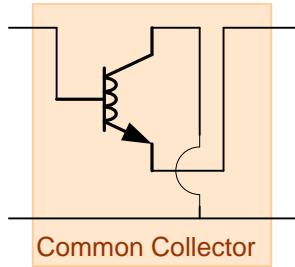Two-port model for Common Collector Configuration



$$R_{iX} = r_{\pi}$$

$$A_{VOr} = 1$$

$$R_{oX} = \left(\frac{1}{g_m + g_{\pi} + g_o} \right) \cong \frac{1}{g_m}$$



$$A_{V0} = \left(\frac{g_m + g_{\pi}}{g_m + g_{\pi} + g_o} \right) \cong 1$$

Common Collector Configuration

Consider the following CC application

Determine R_{in} , R_o , and A_v

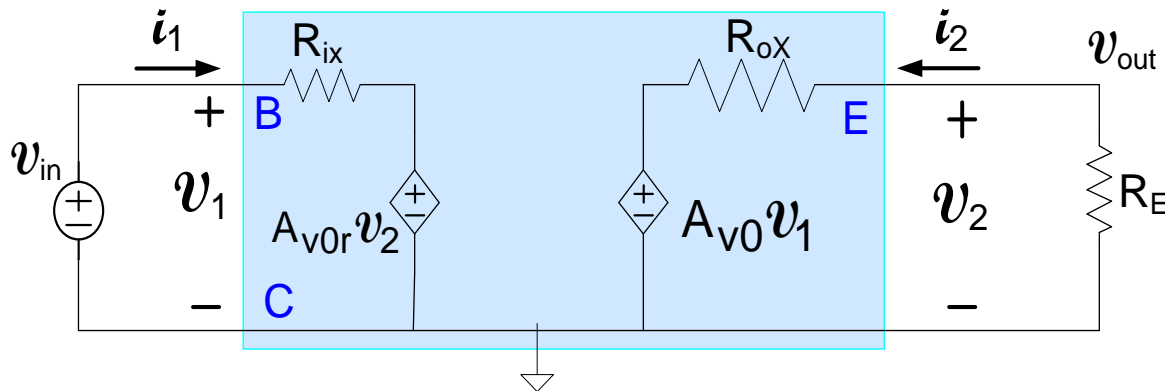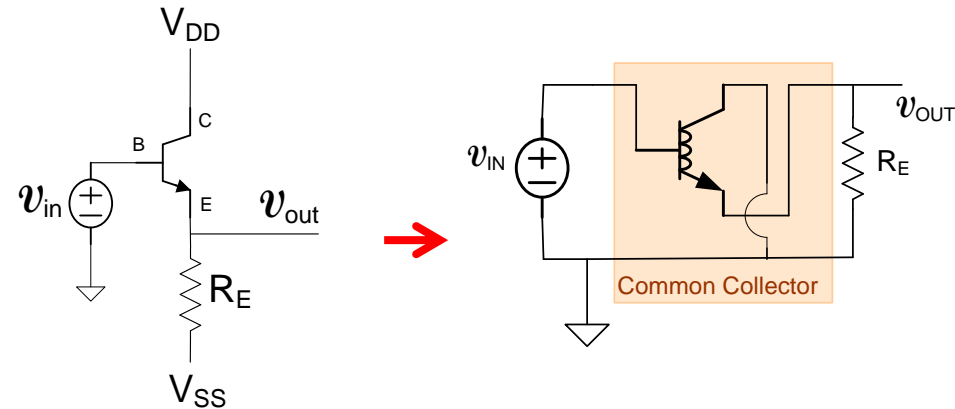(this is not asking for a two-port model for the CC application – R_{in} and A_v defined for no additional load on output, R_o defined for short-circuit input)



$$A_v = A_{v0} \frac{g_{ox}}{g_{ox} + g_E} = \frac{g_m + g_\pi}{g_m + g_\pi + g_o} \left(\frac{g_m + g_\pi + g_o}{g_m + g_\pi + g_o + g_E} \right) = \frac{g_m + g_\pi}{g_m + g_\pi + g_o + g_E} \cong \frac{g_m}{g_m + g_E} \stackrel{\text{if } g_m \gg g_E}{\cong} 1$$


$$v_{in} = i_1 R_{ix} + A_{v0r} A_{v0} \frac{g_{oX}}{g_{oX} + g_E} v_{in} \quad \rightarrow \quad R_{in} = \frac{r_\pi}{1 - \frac{g_m + g_\pi}{g_m + g_\pi + g_o + g_E}} = r_\pi \frac{g_m + g_\pi + g_o + g_E}{g_o + g_E} \stackrel{g_E \gg g_o}{\cong} r_\pi + \beta R_E$$

$$R_o \cong \frac{1}{g_m + g_E + g_o + g_\pi} = \frac{1}{g_m + g_E} = \frac{R_E}{1 + g_m R_E} \stackrel{g_m \gg g_E}{\cong} \frac{1}{g_m}$$


Common Collector Configuration

Consider the following CC application

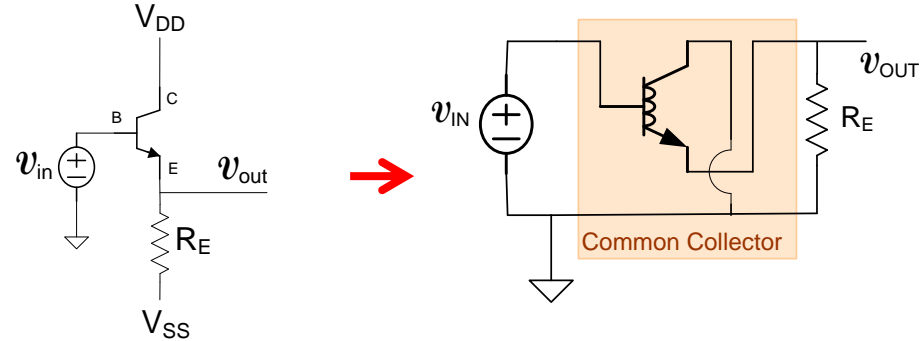(this is not asking for a two-port model for the CC application, - R_{in} and A_v defined for no additional load on output, R_o defined for short-circuit input -)



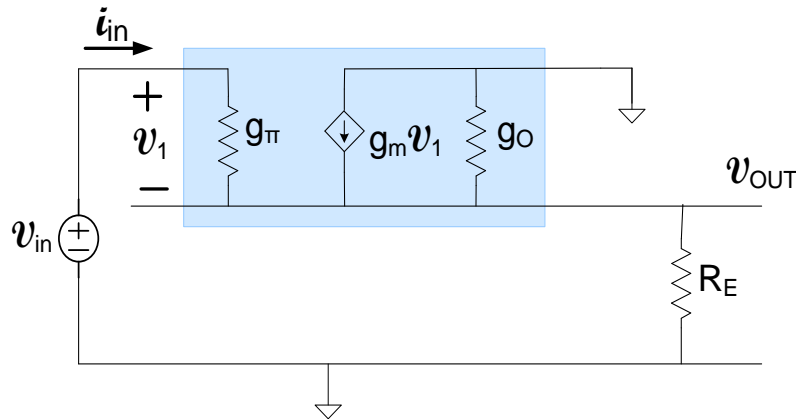Alternately, this circuit can also be analyzed directly



$$\left. \begin{aligned} v_{out} (g_E + g_o + g_\pi) &= v_{in} g_\pi + g_m v_1 \\ v_{in} &= v_1 + v_{out} \end{aligned} \right\}$$

$$A_v = \frac{v_{out} (g_m + g_E + g_o + g_\pi) = v_{in} (g_\pi + g_m)}{g_m + g_E + g_o + g_\pi} \cong \frac{g_m}{g_m + g_E} = \frac{I_{CQ} R_E}{I_{CQ} R_E + V_t}$$




$$\left. \begin{aligned} i_{in} &= g_\pi (v_{in} - v_{out}) \\ v_{out} (g_m + g_E + g_o + g_\pi) &= v_{in} (g_\pi + g_m) \end{aligned} \right\}$$

$$R_{in} = r_\pi \frac{g_m + g_\pi + g_o + g_E}{g_o + g_E} \stackrel{g_E \gg g_o}{\cong} r_\pi + \beta R_E$$

Common Collector Configuration

Consider the following CC application

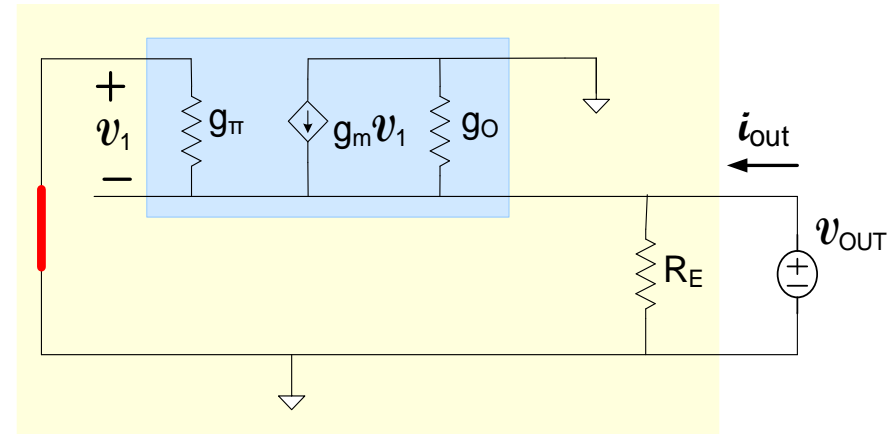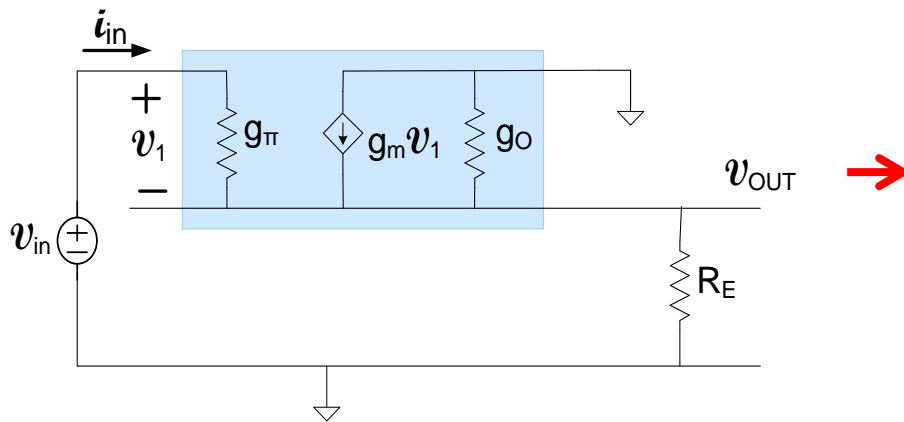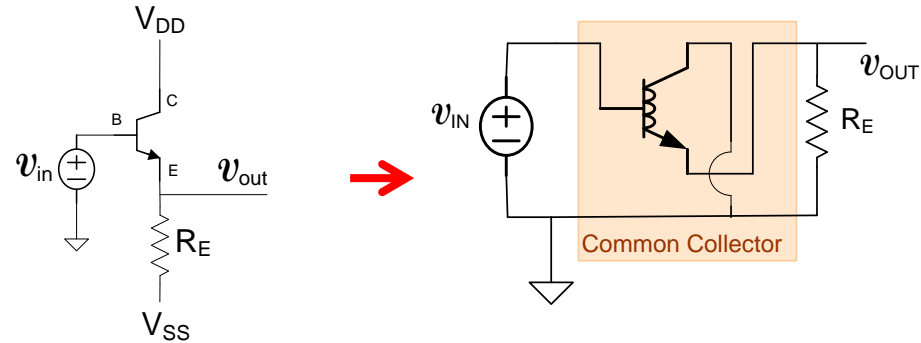(this is not asking for a two-port model for the CC application, - R_{in} and A_v defined for no additional load on output, R_o defined for short-circuit input -)



To obtain R_o , set $v_{in} = 0$


$$i_{out} = v_{out} (g_E + g_o + g_\pi) - g_m (-v_{out})$$

$$R_{out} = \frac{1}{g_m + g_\pi + g_o + g_E} \stackrel{g_E \ll g_o}{\cong} \frac{1}{g_m}$$

Common Collector Configuration

Consider the following CC application

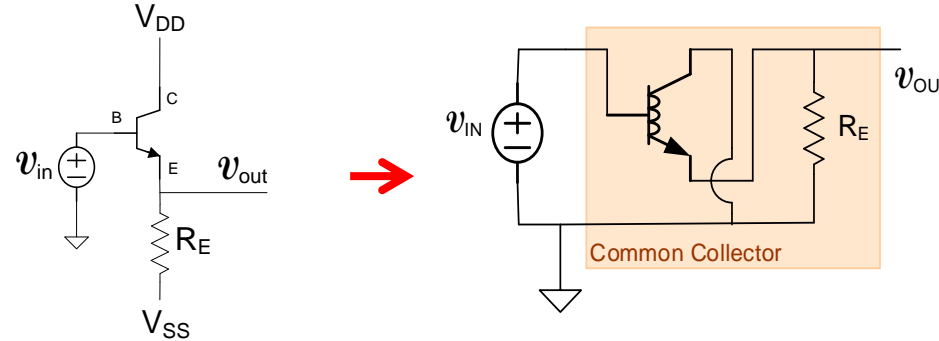(this is not asking for a two-port model for the CC application, - R_{in} and A_v defined for no additional load on output, R_o defined for short-circuit input -)




$$A_v = \frac{g_\pi + g_m}{g_m + g_E + g_o + g_\pi} \cong \frac{g_m}{g_m + g_E} = \frac{I_{CQ} R_E}{I_{CQ} R_E + V_t} \cong 1$$

$$R_{in} = r_\pi \frac{g_m + g_\pi + g_o + g_E}{g_o + g_E} \stackrel{g_E \gg g_o}{\cong} r_\pi + \beta R_E$$

$$R_{out} = \frac{1}{g_m + g_\pi + g_o + g_E} \stackrel{g_E \ll g_o}{\cong} \frac{1}{g_m}$$

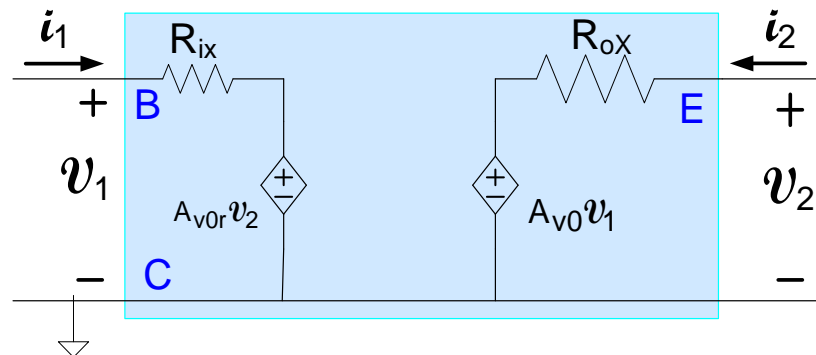Question: Why are these not the two-port parameters of this circuit?



- R_{in} defined for open-circuit on output instead of short-circuit (see previous slide : -2 slides)
- $A_{v0r} \neq 0$



Common Collector Configuration

For this CC application

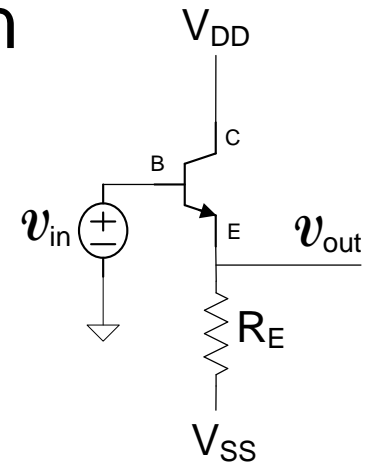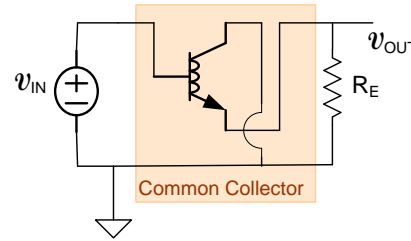(this is not a two-port model for this CC application)



Small signal parameter domain

$$A_V = \frac{g_\pi + g_m}{g_m + g_E + g_0 + g_\pi} \stackrel{\text{if } g_m \gg g_E}{\cong} 1$$

$$R_{in} \stackrel{g_E \gg g_0}{\cong} r_\pi + \beta R_E$$

$$R_0 \cong \frac{R_E}{1 + g_m R_E} \stackrel{g_m R_E \gg 1}{\cong} \frac{1}{g_m}$$

Operating point and model parameter domain

$$A_V \cong \frac{I_{CQ} R_E}{I_{CQ} R_E + V_t} \stackrel{I_{CQ} R_E \gg V_t}{\cong} 1$$

$$R_{in} \stackrel{I_{CQ} R_E \gg V_t}{\cong} \beta R_E$$

$$R_0 \stackrel{I_{CQ} R_E \gg V_t}{\cong} \frac{V_t}{I_{CQ}}$$


Characteristics:

- Output impedance is low
- A_{V0} is positive and near 1
- Input impedance is very large
- Widely used as a buffer
- Not completely unilateral but output-input transconductance (or A_{Vr}) is small and effects are generally negligible though magnitude same as A_V

Common Collector/Common Drain Configurations

For these CC/CD applications

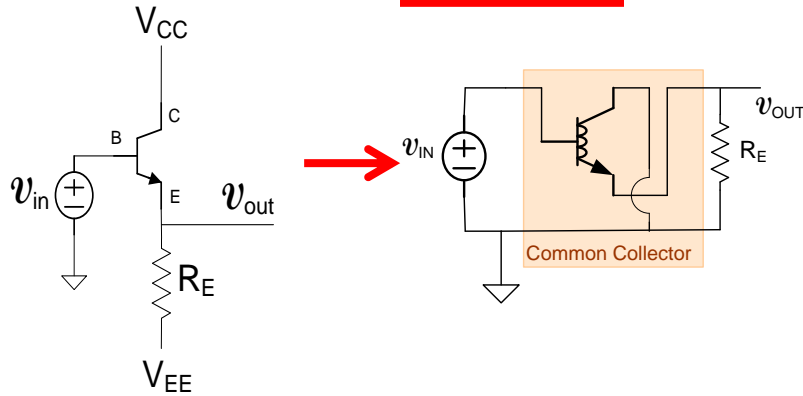(not two-port models for these applications)



$$A_V = \frac{g_\pi + g_m}{g_m + g_E + g_0 + g_\pi} \quad \text{if } g_m \gg g_E \cong 1$$


$$R_{in} \stackrel{g_E \gg g_o}{\cong} r_\pi + \beta R_E$$

$$R_0 \cong \frac{R_E}{1 + g_m R_E} \stackrel{g_m R_E \gg 1}{\cong} \frac{1}{g_m}$$

In terms of operating point and model parameters:

$$A_V \cong \frac{I_{CQ} R_E}{I_{CQ} R_E + V_t} \stackrel{I_{CQ} R_E \gg V_t}{\cong} 1 \quad R_0 \cong \frac{V_t}{I_{CQ}}$$
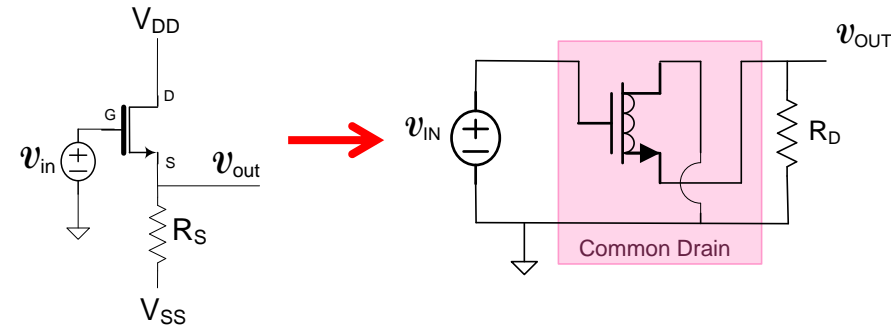
$$R_{in} \stackrel{I_{CQ} R_E \gg V_t}{\cong} \beta R_E$$



$$A_V = \frac{g_m}{g_m + g_S + g_0} \quad \text{if } g_m \gg g_S \cong 1$$

$$R_{in} = \infty$$

$$R_0 \cong \frac{R_S}{1 + g_m R_S} \stackrel{g_m R_S \gg 1}{\cong} \frac{1}{g_m}$$

$$A_V \cong \frac{2I_{DQ} R_S}{2I_{DQ} R_S + V_{EBQ}} \stackrel{\text{if } 2I_{DQ} R_S \gg V_{EBQ}}{\cong} 1$$







$$R_0 \cong \frac{V_{EBQ} R_S}{V_{EBQ} + 2I_{DQ} R_S} \stackrel{2I_{DQ} R_S \gg V_{EBQ}}{\cong} \frac{V_{EBQ}}{2I_{DQ}}$$

$$R_{in} = \infty$$

- Output impedance is low
- A_{V0} is positive and near 1
- Input impedance is very large



- Widely used as a buffer
- Not completely unilateral but output-input transconductance is small

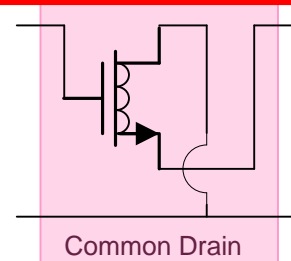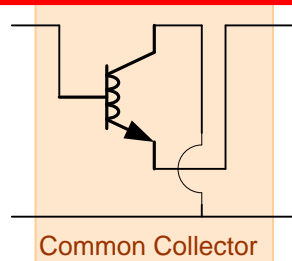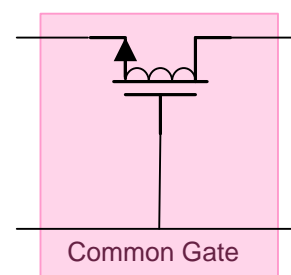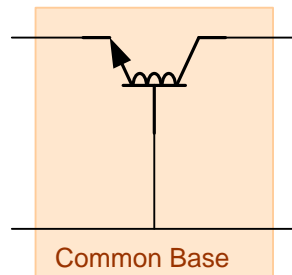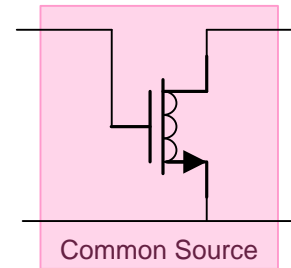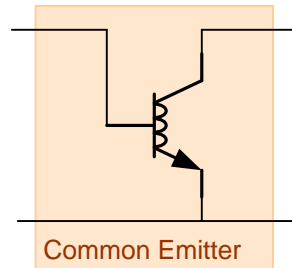Consider Common Base/Common Gate Two-port Models



Will focus on Bipolar Circuit since MOS counterpart is a special case obtained by setting $g_{\pi}=0$

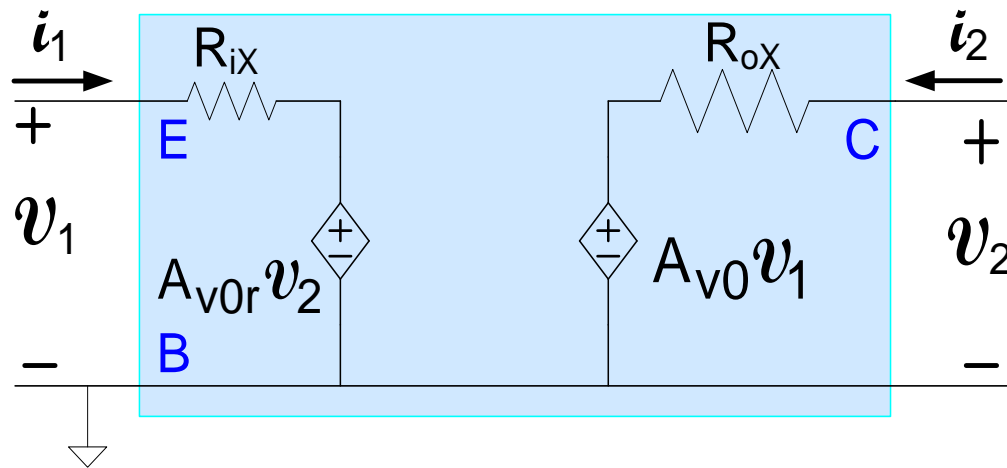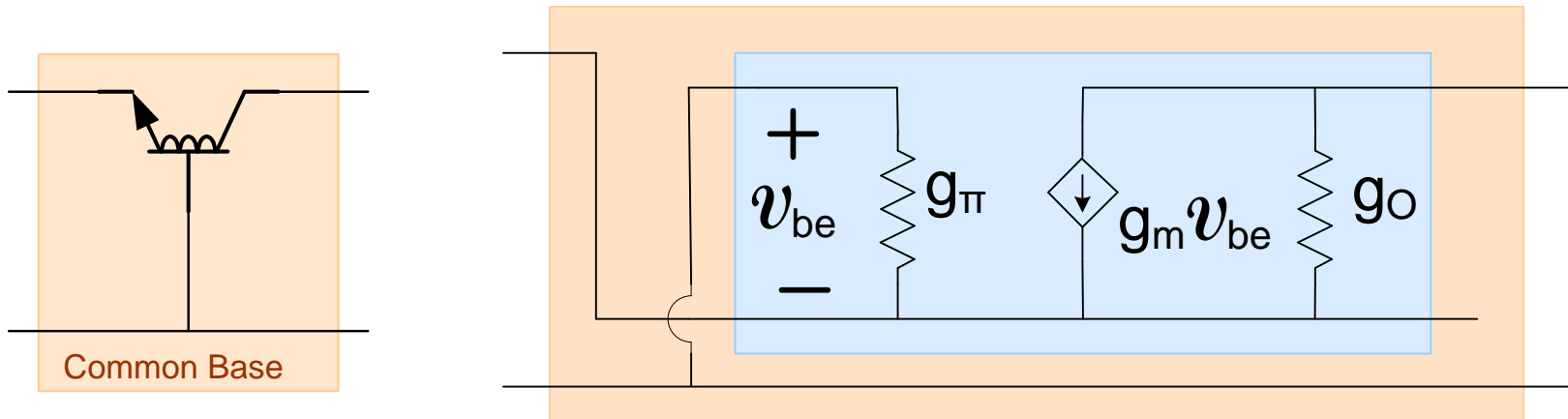
Two-port model for Common Base Configuration



$\{R_{iX}, A_{v0}, A_{v0r}$ and $R_{oX}\}$

Two-Port Models of Basic Amplifiers widely used for Analysis and Design of Amplifier Circuits

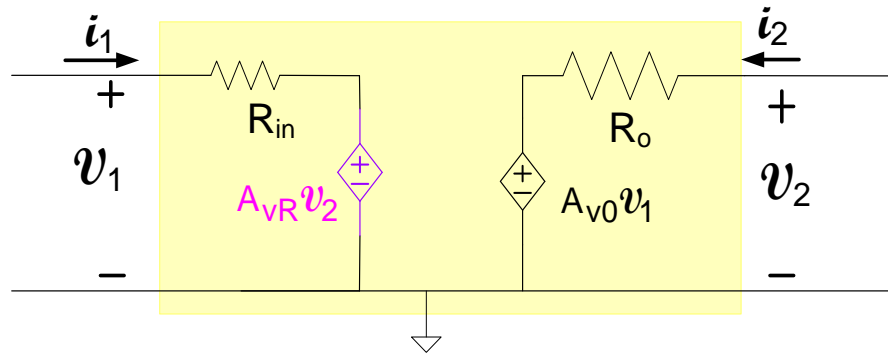Methods of Obtaining Amplifier Two-Port Network



1. $v_{\text{TEST}} : i_{\text{TEST}}$ Method

→ 2. Write $v_1 : v_2$ equations in standard form


$$v_1 = i_1 R_{\text{IN}} + A_{\text{VR}} v_2$$

$$v_2 = i_2 R_{\text{O}} + A_{\text{V0}} v_1$$

3. Thevenin-Norton Transformations

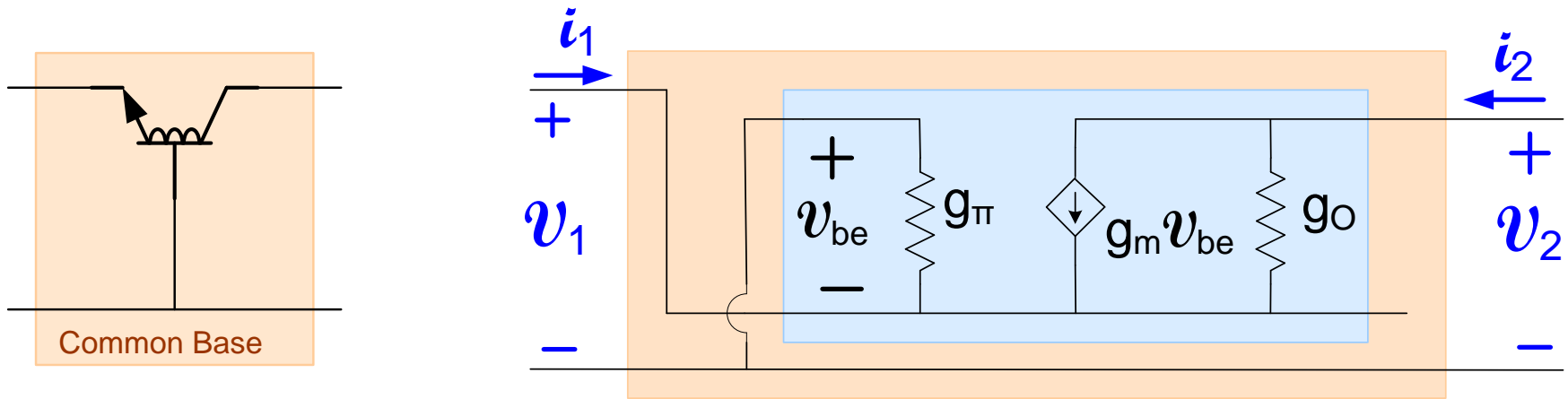4. Ad Hoc Approaches

Two-port model for Common Base Configuration



From KCL

$$\left. \begin{aligned} i_1 &= v_1 g_\pi + (v_1 - v_2) g_o + g_m v_1 \\ i_2 &= (v_2 - v_1) g_o - g_m v_1 \end{aligned} \right\}$$

These can be rewritten as


$$v_1 = \left(\frac{1}{g_m + g_\pi + g_o} \right) i_1 + \left(\frac{g_o}{g_m + g_\pi + g_o} \right) v_2$$

$$v_2 = \left(\frac{1}{g_o} \right) i_2 + \left(1 + \frac{g_m}{g_o} \right) v_1$$

It thus follows that:

$$R_{iX} = \frac{1}{g_m + g_\pi + g_o} \cong \frac{1}{g_m} \quad A_{vOr} = \frac{g_o}{g_m + g_\pi + g_o} \quad A_{vO} = 1 + \frac{g_m}{g_o} \cong \frac{g_m}{g_o} \quad R_{oX} = \frac{1}{g_o}$$



Standard Form for Amplifier Two-Port

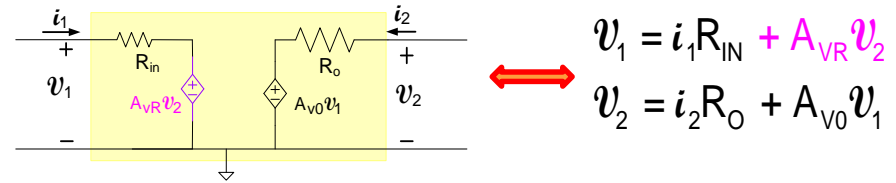


$$\begin{aligned} v_1 &= i_1 R_{iN} + A_{vR} v_2 \\ v_2 &= i_2 R_{o} + A_{vO} v_1 \end{aligned}$$

$v_1 : v_2$ equations in standard form

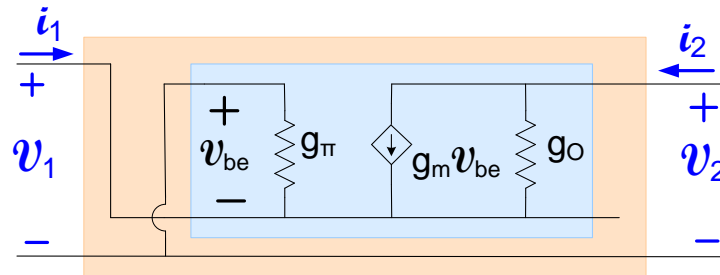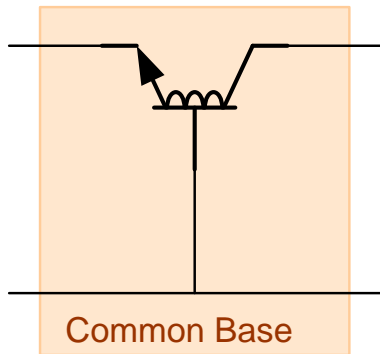Two-port model for Common Base Configuration



Two-port Common Base Model

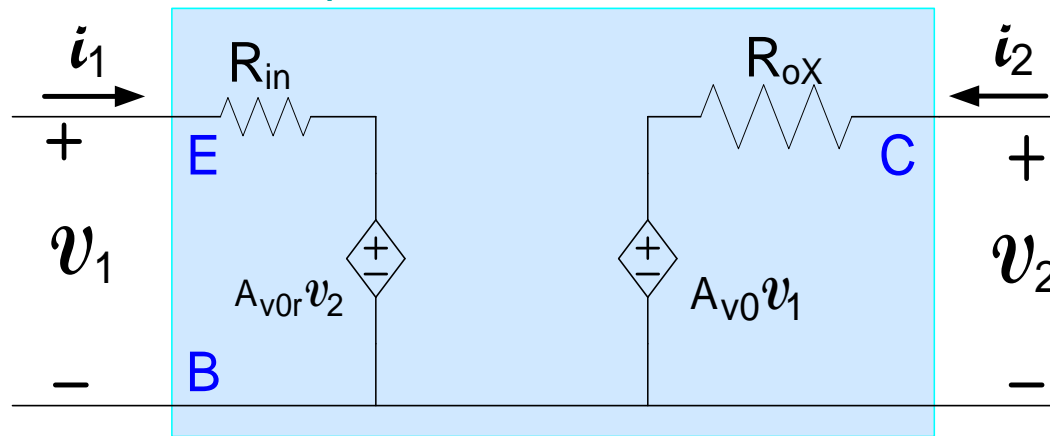

$$R_{iX} = \frac{1}{g_m + g_\pi + g_o} \cong \frac{1}{g_m}$$

$$A_{V0} = 1 + \frac{g_m}{g_o} \cong \frac{g_m}{g_o}$$



$$A_{V0r} = \frac{g_o}{g_m + g_\pi + g_o} \cong \frac{g_o}{g_m}$$

$$R_{oX} = \frac{1}{g_o}$$

Common Base Configuration

Consider the following CB application

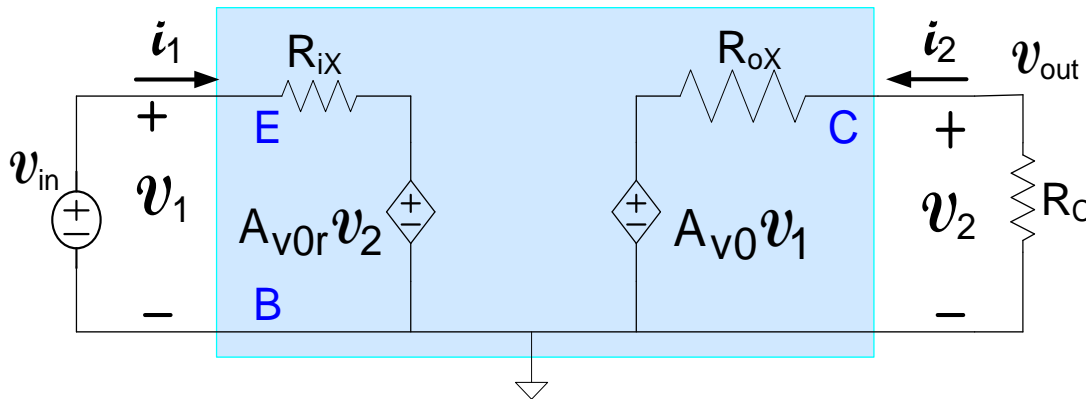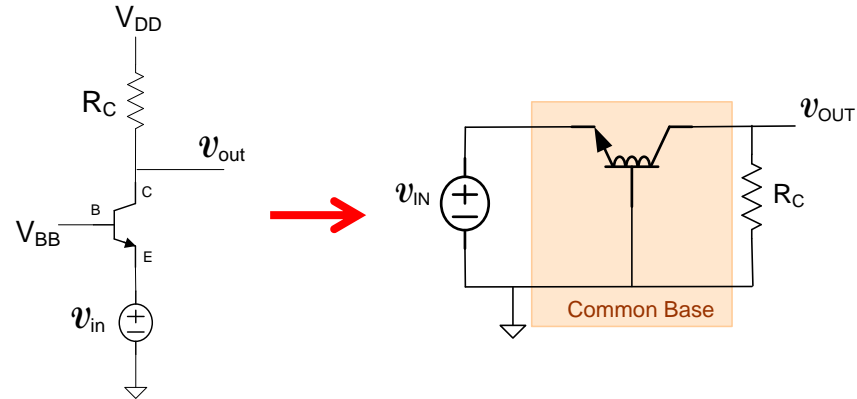(this is not asking for a two-port model for this CB application - - R_{in} and A_v defined for no load on output, R_o defined for short-circuit input)



$$A_v = A_{v0} \frac{R_C}{R_C + R_{oX}} = \left(\frac{g_m + g_0}{g_0} \right) \left(\frac{g_0}{g_C + g_0} \right) = \frac{g_m + g_0}{g_C + g_0} \cong g_m R_C$$


$$R_{in} = \frac{v_{in}}{i_1} = \frac{i_1 R_{iX} + A_{v0} v_{out}}{i_1} \longrightarrow R_{in} = \frac{R_{iX}}{1 - A_{v0} A_v} = \frac{R_{iX}}{g_C (g_m + g_\pi + g_0) + g_\pi g_0} \cong \frac{1}{g_m}$$

$$R_{out} = R_C // R_{oX} \longrightarrow R_{out} = \frac{R_C}{1 + g_0 R_C}$$


Common Base Configuration

Consider the following CB application

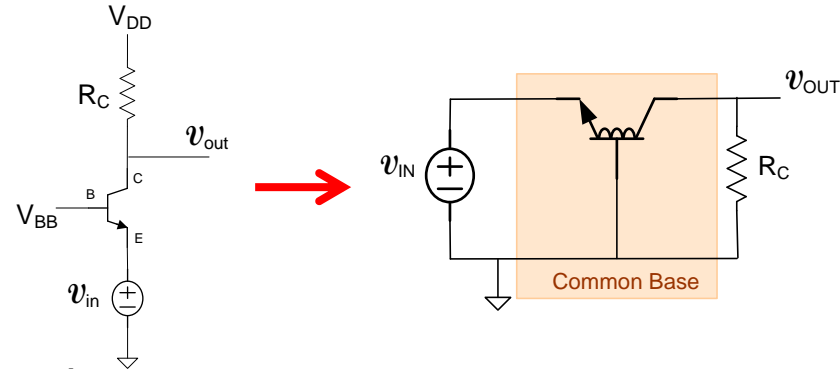(this is not asking for a two-port model for this CB application – R_{in} and A_V defined for no load on output, R_o defined for short-circuit input)



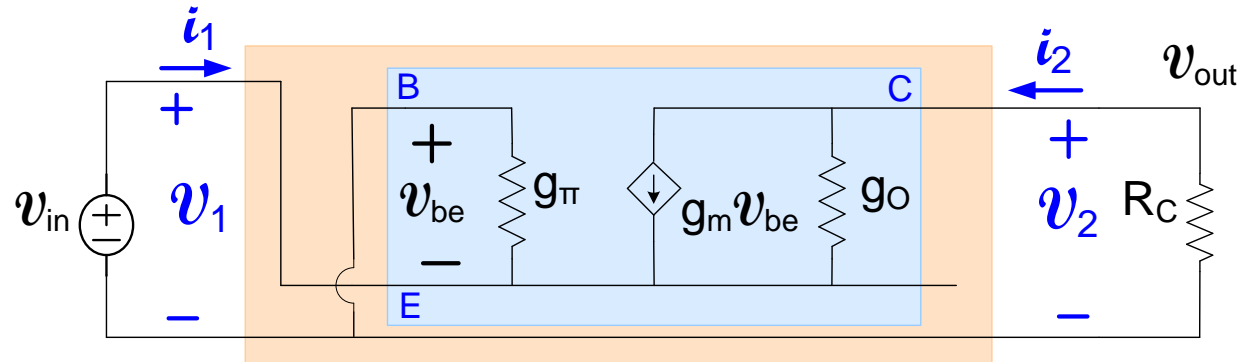Alternately, this circuit can also be analyzed directly



By KCL at the output node, obtain

$$(g_C + g_0)v_o = (g_m + g_0)v_{in} \quad \longrightarrow \quad A_V = \frac{g_m + g_0}{g_C + g_0} \cong g_m R_C$$


By KCL at the emitter node, obtain

$$i_1 = (g_m + g_\pi + g_0)v_{in} - g_0 v_{out} \quad \longrightarrow \quad R_{in} = \frac{g_0 + g_C}{g_C (g_m + g_\pi + g_0) + g_\pi g_0} \cong \frac{1}{g_m}$$

$$R_{out} = R_C // r_o \quad \longrightarrow \quad R_{out} = \frac{R_C}{1 + g_0 R_C} \cong R_C$$

Common Base Application

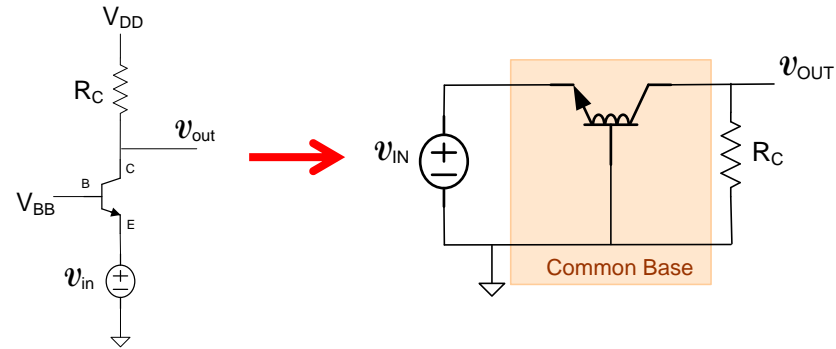(this is not a two-port model for this CB application)



$$A_V \cong g_m R_C$$
$$R_{in} \cong \frac{1}{g_m}$$
$$R_{out} \cong R_C$$

$R_c \ll r_o$

$$A_V \cong \frac{I_{CQ} R_C}{V_t}$$
$$R_{in} \cong \frac{V_t}{I_{CQ}}$$
$$R_{out} \cong R_C$$


$R_c \ll r_o$

Characteristics:


- Output impedance is mid-range
- A_{V0} is large and positive (equal in mag to that to CE)
- Input impedance is very low
- Not completely unilateral but output-input transconductance is small

Common Base/Common Gate Application

(these are not a two-port models)

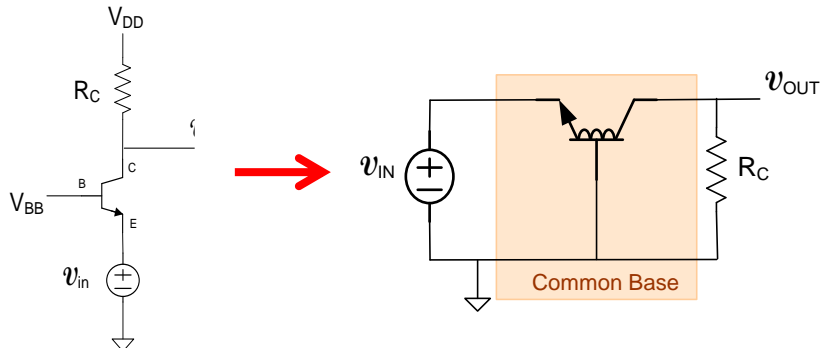
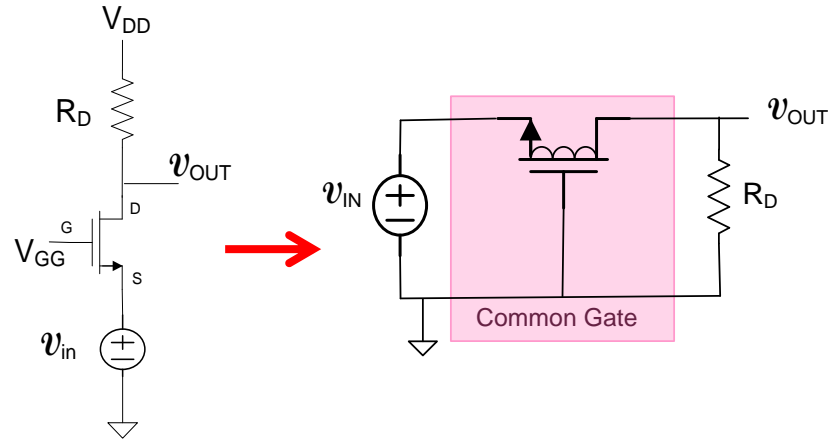
$$A_V \cong g_m R_C \quad R_{in} \cong \frac{1}{g_m} \quad R_{out} \cong R_C \quad R_C \ll r_o$$



$$A_V \cong g_m R_D \quad R_{in} \cong \frac{1}{g_m} \quad R_{out} \cong R_D \quad R_D \ll r_o$$


In terms of operating point and model parameters:

$$A_V \cong \frac{I_{CQ} R_C}{V_t} \quad R_{in} \cong \frac{V_t}{I_{CQ}} \quad R_{out} \cong R_C \quad I_{CQ} R_C \ll V_{AF} \quad A_V \cong \frac{2I_{DQ} R_D}{V_{EBQ}} \quad R_{in} \cong \frac{V_{EBQ}}{2I_{DQ}} \quad R_{out} \cong R_D \quad I_{DQ} R_D \ll \frac{1}{\lambda}$$


Characteristics:

- Output impedance is mid-range
- A_{V0} is large and positive (equal in mag to that to CE)
- Input impedance is very low
- Not completely unilateral but output-input transconductance is small

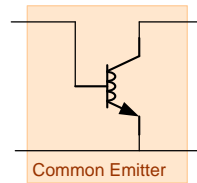
The three basic amplifier types for both MOS and bipolar processes




Common Emitter

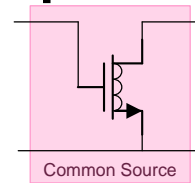


Common Source

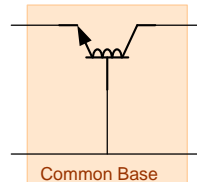


Common Base

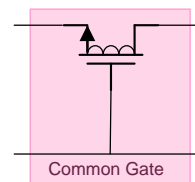

Common Gate

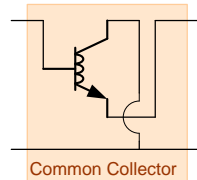


Common Collector

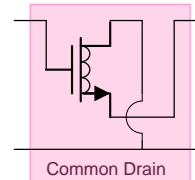


Common Drain

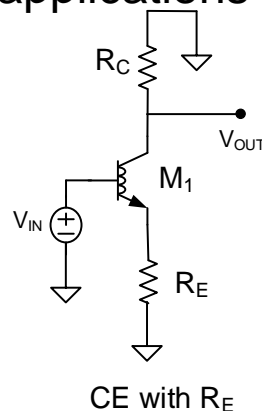- Have developed both two-ports and a widely used application of all 6
- A fourth structure (two additional applications) is also quite common so will be added to list of basic applications




CE with R_E

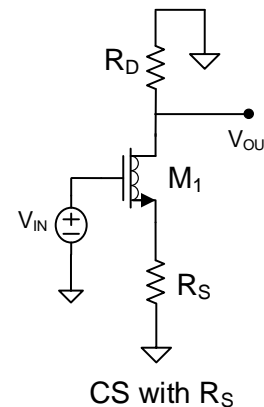

CS with R_S

Common Emitter with Emitter Resistor Configuration Application

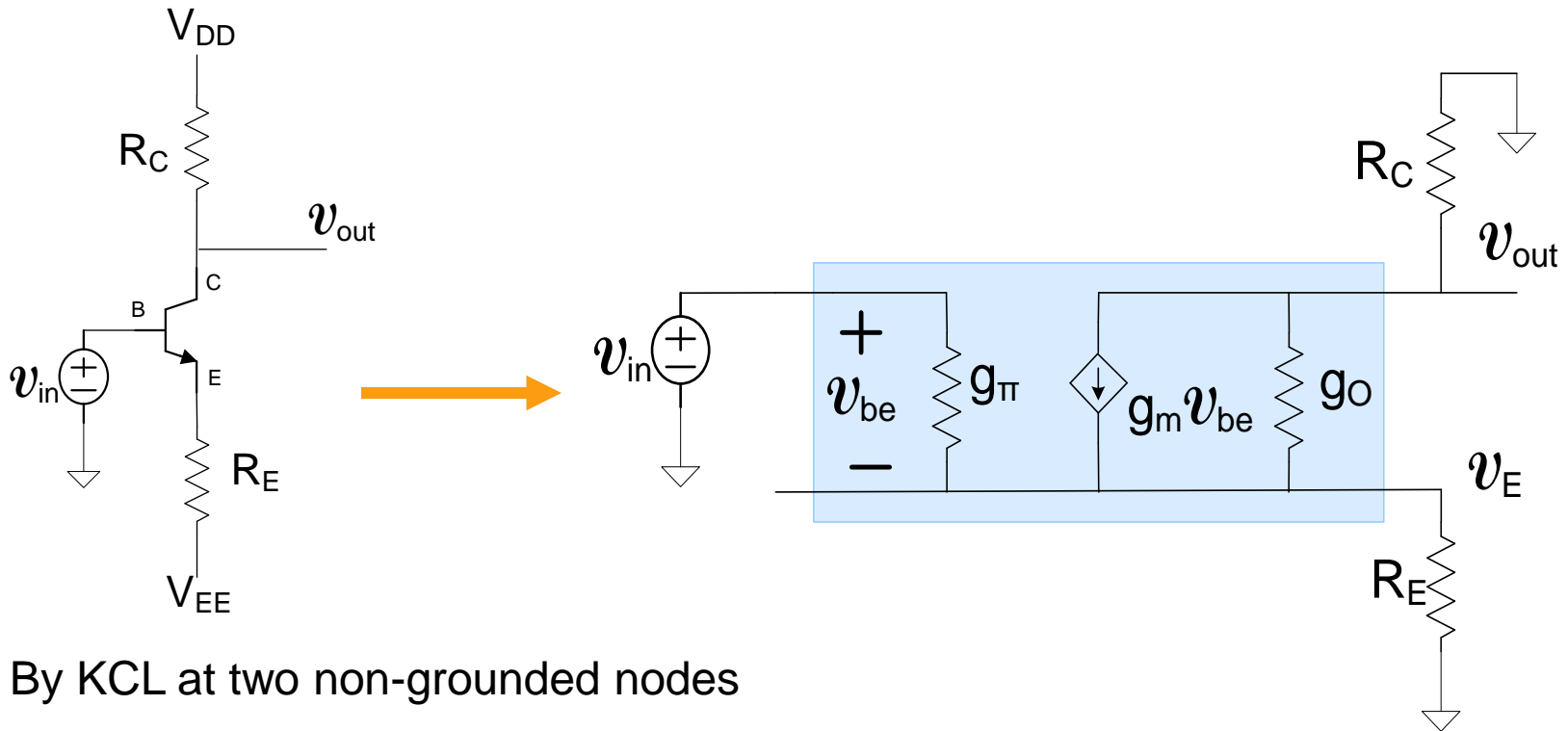(this is not a two-port model for this CE with R_E application)



By KCL at two non-grounded nodes


$$v_{out} (g_C + g_o) + (v_{in} - v_E) g_m = g_o v_E$$

$$v_E (g_E + g_o + g_{\pi}) - (v_{in} - v_E) g_m = g_o v_{out} + g_{\pi} v_{in}$$

$$A_V = \frac{v_{out}}{v_{in}} = \frac{-g_m g_E + g_o g_{\pi}}{g_C g_m + g_C (g_o + g_{\pi} + g_E) + g_o (g_{\pi} + g_E)} \cong -\frac{R_C}{R_E}$$

Common Emitter with Emitter Resistor Configuration Application

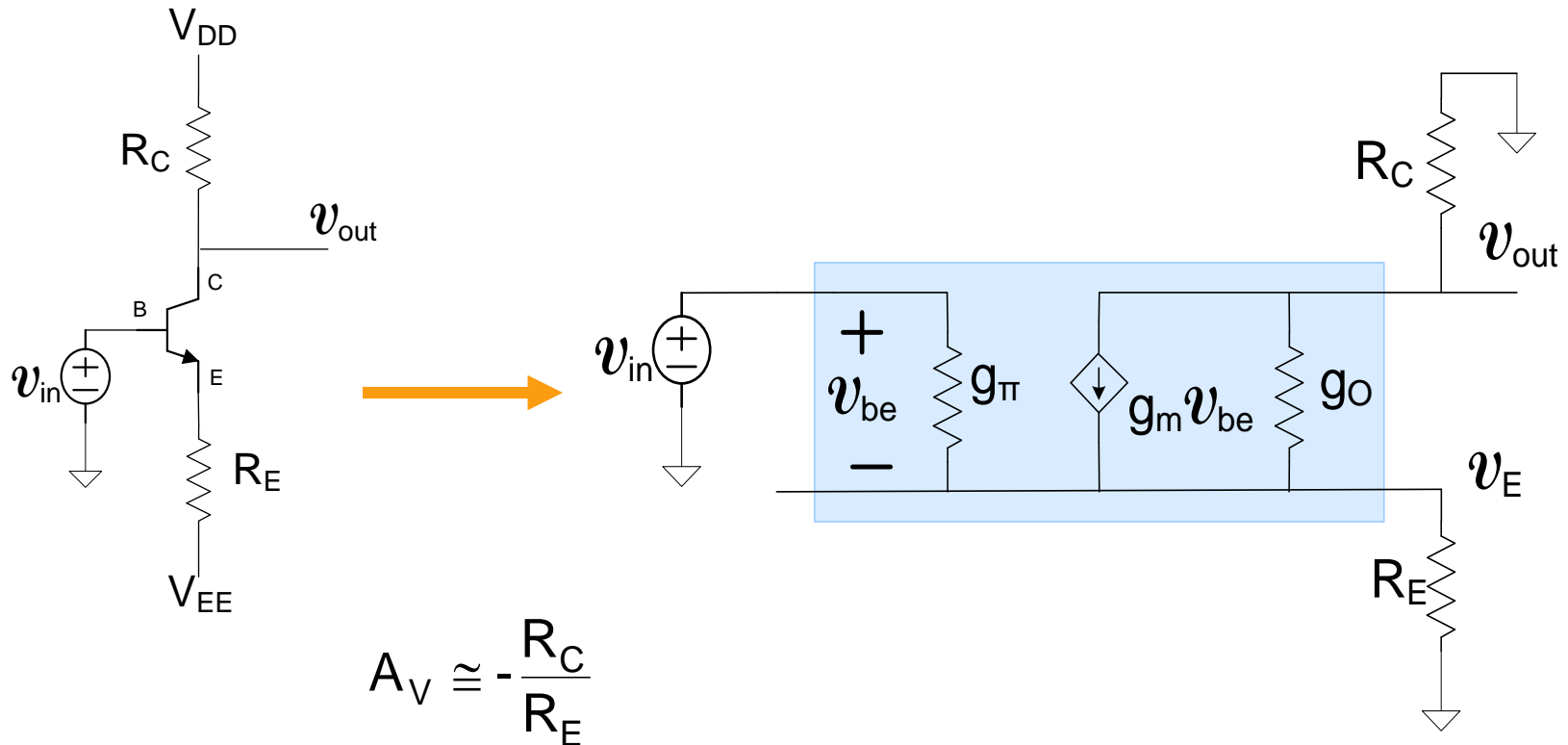(this is not a two-port model for this CE with R_E application)



$$A_V \cong -\frac{R_C}{R_E}$$

It can also be shown that


$$R_{in} \cong r_{\pi} + \beta R_E$$

$$R_{out} \cong R_C$$

Nearly unilateral (is unilateral if $g_o=0$)

Common Emitter with Emitter Resistor Configuration Application

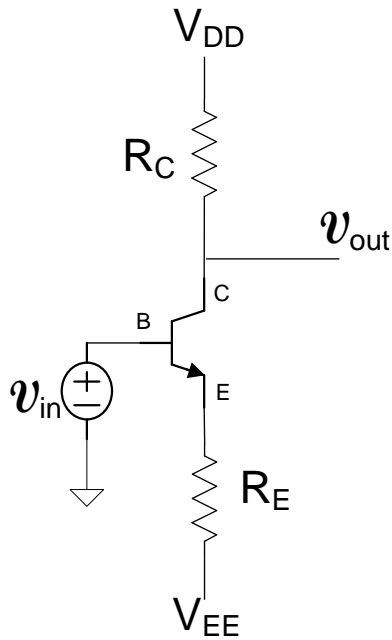(this is not a two-port model for this CE with R_E application)



$$A_V \cong -\frac{R_C}{R_E}$$

$$R_{in} \cong r_{\pi} + \beta R_E$$









$$R_{out} \cong R_C$$

(this is not a two-port model)

Characteristics:









- Analysis would simplify if g_0 were set to 0 in model
- Gain can be accurately controlled with resistor ratios
- Useful for reasonably accurate low gains
- Input impedance is high

Basic Amplifier Gain Table

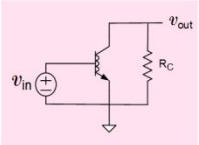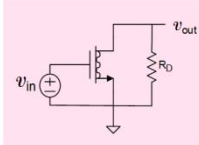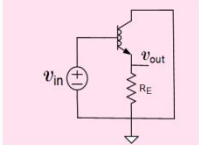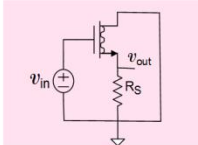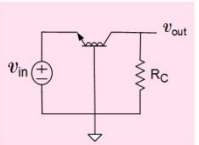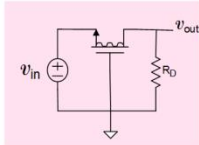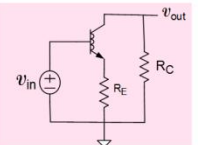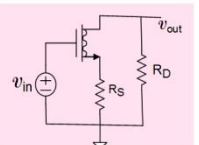	CE/CS		CC/CD		CB/CG		CEwRE/CSwRS	
	BJT	MOS	BJT	MOS	BJT	MOS	BJT	MOS
A_V	 $-g_m R_C$ $\frac{I_{CQ} R_C}{V_t}$	 $-\frac{2I_{DQ} R_D}{V_{EB}}$	 $\frac{g_m}{g_m + g_E}$ $\frac{I_{CQ} R_E}{I_{CQ} R_E + V_t}$	 $\frac{2I_{DQ} R_E}{2I_{DQ} R_E + V_{EB}}$	 $g_m R_C$ $\frac{I_{CQ} R_C}{V_t}$	 $\frac{2I_{DQ} R_C}{V_{EB}}$	 $-\frac{R_C}{R_E}$	
R_{in}	$\frac{\beta V_t}{I_{CQ}}$	r_{π} ∞	$r_{\pi} + \beta R_E$ $\beta \left(\frac{V_t}{I_{CQ}} + R_E \right)$	∞	g_m^{-1} $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	$r_{\pi} + \beta R_E$ $\beta \left(\frac{V_t}{I_{CQ}} + R_E \right)$	∞
R_{out}	R_C	R_C	g_m^{-1} $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	R_C	R_C	R_C	R_C

(not two-port models for the four structures)

Basic Amplifier Gain Table

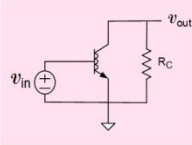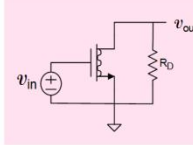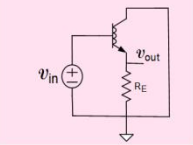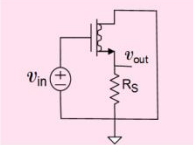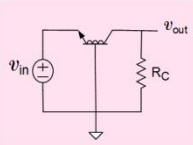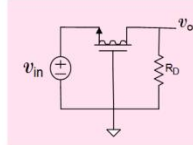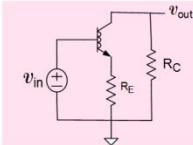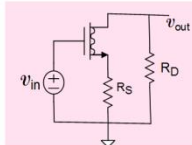	CE/CS		CC/CD		CB/CG		CEwRE/CSwRS	
	BJT	MOS	BJT	MOS	BJT	MOS	BJT	MOS
A_V	 $-g_m R_C$ $-\frac{I_{CQ} R_C}{V_t}$	 $-\frac{2I_{DQ} R_D}{V_{EB}}$	 $\frac{g_m}{g_m + g_E}$ $\frac{I_{CQ} R_E}{I_{CQ} R_E + V_t}$	 $\frac{2I_{DQ} R_E}{2I_{DQ} R_E + V_{EB}}$	 $g_m R_C$ $\frac{I_{CQ} R_C}{V_t}$	 $\frac{2I_{DQ} R_C}{V_{EB}}$	 $-\frac{R_C}{R_E}$	
R_{in}	$\frac{\beta V_t}{I_{CQ}}$ r_{π}	∞	$\beta \left(\frac{V_t}{I_{CQ}} + R_E \right)$ $r_{\pi} + \beta R_E$	∞	$\frac{V_t}{I_{CQ}}$ g_m^{-1}	$\frac{V_{EB}}{2I_{DQ}}$	$\beta \left(\frac{V_t}{I_{CQ}} + R_E \right)$ $r_{\pi} + \beta R_E$	∞
R_{out}	R_C	R_C	g_m^{-1} $\frac{V_t}{I_{CQ}}$	$\frac{V_{EB}}{2I_{DQ}}$	R_C	R_C	R_C	R_C

Can use these equations only when small signal circuit is EXACTLY like that shown !!

End of Lecture 32