 


VHDL Modeling for Synthesis


Hierarchical Design

Textbook Section 4.8: Add and Shift Multiplier

“Add and shift” binary multiplication




System Example: 8x8 multiplier

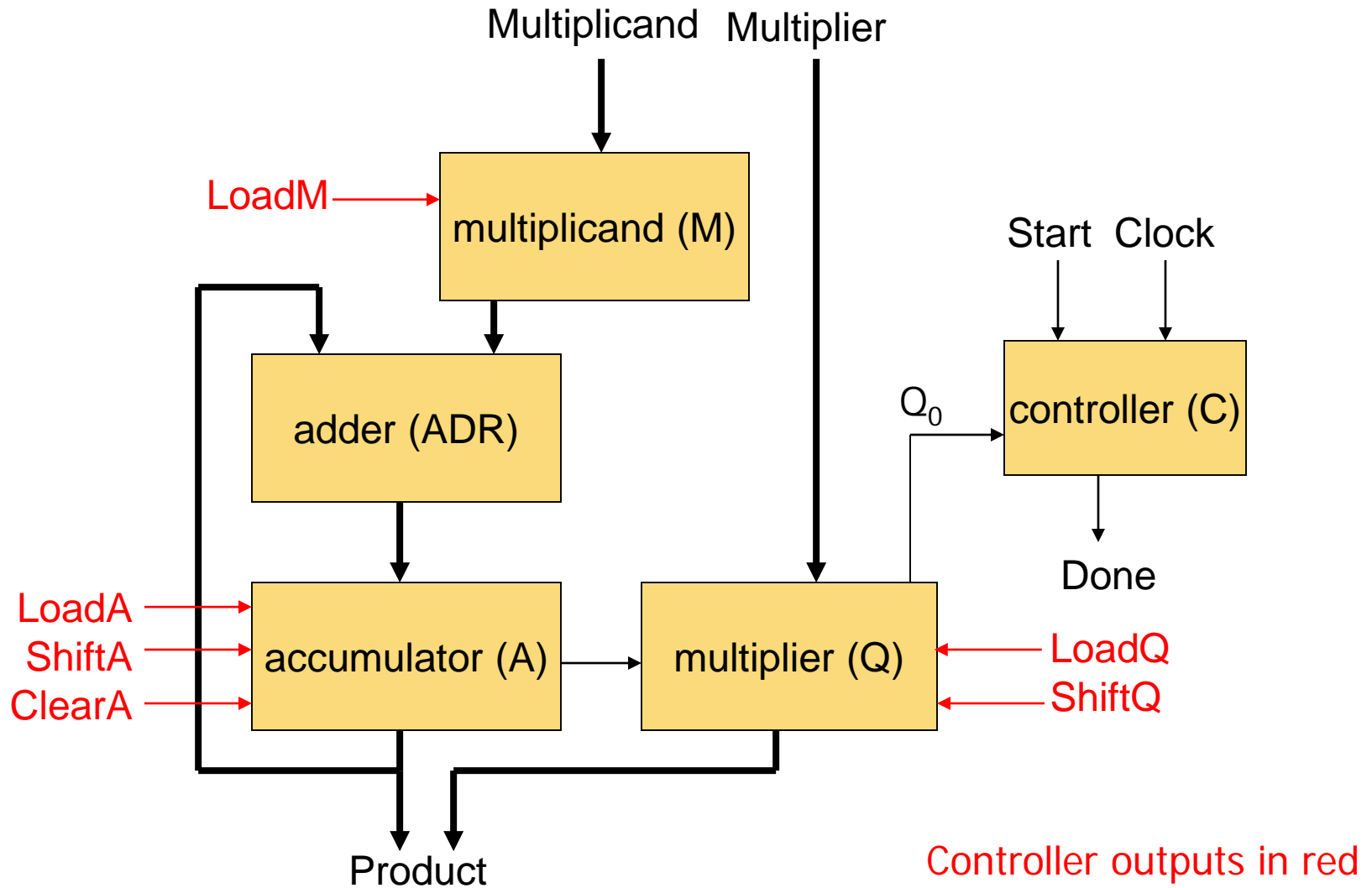


Roth example: Block diagram with control signals

FIGURE 4-25: Block Diagram for Binary Multiplier

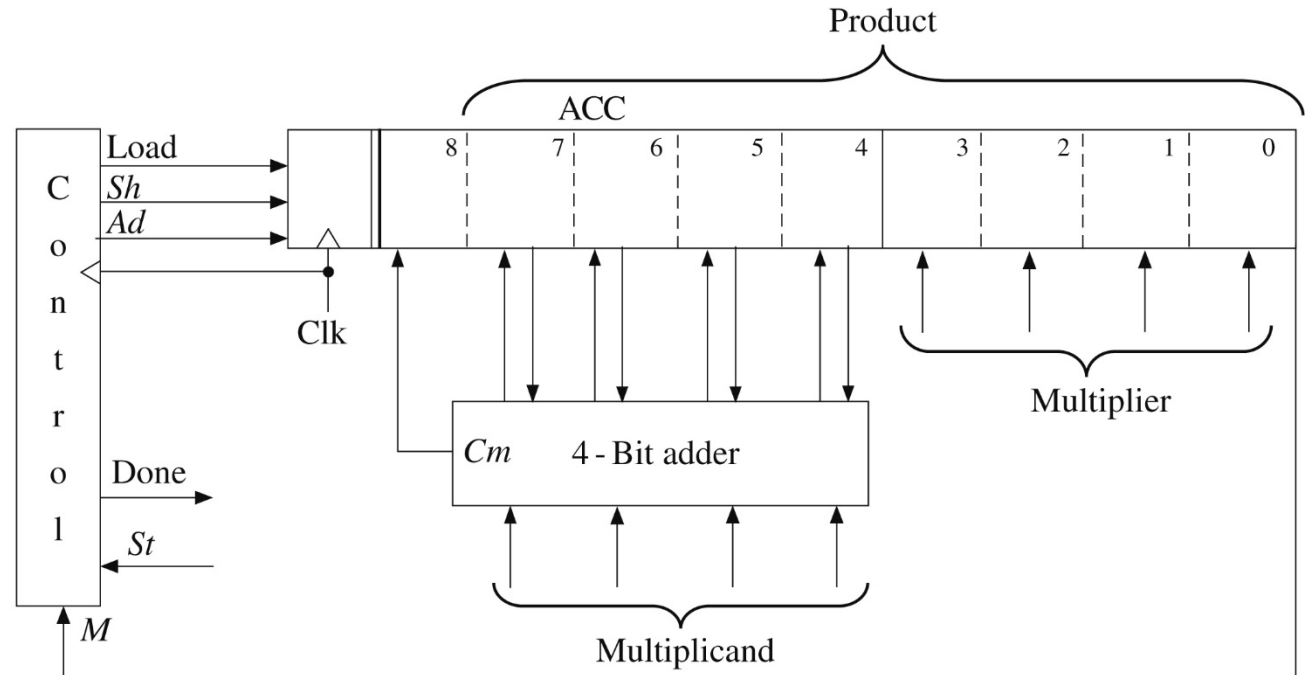


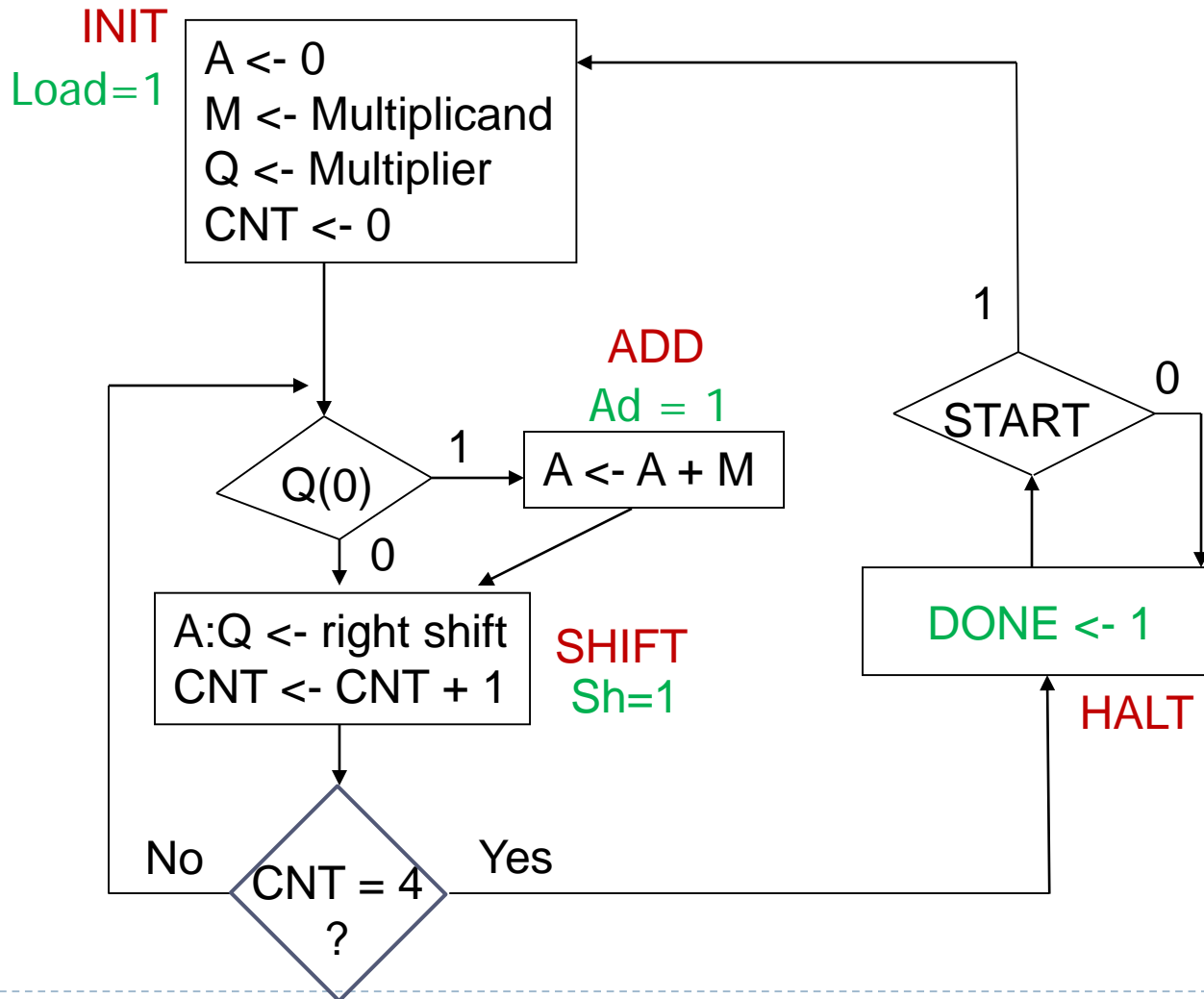“Add and shift” multiply algorithm (Moore model)



Example: $6 \times 5 = 110 \times 101$

M	A	Q	CNT	State	
110	0000	101	0	INIT	Multiplicand->M, 0->A, Multiplier->Q, CNT=0
	+ 110			ADD	(Since Q0=1) A = A+M
	0110	101	0		
	0011	010	1	SHIFT	Shift A:Q, CNT+1=1 (CNT not 3 yet) (skip ADD, since Q0 = 0)
	0001	101	2	SHIFT	Shift A:Q, CNT+1=2 (CNT not 3 yet)
	+ 110			ADD	(Since Q0 = 1) A = A+M
	0111	101	2		
	0011	110	3	SHIFT	Shift A:Q, CNT+1=2 (CNT= 3)
	0011	110	3	HALT	Done = 1


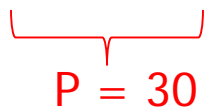


P = 30




Timing considerations

  Be aware of register/flip-flop setup and hold constraints




Revised multiply algorithm

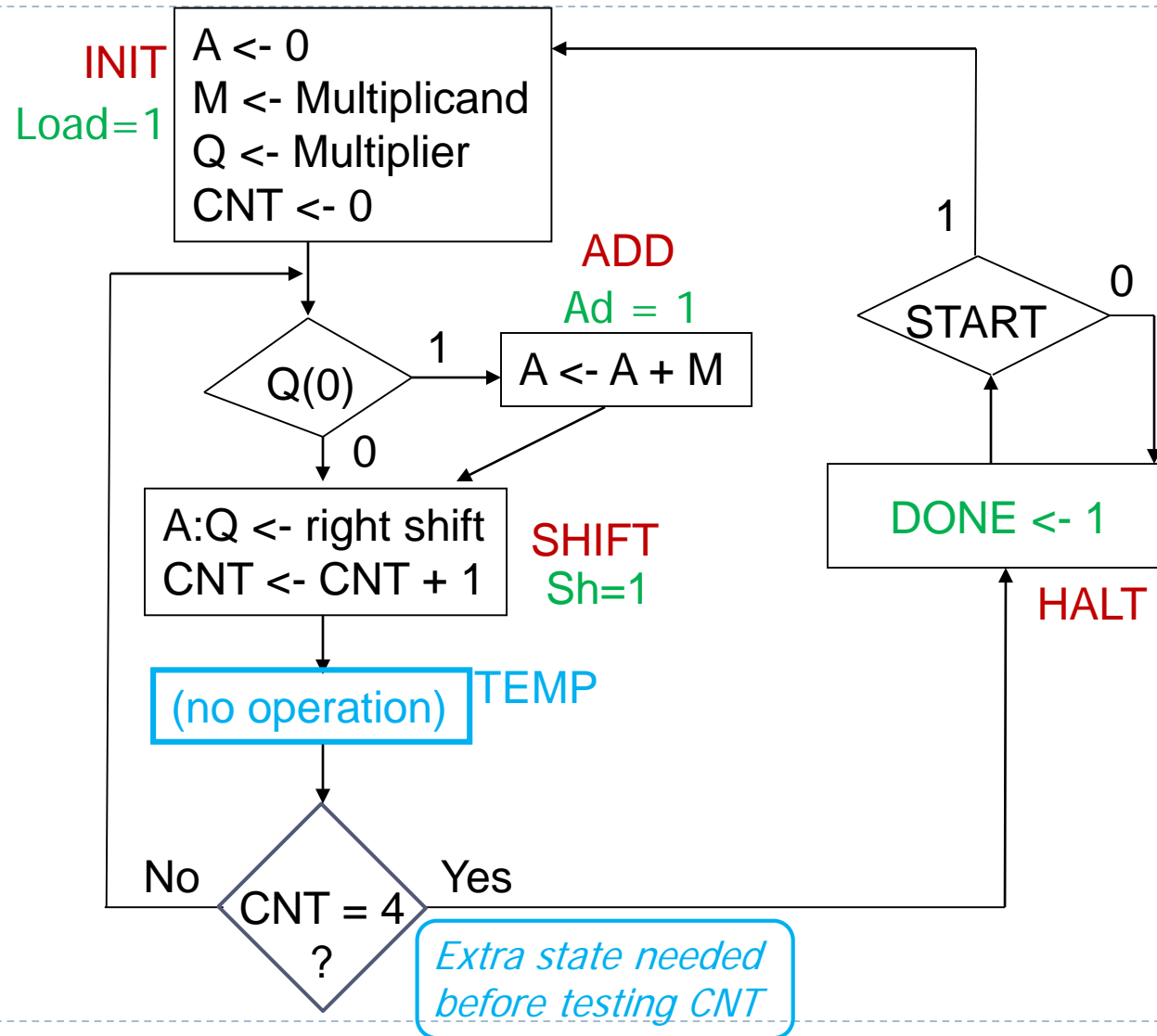


Control algorithm #1 state diagram

FIGURE 4-26: State Graph for Binary Multiplier Control

 


Control algorithm #2 – with bit counter (Mealy model)

FIGURE 4-28:
**Multiplier Control
with Counter**

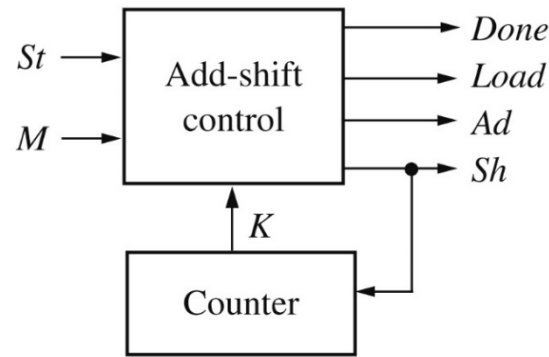


(a) Multiplier control

 

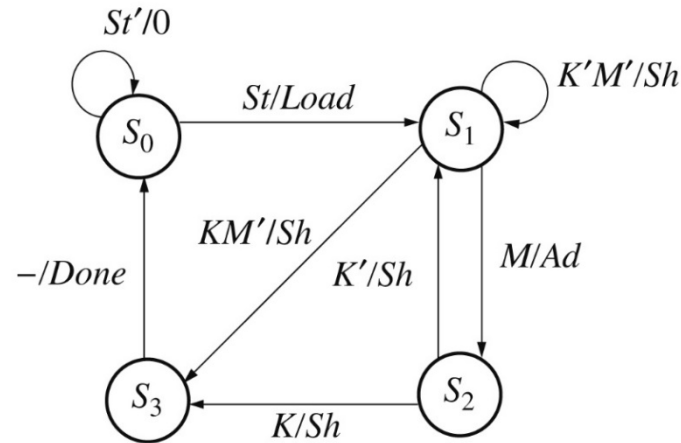(b) State graph for add-shift control

$M = \text{LSB of shifted multiplier}$
 $K = 1 \text{ after } n \text{ shifts}$



(c) Final state graph for add-shift control

Example – showing the counter

**TABLE 4-2:
Operation of
Multiplier Using a
Counter**

Time	State	Counter	Product Register	St	M	K	Load	Ad	Sh	Done
t_0	S_0	00	00000000	0	0	0	0	0	0	0
t_1	S_0	00	00000000	1	0	0	1	0	0	0
t_2	S_1	00	000001011	0	1	0	0	1	0	0
t_3	S_2	00	011011011	0	1	0	0	0	1	0
t_4	S_1	01	001101101	0	1	0	0	1	0	0
t_5	S_2	01	100111101	0	1	0	0	0	1	0
t_6	S_1	10	010011110	0	0	0	0	0	1	0
t_7	S_1	11	001001111	0	1	1	0	1	0	0
t_8	S_2	11	100011111	0	1	1	0	0	1	0
t_9	S_3	00	010001111	0	1	0	0	0	0	1



Multiplier – Top Level

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity MultTop is
```

```
    port (    Multiplier:      in std_logic_vector(3 downto 0);
            Multiplicand:     in std_logic_vector(3 downto 0);
            Product:          out std_logic_vector(7 downto 0);
            Start:            in std_logic;
            Clk:               in std_logic;
            Done:              out std_logic);
```

```
end MultTop;
```

```
architecture Behavioral of MultTop is
```

```
    use work.mult_components.all; -- component declarations
```

```
    -- internal signals to interconnect components
```

```
    signal Mout,Qout:      std_logic_vector (3 downto 0);
```

```
    signal Dout,Aout:     std_logic_vector (4 downto 0);
```

```
    signal Load,Shift,AddA: std_logic;
```



Components package

```
library ieee;
use ieee.std_logic_1164.all;
package mult_components is
component Controller      -- Multiplier controller
  generic (N: integer := 2);
  port ( Clk:  in  std_logic;           --rising edge clock
        Q0:   in  std_logic;           --LSB of multiplier
        Start: in  std_logic;         --start algorithm
        Load: out std_logic;          --Load M,Q; Clear A
        Shift: out std_logic;         --Shift A:Q
        AddA: out std_logic;          --Adder -> A
        Done: out std_logic );        -- Algorithm completed
end component;
component AdderN          -- N-bit adder, N+1 bit output
  generic (N: integer := 4);
  port(A,B: in std_logic_vector(N-1 downto 0);
        S: out std_logic_vector(N downto 0) );
end component;
component RegN           -- N-bit register with load/shift/clear
  generic (N: integer := 4);
  port ( Din:  in  std_logic_vector(N-1 downto 0);  --N-bit input
        Dout: out std_logic_vector(N-1 downto 0);  --N-bit output
        Clk:  in  std_logic;                       --rising edge clock
        Load: in  std_logic;                       --Load enable
        Shift: in std_logic;                       --Shift enable
        Clear: in std_logic;                       --Clear enable
        SerIn: in std_logic );                    --Serial input
end component;
```



Multiplier – Top Level (continued)

begin

C: **Controller** generic map (2) -- Controller with 2-bit counter
port map (Clk,Qout(0),Start,Load,Shift,AddA,Done);

A: **AdderN** generic map (4) -- 4-bit adder; 5-bit output includes carry
port map (Aout(3 downto 0),Mout,Dout);

M: **RegN** generic map (4) -- 4-bit Multiplicand register
port map (Multiplicand,Mout,Clk,Load,'0','0','0');

Q: **RegN** generic map (4) -- 4-bit Multiplier register
port map (Multiplier,Qout,Clk,Load,Shift,'0',Aout(0));

ACC: **RegN** generic map (5) -- 5-bit Accumulator register
port map (Dout,Aout,Clk,AddA,Shift,Load,'0');

Product <= Aout(3 downto 0) & Qout; -- 8-bit product

end Behavioral;



Generic N-bit shift/load register entity

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RegN is
  generic (N: integer := 4);
  port ( Din: in std_logic_vector(N-1 downto 0); --N-bit input
        Dout: out std_logic_vector(N-1 downto 0); --N-bit output
        Clk: in std_logic; --Clock (rising edge)
        Load: in std_logic; --Load enable
        Shift: in std_logic; --Shift enable
        Clear: in std_logic; --Clear enable
        SerIn: in std_logic; --Serial input
  );
end RegN;
```



Generic N-bit register architecture

architecture Behavioral of RegN is

```
    signal Dinternal: std_logic_vector(N-1 downto 0); -- Internal state
begin

process (Clk)
begin
    if (rising_edge(Clk)) then
        if (Clear = '1') then
            Dinternal <= (others => '0');           -- Clear
        elsif (Load = '1') then
            Dinternal <= Din;                       -- Load
        elsif (Shift = '1') then
            Dinternal <= SerIn & Dinternal(N-1 downto 1); -- Shift
        end if;
    end if;
end process;

Dout <= Dinternal;           -- Drive outputs**

end Behavioral;
```

** With this **inside** the process, extra FFs were synthesized



N-bit adder (behavioral)

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity AdderN is
  generic (N: integer := 4);
  port(   A: in std_logic_vector(N-1 downto 0); -- N bit Addend
         B: in std_logic_vector(N-1 downto 0); -- N bit Augend
         S: out std_logic_vector(N downto 0)  -- N+1 bit result, includes carry
        );
end AdderN;

architecture Behavioral of AdderN is

begin

  S <= std_logic_vector(('0' & UNSIGNED(A)) + UNSIGNED(B));

end Behavioral;
```



Multiplier Controller

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.NUMERIC_STD.ALL;
```

```
entity Controller is
```

```
  generic (N: integer := 2);
```

```
  port ( Clk:   in std_logic;
```

```
        Q0:   in std_logic;
```

```
        Start: in std_logic;
```

```
        Load:  out std_logic;
```

```
        Shift: out std_logic;
```

```
        AddA:  out std_logic;
```

```
        Done:  out std_logic
```

```
    );
```

```
end Controller;
```

```
-- # of counter bits
```

```
-- Clock (use rising edge)
```

```
-- LSB of multiplier
```

```
-- Algorithm start pulse
```

```
-- Load M,Q and Clear A
```

```
-- Shift A:Q
```

```
-- Load Adder output to A
```

```
-- Indicate end of algorithm
```



Multiplier Controller - Architecture

architecture Behavioral of Controller is

```
type states is (HaltS,InitS,QtempS,AddS,ShiftS);  
signal state: states := HaltS;  
signal CNT: unsigned(N-1 downto 0);
```

*QtempS included
for correct timing*

```
begin
```

```
-- Moore model outputs to control the datapath
```

```
Done  <= '1' when state = HaltS  else '0';  -- End of algorithm  
Load  <= '1' when state = InitS   else '0';  -- Load M/Q, Clear A  
AddA  <= '1' when state = AddS    else '0';  -- Load adder to A  
Shift <= '1' when state = ShiftS  else '0';  -- Shift A:Q
```



Controller – State transition process

```
process(clk)
begin
  if rising_edge(Clk) then
    case state is
      when HaltS    => if Start = '1' then          -- Start pulse applied?
                        state <= InitS;           -- Start the algorithm
                      end if;
      when InitS    => state <= QtempS;             -- Test Q0 at next clock**
      when QtempS  => if (Q0 = '1') then
                        state <= AddS;            -- Add if multiplier bit = 1
                      else
                        state <= ShiftS;         -- Skip add if multiplier bit = 0
                      end if;
      when AddS     => state <= ShiftS;           -- Shift after add
      when ShiftS  => if (CNT = 2**N - 1) then
                        state <= HaltS;         -- Halt after 2^N iterations
                      else
                        state <= QtempS;       -- Next iteration of algorithm: test Q0 **
                      end if;
    end case;
  end if;
end process;
```

** QtempS allows Q0 to load/shift before testing it (timing issue)

Controller – Iteration counter

```
process(Clk)
begin
  if rising_edge(Clk) then
    if state = InitS then
      CNT <= to_unsigned(0,N);      -- Reset CNT in InitS state
    elsif state = ShiftS then
      CNT <= CNT + 1;              -- Count in ShiftS state
    end if;
  end if;
end process;
```



Multiplier test bench (main process)

Clk <= not Clk after 10 ns; -- 20ns period clock

process

begin

for i in 15 downto 0 loop -- 16 multiplier values

Multiplier <= std_logic_vector(to_unsigned(i,4));

for j in 15 downto 0 loop -- 16 multiplicand values

Multiplicand <= std_logic_vector(to_unsigned(j,4));

Start <= '0', '1' after 5 ns, '0' after 40 ns; -- 40 ns Start pulse

wait for 50 ns;

wait until Done = '1'; -- Wait for completion of algorithm

assert (to_integer(UNSIGNED(Product)) = (i * j)) -- Check Product

report "Incorrect product" severity NOTE;

wait for 50 ns;


end loop;

end loop;

end process;



Simulation results

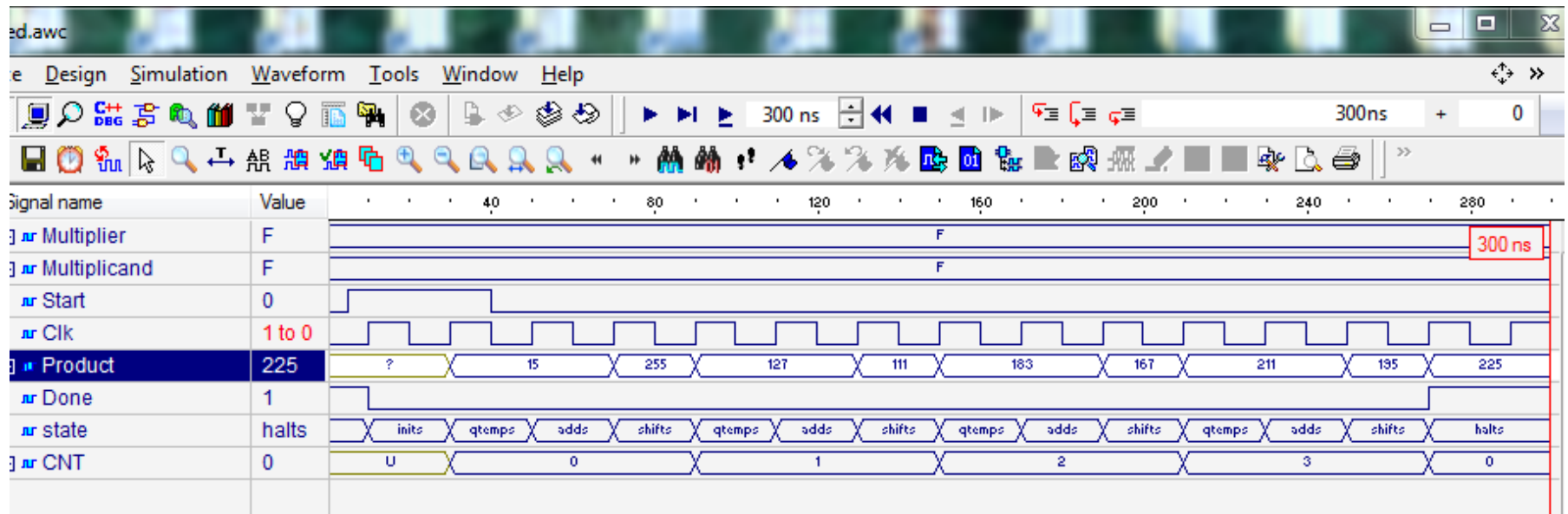

Behavioral model (non-hierarchical)

FIGURE 4-27: Behavioral Model for 4×4 Binary Multiplier

```
-- This is a behavioral model of a multiplier for unsigned
-- binary numbers. It multiplies a 4-bit multiplicand
-- by a 4-bit multiplier to give an 8-bit product.

-- The maximum number of clock cycles needed for a
-- multiply is 10.

library IEEE;
use IEEE.numeric_bit.all;

entity mult4X4 is
  port(Clk, St: in bit;
        Mplier, Mcand: in unsigned(3 downto 0);
        Done: out bit);
end mult4X4;

architecture behave1 of mult4X4 is
signal State: integer range 0 to 9;
signal ACC: unsigned(8 downto 0); -- accumulator
alias M: bit is ACC(0);          -- M is bit 0 of ACC
begin
  process(Clk)
  begin
    if Clk'event and Clk = '1' then -- executes on rising edge of clock
      case State is
        when 0 =>                -- initial State
          if St = '1' then
            ACC(8 downto 4) <= "00000"; -- begin cycle
            ACC(3 downto 0) <= Mplier;  -- load the multiplier
            State <= 1;
          end if;
      end if;
    end if;
  end process;
end behave1;
```


Behavioral model (continued)

```
when 1 | 3 | 5 | 7 =>    -- "add/shift" State
  if M = '1' then      -- add multiplicand
    ACC(8 downto 4) <= '0' & ACC(7 downto 4) + Mcand;
    State <= State + 1;
  else
    ACC <= '0' & ACC(8 downto 1);    -- shift accumulator right
    State <= State + 2;
  end if;
when 2 | 4 | 6 | 8 =>    -- "shift" State
  ACC <= '0' & ACC(8 downto 1);    -- right shift
  State <= State + 1;
when 9 =>                -- end of cycle
  State <= 0;
end case;
end if;
end process;
Done <= '1' when State = 9 else '0';
end behave1;
```



Array multiplier (combinational)

TABLE 4-3: Four-bit Multiplier Partial Products

					X_3	X_2	X_1	X_0	Multiplicand	
					Y_3	Y_2	Y_1	Y_0	Multiplier	
					<hr/>					
					$X_3 Y_0$	$X_2 Y_0$	$X_1 Y_0$	$X_0 Y_0$	Partial product 0	
					$X_3 Y_1$	$X_2 Y_1$	$X_1 Y_1$	$X_0 Y_1$	Partial product 1	
					C_{12}	C_{11}	C_{10}		First row carries	
					<hr/>					
					C_{13}	S_{13}	S_{12}	S_{11}	S_{10}	First row sums
					$X_3 Y_2$	$X_2 Y_2$	$X_1 Y_2$	$X_0 Y_2$	Partial product 2	
					C_{22}	C_{21}	C_{20}		Second row carries	
					<hr/>					
					C_{23}	S_{23}	S_{22}	S_{21}	S_{20}	Second row sums
					$X_3 Y_3$	$X_2 Y_3$	$X_1 Y_3$	$X_0 Y_3$	Partial product 3	
					C_{32}	C_{31}	C_{30}		Third row carries	
					<hr/>					
C_{33}	S_{33}	S_{32}	S_{31}	S_{30}					Third row sums	
P_7	P_6	P_5	P_4	P_3	P_2	P_1	P_0		Final product	



FIGURE 4-30: VHDL Code for 4 × 4 Array Multiplier

Array multiplier model

```

entity Array_Mult is
  port(X, Y: in bit_vector(3 downto 0);
        P: out bit_vector(7 downto 0));
end Array_Mult;

architecture Behavioral of Array_Mult is
  signal C1, C2, C3: bit_vector(3 downto 0);
  signal S1, S2, S3: bit_vector(3 downto 0);
  signal XY0, XY1, XY2, XY3: bit_vector(3 downto 0);
  component FullAdder
    port(X, Y, Cin: in bit;
          Cout, Sum: out bit);
  end component;
  component HalfAdder
    port(X, Y: in bit;
          Cout, Sum: out bit);
  end component;
begin
  XY0(0) <= X(0) and Y(0); XY1(0) <= X(0) and Y(1);
  XY0(1) <= X(1) and Y(0); XY1(1) <= X(1) and Y(1);
  XY0(2) <= X(2) and Y(0); XY1(2) <= X(2) and Y(1);
  XY0(3) <= X(3) and Y(0); XY1(3) <= X(3) and Y(1);

  XY2(0) <= X(0) and Y(2); XY3(0) <= X(0) and Y(3);
  XY2(1) <= X(1) and Y(2); XY3(1) <= X(1) and Y(3);
  XY2(2) <= X(2) and Y(2); XY3(2) <= X(2) and Y(3);
  XY2(3) <= X(3) and Y(2); XY3(3) <= X(3) and Y(3);

  FA1: FullAdder port map (XY0(2), XY1(1), C1(0), C1(1), S1(1));
  FA2: FullAdder port map (XY0(3), XY1(2), C1(1), C1(2), S1(2));
  FA3: FullAdder port map (S1(2), XY2(1), C2(0), C2(1), S2(1));
  FA4: FullAdder port map (S1(3), XY2(2), C2(1), C2(2), S2(2));
  FA5: FullAdder port map (C1(3), XY2(3), C2(2), C2(3), S2(3));
  FA6: FullAdder port map (S2(2), XY3(1), C3(0), C3(1), S3(1));
  FA7: FullAdder port map (S2(3), XY3(2), C3(1), C3(2), S3(2));
  FA8: FullAdder port map (C2(3), XY3(3), C3(2), C3(3), S3(3));
  HA1: HalfAdder port map (XY0(1), XY1(0), C1(0), S1(0));
  HA2: HalfAdder port map (XY1(3), C1(2), C1(3), S1(3));
  HA3: HalfAdder port map (S1(1), XY2(0), C2(0), S2(0));
  HA4: HalfAdder port map (S2(1), XY3(0), C3(0), S3(0));

  P(0) <= XY0(0); P(1) <= S1(0); P(2) <= S2(0);
  P(3) <= S3(0); P(4) <= S3(1); P(5) <= S3(2);
  P(6) <= S3(3); P(7) <= C3(3);
end Behavioral;

-- Full Adder and half adder entity and architecture descriptions
-- should be in the project

```