

WEBENCH® Power Designer

Power Supply Design Made Easy

Dr Ali Shirsavar
Biricha Digital Power Ltd
Parkway Drive
Reading
RG4 6XG
Dec - 2013



© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA


Introduction to Power Management

- The voltage of the power supply and/or battery feeding our PCB is seldom at the correct level that we need for our circuitry:
 - Example: A standard desktop PC in Europe is fed with 230V but the motherboard needs: +12V, -12V, +5V and +3.3V
- We need to step up and step down (convert) our voltage levels ALL THE TIME depending on the voltage available to us at our input connector and what the circuitry actually needs
 - There are two major methods to do this:
 - Linear Regulators (also known as series pass regulator, series regulator or LDOs) and
 - Switching Regulators (known as switch mode power supplies, or switching power supplies and power “converters”)
 - Note that (beyond very low currents) zener diodes or potential dividers are not good choices for this purpose!


© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

Introduction to Power Management

- LDO

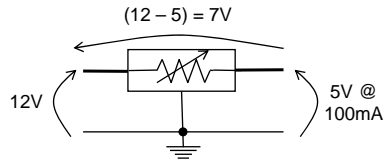

- Switching Regulator

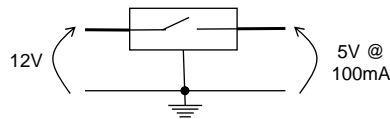

Why Do We Need a Converter/Regulator

- Of course the first job of the converter/regulator is to convert our input voltage to the output voltage level that our circuit requires
 - e.g. Input voltage $V_{in} = 12V$ but we actually need 5V for our ICs
- The second job is to regulate!
 - If there is a increase/decrease in the amount of current that we draw, the output voltage should not fall/rise
 - This is called *Load Regulation*
 - If there is a change in the input voltage of our power supply the output voltage should not change
 - This is called *Line Regulation*
- There are other desirable characteristics such as: transient response, efficiency, EMI, cost, size, etc but we will talk about these later


Linear Regulators

- Two major types (even though many people call all of them LDOs):
 - Standard
 - e.g. LM78LXX
 - Requires higher input voltage of around 2V; e.g. LM78L05 will give you a regulated output of 5V @100mA but V_{in} must be $> 7V$
 - Low Drop Out (LDO):
 - e.g. TPS793xx
 - Requires less dropout voltage than “standard type”. The input voltage typically needs to be only 0.6V higher than the output voltage
- They work by operating a transistor in the linear region (i.e. like a variable resistor), sensing the output voltage (V_{out}) and automatically changing this variable resistor value such that V_{out} remains constant
- Advantages:
 - Cheap & easy, quiet, small
- Disadvantages:
 - Very inefficient, low current only, limited V_{in} and V_{out} ranges

So What is Wrong with Linear Regulators?

- Let's say our input voltage is 12V and we need a 5V, 100mA supply
 - Ignoring the ground current, we will have 7V drop across our regulator

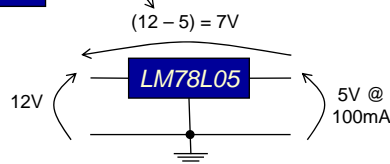Head for Linear Regulator ~ 2V
Head needed for LDO ~ 0.6V




- Output Power = $5V \times 100mA = 500mW$
- Power Loss in regulator = $7V \times 100mA = 700mW$
- Efficiency = $500mW / (1200mW) = 41.6\%$!

A switching regulator can be MUCH MORE efficient (+90%)

Switching Regulators (Power Converters)

- Imagine that we want to dim an old fashioned incandescent light bulb whereby the switch is on 100% of the time,
 - if we place a resistor in series with it and keep the switch on all the time then we dim the light but we waste energy in the resistor (this is like the linear regulator)
 - If instead of the resistor if we turn the switch off for 50% of the time and then turn it on for 50% of the time then we will dim the light by 50%
 - Obviously if we switch at a slow rate (once per second) then we would see the light flicker, but if we switch at a very fast rate then we would not see the flicker
 - This is the basic principle by which step down switching power supplies work

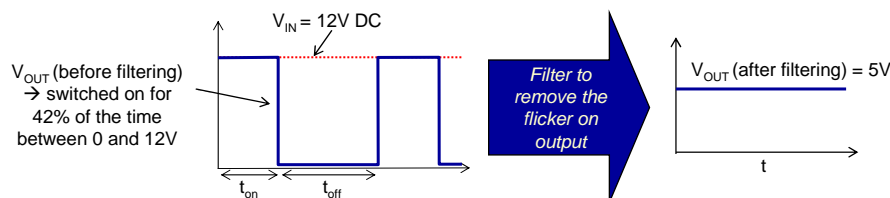

Switching Regulator Design Challenges

- Designing switch mode power supplies without software tools is **HARD!**
 - Need an understating of power electronics
 - Good understanding of control theory is essential for stability
 - There are many things that can go wrong... usually with a bang!
 - Need to understand the effect of parasitics and thermal management
 - Component selection is difficult and must be chosen so that they can tolerate the worse case scenario
 - Switching regulators are very noisy (from an EMI stand point) and good PCB layout is essential
 - Custom magnetic design is necessary for isolated power supplies
 - Engineers specialising in power can have most of these skills but, for the vast majority of us, all we need is power for our boards


WEBENCH® to the rescue!

Introduction to WEBENCH

- WEBENCH is a free, automatic tool that allows engineers to create reliable power supply circuits over the internet in minutes
- The user inputs circuit performance requirements and specifications and the WEBENCH toolset designs all the necessary circuitry
- Currently the following tools are available:
 - WEBENCH Power Designer
 - WEBENCH LED Designer
 - WEBENCH Sensor Designer
 - WEBENCH Active Filter Designer
 - WEBENCH Amplifier Designer
 - WEBENCH EasyPLL


In this session we will concentrate on WEBENCH Power Designer

Designing with WEBENCH

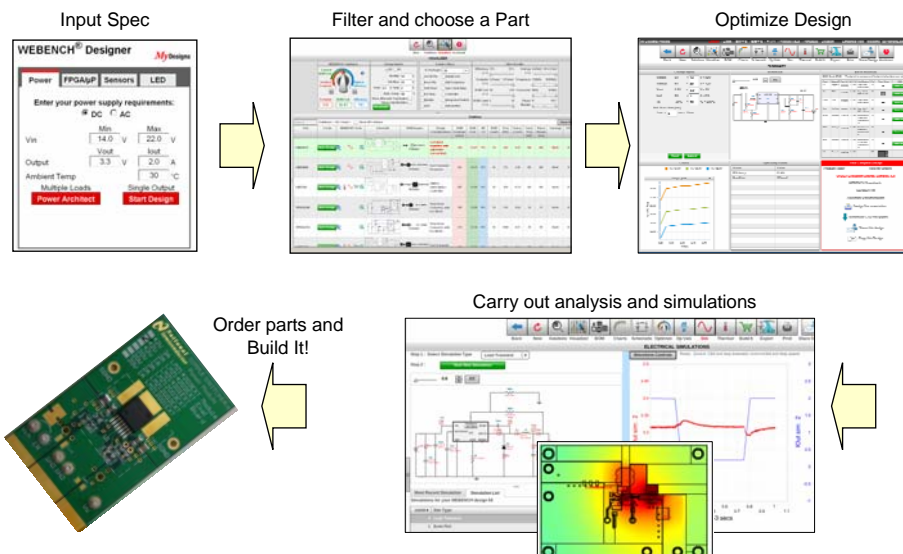

Design Using WEBENCH

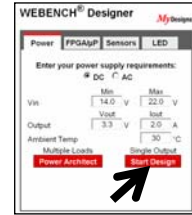- Input your specification and then press Start Design
 - WEBENCH will then open the “Visualizer” which provides you with a list of possible designs (sometimes over 100 designs) using different parts and topologies



WEBENCH Visualizer

Filtering tools

“Advanced Charting” tool allows further filtering

102 solutions

102 complete designs/solutions!
We may want to filter this down based on our requirements

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

Design Using WEBENCH

- Using the Visualizer’s filtering tools we will narrow down the designs to a smaller subset that will fit our requirements and then choose a part
 - WEBENCH will present you with many possible designs (sometimes over 100); so we have a few different filtering tools to help us narrow down the list
 - Before we can make an informed decision on how to select the best design for our application, we need to understand some basic fundamentals of power conversion – we will cover this in the next few slides

Optimizer dial:
Filter by footprint/ η / cost
hint don't use at this early stage

Filter by specification requirements

Change universal specifications

Filter by required features

WEBENCH® Optimizer

Lowest BOM Cost
Smallest Footprint
Footprint: 310
BOM Cost: \$1.61
Efficiency: 79%

Change Inputs
DC AC
Vin Min: 14 V
Vin Max: 22 V
Vout: 3.3 V Iout: 2 A
Amb. Temp: 30 °C
Show Alternate Topologies
Show Only Modules

Feature Filters
IC Package: All
On/Off Pin
Error Pin
Soft Start
Ext Sync
Mushie
LDO
Adj Ipk Lim
Adj Frequency
Sync Switching
Controller
Integrated Switch
Antinoise

Filter Results
Efficiency 70% 93%
Footprint 245mm² 95mm²
BOM Cost 50 118
BOM Count 5 34
Crossover: 0kHz 829kHz
Phase 0° 103°
Margin

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

BIRICHA DIGITAL TEXAS INSTRUMENTS

Simple Buck Converter and Basic Terminology

The switch is usually a MOSFET and we switch it on and off at our switching frequency (f_s) e.g. 200kHz

The inductor L & the capacitor C form a filter to smooth the output (remove the flicker)

The percentage of time that we keep the switch on in one switching period is called Duty (D) and determines our output voltage

200kHz will give a switching period T_s of $1/200\text{kHz} = 5 \mu\text{s}$

$D = \frac{\text{"On" time of switch}}{\text{Switching Period}} = \frac{t_{on}}{T_s}$

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 13

BIRICHA DIGITAL TEXAS INSTRUMENTS

Simple Buck Converter and Basic Terminology

- When the switch is ON
 - Replace the switch with a short
 - Diode is reverse biased (replace with open circuit)
 - Inductor current will rise linearly


- When the switch is OFF
 - Replace switch with open circuit
 - Diode is forward biased (replace with short circuit)
 - Inductor current will fall linearly

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 14

BIRICHA DIGITAL TEXAS INSTRUMENTS

Simple Buck Converter and Basic Terminology

- Observations:
 - At turn on inductor current rises linearly
 - At turn off it falls linearly
 - Inductor current ripple is proportional to how long the switch is on and off
 - If we have a longer turn on period and turn off period, (i.e. slower switching frequency) we will have a larger ripple
 - Inductor Ripple Current is one of the most important design parameters → we will talk about this in more detail later but for now:

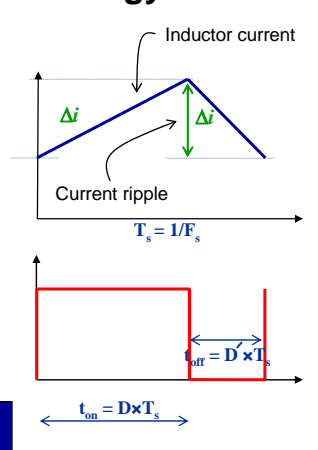


The faster the switching frequency, the smaller the inductor current ripple
OR
If we switch faster we can use a smaller inductor (we will talk about switching losses later)

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 15

BIRICHA DIGITAL TEXAS INSTRUMENTS

What Do We Mean by Conduction Mode?

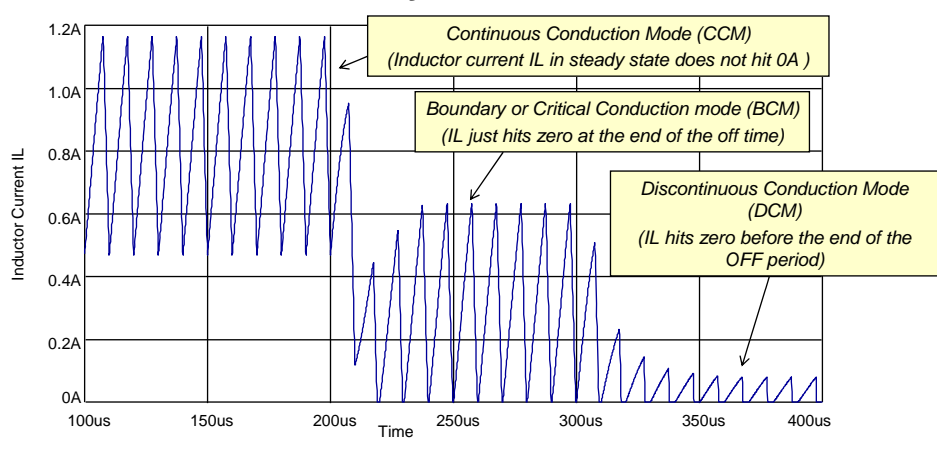

Whether or not the inductor current at steady state is in DCM or CCM will have implications on how our power supply behaves
WEBENCH will look after this for us but we need to understand the terminology used

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 16

WEBENCH Power Designer*

- You can use WEBENCH to create customized power supplies or DC-DC converters for your circuits
 - This environment gives you end-to-end power supply designs and prototyping tools
- WEBENCH tools enable you to solve switching-power-supply design problems before you build your prototype
 - This alleviates the time and trouble associated with traditional power supply design methods
- Included in the WEBENCH toolset is a device selection tool
 - This tool helps you find the best switching regulator or MOSFET controller for your power supply circuit. It even selects the most appropriate passive components

Topologies Used in WEBENCH

- WEBENCH supports the following topologies
 - Buck
 - Boost
 - Inverting Buck-Boost
 - SEPIC
 - Flyback
- These topologies cover almost all your point of load (POL) needs
 - There are other topologies not supported by WEBENCH but these are for very high power off-line power supplies and rarely used for POL power distribution within a PCB
- WEBENCH automatically recommends the most suitable topology for you
 - But we will compare these topologies so that you have a better insight as to which topology is most suitable for your application

BIRICHA DIGITAL TEXAS INSTRUMENTS

Topology Selection Guide

$V_{out} = V_{in} \times D$

- Buck Converters
 - Standard Buck (as shown)
 - Step down only
 - Most popular converter for PoL
 - Switch is not referenced to ground
 - high-side switch i.e. more expensive gate driver
 - Synchronous Buck
 - Replaces or complements the diode with an extra switch (and a low side gate driver) to improve efficiency
 - But efficiency is not that great if converter is operated under discontinuous conduction mode (DCM)
 - Synchronous Buck with Diode Emulation
 - Similar to Synchronous Buck but solves the DCM efficiency performance issue
 - But more expensive IC

Normal buck

Synchronous buck

* Image taken from www.ti.com/lit/sg/slouw001e/slouw001e.pdf
 © Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 19

BIRICHA DIGITAL TEXAS INSTRUMENTS

Topology Selection Guide

- Boost
 - Step up only
 - Switch is referenced to ground (low-side switch)
 - Can use a cheaper gate driver
 - Used when the voltage you need on your PCB needs to be higher than the input voltage
 - Better used with current mode control as opposed to voltage mode if operated in continuous conduction mode
 - We will talk about conduction modes and control methods soon
 - Major draw back is that there is no ability to limit the current (i.e. can't turn off the switch to stop the current!)

$V_{out} = V_{in} \times \frac{1}{(1 - D)}$

* Image taken from www.ti.com/lit/sg/slouw001e/slouw001e.pdf
 © Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 20

BIRICHA DIGITAL TEXAS INSTRUMENTS

Topology Selection Guide

- Inverting Buck-Boost
 - Can step both up and down
 - Common in battery operated devices where, depending on the battery charge, you may want to either buck or boost
 - But V_{out} always has a reverse polarity with respect to the V_{in}
 - Most popular when you have a positive voltage on your input but on your PCB you need a negative voltage
 - Best used with current mode control when in CCM
 - Very noisy from an EMI point of view
 - The switch can be either on the high side or on the low side
 - High side switch needs a more expensive gate driver
 - Low side switch is cheaper but the load is then referenced to ground

$$V_{out} = V_{in} \times \frac{D}{(1 - D)}$$

* Image taken from www.ti.com/lit/sg/sl0001e/sl0001e.pdf
 © Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 21

BIRICHA DIGITAL TEXAS INSTRUMENTS

Topology Selection Guide

- Flyback
 - Transformer isolated version of Inverting Buck-Boost
 - Depending on how the transformer is wound it can have both positive and negative output voltage
 - Because of the transformer can buck down from much higher input voltage rails
 - Can have multiple output voltage of different polarities (e.g. +- 12V) by having more than one secondary winding - but only one voltage rail can be controlled
 - For DC/DC conversion it is most commonly used with current mode control in CCM
 - Very noisy but cheap
 - The switch is usually placed on the low side so that a cheaper gate driver can be used but it can also be placed on the high-side


$$V_{out} = V_{in} \times \frac{N_s}{N_p} \frac{D}{(1 - D)}$$

* Image taken from www.ti.com/lit/sg/sl0001e/sl0001e.pdf
 © Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 22

Topology Selection Guide

- SEPIC (Single Ended Primary Inductor Converter)
 - Can step up and down (like buck boost) but does not invert the polarity
 - Common in battery operated devices, where depending on the battery charge you may want to either buck or boost
 - Unlike Boost it can be shut-down
 - Transfer function is complex (use WEBENCH for stable design)
 - Therefore typically used when fast transient response is not required
 - Needs just a single low-side switch
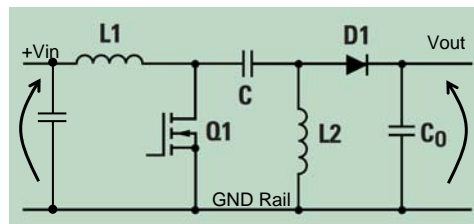
$$V_{out} = V_{in} \times \frac{D}{(1-D)}$$



* Image taken from www.ti.com/lit/sg/sl0001e/sl0001e.pdf
© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

23

Control Method Selection Guide

- WEBENCH uses the following control methods
 - Voltage mode
 - Cheap and simple; works well for Buck but not suitable for CCM Boost, Buck-Boost, Flyback or SEPIC
 - Poor/slow transient performance under DCM conditions
 - Current mode
 - Faster transient response than voltage mode during line voltage transients
 - Good performance in both DCM and CCM
 - Ideal for Boost, Buck-Boost, Flyback and SEPIC in CCM
 - Poor performance when duty is small (e.g. if you step-down too much)
 - Needs slope compensation and leading edge blanking (i.e. bit of a pain!)
 - Emulated current mode
 - Similar to current mode but can operate under low duties
 - But based on a mathematic model which will not be perfect
 - Constant On Time
 - Cheap and easy and always stable with fast response
 - Better efficiency under low loads (unless pulse skipping used in other control methods)
 - But will have more ripple than other control methods
 - Variable frequency so unpredictable EMI spectrum + harder to design EMI filter

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

24

Choosing the Right Switching Frequency

- Our switching frequency (Fs) directly impacts the size of our power supply
 - We saw earlier that the higher the switching frequency the smaller the current ripple on our inductor
 - i.e. the higher the switching frequency, the smaller the inductor
 - This also applies to our output capacitor, so the entire power supply will get smaller
 - This is why the switching frequency of the PSU for small hand held devices needs to be so high
 - There is a limit as to the ripple we can have on our inductor as you must not saturate the inductor → WEBENCH automatically selects a correctly sized inductor
- Our switching frequency directly impacts our efficiency
 - The higher the switching frequency the poorer the efficiency
 - Every time we turn a switch on or off we will waste some energy; these are called Switching Losses → if we switch faster we will have higher switching losses
 - Every time we magnetize and de-magnetize our inductor we will lose some energy in the magnetic material of our inductor; these are called Core Losses → if we switch faster we will have higher core losses
- Of course both of the above will have an impact on cost

WEBENCH can optimize your design for efficiency or size or cost depending on your requirements


Choosing the Right Part/Device for Your Application


- There are 4 major categories of ICs that WEBENCH designs with:
 - LDOs
 - Not recommended for good efficiency, output current above 500mA or large voltage drops
 - Switching Power Modules
 - Switching Regulators
 - Switching Controllers
- Within seconds WEBENCH calculates over 100 designs with this parts
- Which one is the most suitable for your application?
 - We will now quickly go through these categories
 - Once you know what the differences are you can very quickly use WEBENCH's filtering tools to narrow down these 100 designs to just a handful most suitable for your application

BIRICHA DIGITAL TEXAS INSTRUMENTS


Which Device is Best for Your Application

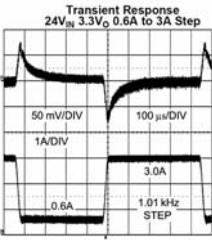- **Switching Modules** (e.g. LMZ14203)
 - Complete solution with internal switch and inductor in one package
 - Very small foot print + everything optimized
 - Some come with EMC compliance
 - But:
 - more expensive (~ 1.5 to 8 USD)
 - More limited as the value of the inductor is fixed
 - Max current delivery of 20A





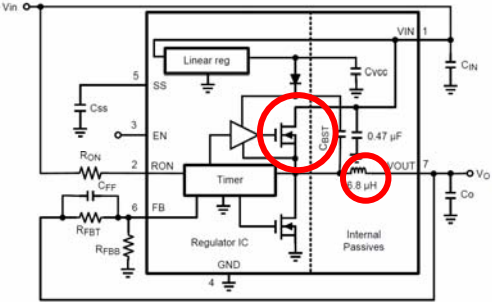Transient Response
24V_{IN} 3.3V_O 0.6A to 3A Step




* Images taken from www.ti.com & device datasheet
© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA


27

BIRICHA DIGITAL TEXAS INSTRUMENTS

Which Device is Best for Your Application

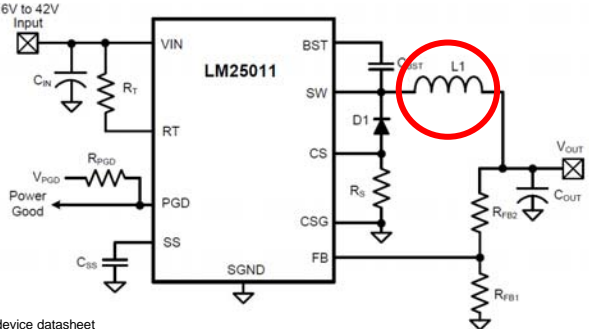- **Switching Regulators** (e.g. LM25011)
 - Complete solution with internal switch but external inductor
 - Small foot print + switch drive circuitry optimized (but not as small as a module)
 - Much cheaper than power modules but need an inductor
 - Can have some more flexibility due to external components






* Images taken from www.ti.com & device datasheet
© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

28

Which Device is Best for Your Application



- **Switching Controllers** (e.g. LM3150)
 - Just the PWM chip; i.e. no internal switch or inductor
 - Largest foot print + most have gate driver inside but not optimized with the switch
 - You have to select the right switch yourself (or use WEBENCH)
 - V cheap but need an extra switch/inductor/compensation etc
 - Gives you complete flexibility in terms of your design at the expense of more development time, larger foot print, extra components & routing etc

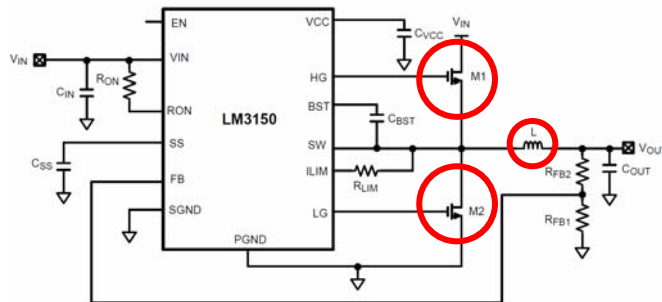

* Images taken from www.ti.com & device datasheet
© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

29

Quick Summary to Selection Guide

- Which topologies to use for various applications:
 - LDOs → Small currents and limited/fixed voltages, poor efficiency
 - Buck → most common step down
 - Boost → most common step up
 - Buck-Boost/SEPIC → most common for battery operation / step up and down
 - Flyback → when you need multiple voltage or need to step down from large input voltage
- Which control mode to use for various applications?
 - COT → cheap and easy, always stable but variable frequency & ripple
 - Voltage mode → most common in Buck, cheap and easy low component count
 - Current mode → most common for CCM in Boost, Buck-Boost, SEPIC, Flyback, very good performance but needs slope compensation and leading edge blanking (a bit of a pain), not great if duty is very small
 - Emulated Current Mode → like current mode but solved the low duty issue, but model based so it all depends on how accurate the model is

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

30

Quick Summary to Selection Guide

- Selecting the switching frequency
 - The higher our F_s , the smaller the PSU but the poorer the efficiency
 - The higher the F_s the smaller the ripple on the inductor → large ripple on inductor could cause saturation and a blown up power supply
 - WEBENCH allows you to automatically optimize this
- Which Device to Select?
 - Switching Modules → (almost) everything internal, smallest foot print, quickest and easiest to set up but more expensive
 - Switching Regulators → Internal switch but external inductor, larger foot print than a module, more flexible due to external components, cheaper (if you don't count the price of the inductor)
 - Switching Controllers → just a PWM controller, so almost everything else is external, largest foot print, largest BoM, development time and routing but most flexible

We are now ready to move on to Step 3 of designing with WEBENCH

Hands-On Demo 1 - Fundamentals

- Step 1: Input your specification:
 - $V_{in} = 22V$, $V_{out} = 3.3V$, $I_{out} = 2A$, Ambient Temp = 30°

WEBENCH[®] Designer My Designs

Power **FPGA/μP** Sensors LED

Enter your power supply requirements:

DC AC

Vin V V

Output V A

Ambient Temp °C

Multiple Loads Single Output

Power Architect **Start Design**

Select your power supply solution

<p>Module</p> <p>Easiest to use Low EMI</p> <p>Choose Part</p>	<p>Integrated</p> <p>Easy to use Cost effective</p> <p>Choose Part</p>	<p>Controller</p> <p>Maximum flexibility High performance</p> <p>Choose Part</p>
--	--	--

Or

Compare All Part Types

Do not show this again

Hands-On Demo 1 - Fundamentals

- Step 2: WEBENCH will create many solutions (~102) and display all of them in the Visualizer
 - We now need to filter these ~102 designs to a smaller subset that meets our design objectives



© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

Note your results may be different

Hands-On Demo 1 - Fundamentals

- Using the filtering tools of the Visualizer let us first see best case scenarios for:
 - Lowest Cost → LM25011 – total BoM Cost = 1.61 USD
 - Highest efficiency → LM3510 - $\eta = 93\%$
 - Smallest footprint → TPS84250 – Total footprint = 245mm² (i.e. ~1.5cm x 1.5cm)

Part	IC Package	BOM Images	Design Considerations	BOM Footprint (mm ²)	BOM Cost	Eff (%)	BOM Count	Freq (kHz)	Vout p. (mV)	Xover Freq (kHz)	Phase Margin (deg)	Topology	LED Temp (deg)	Inst Max (A)	IC Cost	
LM25011	COIL BACK regulator with adjustable current limit			310	15.61	79%	11	569	5.71	NA	NA	Buck	II	67°C	2.60	16.95
LM3150	SIMPLE SWITCHER® Controller			407	12.58	93%	16	429	12.25	NA	NA	Buck	II	71°C	12.80	11.55
TPS84250	Non-Sync Step Down Converter, Integrated			245	16.43	78%	8	400	10.16	55	39	Buck	II	38°C	2.50	15.25

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

Hands-On Demo 2 - Fundamentals

- Let us design a new power supply
 - WEBENCH starts with around 102 designs
 - We are going to assume that for this design, we are short of space and time, but cost is not a big issue
 - Therefore we would like the quickest and smallest possible solution → use “Switching Modules”
 - When we filter down to Switching Modules only, the number of solutions will fall from 102 to 11 (next slide)

Hands-On Demo 2 - Fundamentals

The first (in green) on the list is WEBENCH's top choice

11 solutions

Part	Tools	Schematic	BOM Images	Design Considerations	BOM Footprint (mm ²)	BOM Cost	Eff (%)	BOM Count	Footp (mm ²)	Output p (mV)	Power Freq (kHz)	Phase Margin (deg)	Topology	LDO	Temp (deg)	Out Max (A)	IC Cost
LMZ14203	Open Design			3A SIMPLE SWITCHER Power Module	373	\$6.63	82%	16	528	1.65	NA	NA	Back	II	57°C	1.00	\$6.54
LMZ14203EKT	Open Design			3A SIMPLE SWITCHER Power Module	373	\$17.63	83%	18	528	1.65	NA	NA	Back	II	57°C	1.00	\$16.80
LMZ14202	Open Design			2A SIMPLE SWITCHER Power Module	373	\$7.88	81%	10	535	1.67	NA	NA	Back	II	59°C	2.00	\$6.75
LMZ14202EKT	Open Design			2A SIMPLE SWITCHER Power Module	373	\$14.93	81%	10	535	1.67	NA	NA	Back	II	59°C	2.00	\$17.80

WEBENCH will do Circuit Calculations

WEBENCH will do Thermal Simulations

Circuit Simulations




Can export schematic to CAD package

Buy it option: can buy an entire kit including PCB from Digikey

Hands-On Demo 2 - Fundamentals

- Let us now filter down with 2 more requirements:
 - Max PCB footprint = $2.5\text{cm} \times 2.5\text{cm} = 625\text{mm}^2$
 - Total cost (for 1k units) less than 8.5 USD
- We now see that we have narrowed down our solutions to only 2:
 - LMZ14202 & TPS84250
 - LMZ part is being recommended. It has all the simulations tools and Buy It tools available so we could select this design → Let us look at the datasheet first
 - IMPORTANT: Please DO NOT press Open Design yet; we will do this shortly**

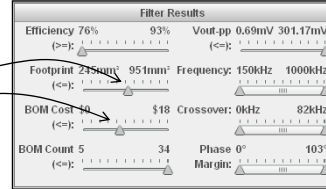

Part	Create	WEBENCH Tools	Schematic	BOM Images	Design Considerations	BOM Footprint (mm ²)	BOM Cost	EW (%)	BOM Count	Freq (kHz)	Vout p-p (mV)	Over Freq (dB)	Phase Margin (deg)	Topology	LDO	Temp (deg)	Inst Max (A)	R. Cost
LMZ14202	Open Design				3A SIMPLE SWITCHER Power Module	373	\$7.88	81%	19	535	1.82	NA	NA	Buck	II	59°C	2.86	\$4.75
TPS84250	Open Design				Non-Sync Step Down Converter, Integrated	245	\$6.43	79%	8	499	16.16	55	59	Buck	II	10°C	3.59	\$5.35


Hands-On Demo 2 - Fundamentals

- Step 3: “Open Design” (you may have to log in)
 - In Steps 1 & 2 we typed in our specification and then filtered down our solutions to just one or two
 - Now we select the most appropriate by pressing “Open design”
 - We can now optimize our selected design even further to make find a best fit solution for our application

Part	Create	WEBENCH Tools	Schematic	BOM Images	Design Considerations
LMZ14202	Open Design				3A SIMPLE SWITCHER Power Module
TPS84250	Open Design				Non-Sync Step Down Converter, Integrated


Hands-On Demo 2 - Fundamentals

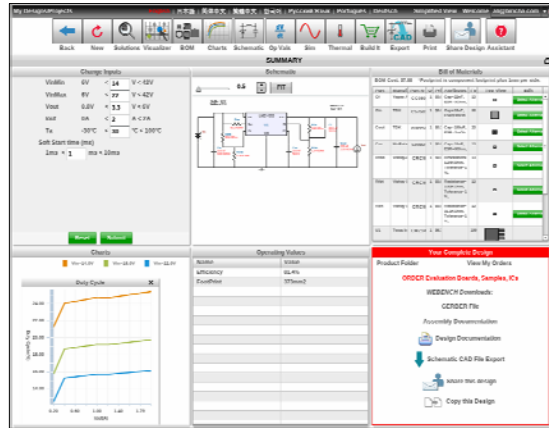- Step 4: Modifying/Optimising our Design using WEBENCH Dashboard
 - Depending on the device used some of the options on this page will be different
 - We are using a fully integrated “Module” so we don’t have that many options, but this is a good start; we will explore more complicated designs later



WEBENCH Dashboard and Controls

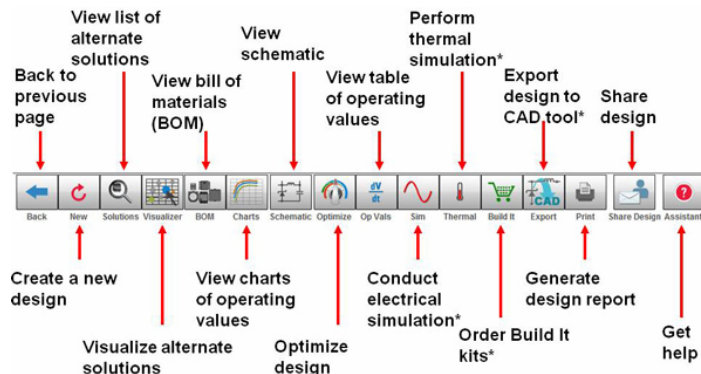- Dashboard navigation icons after opening the design



*Not all parts have these features

BIRICHA DIGITAL TEXAS INSTRUMENTS

Hands-On Demo 3 – The Schematic

- Let us look at the Schematic first
 - From the navigation icons on top of the page click on the schematic
 - If you further click on a component you will get more information

Back New Solutions Visualizer BOM Charts Schematic Op Vals Sim Thermal Build It Export Print Share Design Assistant

VinMin = 14 V
VinMax = 22 V

Vout = 3.3 V
Iout = 2 A

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 41

BIRICHA DIGITAL TEXAS INSTRUMENTS

Hands-On Demo 4 – Operating Values

Back New Solutions Visualizer BOM Charts Schematic Op Vals Sim Thermal Build It Export Print Share Design Assistant

Modify Operating Point

Vin: Iout: Recalculate

Name	Value	Category	Description
Vout p-p	1.12mV	Op_Point	Peak-to-peak output ripple voltage
Vout OP	3.3V	Op_Point	Operational Output Voltage
VIN_OP	22V	Op_Point	Vin operating point
Total Pd	1.51W	Power	Total Power Dissipation
Total BOM	7.88\$		Total BOM Cost
Pout	6.6W	General	Total output power
Mode	CCM	General	Conduction Mode
MI Irms	0.98A	Current	Q lavg
M Vds Act	0.12V	General	Voltage drop across the MosFET
Iin Avg	0.36A	Current	Average input current
IOUT_OP	2A	Op_Point	Iout operating point
ICThetaJA	19.3degC/W	Op_Point	IC junction-to-ambient thermal resistance
IC Tolerance	0.02V	General	IC Feedback Tolerance
IC Tj	59.0degC	Op_Point	IC junction temperature
IC Ipk	2.28A	Current	Peak switch current in IC
Frequency	535KHz	General	Switching frequency
FootPrint	373mm2	General	Total Foot Print Area of BOM components
Efficiency	81.4%	Op_Point	Steady state efficiency
Duty Cycle	16.2%	Op_Point	Duty cycle

You can change the operating point and WEBENCH will recalculate all these values

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 42

Hands-On Demo 4 – Operating Values

- What is the efficiency, duty and conduction mode if we run at 14V?

Modify Operating Point			
Vin:	14	Iout:	2.0
<input type="button" value="Recalculate"/>			
Name	Value	Category	Description
Vout p-p	1.00mV	Op. Point	Peak-to-peak output ripple voltage
Vout OP	3.3V	Op. Point	Operational Output Voltage
VIN_OP	14V	Op. Point	Vin operating point
Total Pd	1.20W	Power	Total Power Dissipation
Total BOM	7.88\$		Total BOM Cost
Pout	6.6W	General	Total output power
Mode	CCM	General	Conduction Mode
MI Irms	1.20A	Current	Q Iavg
M Vds Act	0.12V	General	Voltage drop across the MosFET
Iin Avg	0.55A	Current	Average input current
IOUT_OP	2A	Op. Point	Iout operating point
ICThetaJA	19.3degC/W	Op. Point	IC junction-to-ambient thermal resistance
IC Tolerance	0.02V	General	IC Feedback Tolerance
IC Tj	53.2degC	Op. Point	IC junction temperature
IC Ipk	2.25A	Current	Peak switch current in IC
Frequency	53KHz	General	Switching frequency
FootPrint	373mm2	General	Total Foot Print Area of BOM components
Efficiency	84.6%	Op. Point	Steady state efficiency
Duty Cycle	25.4%	Op. Point	Duty cycle

Hands-On Demo 5 – Built It® Tool

- We will talk about simulation capabilities of WEBENCH in another design example
 - For now let us finalize our design and order a custom prototype based on our design (including the PCB) with just one click!

Export to: Kit Quantity: 1 Do you have a coupon?

Part Number	Manufacturer	Component	Qty Avail	Qty Req per Kit	Minimum	Qty Ordered	Prototype Price*	Total	Top View	Edit
CRCW80551K1FKEA	Vishay-Dale	Ron	>10	1	10	1				Select Alternate Part
C2225X3R0J107M	TDK	Cap	>10	1	1	1				Select Alternate Part
CRCW8056K34FKEA	Vishay-Dale	Res	>10	1	10	1				Select Alternate Part
ORM216R71M103KA01D	MuRata	Cap	>10	1	1	1				Select Alternate Part
CRCW80568K1FKEA	Vishay-Dale	Res	>10	1	10	10	\$ 0.09	\$ 0.90		Select Alternate Part
LM214202T2-ADJNOPB	Texas Instruments	UI	>10	1	1	1	\$ 13.79	\$ 13.79		Select Alternate Part
CC0805KRX7R9BB223	Yageo America	Cap	>10	1	1	1	\$ 0.10	\$ 0.10		Select Alternate Part

Part Number	Manufacturer	Component	Qty Avail	Qty Req per Kit	Order Minimum	Qty Ordered	Prototype Price*	Total	Top View	Edit
551600437-001	Texas Instruments	PC Board	>10	1	1	1	\$ 10.20	\$ 10.20		Select Alternate Part
1502-2	KeyStone	J1,J2,J3,J4	>10	4	1	4	\$ 0.31	\$ 1.24		Select Alternate Part

WEBENCH Optimization Tips and Tricks

- In the previous slides we designed a Buck converter starting from a specification to a prototype within minutes
- In the process we became familiar with some of the most important WEBENCH tools
 - Designer, Visualizer, filtering tools and Dashboard
 - Within Dashboard we used
 - Schematic tool
 - Operating Values
 - Built it tool
- We will now design a more complicated power supply and become familiar with the Optimization tools available within WEBENCH

Hands-On Demo 6 - Optimization Tips and Tricks

- Let us design a power supply with the following requirements:
 - Vin 14 – 22V; Vout 3.3 @ 2A
 - Must have Soft Start & integrated switch and full WEBENCH simulation capability
 - Foot print <270 mm²
 - Max BoM cost < 3.50 USD
 - Efficiency > 83%

The screenshot shows the WEBENCH Optimizer interface with the following details:

- Change Inputs:** DC/AC, Vin Min: 14 V, Vin Max: 22 V, Vout: 3.3 V, Iout: 2 A, Amb. Temp: 30 °C.
- Feature Filters:** IC Package: All, On/Off Pin, Error Pin, Soft Start (checked), Ext Sync, Module, LDO, Adj Ipk Lim, Adj Frequency, Sync Switching, Controller, Integrated Switch (checked), Automotive.
- Filter Results:** Efficiency 77% (target 94%), Vout-pp 0.7mV (target 358.61mV), Footprint 245mm² x 929mm² (target 150kHz x 1000kHz), BOM Cost \$2 (target \$18), Crossover: 0kHz (target 82kHz), BOM Count 5 (target 34), Phase Margin: 0° (target 105°).
- Optimizer Metrics:** Footprint: 474, BOM Cost: \$3.24, Efficiency: 85%.

Part	Create	WEBENCH Tools	Schematic	BOM Images	Design Considerations	BOM Footprint (mm ²)	BOM Cost	Eff (%)	BOM Count	Freq (kHz)	Vout p-p (mV)	Xover Freq (kHz)	Phase Margin (deg)	Topology	LDO	Temp (deg)	Iout Max (A)
LM25576	Open Design				Fast Transient Response	47	\$3.24	85%	16	572	2.49	NA	NA	Buck	H	40°C	3.00
TP554340	Open Design				Step Down Converter with Eco Mode	329	\$3.63	86%	11	519	6.44	34	71	Buck	H	35°C	3.50

Hands-On Demo 6 - Optimization Tips and Tricks

WEBENCH Designer (Release Date: Wed Apr 17 14:11:12 2013, 520418 bytes) - Mozilla Firefox

My Design/Projects

Back New Solutions Visualization BOM Charts Schematic Optimizer Top Tools Size Terminal Build B Export Print Users Design Assistant

SUMMARY

Optimization Dial: Lowest BOM Cost, Medium Efficiency

Optimized: BOM Cost: \$3.28, Efficiency: 82%

Advanced Options: Soft Start Delay: 100ms, Rise/Fall Time: 100ns, Frequency: 50kHz, Current Sense: 100mA

Charts: Efficiency vs. Load Regulation

Schematic: Power supply circuit diagram

BOM of Materials: Table listing components like capacitors, diodes, and ICs with their quantities and costs.


Your Complete Design: Links for evaluation, assembly, and export.

You can use this dial to change your optimization parameters/priorities depending on your requirements


Click here to get WEBENCH to optimize your design

Hands-On Demo 6 - Optimization Tips and Tricks

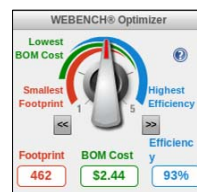
- WEBENCH calculates many different designs based on the selected part (LM2576) and displays the top 5 based on the position of the Optimizer dial
 - Dial set to 3 usually gives the best compromise between efficiency and size (Pls. Don't change from this position for this exercise)



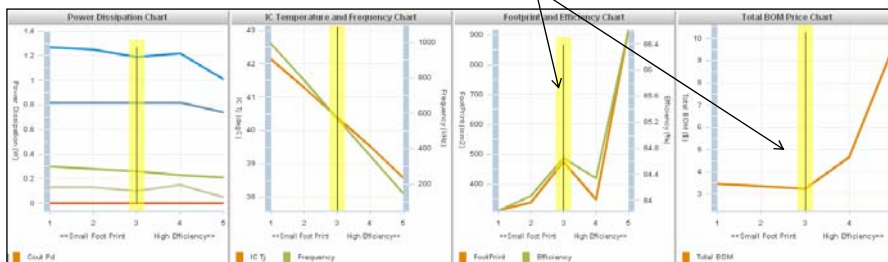The yellow line represents the position of the dial; we can see that by setting the dial to 5 we will get a significant improvement in efficiency but a much larger footprint



Optimizer Dial

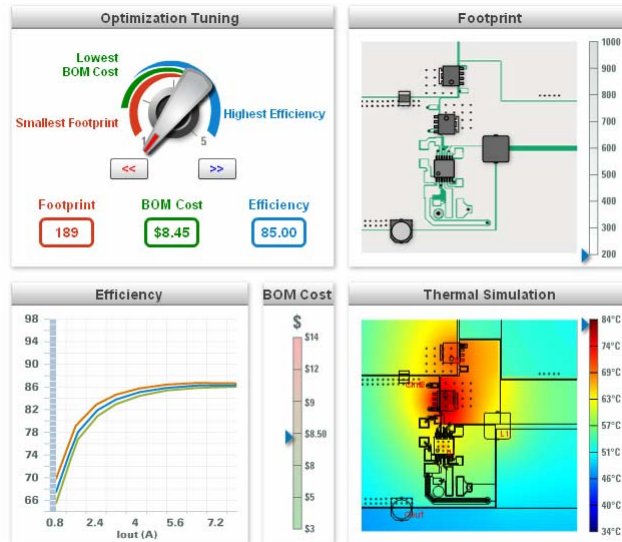

Images taken from www.ti.com
 © Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

Optimizer Dial

Optimization Setting	Frequency	Component Selection	Summary
1 – Smallest footprint	Highest	<ul style="list-style-type: none"> • Smallest footprint • Don't care about cost 	Smallest size but lowest efficiency
2 – Lowest cost	High	<ul style="list-style-type: none"> • Lowest cost 	High frequency means smaller / cheaper components
3 – Balanced	Medium	<ul style="list-style-type: none"> • In stock • Low cost 	Balanced approach using IC's middle frequency
4 – High efficiency	Low	<ul style="list-style-type: none"> • Low DCR, ESR, Vf • Low cost 	Higher efficiency, with low cost but larger parts
5 – Highest efficiency	Lowest	<ul style="list-style-type: none"> • Low DCR, ESR, Vf • Don't care about cost 	Highest efficiency but largest parts

Table taken from <http://www.ti.com/lscs/ti/analog/webench/optimizer.page>
 © Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

BIRICHA DIGITAL TEXAS INSTRUMENTS

Hands-On Demo 7 – Simulation Tool – Bode Plots

You can also do:
Load transients,
Line transients
Start up
& Steady state

By clicking on the schematic, you can change the simulation parameters

Click and pull down and right to zoom in
And left and up to zoom out

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 51

BIRICHA DIGITAL TEXAS INSTRUMENTS

Understanding Bode Plots

- Analog PSUs are (almost) always designed in the frequency domain
 - We modulate our PWM duty with a small sinusoid of a certain frequency (say 10 Hz) and we measure how the gain and phase of this sinusoid is modified by the time it goes through our plant (i.e. PSU)
 - We increase the frequency of our injected sinusoid and measure again, we repeat this for all frequencies of interest (say 1Hz to $\frac{1}{2} F_s$) and plot the Bode plot

In short we plot the “open loop” gain and phase of the PSU (i.e. its Bode plot) and design the compensator such that we get appropriate gain and phase margins

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 52

BIRICHA DIGITAL TEXAS INSTRUMENTS

Typical Voltage Mode Analog PSU

- Typically we tune the compensator by selecting the position of poles and zeros so as to achieve the desirable gain and phase margins
- To do this we need the Transfer Functions $H_c(s)$ & $H_p(s)$

Power Stage:
Buck, Boost, Flyback etc

Open loop gain = Gain of the compensator x Gain of the Boost Power stage

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 53

BIRICHA DIGITAL TEXAS INSTRUMENTS

Quick Review of Analog Transfer Functions H(s)


- Transfer function $H(s)$:
 - Is a mathematical representation of the relationship between the input and the output of our continuous time system
 - In our case $H_p(s)$ is our plant's transfer function (i.e. the power stage) and $H_c(s)$ is our compensator's transfer function
 - For both of the above, we are interested in the relationship between the output voltage and the input voltage:

$$H(s) = \frac{Y(s)}{X(s)} = \frac{V_{out}}{V_{in}}$$
 - It follows, therefore, that if we have the transfer function for our system, then for any given input we can calculate the output

$$Y(s) = X(s) H(s)$$
 - In our case, our inputs will be sinusoidal voltages of various frequencies so that we can plot the Bode plot

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 54

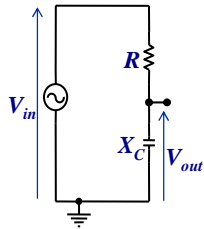Example: A Simple 1st Order Transfer Function



$$s = \text{Laplace Operator} = j\omega = j2\pi f$$

$$V_{out} = V_{in} \frac{X_c}{(X_c + R)} \quad \text{Where : } X_c = \frac{1}{j\omega C} = \frac{1}{sC}$$

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{\frac{1}{sC}}{\left(\frac{1}{sC} + R\right)}$$

$$H(s) = \frac{1}{(1 + sRC)}$$

Observations:

- Laplace is only a “mathematical trick” used to help us analyze circuits
- s is a function of frequency ω in rad/s or $2\pi f$ in Hz
- As we vary s from $-\infty \rightarrow \infty$ the “numerical value” of $H(s)$ varies
- When $s = -1/RC$ “Numerical Value” of $H(s)$ will become ∞ . This value of s is called the “POLE” of our system
 - IMPORTANT: this does not necessarily mean that the output of our system becomes infinite. This only means that the “numerical value” of our transfer function will become infinite
 - To find the amplitude of the output of our system we need to calculate our “gain”. We will do this next
 - For a stable system all poles must always have a negative value i.e. be on the left hand side of the s-plane

Calculating Gain and Phase from H(s)

• Transfer function $\rightarrow H(s) = \frac{1}{(1 + j 2\pi f RC)}$



• Gain: $\sqrt{\text{Re}^2 + \text{Im}^2} \rightarrow |H(s)| = \frac{1}{\sqrt{(1^2 + (2\pi f RC)^2)}}$

• Phase:

$$\phi = \tan^{-1}\left(\frac{\text{Im}}{\text{Re}}\right) \quad \&$$

$$\tan^{-1}\left(\frac{Z_1}{Z_2}\right) = \tan^{-1}(Z_1) - \tan^{-1}(Z_2) \rightarrow \tan^{-1}\left(\frac{0}{1}\right) - \tan^{-1}\left(\frac{2\pi f RC}{1}\right) = -\tan^{-1}(2\pi f RC)$$

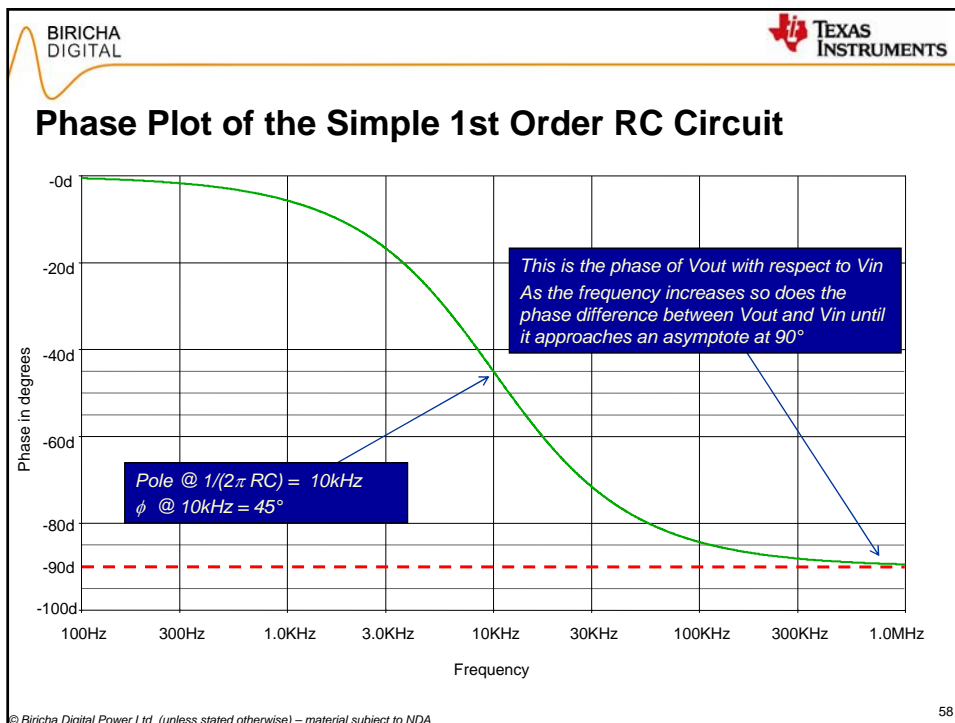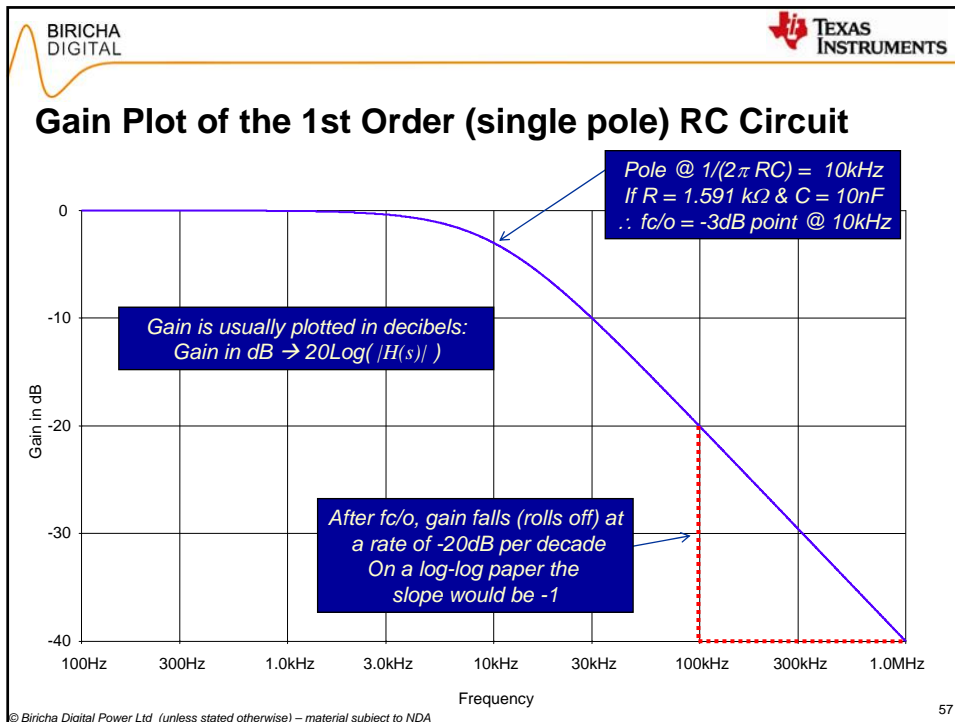- We can now plot Gain and Phase with respect to the frequency



Poles and Zeros

- The circuit in the previous slide had a single pole
 - Where “pole” was defined as the value of s where the **denominator** of $H(s) \rightarrow 0$
 - This would lead to the numerical value of $H(s) \rightarrow \infty$
 - Every pole in our system (located at a negative value of s) causes the gain to fall (roll-off) at a rate of -20dB per decade and
 - Introduces a phase lag of 90 degree
- If we have a transfer function such that its “**numerator**” can become 0 for a certain value of s then we have a “**zero**” on our transfer function:

$$H(s) = \frac{(s + \alpha)}{(s + \beta)}$$

← Zero @ $-\alpha$ &
 ← Pole @ $-\beta$

- Every zero in our system (located at a negative value of s) causes the gain to rise at a rate of 20dB per decade and
- Introduces a phase lead of 90°

H(s) of a 2nd Order System

- For BDP-106 @ full load:
 - $L = 22\mu\text{H}$ $C = 440\mu\text{F}$ & $R = 1.8\Omega$
 - ESR is assumed to be 0 for now!
- Transfer Function $H_p(s)$:


$$H_p(s) = \frac{1}{s^2 LC + s\left(\frac{L}{R}\right) + 1}$$



- The denominator of $H_p(s)$ is a 2nd Order Polynomial

- It has 2 poles @

$$\frac{1}{2\pi\sqrt{LC}}$$

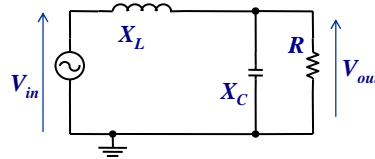- This is the resonance frequency F_r of our system
- At resonance we “may” see a bump on our gain plot. The size of the bump is dependant on the load resistor (as well as other things)
- We have two poles so we call this a 2nd order system



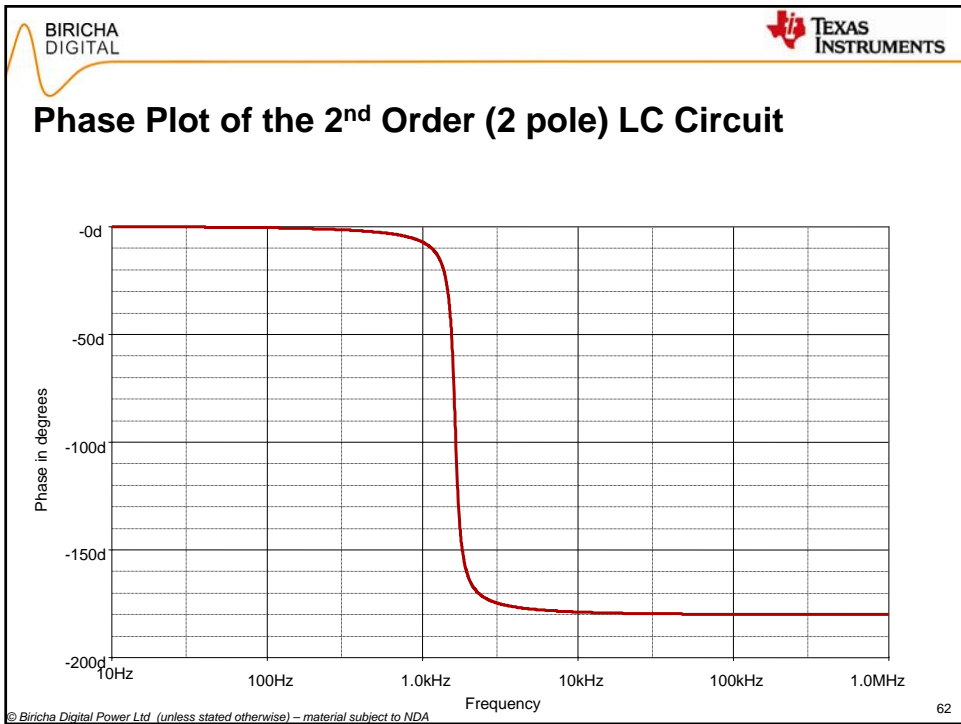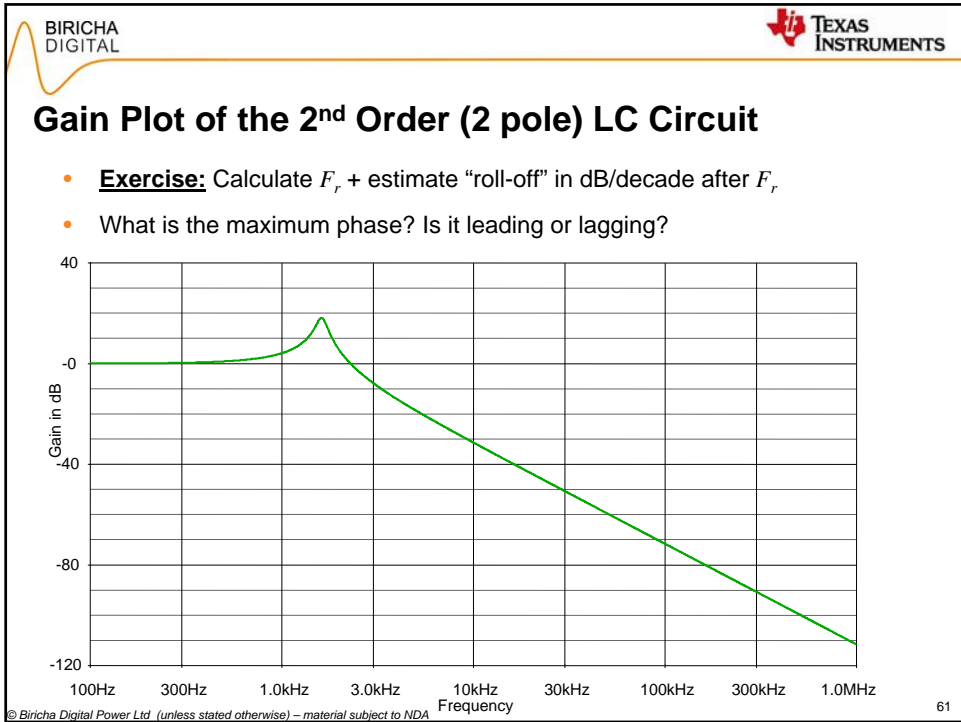

Gain Margin, Phase Margin and Crossover Frequency


- We need to define a few variables to allow us to design a stable power supply

Gain Margin (GM) = How much the gain is below 0 dB when Phase = 180°

DC Gain = say 21dB

Crossover frequency F_x
i.e. frequency at which gain crosses 0 dB \approx 6kHz
Important:
Slope @ F_x = -40 dB/decade

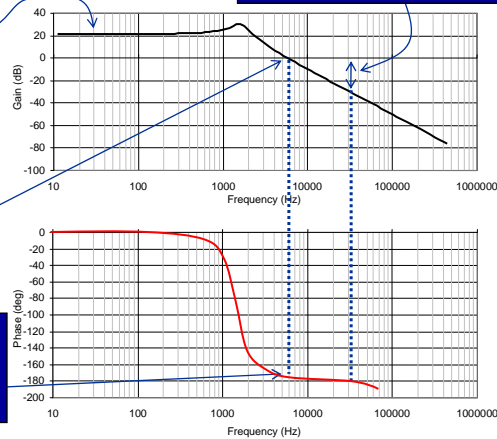
Phase Margin (ϕ_M)
i.e. Phase left before reaching -180° when the gain = 0 dB
In this case \approx 10°




Power Supply Stability Criterion

- When considering the **Open loop** frequency response:
 - 1 - At crossover frequency (F_x), the Phase Margin (ϕ_M) must be more than 40° to 45°
 - $\phi_M \rightarrow$ the amount by which the phase shift is less than 180° at F_x
 - The lower the phase margin, the faster the transient response (in time domain) but the higher the risk of instability
 - 2 - At F_x , the slope of the open loop gain plot should be no more than -20 dB/decade
 - PSU jargon
 - 20 dB/decade \rightarrow -1 slope
 - 40 dB/decade \rightarrow -2 slope
 - 3 - Gain Margin G_M should be at least 10 dB
 - $G_M \rightarrow$ The amount by which the gain is lower than 0 dB when the phase = 180°

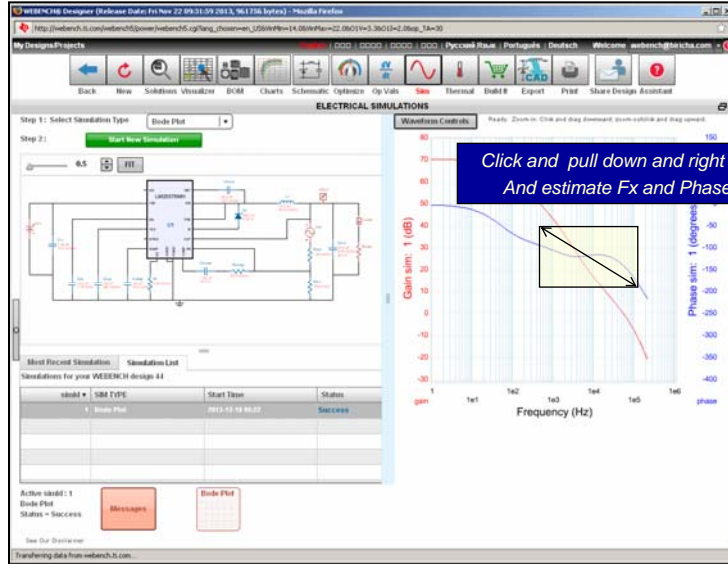Hands-On Demo 7 – Simulation Tool – Bode Plots



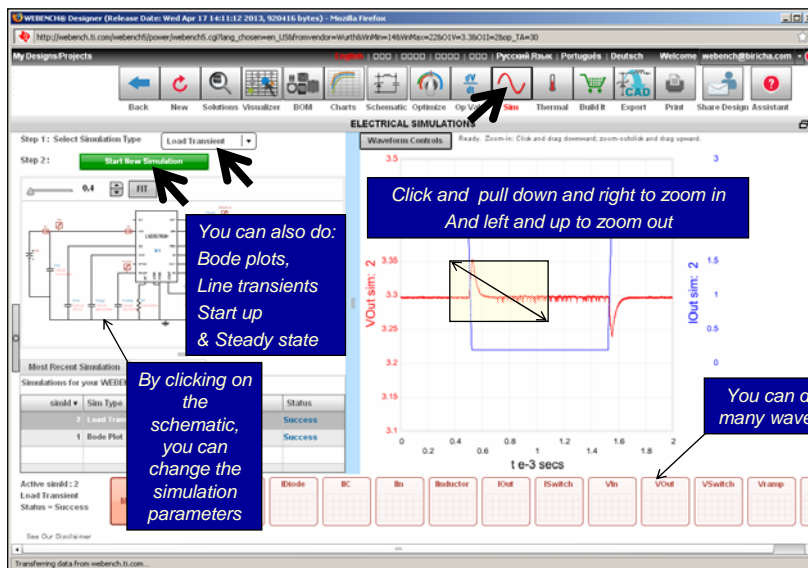Hands-On Demo 7 – Simulation Tool – Load Transients



Thermal Simulation with WebTHERM™


- WebTHERM™ online tool simulates the thermal behavior of an electronic printed circuit board
 - Using validated thermal models for the components and the reference PCB
 - The user defines the environment, air flow, copper thickness, presence of fan/heat sink, etc
 - Takes into account the thermal interaction of different components adjacent to each other
 - The WebTHERM tools helps the user identify heat problems on the printed circuit board
 - i.e. the board goes into production.
 - A simulation typically takes two to three minutes to complete,
 - After the simulation is complete, the user can view the result, a full colour plot of the temperature across the board
 - The temperature of each component is also listed in an accompanying table
 - If desired, the user can adjust the parameters and resubmit the job for simulation

Taken from: www.ti.com/lscs/ti/analog/webench/thermal-simulation.page

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

67

Hands-On Demo 8 – Thermal Simulation

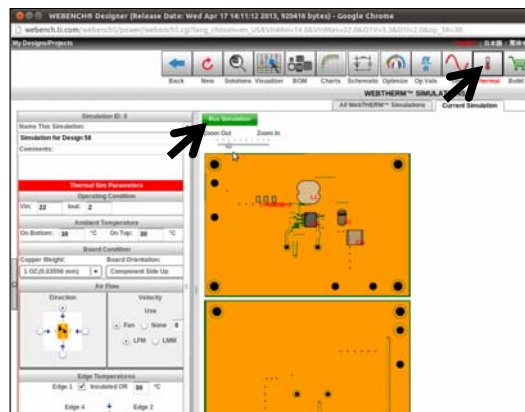

WEBTHERM™ SIMULATIONS						
All WebTHERM™ Simulations Current Simulation						
ID	Name	Status	Submitted Date	Run Date	Comments	Open
1	Simulation for Design 57	Completed	Jun 09, 2013 02:49 PM	Jun 09, 2013 02:49 PM		View

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA

68

Hands-On Demo 8 – Thermal Simulation

Simulation ID: 1

Name This Simulation: Simulation for Design 58

Comments:

Thermal Site Parameters

Operating Condition

Vin: 22 Invt: 2

Ambient Temperature

On Bottom: 30 °C On Top: 30 °C

Board Condition

Copper Weight: Board Orientation: Component Side Up

Direction: Air Flow: Velocity: Use: Fall, Rise, None

Edge Temperatures

Edge 1: Insulated OR 100 °C

Edge 2: Insulated OR 100 °C

Edge 3: Insulated OR 100 °C

Edge 4: Insulated OR 100 °C

Layer	Max T	PDiss.	Manufacture	Part Number
PCB - Top	72°C			
IC - D16	67°C	1.76 W	Texas Instruments	LM2596SM-ADJ300
L1	59°C	0.2 W	Bourns	SRM040-SR2V
R11	72°C	0.03 W	Diodes Inc.	B348A-SLF
Cool	57°C	1.13e-4 W	Multifuse	GMF0205040220MEX
Clk	57°C	1.06e-2 W	TDK	CST1607R010088
PCB - Bottom	49°C			

Hands-On Demo 8 – Thermal Simulation

Simulation ID: 1

Name This Simulation: Simulation for Design 58

Comments:

Thermal Site Parameters

Operating Condition

Vin: 22 Invt: 2

Ambient Temperature

On Bottom: 30 °C On Top: 30 °C

Board Condition

Copper Weight: Board Orientation: Component Side Up

Direction: Air Flow: Velocity: Use: Fall, Rise, None

Edge Temperatures

Edge 1: Insulated OR 100 °C

Edge 2: Insulated OR 100 °C

Edge 3: Insulated OR 100 °C

Edge 4: Insulated OR 100 °C

Layer	Max T	PDiss.	Manufacture	Part Number
PCB - Top	72°C			
IC - D16	67°C	1.76 W	Texas Instruments	LM2596SM-ADJ300
L1	59°C	0.2 W	Bourns	SRM040-SR2V
R11	72°C	0.03 W	Diodes Inc.	B348A-SLF
Cool	57°C	1.13e-4 W	Multifuse	GMF0205040220MEX
Clk	57°C	1.06e-2 W	TDK	CST1607R010088
PCB - Bottom	49°C			

BIRCHA DIGITAL TEXAS INSTRUMENTS

Hands-On Demo 9 – CAD Export

- Example export to Design Spark

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 71

BIRCHA DIGITAL TEXAS INSTRUMENTS

Hands-On Demo 10 – Share you Design

- Share this design

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 72

BIRICHA DIGITAL TEXAS INSTRUMENTS

Advanced Optimization with Charting Tools

- You can further optimize your design using the “Advanced Charting Tool”
 - In its most basic form it allows you to graphically select a design that you want open based on TI part number
 - If used before opening a design, it is simply a graphical alternative to using the sliders that we have used so far
 - IMPORTANT:** However *after* opening a design, it can be used as a very powerful tool to optimize and select each individual component
 - We will now use this tool to select an alternative inductor for our design

If you hover your mouse over any of the circles you will see the details of the design

Part: LM25011
 BasePN: LM25011
 Topology: Buck
 Efficiency: 79%
 Footprint: 310mm²
 Frequency: 569kHz
 Vout p-p: 9.21mV
 BOM Cost: \$1.61
 BOM Count 14

© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 73

BIRICHA DIGITAL TEXAS INSTRUMENTS

Hands-On Demo 11 – Alternative Component Selection

Back New Solutions Visualizer **BOM** Schematic Optimize Op Vals Sim Thermal BOM Export Print Share Design Assistant

BILL OF MATERIALS


Export to: BOM Cost: \$3.24 Footprint is component footprint plus trim per side.

Part	Manufacturer	Part Number	Quantity	Price	Attributes	Footprint	Top View	Edit
Cboot	Kemet	C0005C223K3RAC1U	1	\$6.01	Cap=22uF, ESR=4.1250ohm, VDC=50V	13		Select Alternate Part
Chyp	AVX	08053C104KAT2A	1	\$6.01	Cap=100nF, ESR=0.280ohm, VDC=25V	13		Select Alternate Part
Ccomp	MuRata	GRM216R71E152KA0	1	\$6.01	Cap=1.5uF, ESR=40ohm, VDC=25V	13		Select Alternate Part
Cin	TDK	C3216X7R1H105K	1	\$6.04	Cap=1uF, ESR=0.010ohm, VDC=50V	19		Select Alternate Part
Coat	MuRata	GRM216R6J226ME3	3	\$6.05	Cap=22uF, ESR=30ohm, VDC=6.3V	13		Select Alternate Part
Cramp	Kemet	C0805C101J5GAC1U	1	\$6.01	Cap=100pF, ESR=0.0740ohm, VDC=50V	13		Select Alternate Part
Cos	MuRata	GRM155R71E822KA0	1	\$6.01	Cap=8.2uF, ESR=40ohm, VDC=25V	8		Select Alternate Part
D1	Diodes Inc.	B340A-13-F	1	\$6.11	VF@Io=0.5V, Io=3A, VR98=80V	27		Select Alternate Part
L1	Wurth Elektronik eS	7447714100	1	\$6.05	L=1uH, DCR=8.0730ohm, IBC=3.2A	196		Select Alternate Part
Rcomp	Vishay Dale	CRCW080520R0FREA	1	\$6.01	Resistance=20kOhm, Tolerance=1%, Power=0.125W	13		Select Alternate Part
Rth1	Vishay Dale	CRCW08051R00FREA	1	\$6.01	Resistance=1000Ohm, Tolerance=1%, Power=0.125W	13		Select Alternate Part
Rth2	Vishay Dale	CRCW08051R00FREA	1	\$6.01	Resistance=1.09kOhm, Tolerance=1%, Power=0.125W	13		Select Alternate Part
Rt	Vishay Dale	CRCW08058K66FREA	1	\$6.01	Resistance=8.66kOhm, Tolerance=1%, Power=0.125W	13		Select Alternate Part
UI	Texas Instruments	LM25750B1NOPB	1	\$2.00		71		Select Alternate Part


© Biricha Digital Power Ltd (unless stated otherwise) – material subject to NDA 74

Hands-On Demo 11 – Alternative Component Selection

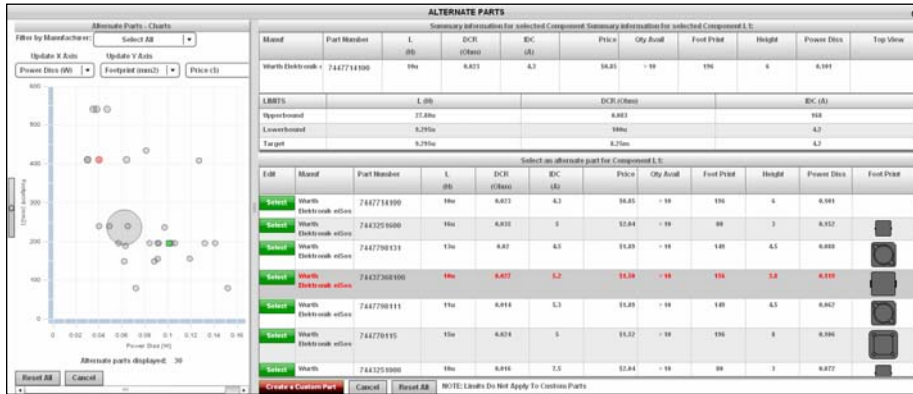- Using the advanced charting tools we can select a more suitable inductor for our power supply



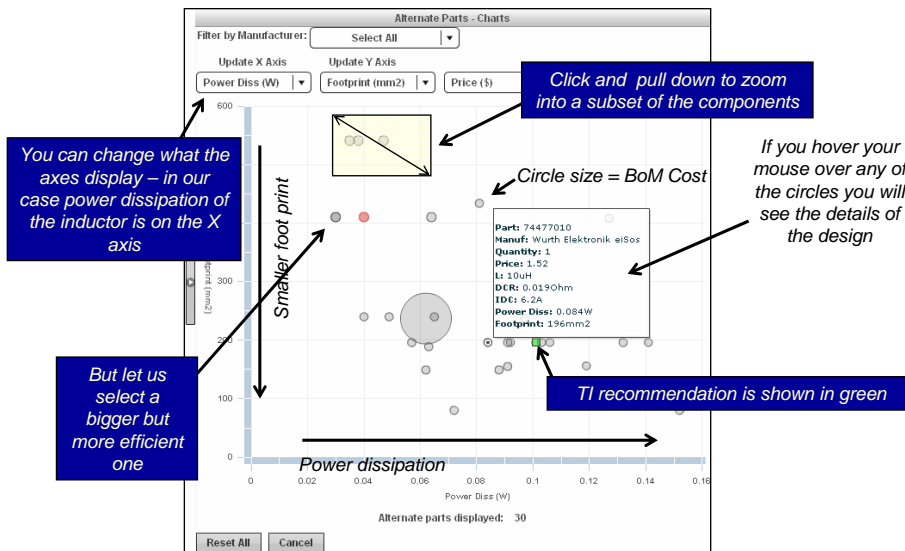Hands-On Demo 11 – Alternative Component Selection



Hands-On Demo 11 – Alternative Component Selection

- Note that a new more efficient but larger component has now been selected
 - We can now run our simulation and analysis based on this new component
 - When we are happy we can finalize our design and print the final report

Manuf	Part Number	L (in)	DCR (mOhm)	EC (in)	Price	Qty Avail	Foot Print	Height	Power Diss	Top View
Würth Elektronik	7447714100	9in	8.075	4.3	10.00	> 10	9in	6	6.500	

Manuf	Part Number	L (in)	DCR (mOhm)	EC (in)	Price	Qty Avail	Foot Print	Height	Power Diss	Foot Print
Würth Elektronik	7443631000	10in	7.500	8	14.75	> 10	14in	14	6.833	

Hands-On Demo 12 - Automatic Report Generation



Q	Qty	Part Number	Description	Value	Unit	Price	Foot Print	Height	Power Diss
1	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000
2	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000
3	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000
4	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000
5	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000
6	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000
7	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000
8	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000
9	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000
10	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000
11	1	LM5022H	DCM-REG-1.5V	1.5V	1	10.00	10in	10	10.000

Concluding Remarks and Summary

- WEBENCH is a very powerful tool to assist you in your PoL PSU Designs
 - Based on your specifications, it automatically designs 100+ of PSUs
- We've learned how to:
 - Filter down our designs and select the most appropriate part based on your efficiency/footprint/cost requirements
 - Optimize our design and carry out electrical and thermal simulations
 - Change components within your BoM
 - Create schematics and import to CAD packages
 - Print the final report and order BoM including the PCB within a few clicks
- In this seminar we only covered Power Designer; there is also:
 - WEBENCH Power Architect
 - WEBENCH LED Designer
 - WEBENCH Sensor Designer
 - WEBENCH Active Filter Designer
 - WEBENCH Amplifier Designer
 - WEBENCH EasyPLL



www.ti.com/webench

Please complete our feedback form on:
www.surveymonkey.com/s/webench-ch

End of Seminar
Thank you for attending