

week 10


AC circuits

Applications

(leave for next week)


LC circuit

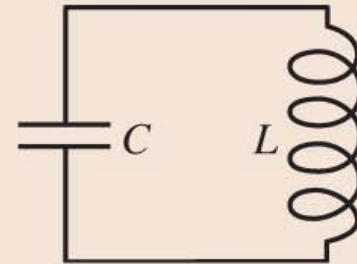
Oscillates at $\omega = \sqrt{\frac{1}{LC}}$



LR circuit

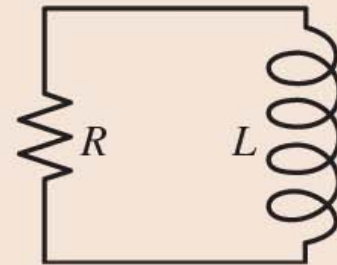Exponential change with $\tau = \frac{L}{R}$




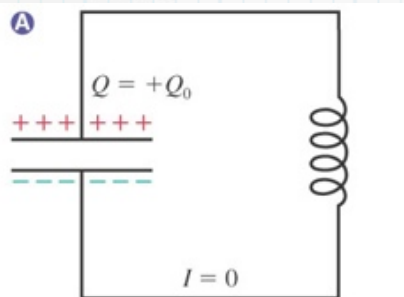

Maximum capacitor charge is like a fully stretched spring.


The current continues until the initial capacitor charge is restored.

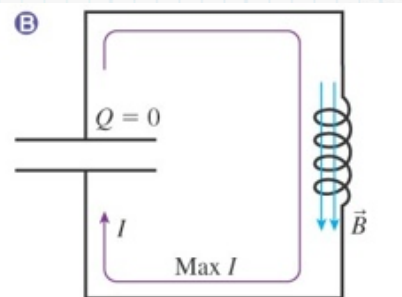The capacitor discharges until the current is a maximum.




Maximum current is like the block having maximum speed.

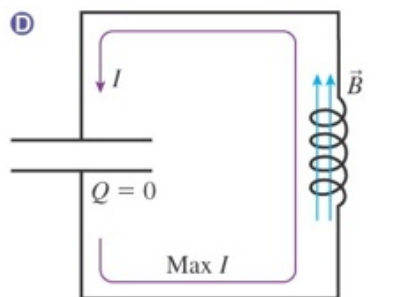The current can't stop. It continues until the capacitor is fully recharged with the opposite polarization.



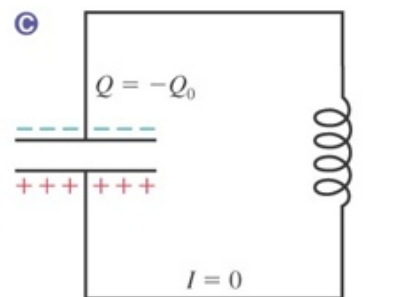
Now the discharge goes in the opposite direction.



An inductor (inductance L) and a resistor (resistance R) are connected to a source of emf as shown. When switch S is closed, a current begins to flow and grows until it reaches a final value.

The *final value of the current*

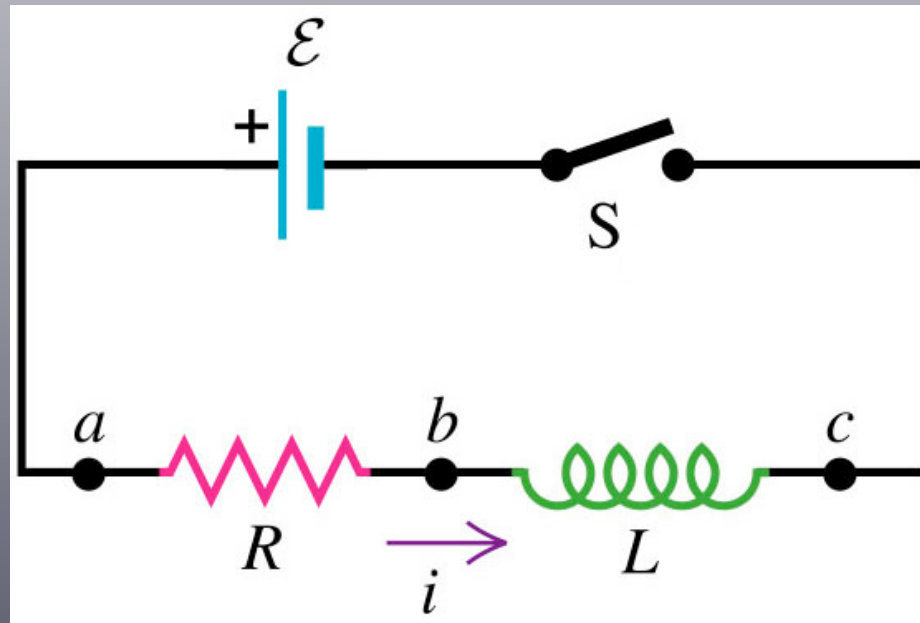
1. is directly proportional to both R and L
2. is directly proportional to R and inversely proportional to L
3. is inversely proportional to R and directly proportional to L
4. is inversely proportional to both R and L
5. is independent of L



An inductor (inductance L) and a resistor (resistance R) are connected to a source of emf as shown. When switch S is closed, a current begins to flow and grows until it reaches a final value.

The *final value of the current*

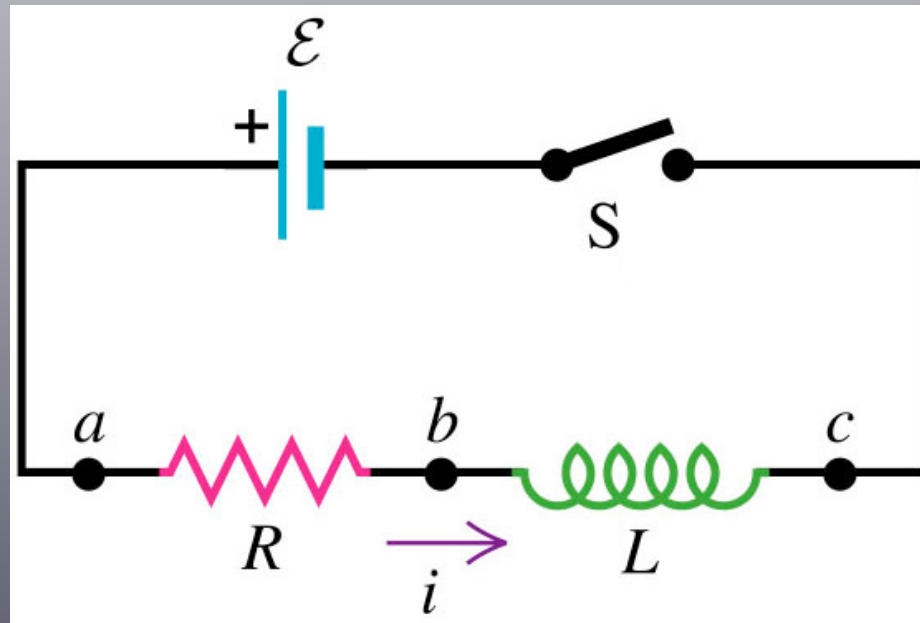1. is directly proportional to both R and L
2. is directly proportional to R and inversely proportional to L
3. is inversely proportional to R and directly proportional to L
4. is inversely proportional to both R and L
5. is independent of L



Rank in order, from largest to smallest, the time constants τ_a , τ_b , and τ_c of these three circuits.




1. $\tau_a > \tau_b > \tau_c$

2. $\tau_b > \tau_a > \tau_c$

3. $\tau_b > \tau_c > \tau_a$

4. $\tau_c > \tau_a > \tau_b$

5. $\tau_c > \tau_b > \tau_a$

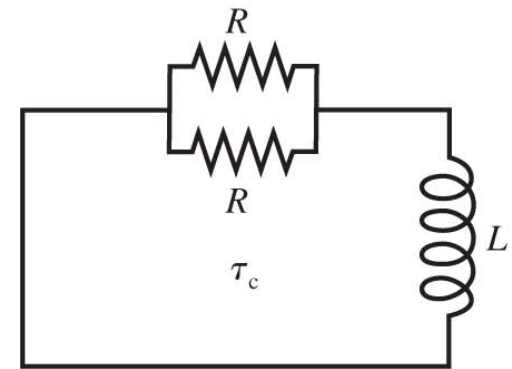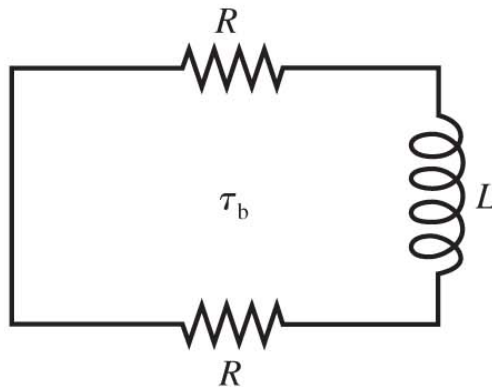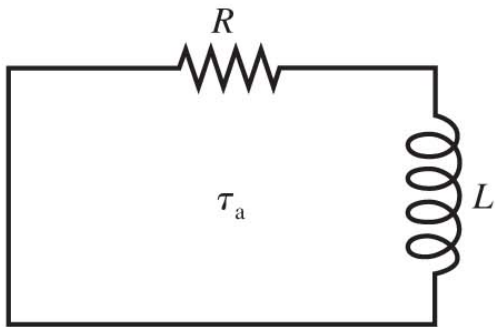

Rank in order, from largest to smallest, the time constants τ_a , τ_b , and τ_c of these three circuits.




1. $\tau_a > \tau_b > \tau_c$

2. $\tau_b > \tau_a > \tau_c$

3. $\tau_b > \tau_c > \tau_a$

4. $\tau_c > \tau_a > \tau_b$

5. $\tau_c > \tau_b > \tau_a$

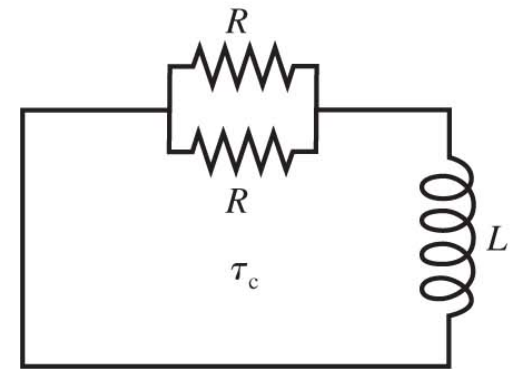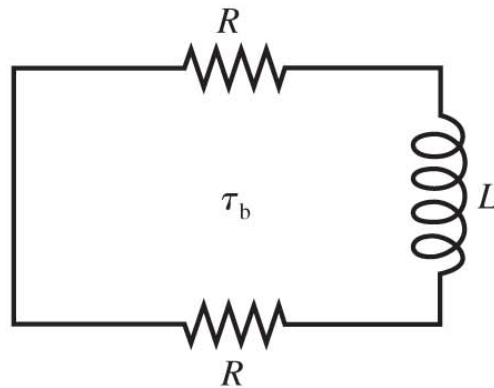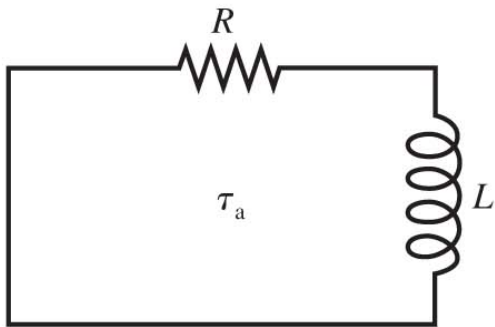


The switch in the figure has been open for a long time. It is closed at $t = 0$ s.

(a) What is the current through the battery immediately after the switch is closed?

(b) What is the current through the battery after the switch has been closed for a long time?

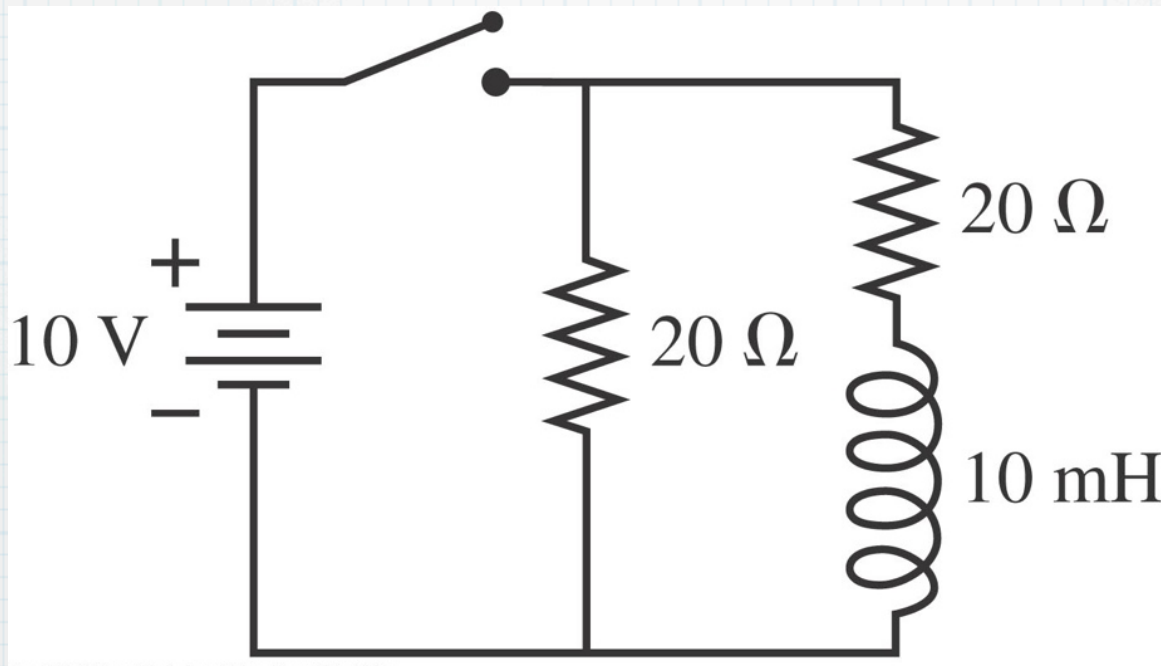(c) What is meant by a "long time" in (b)?




Ans: (a) 0.50 A (b) 1.0 A (c) a time much longer than 0.5 ms

An inductor (inductance L) and a capacitor (capacitance C) are connected as shown.

If the values of both L and C are doubled, what happens to the *time* required for the capacitor charge to oscillate through a complete cycle?

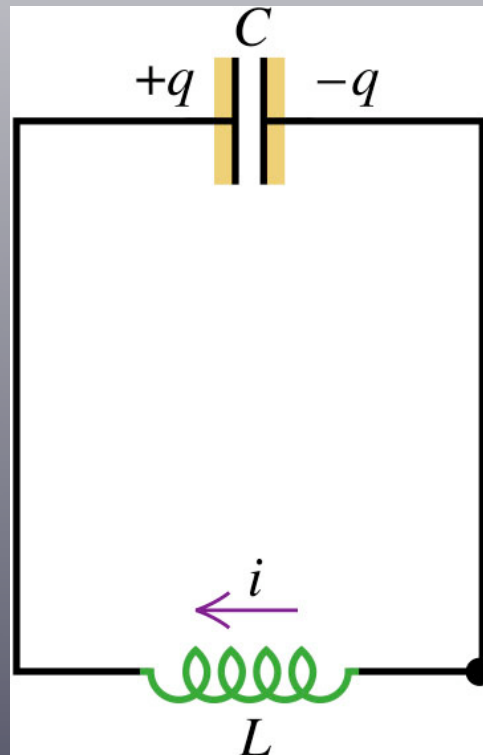1. it becomes 4 times longer
2. it becomes twice as long
3. it is unchanged
4. it becomes 1/2 as long
5. it becomes 1/4 as long




An inductor (inductance L) and a capacitor (capacitance C) are connected as shown.

If the values of both L and C are doubled, what happens to the *time* required for the capacitor charge to oscillate through a complete cycle?

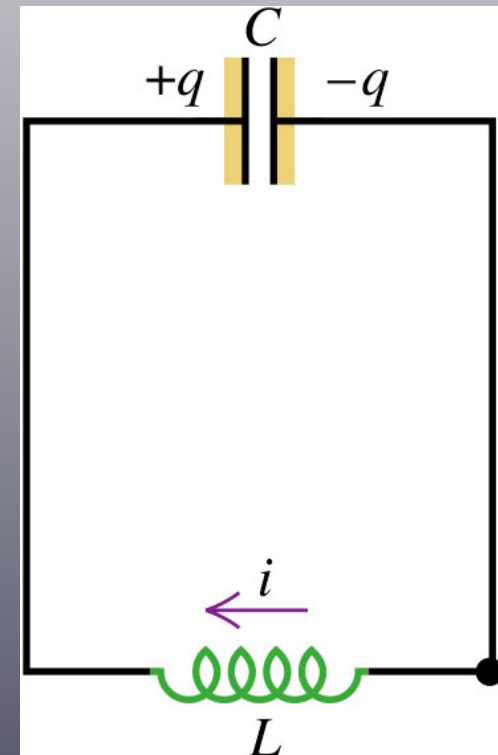1. it becomes 4 times longer
2. it becomes twice as long
3. it is unchanged
4. it becomes 1/2 as long
5. it becomes 1/4 as long

Recall the angular frequency is $\omega = \sqrt{1/LC}$.
The period T satisfies $\omega T = 2\pi$, so
 $T = 2\pi \sqrt{LC}$.


Therefore, doubling both L and C increases T by the square root of 2^2



34-76. The switch in the figure has been in position 1 for a long time. It is changed to position 2 at $t=0$ s.

(a) What is the maximum current through the inductor?

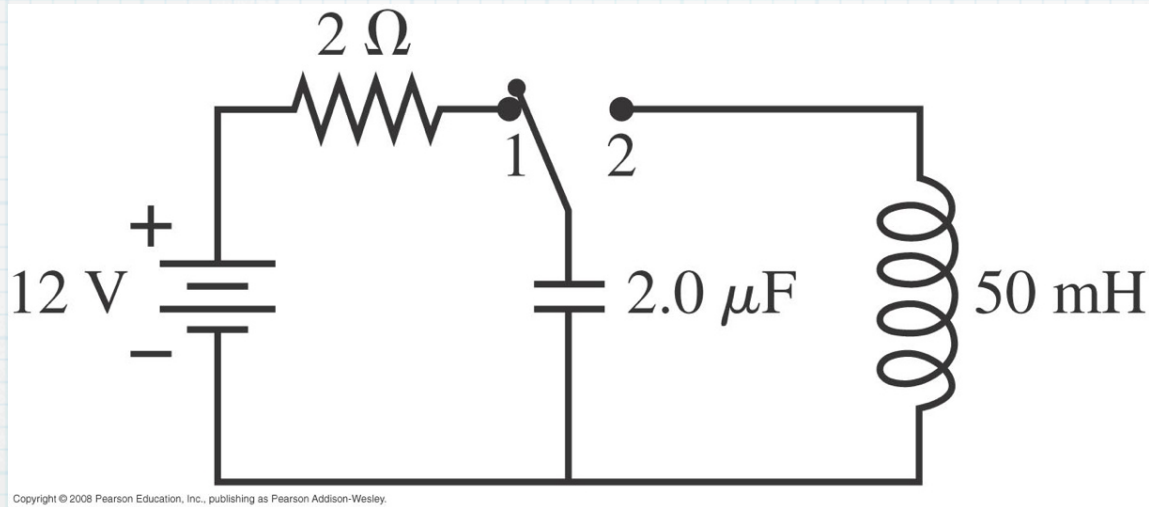(b) What is the first time at which the current is maximum?



Ans: (a) 76 mA; (b) $T=2.0$ ms, $t_{\max}=T/4=0.50$ ms


Important Concepts

AC circuits are driven by an emf

$$\mathcal{E} = \mathcal{E}_0 \cos \omega t$$

that oscillates with angular frequency $\omega = 2\pi f$.

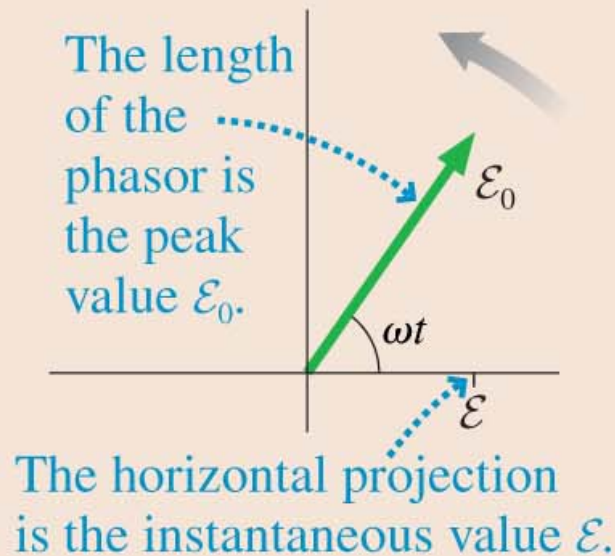Phasors can be used to represent the oscillating emf, current, and voltage.



Important Concepts

Basic circuit elements

Element	i and v	Resistance/ reactance	I and V	Power
Resistor	In phase	R is fixed	$V = IR$	$V_{\text{rms}} I_{\text{rms}}$
Capacitor	i leads v by 90°	$X_C = 1/\omega C$	$V = IX_C$	0
Inductor	i lags v by 90°	$X_L = \omega L$	$V = IX_L$	0

For many purposes, especially calculating power, the **root-mean-square** (rms) quantities


$$V_{\text{rms}} = V/\sqrt{2} \quad I_{\text{rms}} = I/\sqrt{2} \quad \mathcal{E}_{\text{rms}} = \mathcal{E}_0/\sqrt{2}$$

are equivalent to the corresponding DC quantities.

Key Skills

Phasor diagrams

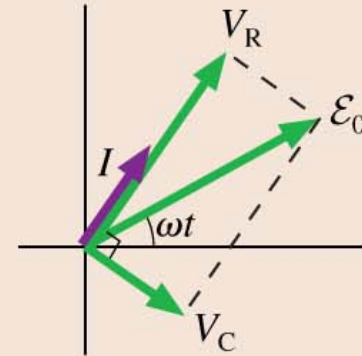- Start with a phasor (v or i) common to two or more circuit elements.
- The sum of instantaneous quantities is vector addition.
- Use the Pythagorean theorem to relate peak quantities.



For an RC circuit, shown here,

$$v_R + v_C = \mathcal{E}$$

$$V_R^2 + V_C^2 = \mathcal{E}_0^2$$

Key Skills

Kirchhoff's laws

Loop law The sum of the potential differences around a loop is zero.


Junction law The sum of currents entering a junction equals the sum leaving the junction.

Instantaneous and peak quantities

Instantaneous quantities v and i generally obey different relationships than peak quantities V and I .

Applications


RC filter circuits

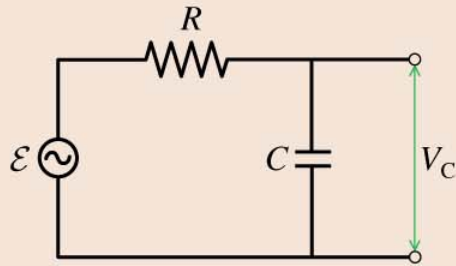

$$V_C = \mathcal{E}_0 X_C / \sqrt{R^2 + X_C^2}$$

$$V_C \rightarrow \mathcal{E}_0 \text{ as } \omega \rightarrow 0$$

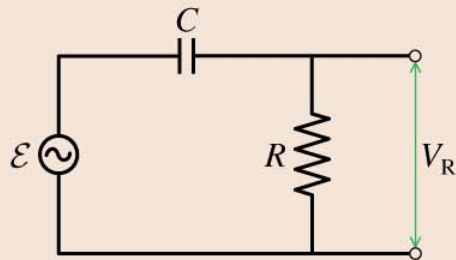A **low-pass filter** transmits low frequencies and blocks high frequencies.




$$V_R = \mathcal{E}_0 R / \sqrt{R^2 + X_C^2}$$

$$V_R \rightarrow \mathcal{E}_0 \text{ as } \omega \rightarrow \infty$$

A **high-pass filter** transmits high frequencies and blocks low frequencies.

Applications

Series RLC circuits

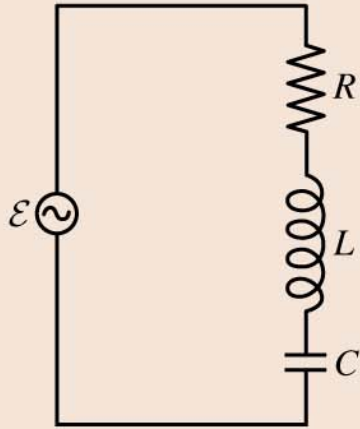

$I = \mathcal{E}_0/Z$ where Z is the **impedance**

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$V_R = IR \quad V_L = IX_L \quad V_C = IX_C$$


When $\omega = \omega_0 = 1/\sqrt{LC}$ (the **resonance frequency**), the current in the circuit is a maximum $I_{\max} = \mathcal{E}_0/R$.

In general, the current i lags behind \mathcal{E} by the **phase angle** $\phi = \tan^{-1}((X_L - X_C)/R)$.


The power supplied by the emf is $P_{\text{source}} = I_{\text{rms}}\mathcal{E}_{\text{rms}}\cos\phi$, where $\cos\phi$ is called the **power factor**.

The power lost in the resistor is $P_R = I_{\text{rms}}V_{\text{rms}} = (I_{\text{rms}})^2R$.


Resonance

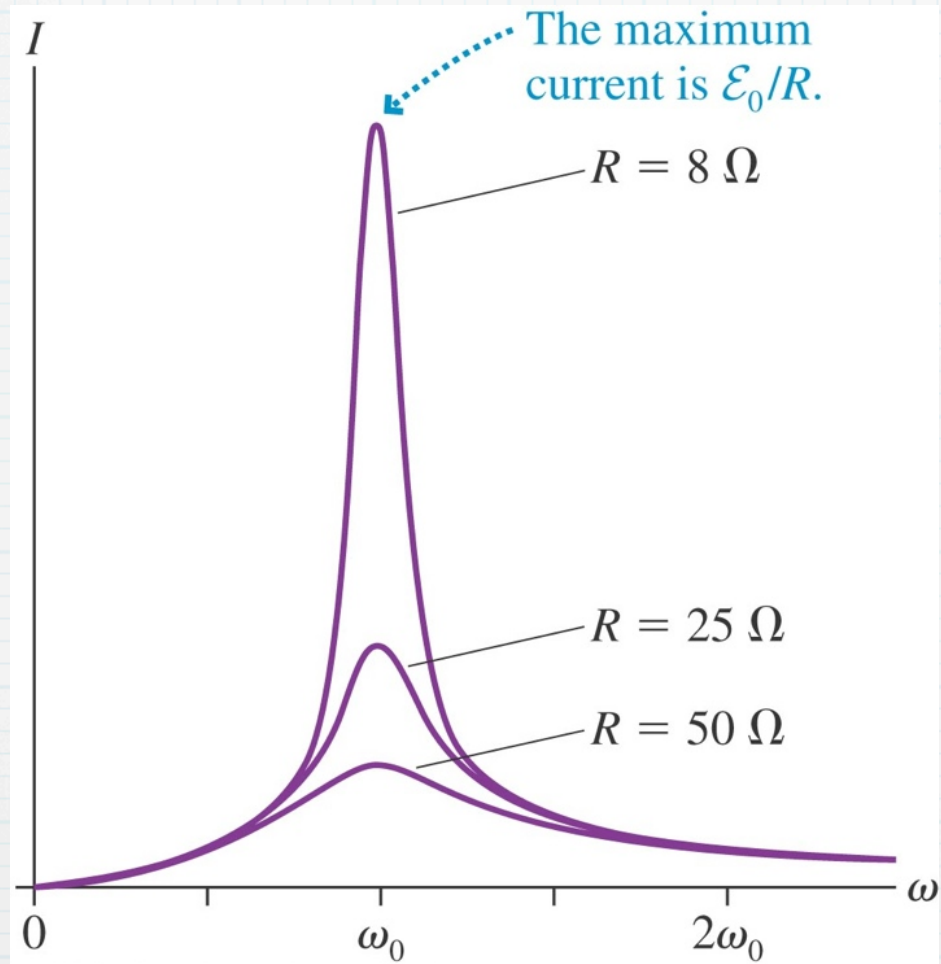

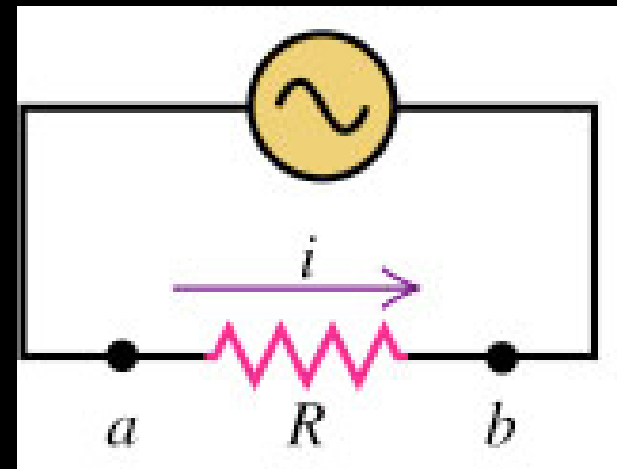
A resistor is connected across an ac source as shown. Which graph correctly shows the instantaneous current through the resistor and the instantaneous voltage $v = v_a - v_b$ across the resistor?



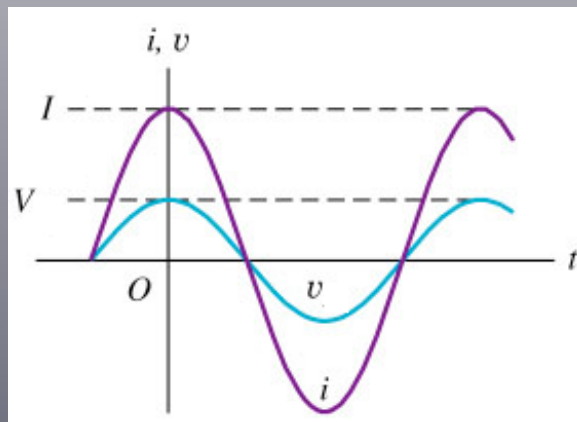
(current “ i ” in purple, voltage “ v ” in blue)



1.

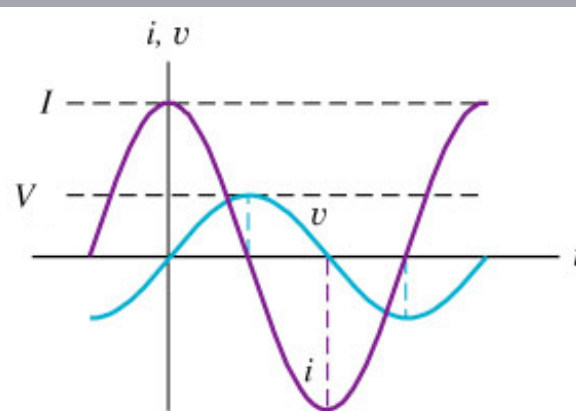


2.

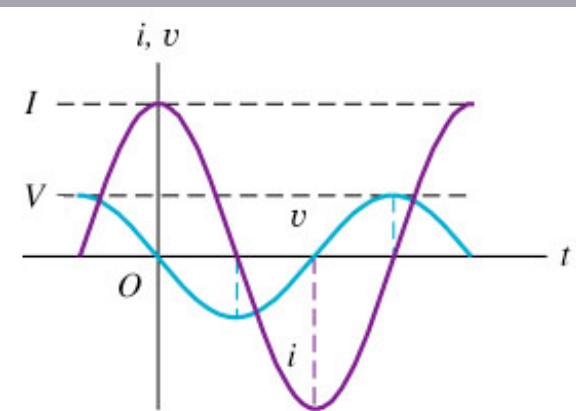


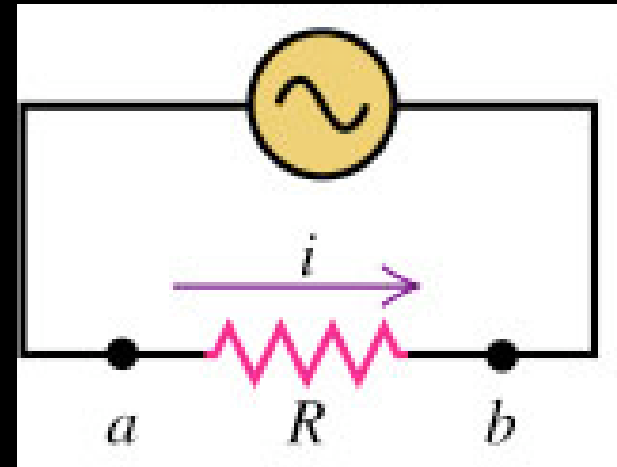3.


A resistor is connected across an ac source as shown. Which graph correctly shows the instantaneous current through the resistor and the instantaneous voltage $v = v_a - v_b$ across the resistor?



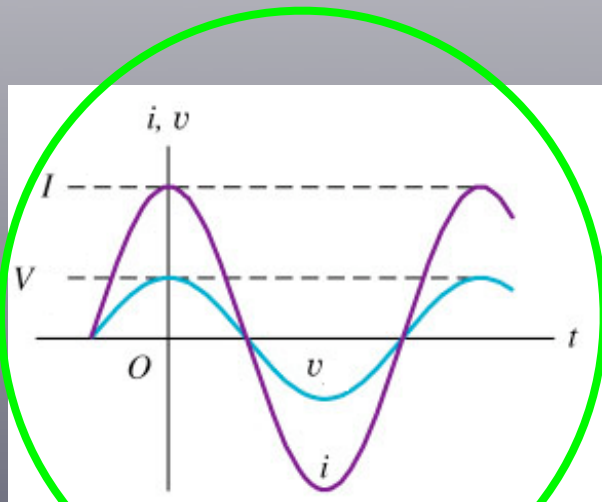
(current “ i ” in purple, voltage “ v ” in blue)



1.

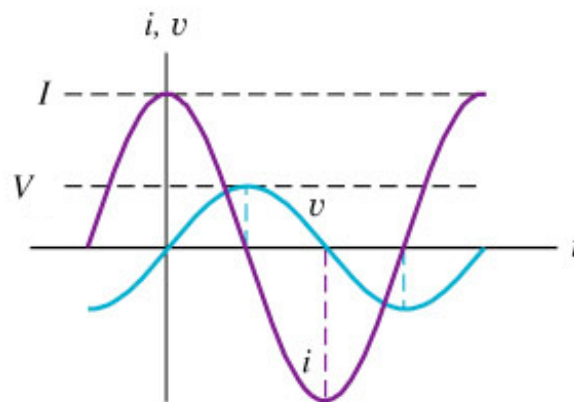


2.

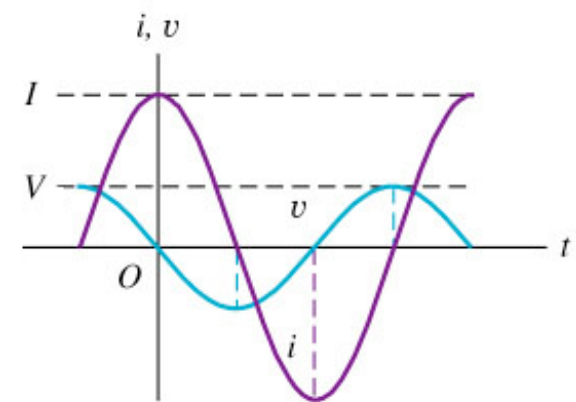


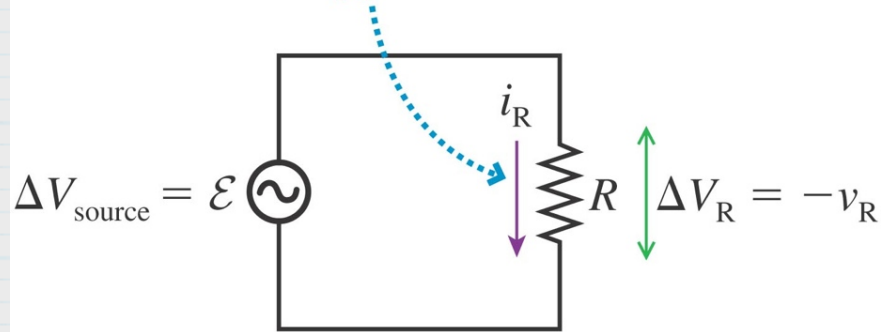3.


This is the current direction when $\mathcal{E} > 0$. A half cycle later it will be in the opposite direction.



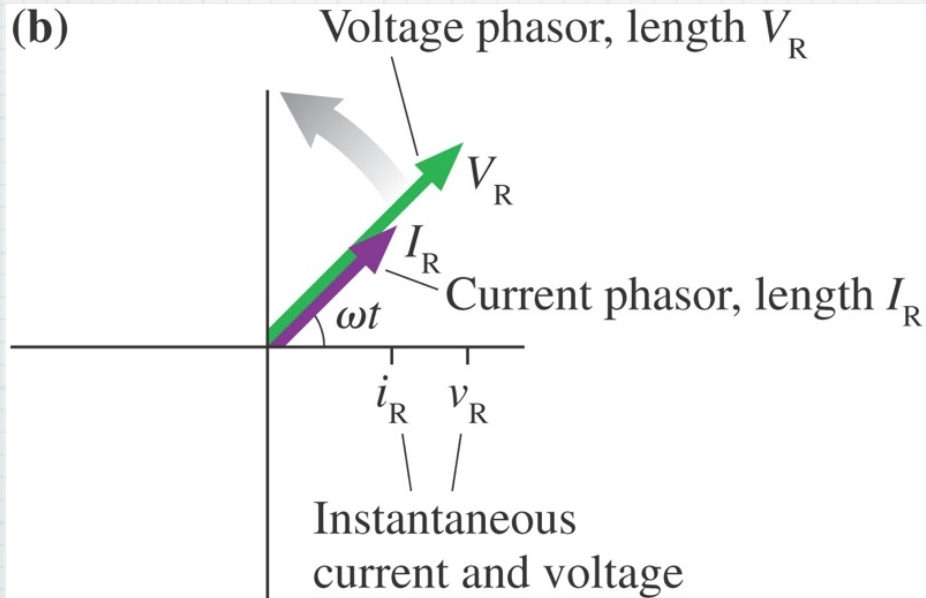Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley




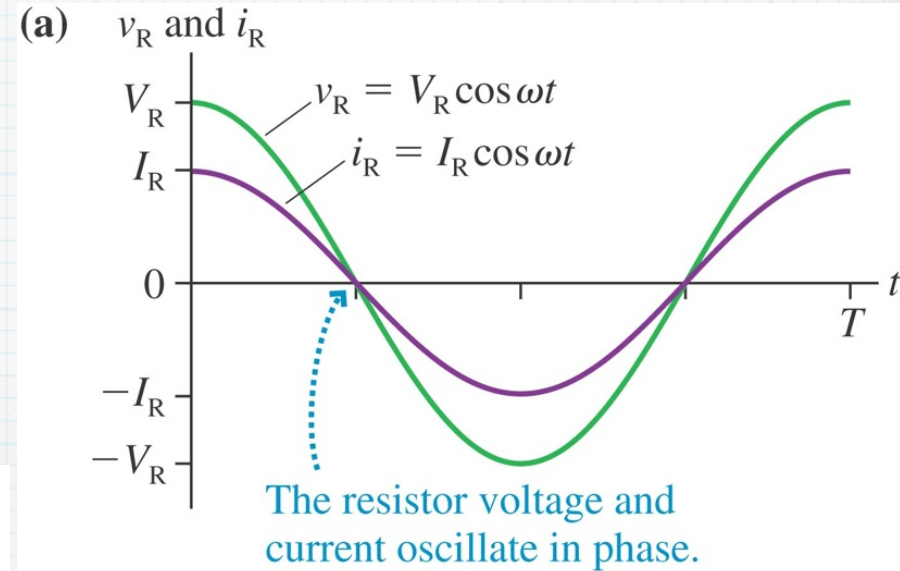Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley




Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley

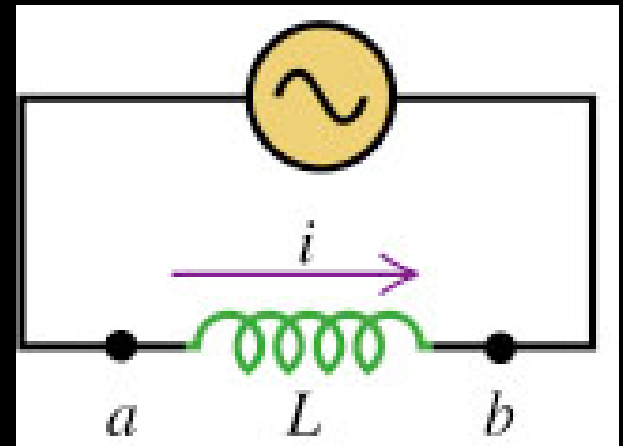
An inductor is connected across an ac source as shown. Which graph correctly shows the instantaneous current through the inductor and the instantaneous voltage $v = v_a - v_b$ across the inductor?



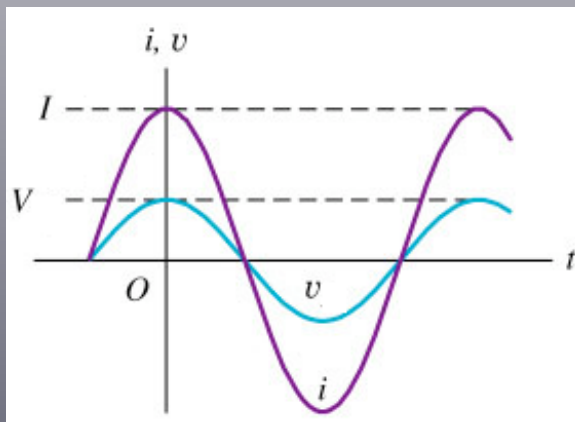
(current “ i ” in purple, voltage “ v ” in blue)



1.

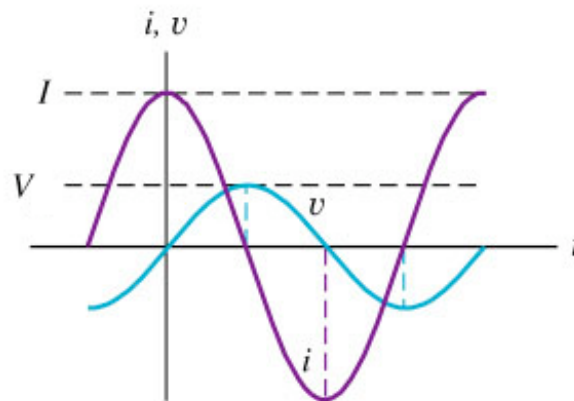


2.

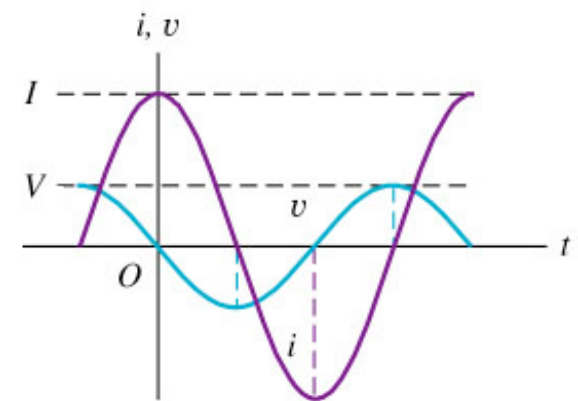


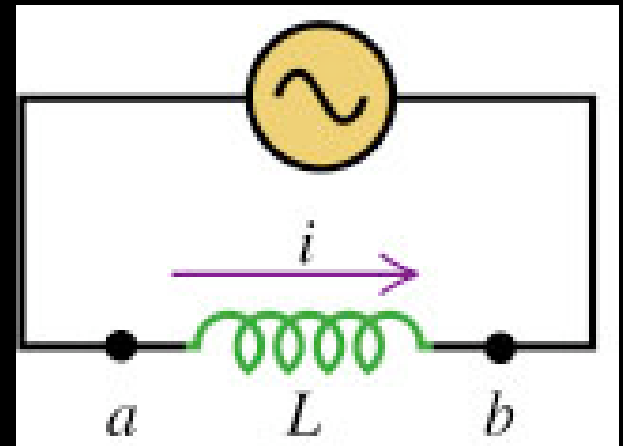3.


An inductor is connected across an ac source as shown. Which graph correctly shows the instantaneous current through the inductor and the instantaneous voltage $v = v_a - v_b$ across the inductor?



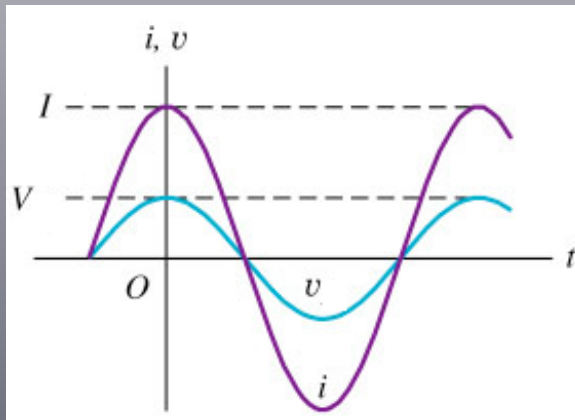
(current “ i ” in purple, voltage “ v ” in blue)



1.

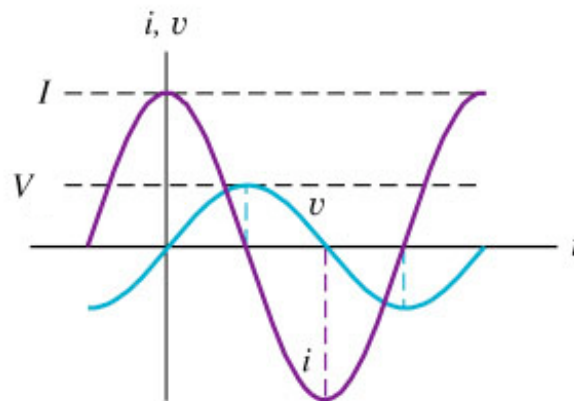


2.

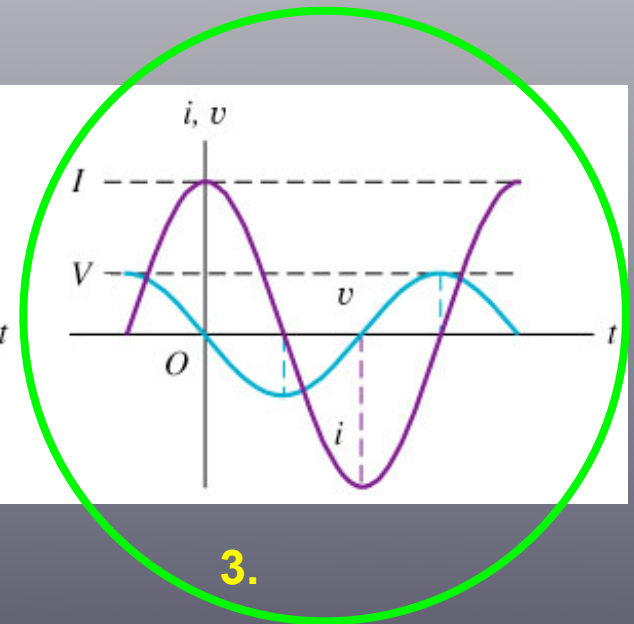


3.

(b)

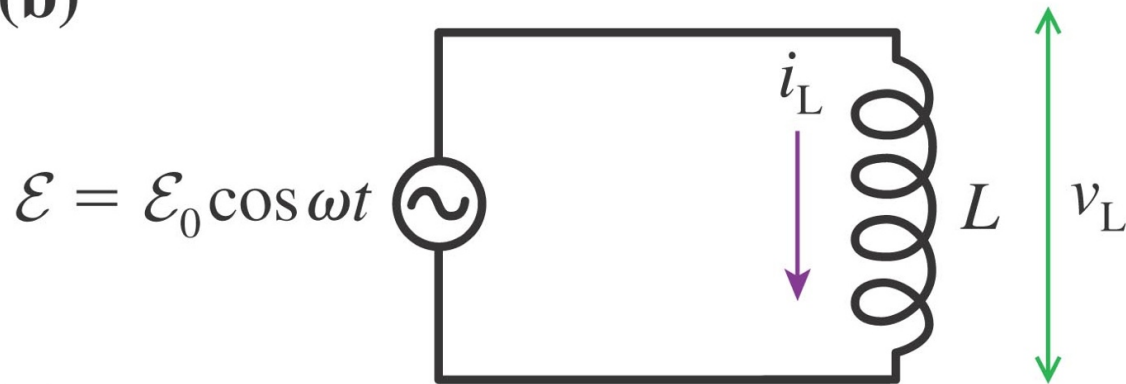


Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley.

(a)

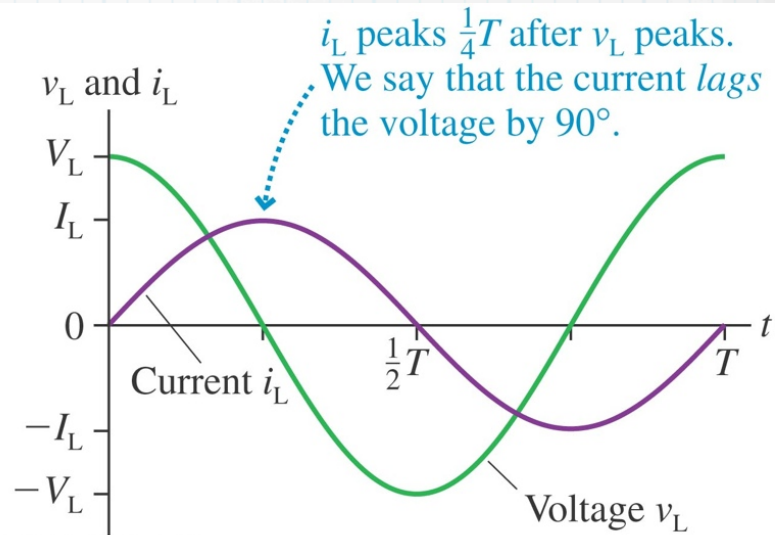


Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley.

(b)

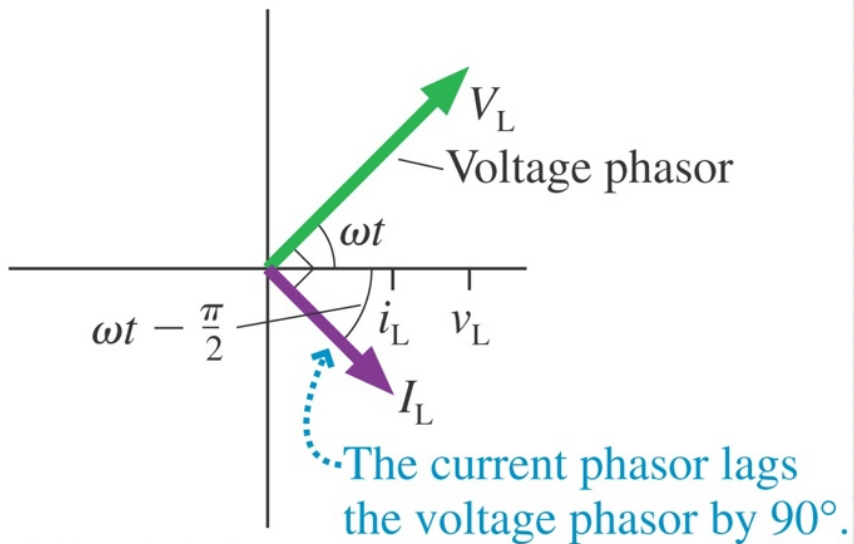


Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley.

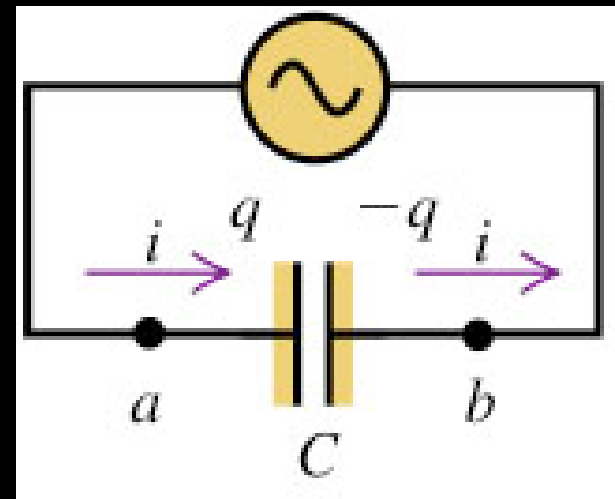
An capacitor is connected across an ac source as shown. Which graph correctly shows the instantaneous current through the capacitor and the instantaneous voltage $v = v_a - v_b$ across the capacitor?



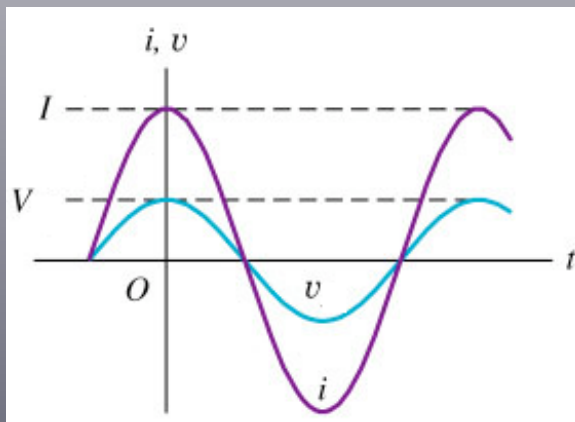
(current “ i ” in purple, voltage “ v ” in blue)



1.

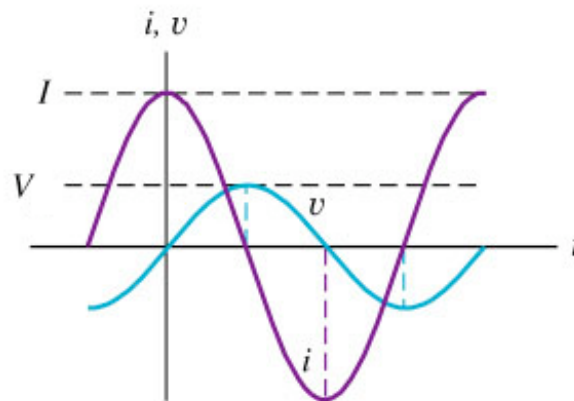


2.

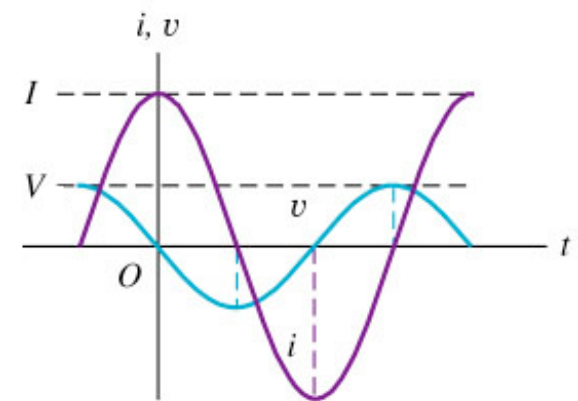


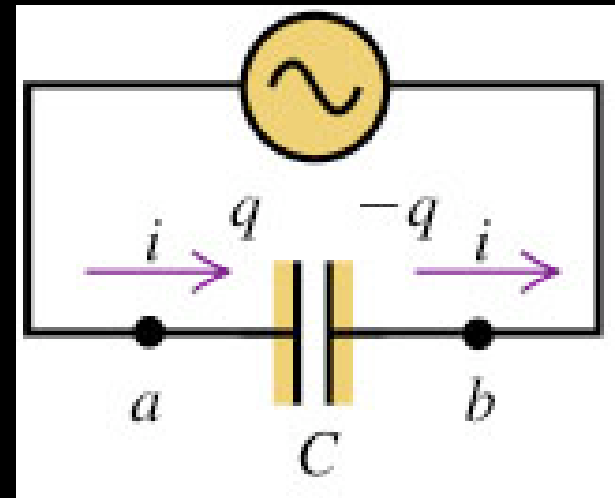3.


An capacitor is connected across an ac source as shown. Which graph correctly shows the instantaneous current through the capacitor and the instantaneous voltage $v = v_a - v_b$ across the capacitor?



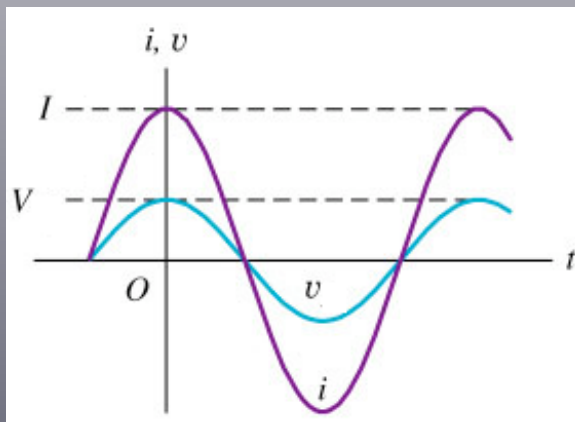
(current “ i ” in purple, voltage “ v ” in blue)



1.

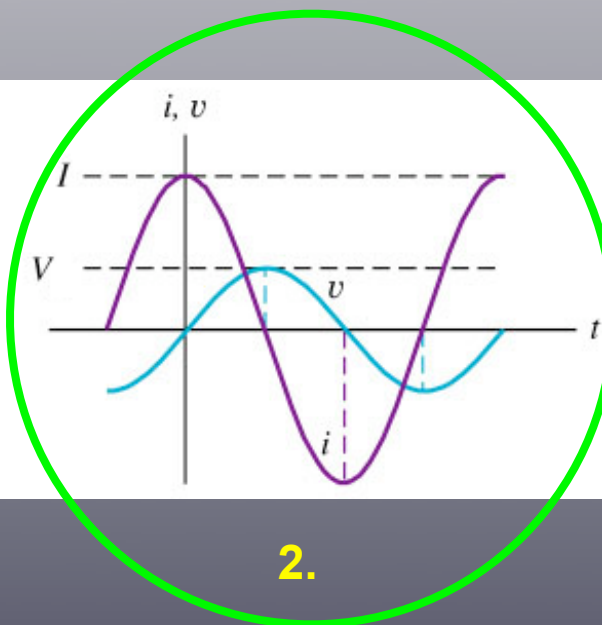


2.

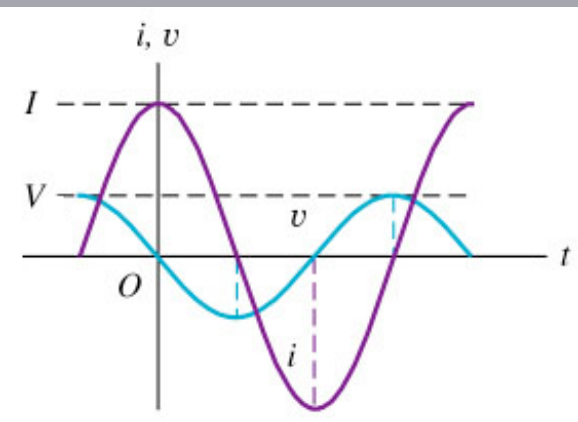

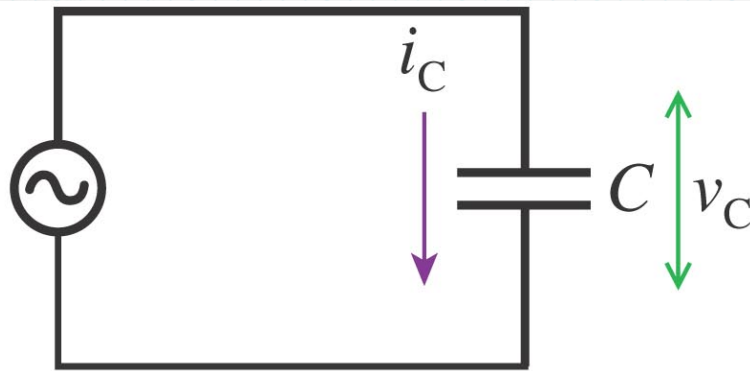3.


(b)

$$\mathcal{E} = \mathcal{E}_0 \cos \omega t$$




Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley.

(b)

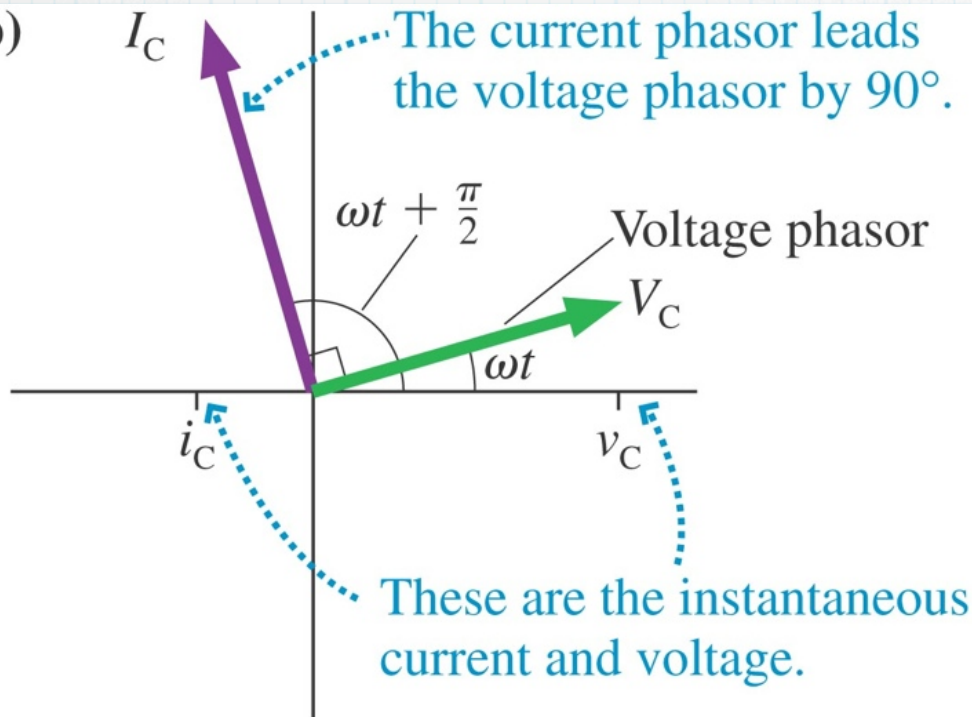

Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley.

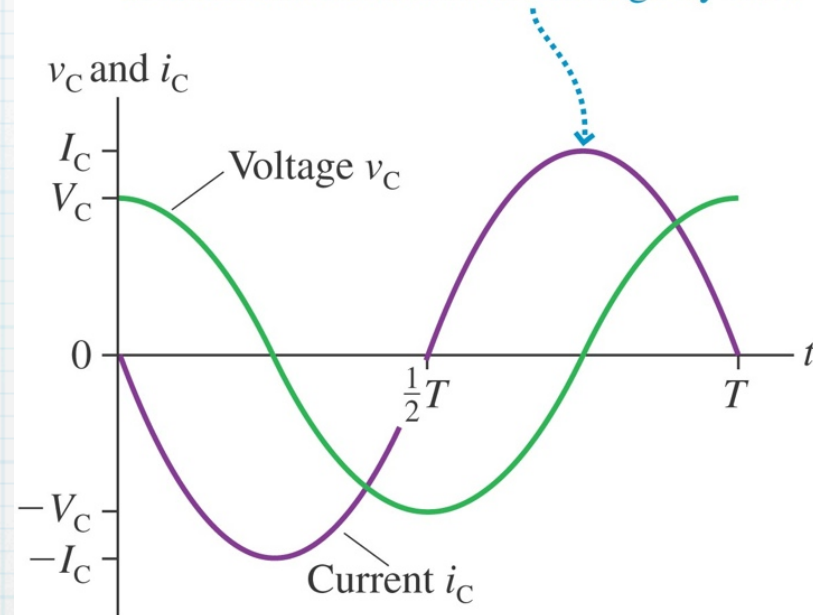(a) i_C peaks $\frac{1}{4}T$ before v_C peaks. We say that the current *leads* the voltage by 90° .




Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley.

The resistor whose voltage and current phasors are shown here has resistance R

1. $> 1 \Omega$.

2. $< 1 \Omega$.

3. It's not possible to tell.

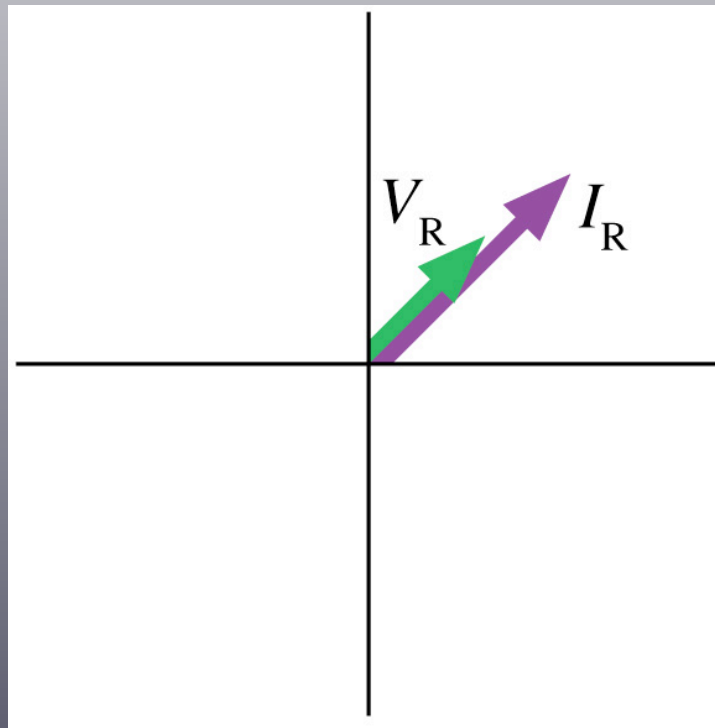


The resistor whose voltage and current phasors are shown here has resistance R

1. $> 1 \Omega$.

2. $< 1 \Omega$.


3. It's not possible to tell.

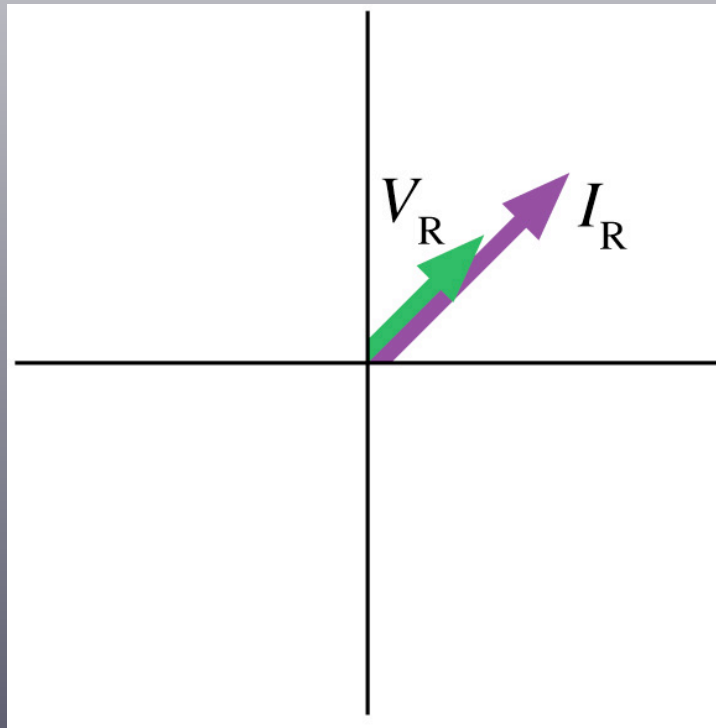

A capacitor is connected to a 15 kHz oscillator. The peak current is 65 mA when the rms voltage is 6.0 V.
What is the value of the capacitance C?

Ans: 81 nF

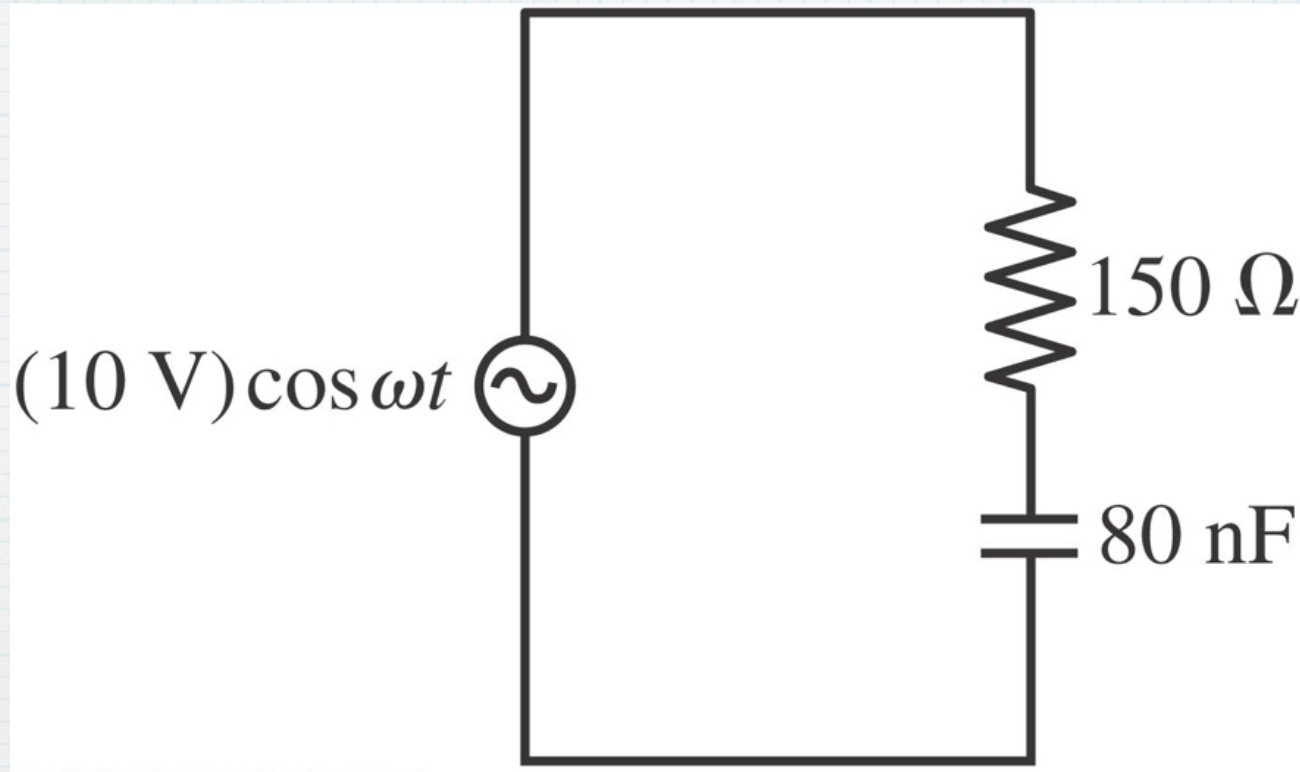In the figure, what are V_R and V_C (the peak potential differences across the resistor and the capacitor) if the emf frequency is 10 kHz?



Ans: $V_R = 6.0\text{ V}$, $V_C = 8.0\text{ V}$

A $500\ \mu\text{H}$ inductor is connected across an AC generator that produces a peak voltage of $5.0\ \text{V}$.


(a) For what frequency is the peak current $50\ \text{mA}$?

(b) What is the instantaneous value of the emf at the instant when $i_L = I_L$ (that is, when the instantaneous current equals the peak current)?

Ans: (a) $32\ \text{kHz}$, (b) 0

An L - R - C series circuit as shown is operating at its resonant frequency. At this frequency, how are the values of the capacitive reactance X_C , the inductive reactance X_L , and the resistance R related to each other?

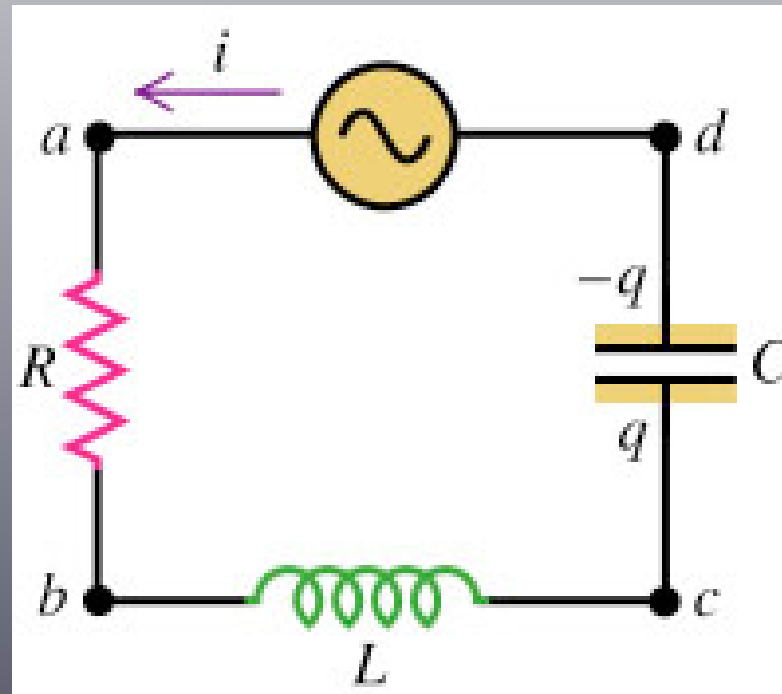1. $X_L = R$; X_C can have any value
2. $X_C = R$; X_L can have any value
3. $X_C = X_L$; R can have any value
4. $X_C = X_L = R$
5. none of the above



An L - R - C series circuit as shown is operating at its resonant frequency. At this frequency, how are the values of the capacitive reactance X_C , the inductive reactance X_L , and the resistance R related to each other?


1. $X_L = R$; X_C can have any value

2. $X_C = R$; X_L can have any value

3. $X_C = X_L$; R can have any value


4. $X_C = X_L = R$

5. none of the above

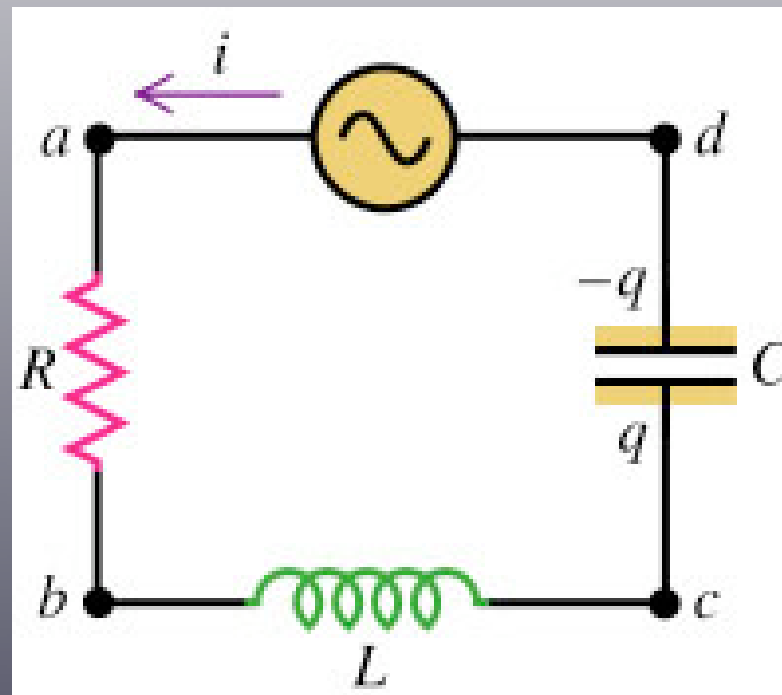

In an L - R - C series circuit as shown, the current has a very small amplitude if the emf oscillates at a very high frequency. Which circuit element causes this behavior?

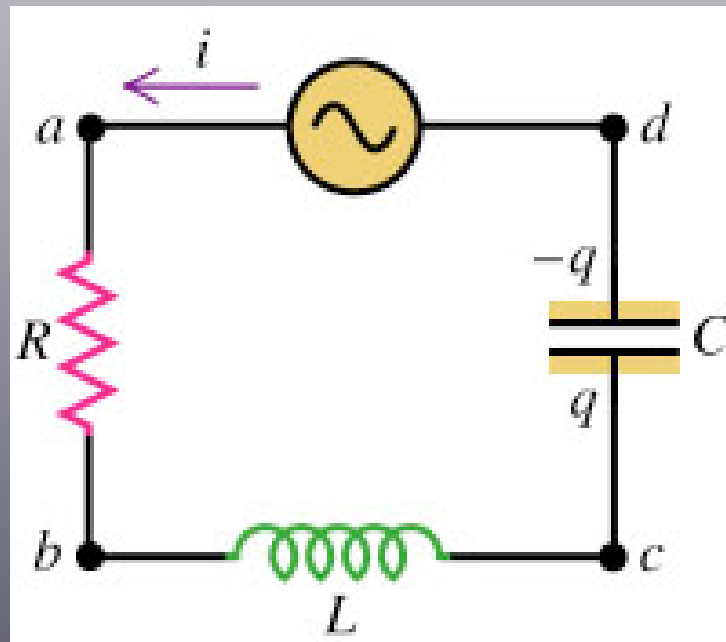1. the resistor R
2. the inductor L
3. the capacitor C
4. misleading question — the current actually has a very large amplitude if the frequency is very high




In an L - R - C series circuit as shown, the current has a very small amplitude if the emf oscillates at a very high frequency. Which circuit element causes this behavior?

1. the resistor R

2. the inductor L


3. the capacitor C

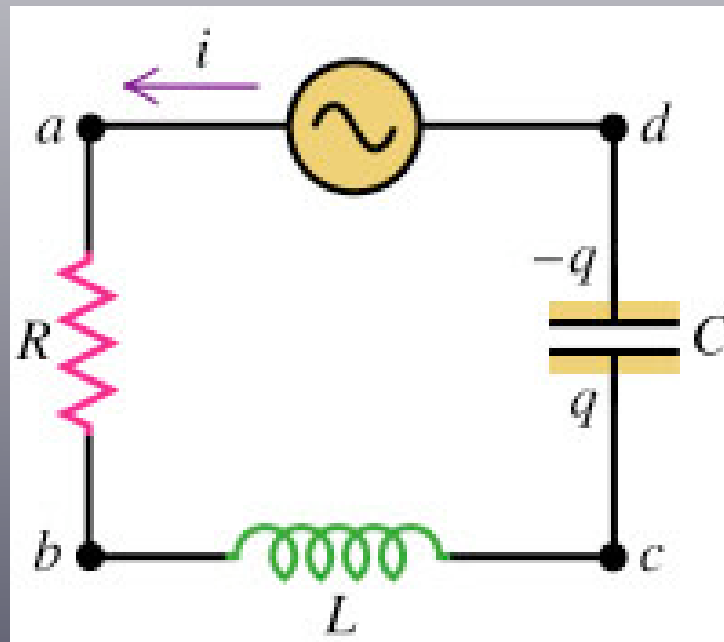4. misleading question — the current actually has a very large amplitude if the frequency is very high



In an L - R - C series circuit as shown, there is a phase angle between the instantaneous current through the circuit and the instantaneous voltage v_{ad} across the entire circuit. For what value of the phase angle is the greatest power delivered to the resistor?

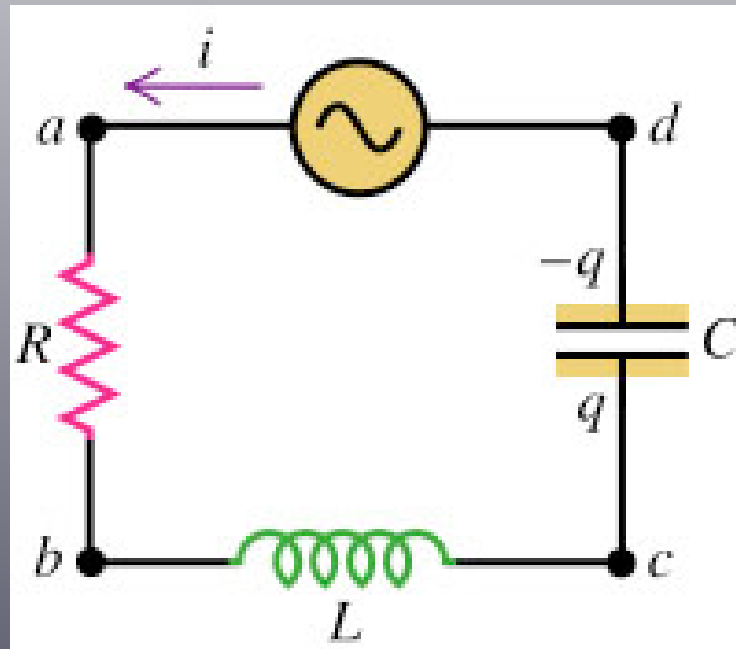1. zero
2. 90°
3. 180°
4. 270°
5. none of the above



In an L - R - C series circuit as shown, there is a phase angle between the instantaneous current through the circuit and the instantaneous voltage v_{ad} across the entire circuit. For what value of the phase angle is the greatest power delivered to the resistor?


1. zero

2. 90°

3. 180°

4. 270°

5. none of the above

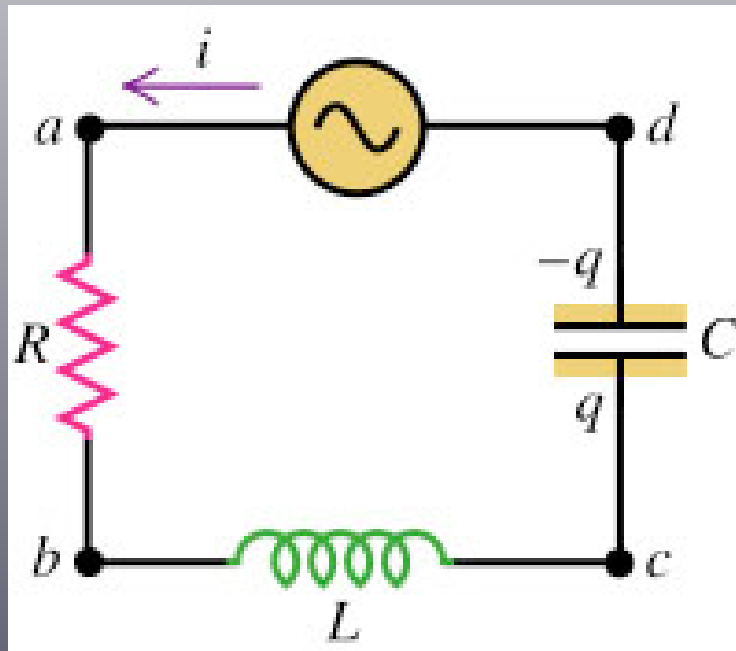

What inductor in series with a $100\ \Omega$ resistor and a $2.5\ \mu\text{F}$ capacitor will give a resonance frequency of $1.0\ \text{kHz}$?

Ans: $10\ \text{mH}$

A series RLC circuit consists of a $50\ \Omega$ resistor, a $3.3\ \text{mH}$ inductor, and a $480\ \text{nF}$ capacitor. It is connected to an oscillator with a peak voltage of $5.0\ \text{V}$. Determine the impedance, the peak current, and the phase angle at frequencies $3000\ \text{Hz}$, $4000\ \text{Hz}$ and $5000\ \text{Hz}$.

Ans:

	$f = 3000\ \text{Hz}$	$f = 4000\ \text{Hz}$	$f = 5000\ \text{Hz}$
$Z\ (\Omega)$	70	50	62
$I\ (\text{A})$	0.072	0.100	0.080
ϕ	-44°	0°	37°


A series RLC circuit has $V_C = 5.0 \text{ V}$, $V_R = 7.0 \text{ V}$, and $V_L = 9.0 \text{ V}$. Is the frequency above, below or equal to the resonance frequency?

1. Above the resonance frequency
2. Below the resonance frequency
3. Equal to the resonance frequency

A series RLC circuit has $V_C = 5.0\text{ V}$, $V_R = 7.0\text{ V}$, and $V_L = 9.0\text{ V}$. Is the frequency above, below or equal to the resonance frequency?

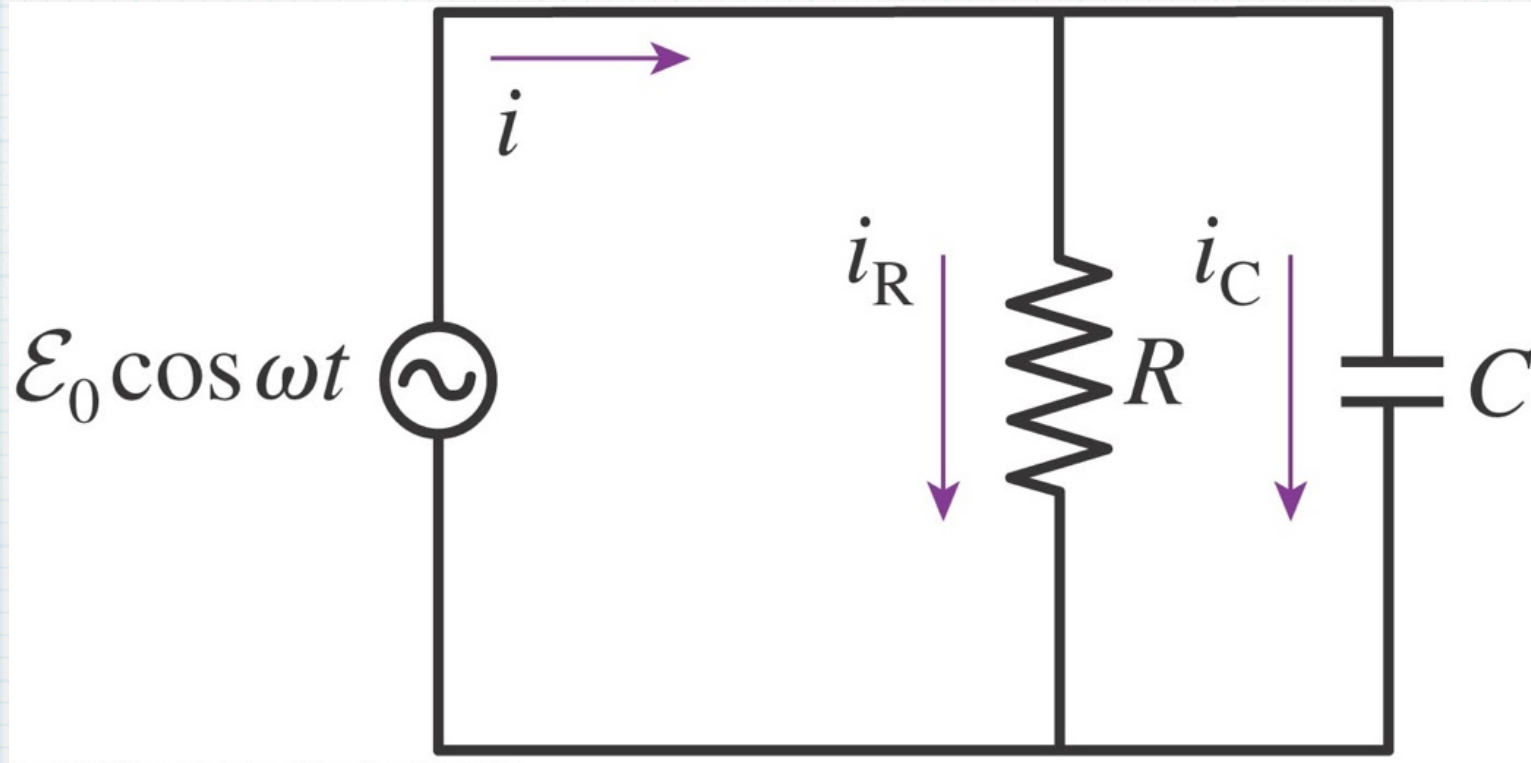1. Above the resonance frequency
2. Below the resonance frequency
3. Equal to the resonance frequency

Here is a parallel RC circuit with an AC source. What are the peak currents i_C , i_R and i ? What is the phase between the current i and the applied emf?



Follow-up: problems 36.70 and 36.71 in your textbook (all parallel or combination of series/parallel LRC circuits)


The emf and the current in a series RLC circuit oscillate as shown. Which of the following would increase the rate at which energy is supplied to the circuit?

1. Decrease \mathcal{E}_0

2. Increase L

3. Increase C

4. Decrease L

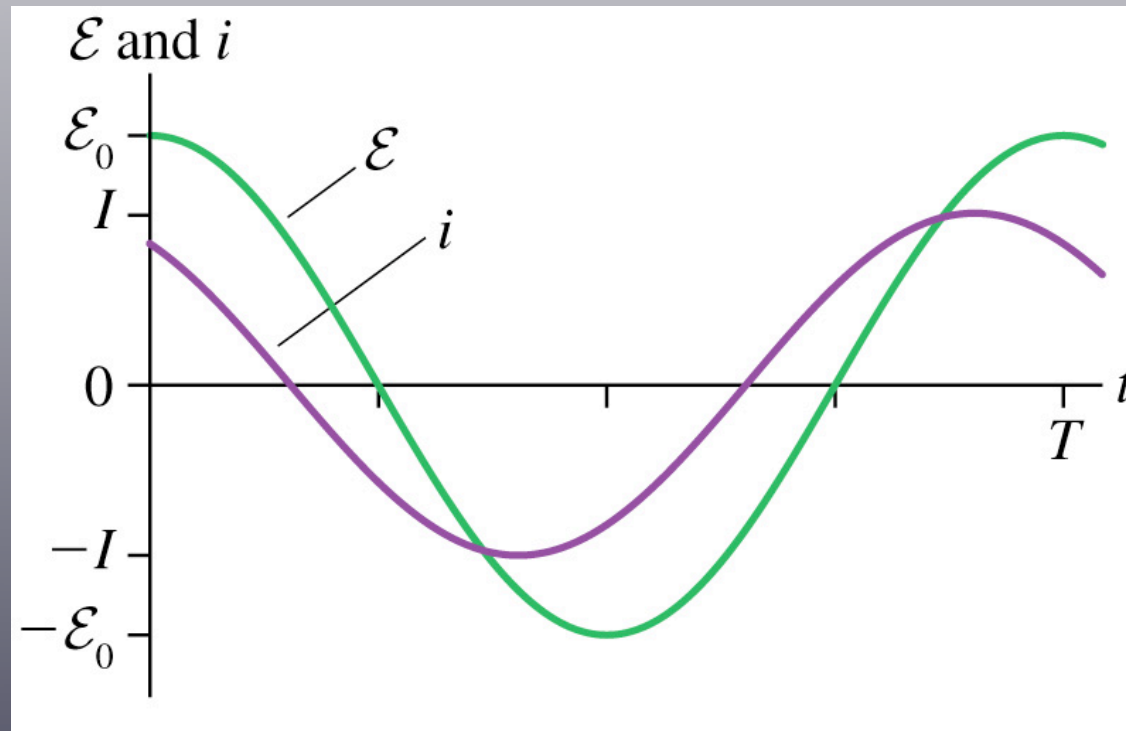


The emf and the current in a series RLC circuit oscillate as shown. Which of the following would increase the rate at which energy is supplied to the circuit?

1. Decrease \mathcal{E}_0

2. Increase L

3. Increase C

4. Decrease L

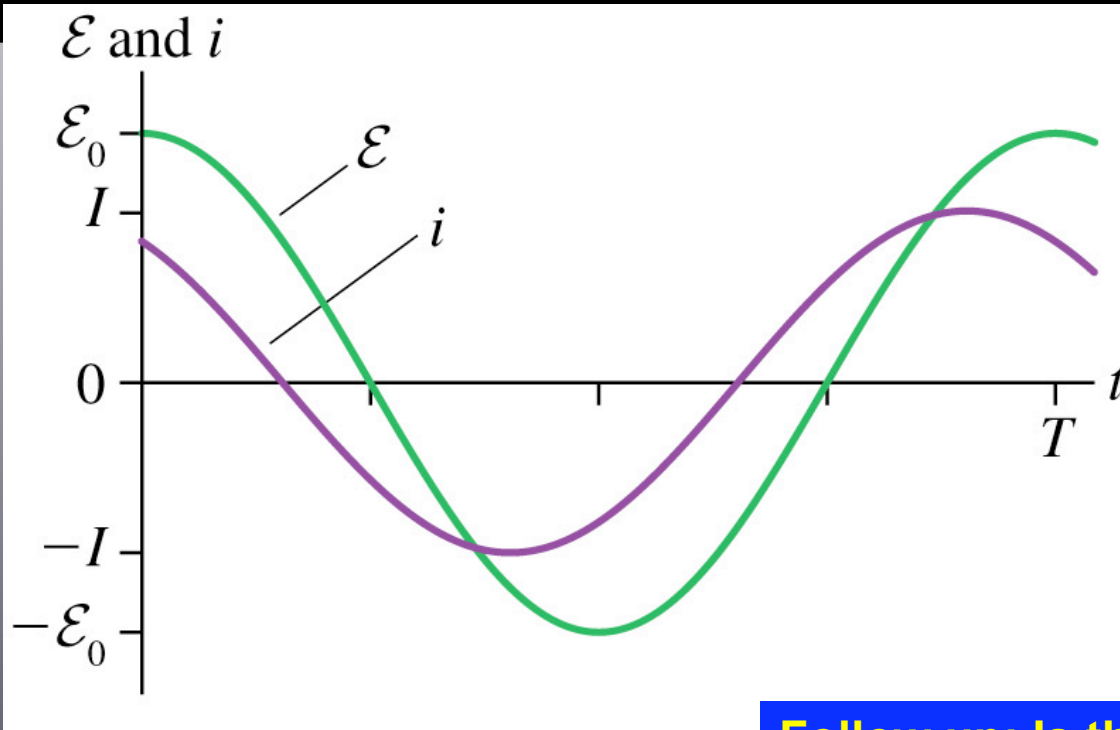

Follow up: Is there another way to increase the rate at which energy is supplied?

A motor attached to a 120 V/60 Hz power line draws an 8.0 A current. Its average energy dissipation is 800 W.

(a) What is the power factor?

(b) What is the rms resistor voltage?

(c) What is the motor's resistance?

(d) How much series capacitance needs to be added to increase the power factor to 1.0?

Ans: (a) 0.833 (b) 100 V (c) 12.5 Ω (d) 320 μF